
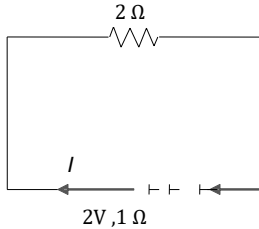


**Single Correct Answer Type**

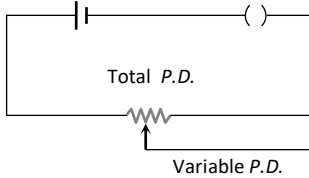1. In the electric circuit shown each cell has an emf of 2V and internal resistance of 1Ω. The external resistance is 2Ω. The value of the current I is(in ampere)




- a) 2                                      b) 1.25                                      c) 0.4                                      d) 1.2
2. A, B, C and D are four resistances of 2Ω, 2Ω, 2Ω and 3Ω respectively. They are used to form a Wheatstone bridge. The resistance D is short circuited with a resistances R in order to get the bridge balanced. The value of R will be
- a) 4 Ω                                      b) 6 Ω                                      c) 8 Ω                                      d) 3 Ω
3. The arrangement as shown in figure is called as




- a) Potential divider                      b) Potential adder                      c) Potential subtractor                      d) Potential multiplier
4. If the balance point is obtained at the 35<sup>th</sup> cm in a meter bridge, the resistances in the left and right gaps are in the ratio of
- a) 7 : 13                                      b) 13 : 7                                      c) 9 : 11                                      d) 11 : 9
5. Two electric bulbs rated  $P_1$  watt  $V$  volts and  $P_2$  watt  $V$  volts are connected in parallel and  $V$  volts are applied to it. The total power will be
- a)  $P_1 + P_2$  watt                      b)  $\sqrt{P_1 P_2}$  watt                      c)  $\frac{P_1 P_2}{P_1 + P_2}$  watt                      d)  $\frac{P_1 + P_2}{P_1 P_2}$  watt
6. In a meter bridge a 30Ω resistance is connected in the left gap and a pair of resistances  $P$  and  $Q$  in the right gap. Measured from the left, the balance point is 37.5 cm, when  $P$  and  $Q$  are in series and 71.4 cm when they are parallel. The values of  $P$  and  $Q$  (in ohm) are
- a) 40, 10                                      b) 35, 15                                      c) 30, 20                                      d) 25, 25
7. In an experiment to measure the internal resistance of a cell by potentiometer, it is found that the balance point is at a length of 2m when the cell is shunted by a 5Ω resistance; and is at a length of 3m when the cell is shunted by a 10Ω resistance. The internal resistance of the cell is, then
- a) 1.5Ω                                      b) 10Ω                                      c) 15Ω                                      d) 1Ω
8. Two electroplating cells, one of silver and another of aluminium are connected in series. The ratio of the number of silver atoms to that of aluminium atoms deposited during time  $t$  will be
- a) 1 : 3                                      b) 3 : 1                                      c) 1 : 9                                      d) 9 : 1
9. A coil of wire of resistance 50 Ω is embedded in a block of ice and a potential difference of 210 V is applied across it. The amount of ice which melts in 1 sec is
- a) 0.262 g                                      b) 2.62 g                                      c) 26.2 g                                      d) 0.0262 g
10. The resistance of 1 A ammeter is 0.018Ω. To convert it into 10 A ammeter, the shunt resistance required will be
- a) 0.18 Ω                                      b) 0.0018 Ω                                      c) 0.002 Ω                                      d) 0.12 Ω
11. When current flows through a conductor, then the order of drift velocity of electrons will be
- a)  $10^{10} m/sec$                                       b)  $10^{-2} cm/sec$                                       c)  $10^4 cm/sec$                                       d)  $10^{-1} cm/sec$

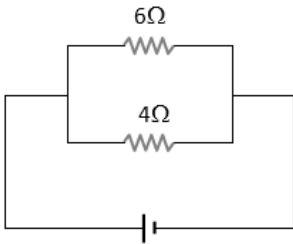
12. Which of the following statements is wrong
- Voltmeter should have high resistance
  - Ammeter should have low resistance
  - Ammeter is placed in parallel across the conductor in a circuit
  - Voltmeter is placed in parallel across the conductor in a circuit
13. A material  $B$  has twice the specific resistance of  $A$ . A circular wire made of  $B$  has twice the diameter of a wire made of  $A$ . Then for the two wires to have the same resistance, the ratio  $l_B/l_A$  of their respective lengths must be
- 1
  - 1/2
  - 1/4
  - 2
14. In the circuit shown below, the power developed in the  $6\Omega$  resistor is 6 watt. The power in watts developed in the  $4\Omega$  resistor is




- 16
  - 9
  - 6
  - 4
15. The value of internal resistance of an ideal cell is
- Zero
  - $0.5\ \Omega$
  - $1\ \Omega$
  - Infinity
16. If the electronic charge is  $1.6 \times 10^{-19}$  C, then the number of electrons passing through a section of wire per second, when the wire carries a current of 2 A is
- $1.25 \times 10^{17}$
  - $1.6 \times 10^{17}$
  - $1.25 \times 10^{19}$
  - $1.6 \times 10^{19}$
17. Two bulbs are working in parallel order. Bulb  $A$  is brighter than bulb  $B$ . If  $R_A$  and  $R_B$  are their resistance respectively then
- $R_A > R_B$
  - $R_A < R_B$
  - $R_A = R_B$
  - None of these
18. The amount of chlorine produced per-second through electrolysis in a plate which consumes 100 KW power at 200 V is (Given, electrochemical equivalent of chlorine =  $0.367 \times 10^{-3} \text{gC}^{-1}$ )
- 18.35 g
  - 1.835 g
  - 183.5 g
  - 0.1835 g
19. Three resistors each of 2 ohm are connected together in a triangular shape. The resistance between any two vertices will be
- $4/3 \text{ohm}$
  - $3/4 \text{ohm}$
  - 3 ohm
  - 6 ohm
20. Two different conductors have same resistance at  $0^\circ\text{C}$ . It is found that the resistance of the first conductor at  $t_1^\circ\text{C}$  is equal to the resistance of the second conductor at  $t_2^\circ\text{C}$ . The ratio of the temperature coefficients of resistance of the conductors,  $\frac{\alpha_1}{\alpha_2}$  is
- $\frac{t_1}{t_2}$
  - $\frac{t_2 - t_1}{t_2}$
  - $\frac{t_2 - t_1}{t_1}$
  - $\frac{t_2}{t_1}$
21. Which of the following set up can be used to verify the Ohm's law?

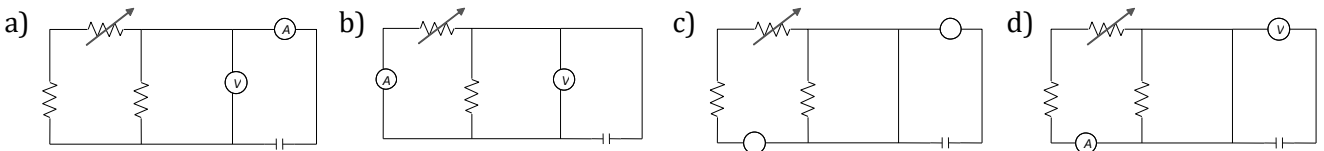


- $2.5 \times 10^{-4} \text{ohm}$
  - $1.25 \times 10^{-3} \text{ohm}$
  - $0.05 \text{ohm}$
  - $2.5 \text{ohm}$
23. The resistivity of a potentiometer wire is  $40 \times 10^{-8} \text{ohm} - \text{m}$  and its area of cross-section is  $8 \times 10^{-6} \text{m}^2$ . If 0.2 amp current is flowing through the wire, the potential gradient will be
- $10^{-2} \text{volt/m}$
  - $10^{-1} \text{volt/m}$
  - $3.2 \times 10^{-2} \text{volt/m}$
  - 1 volt/m
24. In the circuit shown here, the readings of the ammeter and voltmeter are

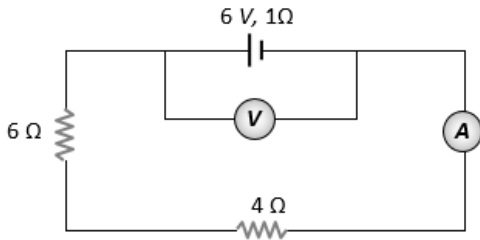

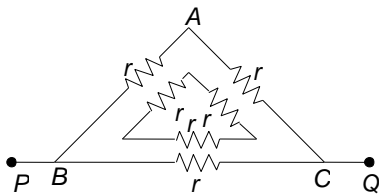- a) 6 A, 60 V  
 b) 0.6 A, 6 V  
 c)  $6/11$  A,  $60/11$  V  
 d)  $11/6$  A,  $11/60$  V
25. A thermocouple of negligible resistance produces an e.m.f. of  $40\mu\text{V}/^\circ\text{C}$  in the linear range of temperature. A galvanometer of resistance  $10\text{ ohm}$  whose sensitivity is  $1\mu\text{A}/\text{div}$ , is employed with the thermocouple. The smallest value of temperature difference that can be detected by the system will be  
 a)  $0.1^\circ\text{C}$                       b)  $0.25^\circ\text{C}$                       c)  $0.5^\circ\text{C}$                       d)  $1^\circ\text{C}$
26. The resistance across R and Q in the figure.



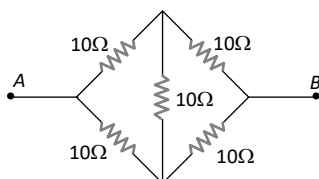- a)  $r/3$                       b)  $r/2$                       c)  $2r$                       d)  $6r$
27. When a current  $I$  flows through a wire, the drift velocity of the electrons is  $v$ . When current  $2I$  flows through another wire of the same material having double the length and double the area of cross-section, the drift velocity of the electrons will be  
 a)  $\frac{v}{8}$                       b)  $\frac{v}{4}$                       c)  $\frac{v}{2}$                       d)  $v$
28. A wire is broken in four equal parts. A packet is formed by keeping the four wires together. The resistance of the packet in comparison to the resistance of the wire will be  
 a) Equal                      b) One fourth                      c) One eight                      d)  $\frac{1}{16}$ th
29. In an electroplating experiment,  $m\text{ gm}$  of silver is deposited when  $4\text{ ampere}$  of current flows for  $2\text{ minute}$ . The amount (in  $\text{gm}$ ) of silver deposited by  $6\text{ ampere}$  of current for  $40\text{ second}$  will be  
 a)  $4m$                       b)  $m/2$                       c)  $m/4$                       d)  $2m$
30. Which of the following relation is wrong?  
 a)  $1\text{ ampere} \times 1\text{ ohm} = 1\text{ volt}$                       b)  $1\text{ watt} \times 1\text{ sec} = 1\text{ joule}$   
 c)  $1\text{ newton per coulomb} = 1\text{ volt per metre}$                       d)  $1\text{ columb} \times 1\text{ volt} = 1\text{ watt}$
31. To convert a  $800\text{ mV}$  range *milli voltmeter* of resistance  $40\ \Omega$  into a galvanometer of  $100\text{ mA}$  range, the resistance to be connected as shunt is  
 a)  $10\ \Omega$                       b)  $20\ \Omega$                       c)  $30\ \Omega$                       d)  $40\ \Omega$
32. The effective resistance between points A and B is



- a)  $10\ \Omega$                       b)  $20\ \Omega$   
 c)  $40\ \Omega$                       d) None of the above three values
33. If the total emf in a thermocouple is a parabolic function expressed as  $E = at + \frac{1}{2}bt^2$ , which of the following relation does not hold good?


a) Neutral temperature  $t_n = -\frac{a}{b}$

b) Temperature of inversion,  $t_i = -\frac{-2a}{b}$

c) Thermoelectric power  $P = a + bt$

d)  $t_n = \frac{a}{b}$

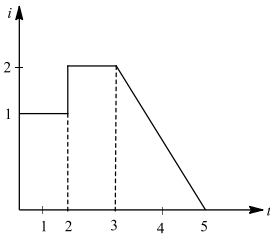34. The plot represents the flow of current through a wire at three different times.



The ratio of charges flowing through the wire at different times is

a) 2 : 1 : 2

b) 1 : 3 : 3

c) 1 : 1 : 1

d) 2 : 3 : 4

35. When the resistance of  $9\ \Omega$  is connected at the ends of a battery, its potential difference decreases from  $40\ volt$  to  $30\ volt$ . The internal resistance of the battery is

a)  $6\ \Omega$

b)  $3\ \Omega$

c)  $9\ \Omega$

d)  $15\ \Omega$

36. A cylindrical metal wire of length  $l$  and cross sectional area  $S$ , has resistance  $R$ , conductance  $G$ , conductivity  $\sigma$  and resistivity  $\rho$ . Which one of the following expressions for  $\sigma$  is valid

a)  $\frac{GR}{\rho}$

b)  $\frac{\rho R}{G}$

c)  $\frac{GS}{l}$

d)  $\frac{Rl}{S}$

37. The heat developed in an electric wire of resistance  $R$  by a current  $I$  for a time  $t$  is


a)  $\frac{I^2 R t}{4.2}\ cal$

b)  $\frac{I^2 t}{4.2 R}\ cal$

c)  $\frac{I^2 R}{4.2 t}\ cal$

d)  $\frac{R t}{4.2 I^2}\ cal$

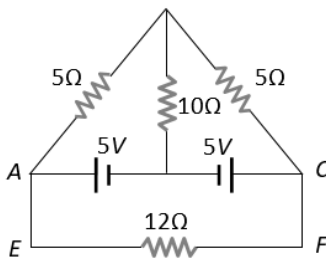38. In the circuit of adjoining figure the current through  $12\ \Omega$  resistor will be



a)  $1\ A$

b)  $\frac{1}{5}\ A$

c)  $\frac{2}{5}\ A$

d)  $0\ A$

39. An electric bulb is designed to draw power  $P_0$  at voltage  $V_0$ . If the voltage is  $V$  it draws a power  $P$ . Then

a)  $P = \left(\frac{V_0}{V}\right)^2 P_0$

b)  $P = \left(\frac{V}{V_0}\right)^2 P_0$

c)  $P = \left(\frac{V}{V_0}\right) P_0$

d)  $P = \left(\frac{V_0}{V}\right) P_0$

40. When two resistances  $R_1$  and  $R_2$  are connected in series and parallel with  $120\ V$  line power consumed will be  $25\ W$  and  $100\ W$  respectively. Then the ratio of power consumed by  $R_1$  to that consumed by  $R_2$  will be

a) 1 : 1

b) 1 : 2

c) 2 : 1

d) 1 : 4

41. For which of the following the resistance decreases on increasing the temperature


a) Copper

b) Tungsten

c) Germanium

d) Aluminium

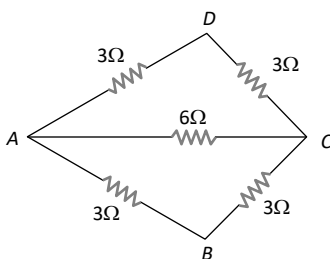42. The effective resistance between the points  $A$  and  $B$  in the figure is



a)  $5\ \Omega$


b)  $2\ \Omega$

c)  $3\ \Omega$

d)  $4\ \Omega$

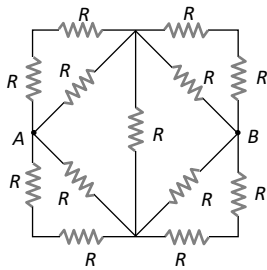
43. How much energy in kilowatt hour is consumed in operating ten  $50\ watt$  bulbs for  $10$  hours per day in a month ( $30$  days)





- a)  $2R \Omega$                       b)  $\frac{4R}{3} \Omega$                       c)  $\frac{2R}{3} \Omega$                       d)  $R \Omega$

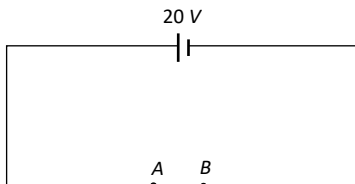51. In the shown circuit, what is the potential difference across A and B



- a) 50 V                      b) 45 V                      c) 30 V                      d) 20 V

52. The internal resistance of a cell is the resistance of

- a) Electrodes of the cell                      b) Vessel of the cell  
c) Electrolyte used in the cell                      d) Material used in the cell


53. In potentiometer a balance point is obtained, when

- a) The e.m.f. of the battery becomes equal to the e.m.f. of the experimental cell  
b) The p.d. of the wire between the +ve end to jockey becomes equal to the e.m.f. of the experimental cell  
c) The p.d. of the wire between +ve point and jockey becomes equal to the e.m.f. of the battery  
d) The p.d. across the potentiometer wire becomes equal to the e.m.f. of the battery

54. A conductor wire having  $10^{29}$  free electrons/ $m^3$  carries a current of 20A. If the cross-section of the wire is  $1mm^2$ , then the drift velocity of electrons will be


- a)  $6.25 \times 10^{-3}ms^{-1}$                       b)  $1.25 \times 10^{-5}ms^{-1}$                       c)  $1.25 \times 10^{-3}ms^{-1}$                       d)  $1.25 \times 10^{-4}ms^{-1}$

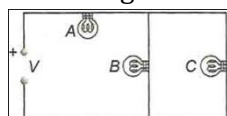55. Figure shown three similar lamps A, B and C connected across a power supply. If the lamp C fuses, how will the light emitted by A and B change?



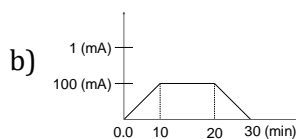- a) No change


Brilliance of A decreases and that of B increases



- c) Brilliance of both A and B increases

d) Brilliance of both A and B decreases

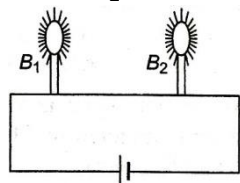56. Bulb  $B_1$  (100 W-250 V) and bulb  $B_2$  (100 W-200 V) are connected across 250 V. What is potential drop across  $B_2$ ?



- a) 200 V                      b) 250 V                      c) 98 V                      d) 48 V


57. The amount of charge required to liberate 9 gm of aluminium (atomic weight =27 and valency = 3) in the process of electrolysis is (Faraday's number =96500 coulombs/gm equivalent)

- a) 321660 coulombs                      b) 69500 coulombs                      c) 289500 coulomb                      d) 96500 coulomb


58. In the circuit shown below, the reading of the voltmeter V is



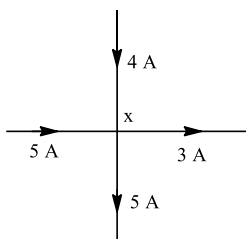
68. Five conductors are meeting at a point  $x$  as shown in the figure. What is the value of current in fifth conductor?



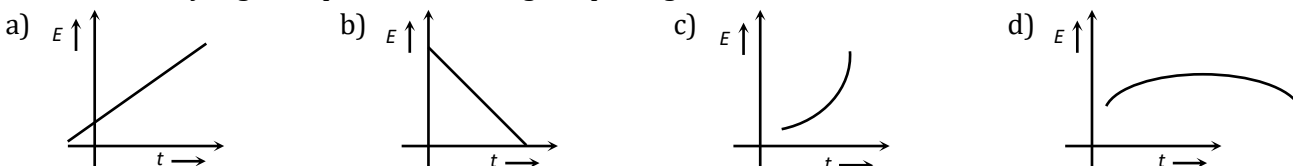
- a) 3 A away from  $x$       b) 1 A away from  $x$       c) 4 A away from  $x$       d) 1 A towards  $x$
69. A heating coil is labelled  $100\text{ W}$ ,  $220\text{ V}$ . The coil is cut in half and the two pieces are joined in parallel to the same source. The energy now liberated per second is
- a) 200 J      b) 400 J      c) 25 J      d) 50 J
70. For comparing the e.m.f.'s of two cells with a potentiometer, a standard cell is used to develop a potential gradient along the wires. Which of the following possibilities would make the experiment unsuccessful
- a) The e.m.f. of the standard cell is larger than the  $E$  e.m.f.'s the two cells  
 b) The diameter of the wires is the same and uniform throughout  
 c) The number of wires is ten  
 d) The e.m.f. of the standard cell is smaller than the e.m.f.'s of the two cells
71. Two different metals are joined end to end. One end is kept at constant temperature and the other end is heated to a very high temperature. The high depicting the thermo e.m.f. is



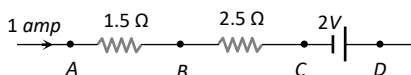
72. In the circuit element given here, if the potential at point  $B$ ,  $V_B = 0$ , then the potentials of  $A$  and  $D$  are given as



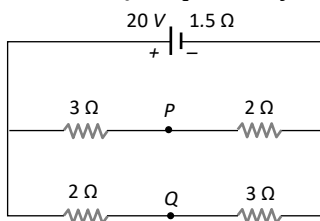- a)  $V_A = -1.5\text{ V}$ ,  $V_D = +2\text{ V}$       b)  $V_A = +1.5\text{ V}$ ,  $V_D = +2\text{ V}$   
 c)  $V_A = +1.5\text{ V}$ ,  $V_D = +0.5\text{ V}$       d)  $V_A = +1.5\text{ V}$ ,  $V_D = -0.5\text{ V}$
73. If in the circuit shown below, the internal resistance of the battery is  $1.5\ \Omega$  and  $V_P$  and  $V_Q$  are the potentials at  $P$  and  $Q$  respectively, what is the potential difference between the points  $P$  and  $Q$



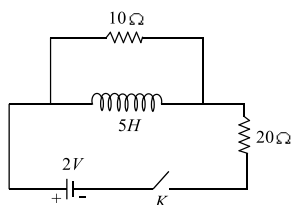
- a) Zero      b) 4 volts ( $V_P > V_Q$ )      c) 4 volts ( $V_Q > V_P$ )      d) 2.5 volts ( $V_Q > V_P$ )
74. Two resistance of  $10\ \Omega$  and  $20\ \Omega$  and an inductor of inductance  $5\text{ H}$  are connected to a battery of  $2\text{ V}$  through a key  $k$  as shown in the figure. At time  $t = 0$ , when the key  $k$  is closed the initial current through the battery is






- a)  $0.2 A$                       b)  $\frac{2}{15} A$                       c)  $\frac{1}{15} A$                       d)  $0$

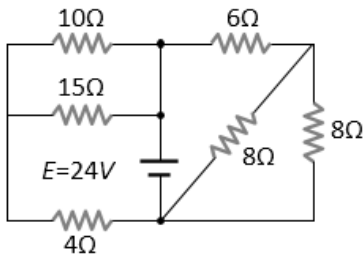75. Find the equivalent resistance across the terminals of source of e.m.f.  $24 V$  for the circuit shown in figure



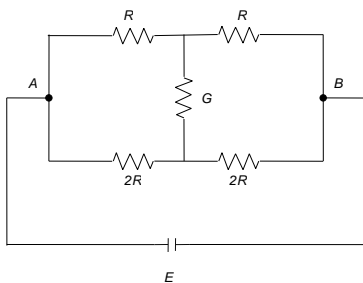
- a)  $15 \Omega$                       b)  $10 \Omega$                       c)  $5 \Omega$                       d)  $4 \Omega$
76. Twelve cells, each having emf  $E$  volts are connected in series and kept in a closed box. Some of these cells are wrongly connected with positive and negative terminals reversed. This 12-cell battery is connected with an ammeter, an external resistance  $R$  ohm and a two-cell battery (two cells of the same type used earlier, connected perfectly in series). The current in the circuit when the 12-cell battery and 2-cell battery aid each other is  $3A$  and  $2A$  when they oppose each other. Then, the number of cell in 12-cell battery that are connected wrongly is
- a)  $4$                               b)  $3$                               c)  $2$                               d)  $1$
77. In hydrogen atom, the electron makes  $6.6 \times 10^{15}$  revolutions per second around the nucleus in an orbit of radius  $0.5 \times 10^{-10}m$ . It is equivalent to a current nearly
- a)  $1 A$                             b)  $1 mA$                         c)  $1 \mu A$                         d)  $1.6 \times 10^{-19} A$
78. Two conductors made of the same material are connected across a common potential difference. Conductor  $A$  has twice the diameter and twice the length of conductor  $B$ . The power delivered to the two conductors  $P_A$  and  $P_B$  respectively is such that  $P_A/P_B$  equals to
- a)  $0.5$                             b)  $1.0$                             c)  $1.5$                             d)  $2.0$
79. Two heater wires of equal length are first connected in series and then in parallel. The ratio of heat produced in the two cases is
- a)  $1 : 4$                             b)  $4 : 1$                             c)  $1 : 2$                             d)  $2 : 1$
80. Consider the following statements regarding the network shown in the figure.
- The equivalent resistance of the network between point  $A$  and  $B$  is independent of value of  $G$ .
  - The equivalent resistance of the network between points  $A$  and  $B$  is  $\frac{4}{3}R$
  - The current through  $G$  is zero.
- Which of the above statements is/is zero true?




- a) 1,2 and 3                      b) 2 and 3                      c) 2 alone                      d) 1 alone
81. In a copper voltmeter experiment, current is decreased to one-fourth of the initial value but is passed for four times the earlier duration. Amount of copper deposited will be
- a) Same                            b) One-fourth the previous value
- c) Four times the previous value                      d)  $\frac{1}{16}$  th the previous value
82. A strip of copper and another of germanium are cooled from room temperature to  $80 K$ . The resistance of
- a) Each of these increases                      b) Each of these decreases

- c) Copper strip increases and that of germanium decreases      d) Copper strip decreases and that of germanium increases

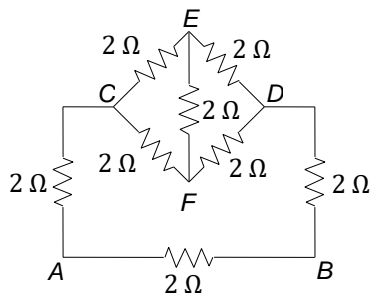
83. The resistance of the following circuit figure between  $A$  and  $B$  is



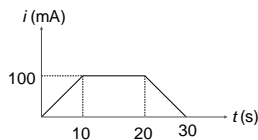
- a)  $(3/2)\ \Omega$       b)  $2\ \Omega$       c)  $4\ \Omega$       d)  $8\ \Omega$
84. The amount of charge  $Q$  passed in time  $t$  through a cross-section of a wire is  $Q = 5t^2 + 3t + 1$ . The value of current at time  $t = 5\text{ s}$  is
- a) 9A      b) 49A      c) 53A      d) None of these
85. Silver and copper voltameter are connected in parallel with a battery of e.m.f. 12 V. In 30 minutes, 1g of silver and 1.8g of copper are liberated. The power supplied by the battery is ( $Z_{Cu} = 6.6 \times 10^{-4}\text{ g/C}$  and  $Z_{Ag} = 11.2 \times 10^{-4}\text{ g/C}$ )
- a) 24.13 J/sec      b) 2.413 J/sec      c) 0.2413 J/sec      d) 2413 J/sec
86. In a copper voltameter, the mass deposited in 30 s is  $m$  gram. If the current-time graph is as shown in figure, the electrochemical equivalent of copper, in  $\text{gC}^{-1}$  is



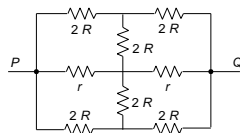- a)  $0.1\ m$       b)  $0.6\ m$       c)  $\frac{m}{2}$       d)  $m$
87. The electron in a hydrogen atom circles around the proton in  $1.5941 \times 10^{-18}\text{ s}$ . The equivalent current due to motion of the electrons is
- a) 127.37 mA      b) 122.49 mA      c) 100.37 mA      d) 94.037 mA
88. The effective resistance between points  $P$  and  $Q$  of the electrical circuit shown in the figure.




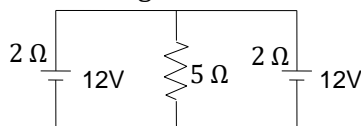- a)  $\frac{2Rr}{R+r}$       b)  $\frac{8R(R+r)}{(3R+r)}$       c)  $2R+4r$       d)  $\frac{5R}{2}+2R$
89. In a thermo-couple, one junction which is at  $0^\circ\text{C}$  and the other at  $t^\circ\text{C}$  the emf is given by  $E = at^2 - bt^2$ . The neutral temperature is given by
- a)  $a/b$       b)  $2a/3b$       c)  $3a/2b$       d)  $b/2a$
90. In the arrangement shown in figure, the current through  $5\ \Omega$  resistor is




- a) 2A      b) Zero      c)  $\frac{12}{7}\text{ A}$       d) 1A
91. A straight conductor of uniform cross-section carries a current  $i$ . If  $s$  is the specific charge of an electron, the momentum of all the free electrons per unit length of the conductor, due to their drift velocity only is
- a)  $is$       b)  $\sqrt{i/s}$       c)  $i/s$       d)  $(i/s)^2$
92. When a copper voltameter is connected with a battery of emf 12V, 2 g of copper is deposited in 30 min. If the same voltameter is connected across 6 V battery, the mass of copper deposited in 45 min would be

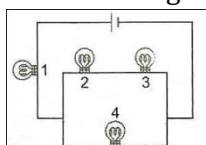- a) 1 g                                      b) 1.5 g                                      c) 2 g                                      d) 2.5 g
93. A resistor  $R$  and  $2\mu\text{F}$  capacitor in series is connected through a switch to 200 V direct supplies. Across the capacitor is a neon bulb that lights up at 120 V. Calculate the value of  $R$  to make the bulb light up 5 s after the switch has been closed ( $\log_{10} 2.5 = 0.4$ )
- a)  $1.7 \times 10^5 \Omega$                                       b)  $2.7 \times 10^6 \Omega$                                       c)  $3.3 \times 10^7 \Omega$                                       d)  $1.3 \times 10^4 \Omega$
94. In above question, if length is doubled, the drift velocity
- a) Is doubled                                      b) Is halved                                      c) Remains same                                      d) Becomes zero
95. Out of five resistances of resistance  $R \Omega$  each 3 are connected in parallel and are joined to the rest 2 in series. Find the resultant resistance
- a)  $\left(\frac{3}{7}\right) R \Omega$                                       b)  $\left(\frac{7}{3}\right) R \Omega$                                       c)  $\left(\frac{7}{8}\right) R \Omega$                                       d)  $\left(\frac{8}{7}\right) R \Omega$
96. If the resistivity of an alloy is  $\rho'$  and that of constituent metal is  $\rho$  then
- a)  $\rho' > \rho$                                       b)  $\rho' < \rho$   
c)  $\rho' = \rho$                                       d) There is no simple relation between  $\rho$  and  $\rho'$
97. The mass of a substance liberated when a charge ' $q$ ' flows through an electrolyte is proportional to
- a)  $q$                                       b)  $1/q$                                       c)  $q^2$                                       d)  $1/q^2$
98. The resistance of a discharge tube is
- a) *Ohmic*                                      b) *Non-ohmic*                                      c) Both (a) and (b)                                      d) Zero
99. If the resistance of a conductor is  $5\Omega$  at  $50^\circ\text{C}$  and  $7\Omega$  at  $100^\circ\text{C}$  then the mean temperature coefficient of resistance of the material is
- a)  $0.008/^\circ\text{C}$                                       b)  $0.006/^\circ\text{C}$                                       c)  $0.004/^\circ\text{C}$                                       d)  $0.001/^\circ\text{C}$
100. The resistance of a galvanometer coil is  $R$ , then the shunt resistance required to convert it into an ammeter of range 4 times, will be
- a)  $4R$                                       b)  $R/3$                                       c)  $R/4$                                       d)  $R/5$
101. All bulbs in figure, are identical. Which bulb lights brightly?




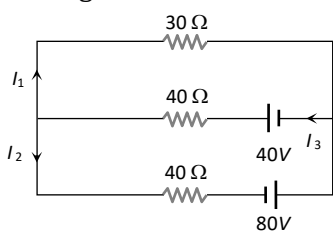- a) 1                                      b) 2                                      c) 3                                      d) 4
102. An ammeter gives full scale deflection when current  $1.0 \text{ A}$  is passed in it. To convert it into  $10 \text{ A}$  range ammeter, the ratio of its resistance and the shunt resistance will be
- a)  $1 : 9$                                       b)  $1 : 10$                                       c)  $1 : 11$                                       d)  $9 : 1$
103. Same current is being passed through a copper voltmeter and a silver voltmeter. The rate of increase in weights of the cathode of the two voltmeters will be proportional to
- a) Atomic masses                                      b) Atomic number                                      c) Relative densities                                      d) None of the above
104. For measurement of potential difference, potentiometer is preferred in comparison to voltmeter because
- a) Potentiometer is more sensitive than voltmeter  
b) The resistance of potentiometer is less than voltmeter  
c) Potentiometer is cheaper than voltmeter  
d) Potentiometer does not take current from the circuit
105. The resistance of an ideal ammeter is
- a) Infinite                                      b) Very high                                      c) Small                                      d) Zero
106. In the given circuit the current  $I_1$  is




- a)  $0.4 \text{ A}$                                       b)  $-0.4 \text{ A}$                                       c)  $0.8 \text{ A}$                                       d)  $-0.8 \text{ A}$

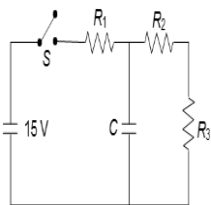107. The chemical equivalent of copper and zinc are 32 and 108 respectively. When copper and silver voltmeters are connected in series and electric current is passed through for sometime, 1.6 g of copper is deposited. Then, the mass of silver deposited will be  
 a) 3.5 g                              b) 2.8 g                              c) 5.4 g                              d) None of these
108. When current is passed in antimony-bismuth couple, then  
 a) The junction becomes hot when the current is from bismuth to antimony  
 b) The junction becomes hot when current flows from antimony to bismuth  
 c) Both junctions becomes hot  
 d) Both junctions becomes cold
109. The current inside a copper voltmeter  
 a) Is half the outside value  
 b) Is the same as the outside value  
 c) Is twice the outside value  
 d) Depends on the concentration of  $CuSO_4$
110.  $I - V$  characteristic of a copper wire of length  $L$  and area of cross-section  $A$  is shown in figure. The slope of the curve becomes



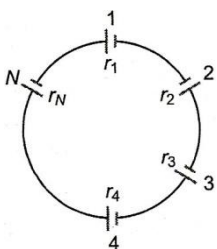
- a) More if the experiment is performed at higher temperature                              b) More if a wire of steel of same dimension is used  
 c) More if the length of the wire increased                              d) Less if the length of the wire increased
111. A heater of 220 V heats a volume of water in 5 min time. A heater of 110 V heats the same volume of water is  
 a) 5 min                              b) 8 min                              c)  $4 \times 10^4$  min                              d) 20 min
112. Two wires having resistance of  $2\Omega$  and  $4\Omega$  are connected to same voltage. Ratio of heat dissipated at resistance is  
 a) 1 : 2                              b) 4 : 3                              c) 2 : 1                              d) 5 : 2
113. A group of  $N$  cells whose emf varies directly with the internal resistance as per the equation  $E_N = 1.5r_N$  are connected as shown in the figure. The current  $I$  in the circuit is




- a) 5.1A                              b) 0.51A                              c) 1.5A                              d) 0.15A
114. For the network shown in the figure the value of the current  $i$  is
- 
- a)  $\frac{9V}{35}$                               b)  $\frac{5V}{18}$                               c)  $\frac{5V}{9}$                               d)  $\frac{18V}{5}$
115. Which of the following is not a correct statement

- a) Resistivity of electrolytes decreases on increasing temperature  
 b) Resistance of mercury falls on decreasing its temperature  
 c) When joined in series a 40 W bulb glows more than a 60 W bulb  
 d) Resistance of 40 W bulb is less than the resistance of 60 W bulb
116. For a certain thermocouple the emf is  $E = aT + bT^2$ , where  $t$  (in°C) is the temperature of hot junction, the cold junction is at 0°C. The value of constants  $a$  and  $b$  are  $10 \times 10^{-6}$  and  $0.02 \times 10^{-6}$  respectively, then the temperature of inversion (in°C) will be  
 a) 150                                      b) 250                                      c) 500                                      d) 750

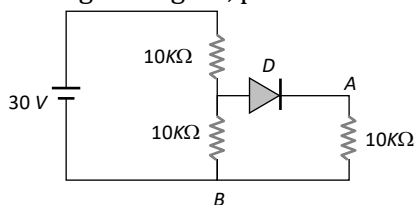
117. In the given figure, potential difference between A and B is



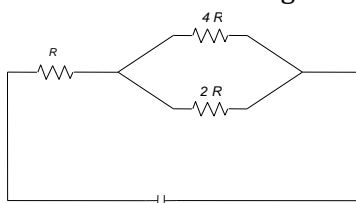- a) 0    b) 5 volt                                      c) 10 volt                                      d) 15 volt
118. A cell of emf  $E$  is connected across a resistance  $R$ . The potential difference between the terminals of the cell is found to be  $V$  volt. Then the internal resistance of the cell must be  
 a)  $(E-V)$                                       b)  $\frac{(E-V)}{V}R$                                       c)  $\frac{2(E-V)R}{E}$                                       d)  $\frac{2(E-V)V}{R}$
119. Electric field ( $E$ ) and current density ( $J$ ) have relation  
 a)  $E \propto J^{-1}$                                       b)  $E \propto J$                                       c)  $E \propto \frac{1}{J^2}$                                       d)  $E^2 \propto \frac{1}{J}$
120. In a network as shown in the figure, the potential difference across the resistance  $2R$  is (the cell has an emf of  $E$  volt and has no internal resistance)



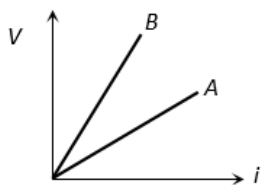- a)  $2E$     b)  $\frac{4E}{7}$     c)  $\frac{E}{7}$     d)  $E$
121. Two identical conductors maintained at same temperatures are given potential differences in the ratio 1 : 2. Then the ratio of their drift velocities is  
 a) 1 : 2    b) 3 : 2    c) 1 : 1    d) 1 : 2<sup>1/2</sup>
122. A 100 W bulb produces an electric field of 2.9 V/m at a point 3 m away. If the bulb is replaced by 400 W bulb without disturbing other conditions, then the electric field produced at the same point is  
 a) 2.9 V/m    b) 3.5 V/m    c) 5 V/m    d) 5.8 V/m
123. The neutral temperature  $t_n = 285^\circ\text{C}$  is constant for a Cu-Fe thermocouple. When the cold junction is at 0°C, the value of inversion temperature is  $t_i = 570^\circ\text{C}$  but if the cold junction is at 10°C, the inversion temperature ( $t_i$ ) will be  
 a) 550°C    b) 560°C    c) 570°C    d) 580°C
124. When a battery connected across a resistor of 16 Ω, the voltage across the resistor is 12 V. When the same battery is connected across a resistor of 10 Ω, voltage across it is 11V. The internal resistance of the battery (in ohm) is  
 a)  $\frac{10}{7}$     b)  $\frac{20}{7}$     c)  $\frac{25}{7}$     d)  $\frac{30}{7}$
125. For obtaining chlorine by electrolysis a current of 100 kW and 125 V is used. (Electro chemical equivalent of chlorine is  $0.367 \times \text{kgC}^{-1}$ ). The amount of chlorine obtained in one minute will be  
 a) 1.7616 g    b) 17.616 g    c) 0.17161 g    d) 1.7616 kg
126.  $V - i$  graphs for parallel and series combination of two identical resistors are as shown in figure. Which graph represents parallel combination



- a) A
- b) B
- c) A and B both
- d) Neither A nor B


127. As the temperature rises the resistance offered by metal

- a) Increase
- b) Decrease
- c) Remains same
- d) None of these

128. A wire 100cm long and 2.0 mm diameter has a resistance of 0.7 ohm, the electrical resistivity of the material is

- a)  $4.4 \times 10^{-6} \text{ ohm} \times m$
- b)  $2.2 \times 10^{-6} \text{ ohm} \times m$
- c)  $1.1 \times 10^{-6} \text{ ohm} \times m$
- d)  $0.22 \times 10^{-6} \text{ ohm} \times m$

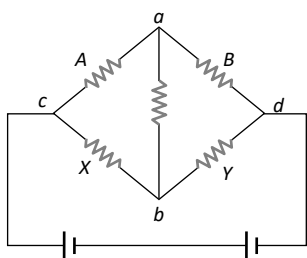129. In the Wheatstone's bridge (shown in figure)  $X = Y$  and  $A > B$ . The direction of the current between  $ab$  will be



- a) From a to b
- b) From b to a
- c) From b to a through c
- d) From a to b through c

130. The chemical equivalent of silver is 108. If the current in a silver voltmeter is 2 amp, the time required to deposit 27 grams of silver will be

- a) 8.57 hrs
- b) 6.70 hrs
- c) 3.35 hrs
- d) 12.50 hrs

131. By increasing the temperature, the specific resistance of a conductor and a semiconductor

- a) Increases for both
- b) Decreases for both
- c) Increases, decreases
- d) Decreases, increases

132. Two electric bulbs whose resistances are in the ratio of 1 : 2 are connected in parallel to a constant voltage source. The powers dissipated in them have the ratio

- a) 1 : 2
- b) 1 : 1
- c) 2 : 1
- d) 1 : 4

133. Two cells of same emf  $E$  but of different internal resistances  $r_1$  and  $r_2$  are connected in series with an external resistance  $R$ . The potential drop across the first cell is found to be zero. The external resistance  $R$  is

- a)  $r_1 + r_2$
- b)  $r_1 - r_2$
- c)  $r_2 - r_1$
- d)  $r_1 r_2$


134. A thermocouple is made from two metals, Antimony and Bismuth. If one junction of the couple is kept hot and the other is kept cold, then, an electric current will

- a) Flow from Antimony to Bismuth at the hot junction
- b) Flow from Bismuth to Antimony at the cold junction
- c) Not flow through the thermocouple
- d) Flow from Antimony to Bismuth at the cold junction


135. The resistivity of a wire

- a) Increase with the length of the wire
- b) Decreases with the area of cross-section
- c) Decreases with the length and increases with the cross-section of wire
- d) None of the above statement is correct

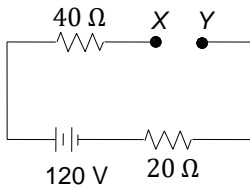
136. In the circuit shown figure potential difference between  $X$  and  $Y$  will be



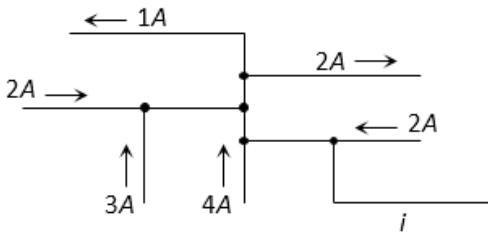- a) Zero                                      b) 20 V                                      c) 60 V                                      d) 120 V
137. Heat produced (cals) in a resistance  $R$  when a current  $I$  amperes flows through it for  $t$  seconds is given by the expression
- a)  $\frac{I^2 R t}{4.2}$                                       b)  $\frac{I R^2 t}{4.2}$                                       c)  $\frac{4.2 I R}{t^2}$                                       d)  $\frac{I R t^2}{4.2}$
138. Kirchoff's second law for the analysis of circuit is based on
- a) Conversion of charge                                      b) Conversion of energy  
c) Conversion of both charge and energy                                      d) Conversion of momentum of electron
139. A constant voltage is applied between the two ends of a uniform metallic wire. Some heat is developed in it. The heat developed is doubled if
- a) Both the length and radius of wire are halved                                      b) Both the length and radius of wire are doubled  
c) The radius of wire is doubled                                      d) The length of wire is doubled
140. If an increase in length of copper wire is 0.5% due to stretching, the percentage increase in its resistance will be
- a) 0.1%                                      b) 0.2%                                      c) 1%                                      d) 2%
141. The figure here shows a portion of a circuit. What are the magnitude and direction of the current  $i$  in the lower right-hand wire



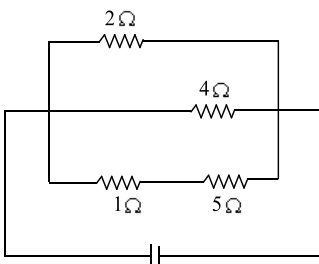- a) 7 A                                      b) 8 A                                      c) 6 A                                      d) 2 A
142. The current flowing through a wire depends on time as  $I = 3t^2 + 2t + 5$ . The charge flowing through the cross-section of the wire in time from  $t = 0$  to  $t = 2$  sec. is
- a) 22 C                                      b) 20 C                                      c) 18 C                                      d) 5 C
143. We have a galvanometer of resistance  $25\Omega$ . It is shunted by a  $2.5\Omega$  wire. The part of total current that flows through the galvanometer is given as
- a)  $\frac{I}{I_0} = \frac{1}{11}$                                       b)  $\frac{I}{I_0} = \frac{1}{10}$                                       c)  $\frac{I}{I_0} = \frac{3}{11}$                                       d)  $\frac{I}{I_0} = \frac{4}{11}$
144. A current of 3 amp. flows through the  $2\Omega$  resistor shown in the circuit. The power dissipated in the  $5\Omega$  resistor is




- a) 1 watt                                      b) 5 watt                                      c) 4 watt                                      d) 2 watt
145. One junction of a certain thermoelectric couple is at a fixed temperature  $T_r$  and the other junction is at temperature  $T$ . The thermo-electromotive force for this is expressed by  $E = k(T - T_r) \left[ T_0 - \frac{1}{2} (T + T_r) \right]$ .


At temperature  $T = \frac{1}{2} T_0$ , the thermoelectric power is

- a)  $\frac{1}{2}kT_0$                       b)  $kT_0$                       c)  $\frac{1}{2}kT_0^2$                       d)  $\frac{1}{2}k(T_0 - T_r)^2$

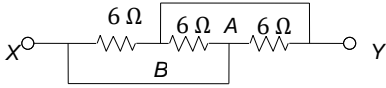
146. In a given network, each resistance has value of  $6\Omega$ . The point  $X$  is connected to point  $A$  by a copper wire of negligible resistance and point  $Y$  is connected to point  $B$  by the same wire. The effective resistance between  $X$  and  $Y$  will be



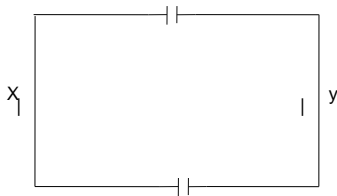- a)  $18\Omega$                       b)  $6\Omega$                       c)  $3\Omega$                       d)  $2\Omega$
147. Faraday's laws of electrolysis are related to
- a) The atomic number of positive ion                      b) The equivalent weight of electrolyte
- c) The atomic number of negative ion                      d) The velocity of positive ion
148. A cell having emf of  $1.5V$ , when connected across a resistance of  $14\Omega$ , produces a voltage of only  $1.4V$  across this resistance. The internal resistance of the cell must be
- a)  $1\Omega$                       b)  $14\Omega$                       c)  $15\Omega$                       d)  $21\Omega$
149. Two similar accumulators each of emf  $E$  and internal resistance  $r$  are connected as shown in the following figure. Then, the potential difference between  $x$  and  $y$  is



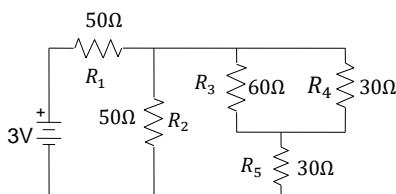- a)  $2E$                       b)  $E$                       c) Zero                      d) None of these
150. In a meter bridge experiment, the ratio of the left gap resistance to right gap resistance is  $2:3$ , the balance point from left is
- a)  $60\text{ cm}$                       b)  $50\text{ cm}$                       c)  $40\text{ cm}$                       d)  $20\text{ cm}$
151. A conductor wire having  $10^{29}$  free electrons/ $\text{m}^3$  carries a current of  $20A$ . If the cross-section of the wire is  $1\text{mm}^2$ , then the drift velocity of electrons will be
- a)  $6.25 \times 10^{-3}\text{ms}^{-1}$                       b)  $1.25 \times 10^{-5}\text{ms}^{-1}$                       c)  $1.25 \times 10^{-3}\text{ms}^{-1}$                       d)  $1.25 \times 10^{-4}\text{ms}^{-1}$
152. A potentiometer wire of length  $10\text{ m}$  and resistance  $20\Omega$  is connected in series with a  $15V$  battery and an external resistance  $40\Omega$ . A secondary cell of emf  $E$  in the secondary circuit is balanced by  $240\text{ cm}$  long the potentiometer wire. The emf  $E$  of the cell is
- a)  $2.4V$                       b)  $1.2V$                       c)  $2.0V$                       d)  $3V$
153. In circuit shown below, the resistances are given in ohm and the battery is assumed ideal with emf equal to  $3V$ . The voltage across the resistance  $R_4$  is



- a)  $0.4V$                       b)  $0.6V$                       c)  $1.2V$                       d)  $1.5V$
154. Constant current is flowing through a linear conductor of non-uniform area of cross-section. The charge flowing per second through the area of conductor at any cross-section is
- a) Proportional to the area of cross-section                      b) Inversely proportional to the area of cross-section
- c) Independent of the area of cross-section                      d) Dependent on the length of conductor
155. Total surface area of a cathode is  $0.05\text{m}^2$  and  $1\text{ A}$  current passes through it for  $1\text{ hour}$ . Thickness of nickle




deposited on the cathode is (Given that density of nickle =  $9g/cc$  and it's E.C.E. =  $3.04 \times 10^{-4} g/C$ )

- a)  $2.4 m$                       b)  $0.24 \mu m$                       c)  $2.4 \mu m$                       d) None of these

156. An AC generator of 220 V have internal resistance  $r = 10 \Omega$  and external resistance  $R = 100 \Omega$ . What is the power developed in the external circuit?

- a) 227 W                      b) 325 W                      c) 400 W                      d) 500 W

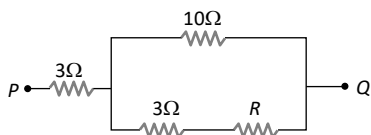157. In the circuit shown here, what is the value of the unknown resistor  $R$  so that the total resistance of the circuit between points  $P$  and  $Q$  is also equal to  $R$



- a) 3 ohm                      b)  $\sqrt{39}$  ohm                      c)  $\sqrt{69}$  ohm                      d) 10 ohm

158. The resistance of a wire is  $R$ . If the length of the wire is doubled by stretching, then the new resistance will be

- a)  $2R$                       b)  $4R$                       c)  $R$                       d)  $\frac{R}{4}$

159. By ammeter, which of the following can be measured

- a) Electric potential                      b) Potential difference                      c) Current                      d) Resistance

160. The maximum power drawn out of the cell from a source is given by (where  $r$  is internal resistance)

- a)  $E^2/2r$                       b)  $E^2/4r$                       c)  $E^2/r$                       d)  $E^2/3r$

161. The emf is thermocouple changes sign at 600 K. If the neutral temperature is  $210^\circ C$ , the temperature of cold junction is

- a) 180 K                      b) 117 K                      c)  $93^\circ C$                       d)  $90^\circ C$

162. How many minimum number of  $2 \Omega$  resistance can be connected to have an effective resistance of  $1.5 \Omega$ ?

- a) 3                      b) 2                      c) 4                      d) 6

163. Equal potentials are applied on an iron and copper wire of same length. In order to have the same current flow in the two wires, the ration  $r$  (iron)/ $r$  (copper) of their radii must be (Given that specific resistance of iron =  $1.0 \times 10^{-7} ohm - m$  and specific resistance of copper =  $1.7 \times 10^{-8} ohm - m$ )

- a) About 1.2                      b) About 2.4                      c) About 3.6                      d) About 4.8


164. A fuse wire of circuit cross-section and having diameter of 0.4 mm, allows 3 A of current to pass through it. But if another fuse wire of same material and circular cross-section and having diameter of 0.6 mm is taken, then the amount of current passed through the fuse is

- a) 3 A                      b)  $3 \times \sqrt{\frac{3}{2}}$  A                      c)  $3 \times \left(\frac{3}{2}\right)^{3/2}$  A                      d)  $3 \times \left(\frac{3}{2}\right)$  A

165. Two identical cells weather connected in parallel or in series gives the same current when connected to an external resistance  $1.5 \Omega$ . Find the value of internal resistance of each cell.

- a) 1  $\Omega$                       b) 0.5  $\Omega$                       c) Zero                      d) 1.5  $\Omega$

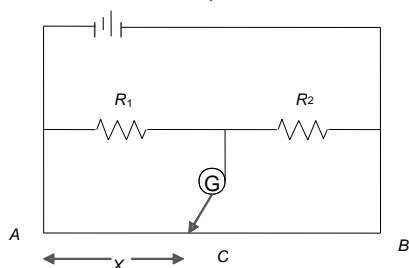
166. In the shown arrangement of the experiment of the meter bridge if  $AC$  corresponding to null deflection of galvanometer is  $x$ , what would be its value if the radius of the wire  $AB$  is doubled?




- a)  $x$                       b)  $x/4$                       c)  $4x$                       d)  $2x$

167. A current of two ampere is flowing through a cell of e. m. f. 5 volt and internal resistance 0.5 ohm from negative to positive electrode. If the potential of negative electrode is 10V, the potential of positive electrode will be

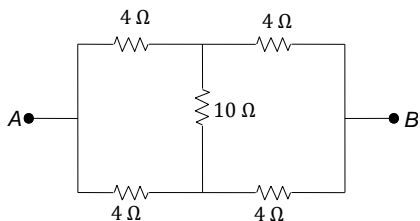
- a) 5 V                                      b) 14 V                                      c) 15 V                                      d) 16 V
168. Two bulbs 25 W, 220 V and 100 W, 220 V are given. Which has higher resistance?  
 a) 25 W bulb                                      b) 100 W bulb  
 c) Both bulbs will have equal resistance                                      d) Resistance of bulbs cannot be compared
169. The temperature of cold, hot junction of a thermocouple is  $0^{\circ}\text{C}$  and  $T^{\circ}\text{C}$  respectively. The thermo-emf produced is  $E = AT - \frac{1}{2} BT^2$ . If  $A = 16$ ,  $B = 0.080$ , the temperature of inversion will be  
 a)  $100^{\circ}\text{C}$                                       b)  $300^{\circ}\text{C}$                                       c)  $400^{\circ}\text{C}$                                       d)  $500^{\circ}\text{C}$
170. The equivalent resistance across A and B is



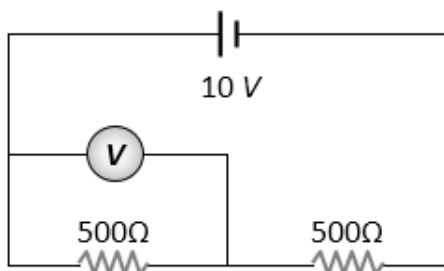- a)  $2\ \Omega$                                       b)  $3\ \Omega$                                       c)  $4\ \Omega$                                       d)  $5\ \Omega$
171. The length of a potentiometer wire is 5m. An electron in this wire experiences a force of  $4.8 \times 10^{-19}\text{N}$ , emf of the main cell used in potentiometer is  
 a) 3 V                                      b) 15 V                                      c) 1.5 V                                      d) 5 V
172. When a piece of aluminium wire of finite length is drawn through a series of dies to reduce its diameter to half its original value, its resistance will become  
 a) Two times                                      b) Four times                                      c) Eight times                                      d) Sixteen times
173. A voltmeter of resistance  $1000\ \Omega$  is connected across a resistance of  $500\ \Omega$  in the given circuit. What will be the reading of voltmeter



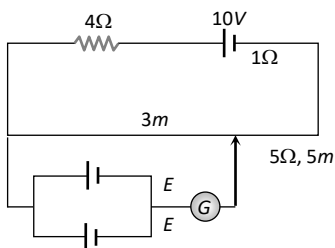- a) 1 V                                      b) 2 V                                      c) 6 V                                      d) 4V
174. A resistance of  $4\ \Omega$  and a wire of length 5 metres and resistance  $5\ \Omega$  are joined in series and connected to a cell of e.m.f. 10 V and internal resistance  $1\ \Omega$ . A parallel combination of two identical cells is balanced across 300 cm of the wire. The e.m.f.  $E$  of each cell is



- a) 1.5 V                                      b) 3.0 V                                      c) 0.67 V                                      d) 1.33 V
175. Current flows through a metallic conductor whose area of cross-section increases in the direction of the current. If we move in this direction,  
 a) The carrier density will change                                      b) The current will change  
 c) The drift velocity will decrease                                      d) The drift velocity will increase
176. The resistance will be least in a wire with dimension  
 a)  $L/2, 2A$                                       b)  $2L, A$                                       c)  $L, A$                                       d) None of these
177. At room temperature, copper has free electron density of  $8.4 \times 10^{28}$  per  $\text{m}^3$ . The copper conductor has a

cross-section of  $10^{-6}m^2$  and carries a current of 5.4 A. The electron drift velocity in copper is

- a) 400 m/s                      b) 0.4 m/s                      c) 0.4 mm/s                      d) 72 m/s

178. A battery is charged at a potential of 15 V in 8 hours when the current flowing is 10 A. The battery on discharge supplies a current of 5 A for 15 hours. The mean terminal voltage during discharge is 14 V. The "Watt – hour" efficiency of battery is

- a) 80%                      b) 90%                      c) 87.5%                      d) 82.5%


179. A combination of two resistance of 2 W and  $\frac{2}{3}$  W connected in parallel is joined across a battery of emf of 3 V and of negligible internal resistance. The energy given out per sec will be

- a)  $\frac{1}{2} \times 3 \times 3$  J                      b)  $\frac{1}{2} \times \frac{1}{3} \times 3 \times 3$  J                      c)  $2 \times 3$  J                      d)  $3 \times 3 \times 2$  J

180. The length of the wire is doubled. Its conductance will be


- a) Unchanged                      b) Halved  
c) Quadrupled                      d) 1/4 of the original value

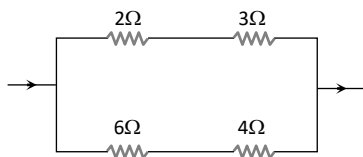181. In the circuit as shown in the figure, the heat produced by 6 ohm resistance due to current flowing in it is 60 calorie per second. The heat generated across 3 ohm resistance per second will be



- a) 30 calorie                      b) 60 calorie                      c) 100 calorie                      d) 120 calorie

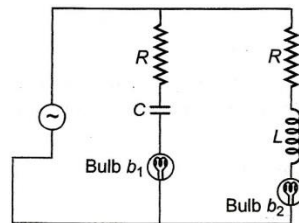182. Two identical incandescent light bulbs are connected as shown in the figure. When the circuit is an AC voltage source of frequency  $f$ , which of the following observations will be correct?



- a) Both bulbs will glow alternatively  
b) Both bulbs will glow with same brightness provided frequency  $f = \frac{1}{2\pi} \sqrt{(1/LC)}$   
c) Bulb  $b_1$  will light up initially and goes off, bulb  $b_2$  will be ON constantly  
d) Bulb  $b_1$  will blink and bulb  $b_2$  will be ON constantly


183. A wire of length 5m and radius 1 mm has a resistance of 1 ohm. What length of the wire of the same material at the same temperature and of radius 2 mm will also have a resistance of 1 ohm

- a) 1.25 m                      b) 2.5 m                      c) 10 m                      d) 20 m

184. It is possible that any some constant value of emf, but the potential difference between the plates is zero?

- a) Not, possible  
b) Yes, if another identical battery is joined in series  
c) Yes, if another identical battery is joined in opposition  
d) Yes, possible, if another similar battery is joined in parallel

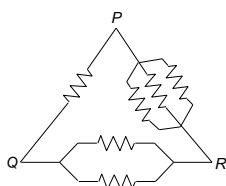185. Six equal resistances are connected between point s P, Q and R as shown in the figure. Then the net resistance will be maximum between




- a) P and Q                      b) Q and R                      c) P and R                      d) Any two points


186. When a  $12\Omega$  resistor is connected with a moving coil galvanometer then its deflection reduces from 50 divisions to 10 divisions. The resistance of the galvanometer is

- a) 24  $\Omega$                       b) 36  $\Omega$                       c) 48  $\Omega$                       d) 60  $\Omega$

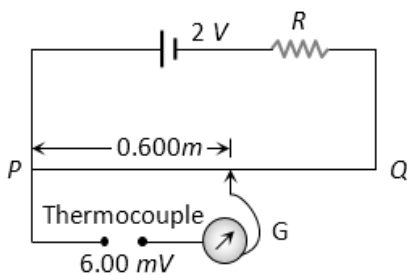
187. A galvanometer having a resistance of  $8\ \text{ohm}$  is shunted by a wire of resistance  $2\ \text{ohm}$ . If the total current is  $1\ \text{amp}$ , the part of it passing through the shunt will be  
 a)  $0.25\ \text{amp}$                       b)  $0.8\ \text{amp}$                       c)  $0.2\ \text{amp}$                       d)  $0.5\ \text{amp}$
188. Resistors of  $1, 2, 3\ \text{ohm}$  are connected in the form of a triangle. If a  $1.5\ \text{volt}$  cell of negligible internal resistance is connected across  $3\ \text{ohm}$  resistor, the current flowing through this resistance will be  
 a)  $0.25\ \text{amp}$                       b)  $0.5\ \text{amp}$                       c)  $1.0\ \text{amp}$                       d)  $1.5\ \text{amp}$
189. A galvanometer of resistance  $50\ \Omega$  is connected to a battery of  $3\text{V}$  along with a resistance of  $2950\ \Omega$  in series. A full scale deflection of  $30$  divisions is obtained in the galvanometer. In order to reduce this deflection to  $20$  divisions, the resistance in series should be  
 a)  $5050\ \Omega$                       b)  $5550\ \Omega$                       c)  $6050\ \Omega$                       d)  $4450\ \Omega$
190. If a  $30\ \text{V}, 90\ \text{W}$  bulb is to be worked on a  $120\ \text{V}$  line, a resistance of how many ohms should be connected in series with the bulb  
 a)  $10\ \text{ohm}$                       b)  $20\ \text{ohm}$                       c)  $30\ \text{ohm}$                       d)  $40\ \text{ohm}$
191.  $n$  equal resistors are first connected in series and then connected in parallel. What is the ratio of the maximum to the minimum resistance  
 a)  $n$                       b)  $\frac{1}{n^2}$                       c)  $n^2$                       d)  $\frac{1}{n}$
192. Figure shows a simple potentiometer circuit for measuring a small e.m.f. produced by a thermocouple. The meter wire  $PQ$  has a resistance  $5\ \Omega$  and the driver cell has an e.m.f. of  $2\ \text{V}$ . If a balance point is obtained  $0.600\text{m}$  along  $PQ$  when measuring an e.m.f. of  $6.00\ \text{mV}$ , what is the value of resistance  $R$



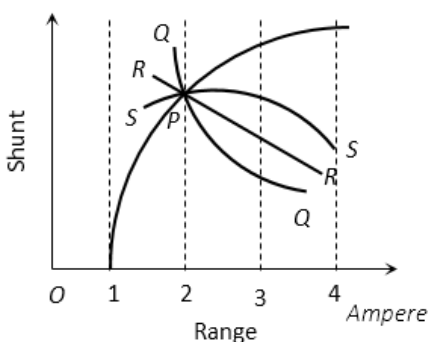- a)  $995\ \Omega$                       b)  $1995\ \Omega$                       c)  $2995\ \Omega$                       d) None of these
193. The ammeter has range  $1\ \text{ampere}$  without shunt. The range can be varied by using different shunt resistances. The graph between shunt resistance and range will have the nature



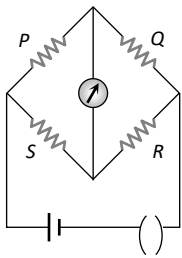- a)  $P$                       b)  $Q$                       c)  $R$                       d)  $S$
194. In a Wheatstone's network  $P = 2\ \Omega, Q = 2\ \Omega, R = 2\ \Omega$  and  $S = 3\ \Omega$ . The resistance with which  $S$  is to be shunted in order that the bridge may be balanced is  
 a)  $1\ \Omega$                       b)  $2\ \Omega$                       c)  $4\ \Omega$                       d)  $6\ \Omega$
195. In the Wheatstone's bridge shown,  $P = 2\ \Omega, Q = 3\ \Omega, R = 6\ \Omega$  and  $S = 8\ \Omega$ . In order to obtain balance, shunt resistance across ' $S$ ' must be



- a)  $2\ \Omega$                       b)  $3\ \Omega$                       c)  $6\ \Omega$                       d)  $8\ \Omega$

196. If an observer is moving with respect to a stationary electron, then he observes

- a) Only magnetic field      b) Only electric field      c) Both (a) and (b)      d) None of the above


197. If  $2.2\text{ kW}$  power is transmitted through a  $100\ \Omega$  line at  $22,000\text{ V}$ , the power loss in the form of heat will be

- a)  $0.1\text{ W}$                       b)  $1\text{ W}$                       c)  $10\text{ W}$                       d)  $100\text{ W}$

198. The resistance of a bulb filament is  $100\ \Omega$  at a temperature of  $100^\circ\text{C}$ . If its temperature coefficient of resistance be  $0.005\text{ per }^\circ\text{C}$ , its resistance will become  $200\ \Omega$  at a temperature of


- a)  $300^\circ\text{C}$                       b)  $400^\circ\text{C}$                       c)  $500^\circ\text{C}$                       d)  $200^\circ\text{C}$

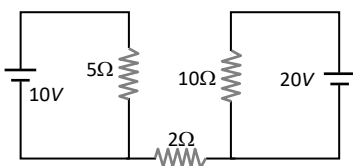199. Find out the value of current through  $2\ \Omega$  resistance for the given circuit



- a)  $5\text{ A}$                       b)  $2\text{ A}$                       c) Zero                      d)  $4\text{ A}$

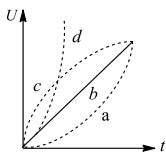200. Which of the plots shown in figure may represent the thermal energy produced in a resistor in a given time as a function of the electric current?



- a) *a*                      b) *b*                      c) *c*                      d) *d*

201. Two resistors of resistances  $200\text{ k}\Omega$  and  $1\text{ M}\Omega$  respectively form a potential divider with outer junctions maintained at potentials of  $+3\text{ V}$  and  $-15\text{ V}$ . Then, the potential at the junction between the resistors is

- a)  $+1\text{ V}$                       b)  $-0.6\text{ V}$                       c)  $0\text{ V}$                       d)  $-12\text{ V}$

202. In a Wheatstone bridge,  $P = 90\ \Omega$ ,  $Q = 110\ \Omega$ ,  $R = 40\ \Omega$  and  $S = 60\ \Omega$  and a cell of  $4\text{ V}$  emf. Then the potential difference between the diagonal along which a galvanometer is connected is

- a)  $-0.2\text{ V}$                       b)  $+0.2\text{ V}$                       c)  $-1\text{ V}$                       d)  $+1\text{ V}$

203. A thermo couple develops  $200\ \mu\text{ V}$  between  $0^\circ\text{C}$  and  $100^\circ\text{C}$ . If it develops  $64\ \mu\text{ V}$  and  $76\ \mu\text{ V}$  respectively between  $(0^\circ\text{C} - 32^\circ\text{C})$  and  $(32^\circ\text{C} - 70^\circ\text{C})$  then what will be the thermo emf it develops between  $70^\circ\text{C}$  and  $100^\circ\text{C}$

- a)  $65\ \mu\text{ V}$                       b)  $60\ \mu\text{ V}$                       c)  $55\ \mu\text{ V}$                       d)  $50\ \mu\text{ V}$


204. In a potentiometer arrangement, a cell of emf  $1.5\text{ V}$  gives a balance point at  $27\text{ cm}$  length of wire. If the cell is replaced by another cell and balance point shifts to  $54\text{ cm}$ , the emf of the second cell is

- a)  $3\text{ V}$                       b)  $1.5\text{ V}$                       c)  $0.75\text{ V}$                       d)  $2.25\text{ V}$

205. Which of the following is not reversible

- a) Joule effect                      b) Peltier effect                      c) Seebeck effect                      d) Thomson effect

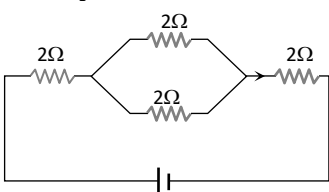206. The equivalent resistance of the circuit shown in the figure is



- a)  $8\ \Omega$                       b)  $6\ \Omega$                       c)  $5\ \Omega$                       d)  $4\ \Omega$

207. A battery having e.m.f.  $5\text{ V}$  and internal resistance  $0.5\ \Omega$  is connected with a resistance of  $4.5\ \Omega$  then the

voltage at the terminals of battery is

- a) 4.5 V                      b) 4 V                      c) 0 V                      d) 2 V

208. If the electric current through an electric bulb is 3.2 A, the number of electrons flow through it in one second is

- a)  $2 \times 10^9$                       b)  $2 \times 10^{19}$                       c)  $3.2 \times 10^{19}$                       d)  $1.6 \times 10^{18}$

209. Two tangent galvanometer A and B are identical except in their number of turns. They are connected in series. On passing a current through them, deflections of  $60^\circ$  and  $30^\circ$  are produced. The ratio of the number of units A and B is

- a) 1:3                      b) 3:1                      c) 1:2                      d) 2:1

210. A solenoid is at potential difference of 60 V and current flowing through it is 15 ampere, then the resistance of coil will be

- a) 4Ω                      b) 8Ω                      c) 0.25Ω                      d) 2Ω


211. A 50 ohm galvanometer gets full scale deflection when a current of 0.01 A passes through the coil. When it is converted to a 10 A ammeter, the shunt resistance is

- a) 0.01 Ω                      b) 0.05 Ω                      c) 2000 Ω                      d) 5000 Ω

212. Sensitivity of potentiometer can be increased by

- a) Increasing the e.m.f. of the cell  
 b) Increasing the length of the potentiometer wire  
 c) Decreasing the length of the potentiometer wire  
 d) None of the above

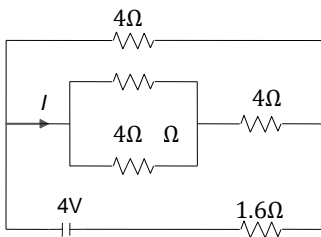213. In the circuit shown the value of  $I$  in ampere is



- a) 1                      b) 0.60                      c) 0.4                      d) 1.5

214. A moving coil galvanometer of resistance 100Ω is used as an ammeter using a resistance 0.1Ω. The maximum deflection current in the galvanometer is  $100\mu\text{A}$ . Find the minimum current in the circuit so that the ammeter shows maximum deflection

- a) 100.1mA                      b) 1000.1mA                      c) 10.01mA                      d) 1.01mA


215. When two identical batteries of internal resistance 1 Ω each are connected in series across a resistor  $R$ , the rate of heat produced in  $R$  is  $J_1$ . When the same batteries are connected in parallel across  $R$ , the rate is  $J_2$ . If  $J_1 = 2.25 J_2$  then the value of  $R$  in Ω is

- a) 4                      b) 6                      c) 4.8                      d) 5.16

216. A metal wire is subjected to a constant potential difference. When the temperature of the metal wire increases, the drift velocity of the electron in it

- a) increases, thermal velocity of the electron decreases  
 b) Decreases, thermal velocity of the electron decreases  
 c) increases, thermal velocity of the electron increases  
 d) Decreases, thermal velocity of the electron increases

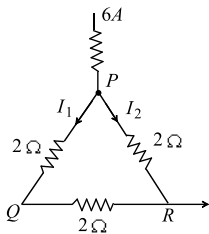217. A current of 6A enters one corner  $P$  of an equilateral triangle  $PQR$  having 3 wires of resistances 2Ω each and leaves by the corner  $R$ . Then the current  $I_1$  and  $I_2$  are



- a) 2A, 4A                      b) 4A, 2A                      c) 1A, 2A                      d) 2A, 3A


218. There is a current of 0.21 A in a copper wire whose area of cross-section is  $10^{-6} \text{m}^2$ . If the number of free electrons per  $\text{m}^3$  is  $8.4 \times 10^{28}$ , then find the drift velocity, ( $e = 1.6 \times 10^{-19} \text{C}$ )

- a)  $2 \times 10^{-5} \text{ms}^{-1}$                       b)  $1.56 \times 10^{-5} \text{ms}^{-1}$                       c)  $1 \times 10^{-5} \text{ms}^{-1}$                       d)  $0.64 \times 10^{-5} \text{ms}^{-1}$

219. If 2.2 kilowatt power is transmitted through a 10 ohm line at 22000 volt, the power loss in the form of heat will be

- a) 0.1 watt                      b) 1 watt                      c) 10 watt                      d) 100 watt

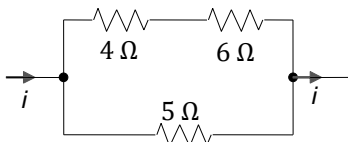220. In the circuit shown in figure the heat produced in the  $5\Omega$  resistor due to the current flowing through it is  $100 \text{Js}^{-1}$ . The heat generated in the  $4\Omega$  resistor is



- a)  $10 \text{Js}^{-1}$                       b)  $20 \text{Js}^{-1}$                       c)  $30 \text{Js}^{-1}$                       d)  $40 \text{Js}^{-1}$

221. Two copper wires have their masses in the ratio 2 : 3 and the lengths in the ratio 3 : 4 the ratio of their resistance is

- a) 4 : 9                      b) 27 : 32                      c) 16 : 9                      d) 27 : 128

222. A battery of emf E and internal resistance r is connected to an external resistance R the condition for maximum power transfer is

- a)  $r < R$                       b)  $r > R$                       c)  $r = 1/R$                       d)  $R = R$

223. The cold junction of a thermocouple is maintained at  $10^\circ\text{C}$ . No thermo e.m.f. is developed when the hot junction is maintained at  $530^\circ\text{C}$ . The neutral temperature is

- a)  $260^\circ\text{C}$                       b)  $270^\circ\text{C}$                       c)  $265^\circ\text{C}$                       d)  $520^\circ\text{C}$


224. An electric heater boils 1 kg of water in a time  $t_1$ . Another heater boils the same amount of water in a time  $t_2$ . When the two heaters are connected in parallel, the time required by them together to boil the same amount of water is

- a)  $t_1 + t_2$                       b)  $t_1 t_2$                       c)  $\frac{t_1 + t_2}{2}$                       d)  $\frac{t_1 t_2}{t_1 + t_2}$

225. A voltmeter having a resistance of 998 ohm is connected to a cell of e.m.f. 2 volt and internal resistance 2 ohm. The error in the measurement of e.m.f. will be


- a)  $4 \times 10^{-1} \text{volt}$                       b)  $2 \times 10^{-3} \text{volt}$                       c)  $4 \times 10^{-3} \text{volt}$                       d)  $2 \times 10^{-1} \text{volt}$

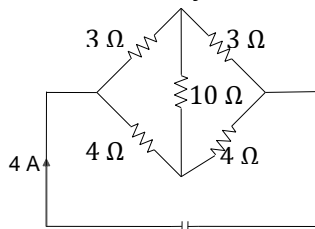226. In the circuit shown, if the  $10\Omega$  resistance is replaced by  $20\Omega$  then what is the amount of current drawn from the battery?



- a) 2.5A                      b) 3A                      c) 3.5A                      d) 4A

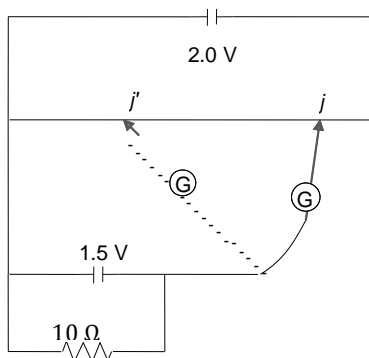227. The figure below shows a 2.0 V potentiometer used for the determination of internal resistance of a 2.5 V cell. The balance point of the cell in the open circuit is 75cm. When a resistor of  $10\Omega$  is used in the external circuit of the cell, the balance point shifts to 65 cm length of potentiometer wire. Then the internal resistance of the cell is



- a)  $2.5 \Omega$                       b)  $2.0 \Omega$                       c)  $1.54 \Omega$                       d)  $1.0 \Omega$
228. A battery of 24 cells, each of emf  $1.5 \text{ V}$  and internal resistance  $2\Omega$  is to be connected in order to send the maximum current through a  $12\Omega$  resistor. The correct arrangement of cells will be
- a) 2 rows of 12 cells connected in parallel                      b) 3 rows of 8 cells connected in parallel  
c) 4 rows of 6 cells connected in parallel                      d) All of these
229. A cell of emf  $E$  and internal resistance  $r$  supplies currents for the same time  $t$  through external resistance  $R_1 = 100 \Omega$  and  $R_2 = 40 \Omega$  separately. If the heat developed in both the cases is the same, then the internal resistance of the cell is given by
- a)  $28.6 \Omega$                       b)  $70 \Omega$                       c)  $63.3 \Omega$                       d)  $140 \Omega$
230. Incandescent bulbs are designed by keeping in mind that the resistance of their filament increases with the increase in temperature. If at room temperature,  $100 \text{ W}$ ,  $60 \text{ W}$  and  $40 \text{ W}$  bulbs have filament resistances  $R_{100}$ ,  $R_{60}$  and  $R_{40}$ , respectively, the relation between these resistances is
- a)  $\frac{1}{R_{100}} = \frac{1}{R_{40}} + \frac{1}{R_{60}}$                       b)  $R_{100} = R_{40} + R_{60}$                       c)  $R_{100} > R_{60} > R_{40}$                       d)  $\frac{1}{R_{100}} > \frac{1}{R_{60}} > \frac{1}{R_{40}}$
231. In a potentiometer circuit there is a cell of e.m.f.  $2 \text{ volt}$ , a resistance of  $5 \text{ ohm}$  and a wire of uniform thickness of length  $1000 \text{ cm}$  and resistance  $15 \text{ ohm}$ . The potential gradient in the wire is
- a)  $\frac{1}{500} \text{ V/cm}$                       b)  $\frac{3}{2000} \text{ V/cm}$                       c)  $\frac{3}{5000} \text{ V/cm}$                       d)  $\frac{1}{1000} \text{ V/cm}$
232. Equal amounts of a metal are converted into cylindrical wire of different lengths  $L$  and cross-sectional area  $A$ . The wire with the maximum resistance is the one, which has
- a) Length= $L$  and area =  $A$   
b) lengths =  $\frac{L}{2}$  and area =  $2A$   
c) lengths =  $2L$  and area =  $\frac{A}{2}$   
d) All have the same resistance, as the amount of the metal is the same
233. Amount of electricity required to pass through the  $\text{H}_2\text{O}$  voltmeter so as to liberate  $11.2 \text{ litre}$  of hydrogen will be
- a)  $1 \text{ faraday}$                       b)  $\frac{1}{2} \text{ faraday}$                       c)  $2 \text{ faraday}$                       d)  $3 \text{ faraday}$
234. Five cells each of internal resistances  $0.2\Omega$  and emf  $2 \text{ V}$  are connected in series with a resistance of  $4\Omega$ . The current through the external resistance is
- a)  $4 \text{ A}$                       b)  $2 \text{ A}$                       c)  $1 \text{ A}$                       d)  $0.5 \text{ A}$
235. 3 identical bulbs are connected in series and these together dissipate a power  $P$ . If now the bulbs are connected in parallel, then the power dissipated will be
- a)  $\frac{P}{3}$                       b)  $3P$                       c)  $9P$                       d)  $\frac{P}{9}$
236. How many coulombs of electric charge must pass through acidulated water in order to release  $22.4 \text{ L}$  Of hydrogen at NTP?
- a)  $96500 \text{ Faraday}$                       b)  $193000 \text{ coulomb}$                       c)  $196500 \text{ Faraday}$                       d)  $96500 \text{ coulomb}$
237. Two identical cells connected in series send  $1.0 \text{ A}$  current through a  $5\Omega$  resistor. When they are connected in parallel, they send  $0.8 \text{ A}$  current through the same resistor. What is the internal resistance of the cell?




- a)  $0.5 \Omega$                       b)  $1.0 \Omega$                       c)  $1.5 \Omega$                       d)  $2.5 \Omega$

238. Which of the following is not equal to watt

- a)  $(Amp)^2 \times ohm$               b)  $Amp/Volt$                       c)  $Amp \times Volt$                       d)  $Joule/sec$

239. The current in the given circuit is

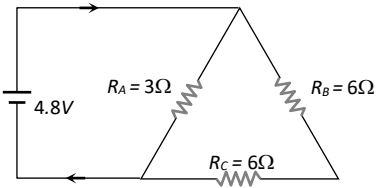

- a)  $8.31 A$                       b)  $6.82 A$                       c)  $4.92 A$                       d)  $2 A$


240. A lamp having tungsten filament consumes  $50 W$ . Assume the temperature coefficient of resistance for tungsten is  $4.5 \times 10^{-3} \text{ } ^\circ\text{C}^{-1}$  and temperature of the surrounding is  $20^\circ\text{C}$ . When the lamp burns, the temperature of its filament becomes  $2500^\circ\text{C}$ , then the power consumed at the moment switch is on, is

- a)  $608 W$                       b)  $710 W$                       c)  $215 W$                       d)  $580 W$

241. A wire of resistance  $R$  is divided in 10 equal parts. These parts are connected in parallel, the equivalent resistance of such connection will be

- a)  $0.01 R$                       b)  $0.1 R$                       c)  $10 R$                       d)  $100 R$

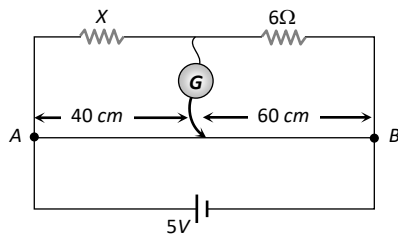242. In the circuit shown, a meter bridge is in its balanced state. The meter bridge wire has a resistance  $0.1 \text{ ohm/cm}$ . The value of unknown resistance  $X$  and the current drawn from the battery of negligible resistance is



- a)  $6 \Omega, 5 \text{ amp}$                       b)  $10 \Omega, 0.1 \text{ amp}$                       c)  $4 \Omega, 1.0 \text{ amp}$                       d)  $12 \Omega, 0.5 \text{ amp}$

243.  $Emf$  is most closely related to

- a) Mechanical force              b) Potential difference              c) Electric field                      d) Magnetic field

244. An electron (charge =  $1.6 \times 10^{-19} \text{ coulomb}$ ) is moving in a circle of radius  $5.1 \times 10^{-11} \text{ m}$  at a frequency of  $6.8 \times 10^{15} \text{ revolutions/sec}$ . The equivalent current is approximately

- a)  $5.1 \times 10^{-3} \text{ amp}$               b)  $6.8 \times 10^{-3} \text{ amp}$               c)  $1.1 \times 10^{-3} \text{ amp}$               d)  $2.2 \times 10^{-3} \text{ amp}$

245. The drift velocity of free electrons in a conductor is ' $v$ ' when a current ' $i$ ' is flowing in it. If both the radius and current are doubled, then drift velocity will be

- a)  $v$                       b)  $\frac{v}{2}$                       c)  $\frac{v}{4}$                       d)  $\frac{v}{8}$


246. If a steady current of  $100 A$  is passed then how much time is taken to deposit  $0.254 \text{ kg}$  of copper on the cathode of copper voltmeter. Use the known value of Faraday constant and relative atomic mass of copper is  $63.5$ .

- a)  $15440 \text{ s}$                       b)  $7720 \text{ s}$                       c)  $3760 \text{ s}$                       d)  $5480 \text{ s}$

247. Two similar cells, whether joined in series or in parallel, have the same current through an external resistance of  $2 \Omega$ . The internal resistance of each cell is

- a)  $1 \Omega$                       b)  $2 \Omega$                       c)  $0.5 \Omega$                       d)  $1.5 \Omega$

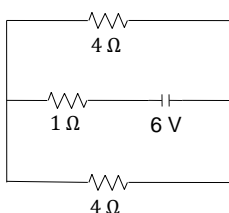248. The current in the  $1\Omega$  resistor shown in the circuit is



a)  $\frac{2}{3}A$

b) 3A

c) 6A

d) 2A

249. An electric heater of 1.08 Kw is immersed in water. After the water has reached a temperature of 100°C, how much time will be required to produce 100 g of steam?

a) 420 s

b) 210 s

c) 105 s

d) 50 s

250. How many calories of heat will be produced approximately in a 210 W electric bulb in 5 min?


a) 80000 cal

b) 63000 cal

c) 1050 cal

d) 15000 cal

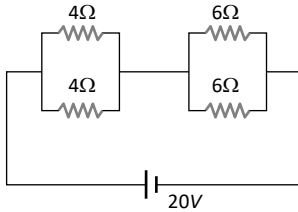251. Four resistances are connected in a circuit in the given figure. The electric current flowing through 4 ohm and 6 ohm resistance is respectively




a) 2 amp and 4 amp

b) 1 amp and 2 amp

c) 1 amp and 1 amp

d) 2 amp and 2 amp

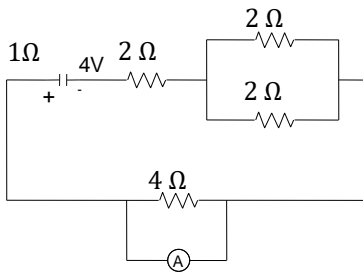252. The current passing through the ideal ammeter in the circuit given below is




a) 1.25A

b) 1A

c) 0.75A

d) 0.5A

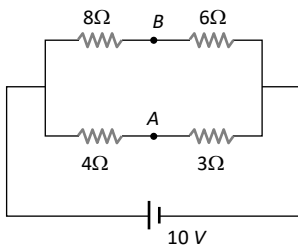253. The potential difference between point A & B is



a)  $\frac{20}{7}V$

b)  $\frac{40}{7}V$

c)  $\frac{10}{7}V$

d) 0

254. According to Joule's law, if the potential difference across a conductor having a material of specific resistance remains constant, then the heat produced in the conductor is directly proportional to


a)  $\rho$

b)  $\rho^2$

c)  $\frac{1}{\sqrt{\rho}}$

d)  $\frac{1}{\rho}$

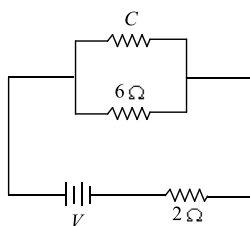255. If power dissipated in the 9 Ω resistor in the circuit shown is 36 Watt, the potential difference across the 2 Ω resistor is



a) 2 volt

b) 4 volt

c) 8 volt

d) 10 volt

256. The resistor of resistance R is connected to 25 V supply and heat produced in it is 25 Js<sup>-1</sup>. The value of R is


a) 225 Ω

b) 1 Ω

c) 25 Ω

d) 50 Ω

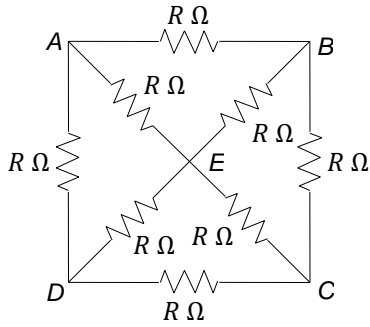257. The resistance between the points *A* and *C* in the figure below is



- a)  $R \Omega$                       b)  $\frac{4}{3} \Omega$                       c)  $\frac{2}{3} R\Omega$                       d)  $\frac{8R}{3}$


258. The deflection in a moving coil galvanometer is reduced to half when it is shunted with a  $40 \Omega$  coil. The resistance of the galvanometer is

- a)  $15 \Omega$                       b)  $20 \Omega$                       c)  $40 \Omega$                       d)  $80 \Omega$

259. The resistance of a cell does not depend on


- a) Current drawn from the cell                      b) Temperature of electrolyte  
c) Concentration of electrolyte                      d) The *e.m.f.* of the cell

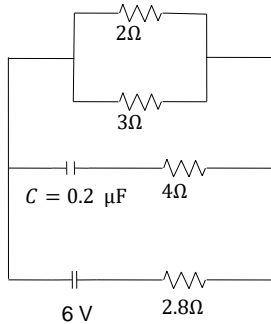260. In the given figure the steady state current in the circuit is



- a) Zero                      b)  $0.6A$                       c)  $0.9A$                       d)  $1.5A$

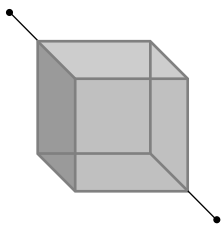261. Twelve wires of equal length and same cross-section are connected in the form of a cube. If the resistance of each of the wires is  $R$ , then the effective resistance between the two diagonal ends would be




- a)  $2 R$                       b)  $12 R$                       c)  $\frac{5}{6} R$                       d)  $8 R$

262. The length of a conductor is doubled and its radius is halved, its specific resistance is

- a) Unchanged                      b) Halved                      c) Doubled                      d) Quadrupled

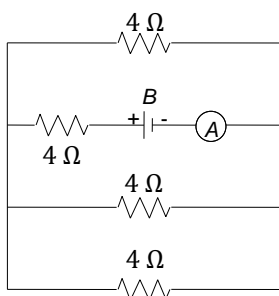263. Four identical resistors of  $4 \Omega$  each are joined in circuit as shown in figure. The cell *B* has emf  $2V$  and its internal resistance is negligible. The ammeter reading is




a)  $\frac{3}{8}A$

b)  $2A$

c)  $\frac{1}{2}A$

d)  $\frac{1}{8}A$

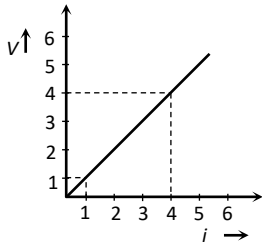264. Variation of current and voltage in a conductor has been shown in the diagram below. The resistance of the conductor is



a)  $4\text{ ohm}$

b)  $2\text{ ohm}$

c)  $3\text{ ohm}$

d)  $1\text{ ohm}$

265. Resistance of rod is  $1\ \Omega$ . It is bent in form of square. What is resistance across adjoint corners?

a)  $1\ \Omega$

b)  $3\ \Omega$

c)  $\frac{3}{16}\ \Omega$

d)  $\frac{3}{4}\ \Omega$

266. The Avogadro's number is  $6 \times 10^{23}$  per gm mole and electronic charge is  $1.6 \times 10^{-19}C$ . The Faraday's number is


a)  $6 \times 10^{23} \times 1.6 \times 10^{-19}$

b)  $\frac{6 \times 10^{23}}{1.6 \times 10^{-19}}$

c)  $\frac{2}{6 \times 10^{23} \times 1.6 \times 10^{-19}}$

d)  $\frac{1.6 \times 10^{-19}}{6 \times 10^{23}}$

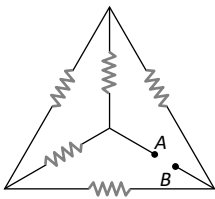267. In the network shown in the figure, each of the resistance is equal to  $2\ \Omega$ . The resistance between the points A and B is



a)  $1\ \Omega$

b)  $4\ \Omega$

c)  $3\ \Omega$

d)  $2\ \Omega$

268. The temperature of cold junction of thermo-couple is  $0^\circ C$ . If the neutral temperature is  $270^\circ C$ , then the inversion temperature is

a)  $540^\circ C$

b)  $520^\circ C$

c)  $640^\circ C$

d)  $580^\circ C$

269. The mobility of free electrons (charge  $e$ , mass  $m$  and relaxation time  $\tau$ ) in a metal is proportional to


a)  $\frac{e}{m}\tau$

b)  $\frac{m}{e}\tau$

c)  $\frac{e}{m\tau}$

d)  $\frac{m}{e\tau}$

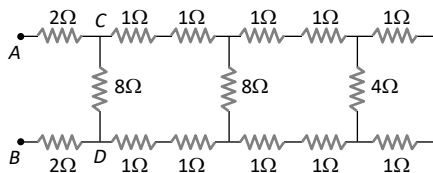270. In the figure shown, the total resistance between A and B is




a)  $12\ \Omega$

b)  $4\ \Omega$

c)  $6\ \Omega$

d)  $8\ \Omega$

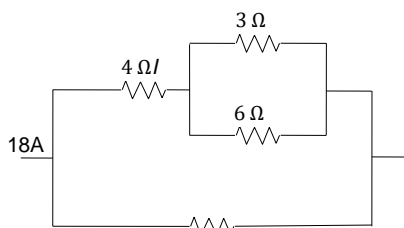271. In the electrical network shown in the figure, the potential difference across  $3\ \Omega$  resistance will be



a)  $12V$

b)  $2.4V$

c)  $24V$

d)  $36V$

272. If  $n$ ,  $e$ ,  $\tau$  and  $m$  respectively represent the density, charge relaxation time and mass of the electron, then the resistance of a wire of length  $l$  and area of cross-section  $A$  will be


a)  $\frac{ml}{ne^2\tau A}$

b)  $\frac{m\tau^2 A}{ne^2 l}$

c)  $\frac{ne^2\tau A}{2ml}$

d)  $\frac{ne^2 A}{2m\tau l}$

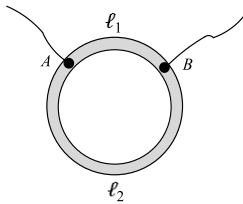273. A ring is made of a wire having a resistance  $R_0 = 12\Omega$ . Find the points  $A$  and  $B$  as shown in the figure, at which a current carrying conductor should be connected so that the resistance  $R$  of the sub circuit between these points is equal to  $\frac{8}{3}\Omega$



a)  $\frac{l_1}{l_2} = \frac{5}{8}$

b)  $\frac{l_1}{l_2} = \frac{1}{3}$

c)  $\frac{l_1}{l_2} = \frac{3}{8}$

d)  $\frac{l_1}{l_2} = \frac{1}{2}$

274. When a Daniel cell is connected in the secondary circuit of a potentiometer, the balancing length is found to be 540 cm. If the balancing length becomes 500 cm when the cell is short circuited with  $1\Omega$ , the internal of the cell is


a)  $0.08\Omega$

b)  $0.04\Omega$

c)  $1.0\Omega$

d)  $1.08\Omega$

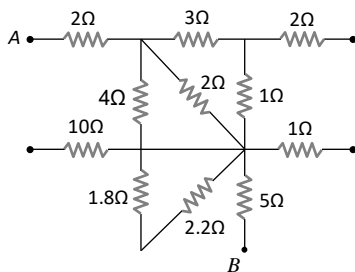275. What is the equivalent resistance between the points  $A$  and  $B$  of the network



a)  $\frac{57}{7}\Omega$

b)  $8\Omega$

c)  $6\Omega$

d)  $\frac{57}{5}\Omega$

276. An electric water kettle rated 2.1 kW is filled with 1.5 kg of water at  $20^\circ\text{C}$ . How many seconds does it take to reach the boiling point of water? Assume that there are no heat losses from the kettle. Specific heat capacity of water is  $4200\text{ Jkg}^{-1}\text{ K}^{-1}$

a) 60

b) 120

c) 240

d) 480

277. A cell can be balanced against 110cm and 100cm of potentiometer wire, respectively with and without being short circuited through a resistance of  $10\Omega$ . Its internal resistance is

a)  $1.0\Omega$

b)  $0.5\Omega$

c)  $2.0\Omega$

d) Zero

278. Kirchhoff's I law and II law of current, prove the

a) Conservation of charge and energy

b) Conservation of current and energy

c) Conservation of mass and charge

d) None of these

279. The resistivity of iron is  $1 \times 10^{-7}\text{ ohm} - \text{m}$ . The resistance of a iron wire of particular length and thickness is  $1\text{ ohm}$ . If the length and the diameter of wire both are doubled, then the resistivity in  $\text{ohm} - \text{m}$  will be


a)  $1 \times 10^{-7}$

b)  $2 \times 10^{-7}$

c)  $4 \times 10^{-7}$

d)  $8 \times 10^{-7}$

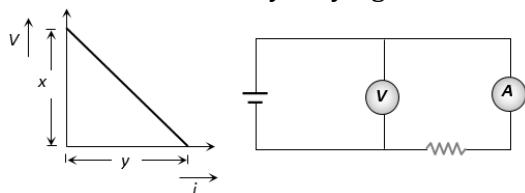280. In an experiment, a graph was plotted of the potential difference  $V$  between the terminals of a cell against the circuit current  $i$  by varying load rheostat. Internal conductance of the cell is given by



a)  $xy$

b)  $\frac{y}{x}$

c)  $\frac{x}{y}$


d)  $(x - y)$

281. For a thermocouple the neutral temperature is  $270^\circ\text{C}$  when its cold junction is at  $20^\circ\text{C}$ . What will be the neutral temperature and the temperature of inversion when the temperature of cold junction is increased

to 40°C

- a) 290°C, 580°C                      b) 270°C, 580°C                      c) 270°C, 500°C                      d) 290°C, 540°C

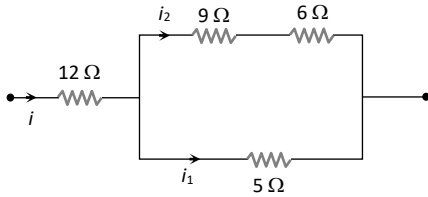282. In the following circuit, 5Ω resistor develops 45 J/s due to current flowing through it. The power developed per second across 12 Ω resistor is



- a) 16 W                                      b) 192 W                                      c) 36 W                                      d) 64 W

283. A current of  $\left(\frac{2}{3}\right)$  A produces a deflection of 60° in a tangent galvanometer. The reduction factor is

- a)  $\left(\frac{2}{3}\right)$  A                                      b) 2A                                      c)  $\left(\frac{2}{3}\right)$  A                                      d)  $\left(\frac{2}{\sqrt{3}}\right)$  A

284. Two sources of equal emf are connected to an external resistance  $R$ . The internal resistances of the two sources are  $R_1$  and  $R_2$  ( $R_2 > R_1$ ). If the potential difference across the source having internal resistance  $R_2$  is zero, then

- a)  $R = R_1 R_2 / (R_1 + R_2)$                                       b)  $R = R_1 R_2 / (R_2 - R_1)$   
 c)  $R = R_2 \times (R_1 + R_2) / (R_2 - R_1)$                                       d)  $R = R_2 - R_1$

285. Which of the following has a negative temperature coefficient

- a) C                                      b) Fe                                      c) Mn                                      d) Ag


286. A cell supplies a current  $i_1$  through a resistance  $R_1$  and a current  $i_2$  through a resistance  $R_2$ . The internal resistance of a cell is

- a)  $R_2 - R_1$                                       b)  $\frac{(i_1 + i_2)}{i_1 - i_2} R_1 R_2$                                       c)  $\frac{i_1 R_2 - i_2 R_1}{i_1 - i_2}$                                       d)  $\frac{i_2 R_2 - i_1 R_1}{i_1 - i_2}$

287. Two ends of a conductor are at different temperatures the electromotive force generated between two ends is


- a) Seebeck electro motive force (e.m.f.)                                      b) Peltier electro motive force (e.m.f.)  
 c) Thomson electro motive force (e.m.f.)                                      d) None of these

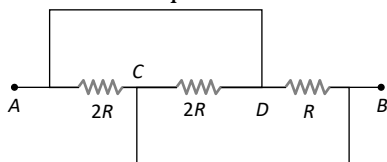288. What is the equivalent resistance between A and B



- a)  $\frac{2}{3}R$                                       b)  $\frac{3}{2}R$                                       c)  $\frac{R}{2}$                                       d) 2R

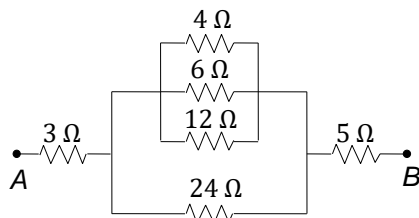289. The effective resistance between points A and B in figure




- a) 10 Ω                                      b) 12 Ω                                      c) 9.85 Ω                                      d) 10.85 Ω

290. The current density (number of free electrons per m<sup>3</sup>) in metallic conductor is of the order of

- a) 10<sup>22</sup>                                      b) 10<sup>24</sup>                                      c) 10<sup>26</sup>                                      d) 10<sup>28</sup>

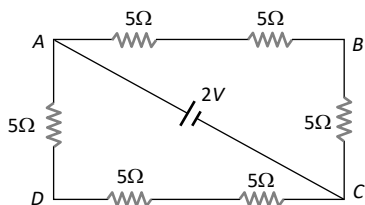291. The potential difference between points A and B of adjoining figure is




- a)  $\frac{2}{3}V$                       b)  $\frac{8}{9}V$                       c)  $\frac{4}{3}V$                       d)  $2V$

292. The potential gradient along the length of a uniform wire is  $10V\text{m}^{-1}$ . The length of the potentiometer wire is 4 m. What is the potential difference across two points on the wire separated by 50cm?


- a) 2.5 V                      b) 5.0 V                      c) 1.25 V                      d) 4.0 V

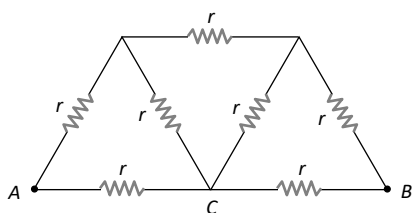293. In the circuit shown, the value of each resistance is  $r$ , then equivalent resistance of circuit between points A and B will be



- a)  $(4/3)r$                       b)  $3r/2$                       c)  $r/3$                       d)  $8r/7$

294. For the circuit shown in the figure

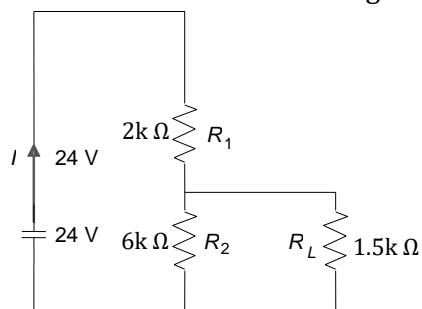

- a) The current  $I$  through the battery is 7.5mA                      b) The potential difference across  $R_L$  is 18 V  
 If  $R_1$  and  $R_2$  are interchanged, magnitude of the  
 c) Ratio of powers dissipated in  $R_1$  and  $R_2$  is 3                      d) power dissipated in  $R_L$  will decrease by a factor of 9

295. A brass rectangular plate  $12\text{cm} \times 3\text{cm}$  is to be electroplated with copper. If we wish to coat it with a layer of 0.02 mm thick both sides, how much time will it take with a constant current of 5A? Given ECE of copper is  $33 \times 10^{-5} \text{g C}^{-1}$  and density of copper is  $8.9 \text{g cm}^{-3}$ .

- a) 388 s                      b) 776 s                      c) 400 s                      d) 800 s


296. You are given several identical resistances each of value  $R = 10\Omega$  and each capable of carrying maximum current of 1 ampere. It is required to make a suitable combination of these resistances to produce a resistance of  $5\Omega$  which can carry a current of 4 ampere. The minimum number of resistances of the type  $R$  that will be required for this job

- a) 4                      b) 10                      c) 8                      d) 20


297. A 12 V lead accumulator is being charged using 24 V supply with an external resistance  $2\Omega$ . The internal resistance of the accumulator is  $1\Omega$ . Find the time in which it will store 360 W-hour energy

- a) 1 hr                      b) 7.5 hr                      c) 10 hr                      d) None of these

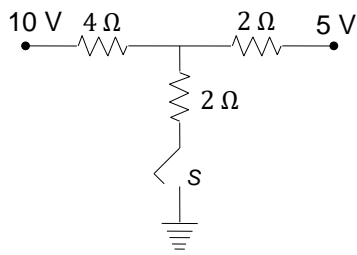
298. As the switch  $S$  is closed in the circuit shown in figure, current passed through it is



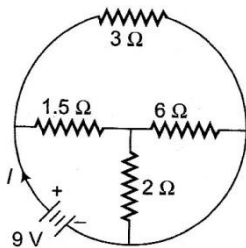- a) Zero                                      b) 1 A                                      c) 2 A                                      d) 1.6 A
299. If nearly  $10^5$  C liberate 1 g equivalent of aluminium, then the amount of aluminium (equivalent weight 9) deposited through electrolysis in 20 min by a current of 50 A will be  
 a) 0.09 g                                      b) 0.6 g                                      c) 5.4 g                                      d) 10.8 g
300. Potential gradient is defined as  
 a) Fall of potential per unit length of the wire  
 b) Fall of potential per unit area of the wire  
 c) Fall of potential between two ends of the wire  
 d) Potential at any one end of the wire
301. The current flowing in a copper voltmeter is 3.2 A. The number of copper ions ( $Cu^{2+}$ ) deposited at the cathode per minute is  
 a)  $0.5 \times 10^{20}$                                       b)  $1.5 \times 10^{20}$                                       c)  $3 \times 10^{20}$                                       d)  $6 \times 10^{20}$
302. The specific resistance of manganin is  $50 \times 10^{-8} \text{ ohm} \times m$ . The resistance of a cube of length 50cm will be  
 a)  $10^{-6} \text{ ohm}$                                       b)  $2.5 \times 10^{-5} \text{ ohm}$                                       c)  $10^{-8} \text{ ohm}$                                       d)  $5 \times 10^{-4} \text{ ohm}$
303. The total current supplied to the given circuit by the battery is



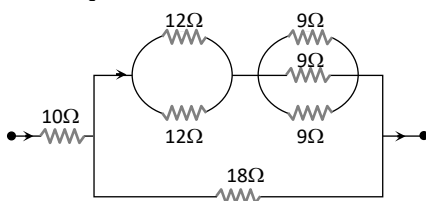- a) 9 A                                      b) 6 A                                      c) 2 A                                      d) 4 A
304. Combination of two identical capacitors, a resistor  $R$  and a DC voltage source of voltage 6 V is used in an experiment on  $C - R$  circuit. It is found that for a parallel combination of the capacitor the time in which the voltage of the fully charged combination reduces to half its original voltage is 10s. For series combination the time needed for reducing the voltage of the fully charged series combination by half is  
 a) 200s                                      b) 10s                                      c) 5s                                      d) 2.5s
305. If  $400\Omega$  of resistance is made by adding four  $100\Omega$  resistance of tolerance 5%, then the tolerance of the combination is  
 a) 20 %                                      b) 5 %                                      c) 10 %                                      d) 15 %
306. A  $5^\circ\text{C}$  rise in temperature is observed in a conductor by passing a current. When the current is doubled the rise in temperature will be approximately  
 a)  $16^\circ\text{C}$                                       b)  $10^\circ\text{C}$                                       c)  $20^\circ\text{C}$                                       d)  $12^\circ\text{C}$
307. In the following circuit,  $18\Omega$  resistor develops  $2J/\text{sec}$  due to current flowing through it. The power developed across  $10\Omega$  resistance is



- a) 125 W                                      b) 10 W                                      c)  $\frac{4}{5} W$                                       d) 25 W
308.  $e = \alpha t - \frac{1}{2}\beta t^2$ , if temperature of cold junction is  $0^\circ\text{C}$  then temperature of inversion is



(if  $\alpha = 500.0\mu V/^{\circ}C, \beta = 5.0\mu V/\text{square}^{\circ}C$ )

- a) 100                                      b) 200                                      c) 300                                      d) 400

309. In  $Cu - Fe$  couple, the flow of current at the temperature of inversion is

- a) From  $Fe$  to  $Cu$  through the hot junction  
 b) From  $Cu$  to  $Fe$  through the hot junction  
 c) Maximum  
 d) None of the above

310. Two wires  $A$  and  $B$  of same material and same mass have radii  $2r$  and  $r$  respectively. If resistance of wire  $A$  is  $34\Omega$ , then resistance of  $B$  will be

- a)  $544\Omega$                                       b)  $272\Omega$                                       c)  $68\Omega$                                       d)  $17\Omega$


311. Three electric bulbs with same voltage ratings of 110 volts but wattage ratings of 40, 60 and 100 watts respectively are connected in series across a 220 volt supply line. If their brightness are  $B_1, B_2, B_3$  respectively, then

- a)  $B_1 > B_2 > B_3$   
 b)  $B_1 > B_2 < B_3$   
 c)  $B_1 = B_2 = B_3$   
 d) Bulbs will burn out due to the high voltage supply

312. Consider a rectangular slab of length  $L$  and area of cross section  $A$ . A current  $I$  is passed through it. If the length is doubled, the potential drop across the end faces

- a) Becomes half of the initial value                                      b) Becomes one-fourth of the initial value  
 c) Becomes double the initial value                                      d) Remains same

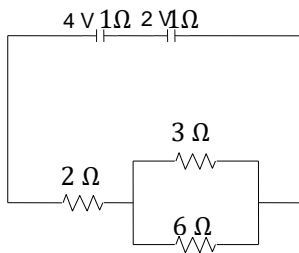313. Two cells having emf 4V, 2V and internal resistances  $1\Omega, 1\Omega$  are connected as shown in figure below. Current through  $6\Omega$  resistance is




- a)  $\frac{1}{3}A$                                       b)  $\frac{2}{3}A$                                       c) 1A                                      d)  $\frac{2}{9}A$

314. Kirchoff's first law *i. e.*  $\sum i = 0$  at a junction is based on the law of conservation of


- a) Charge                                      b) Energy                                      c) Momentum                                      d) Angular momentum

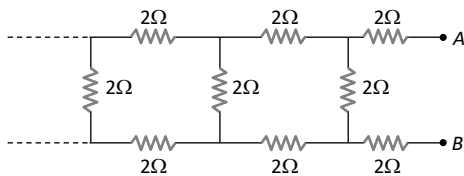315. The equivalent resistance of the following infinite network of resistance is



- a) Less than  $4\Omega$                                       b)  $4\Omega$   
 c) More than  $4\Omega$  but less than  $12\Omega$                                       d)  $12\Omega$




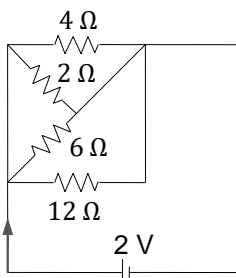
316. The resistance in which the maximum heat is produced is given by







the experiment is

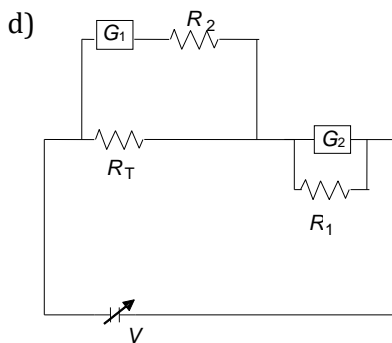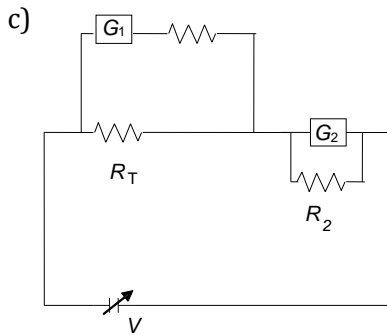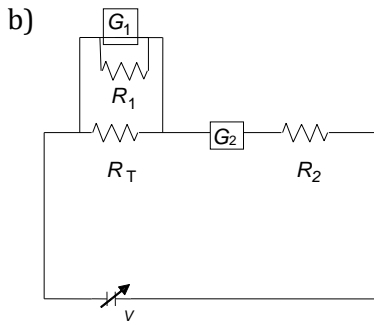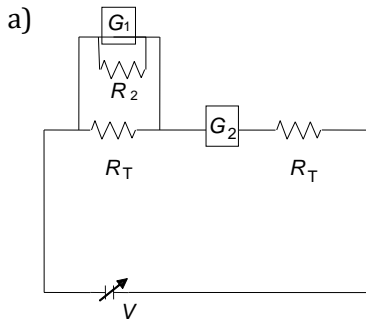

341. To decrease the range of an ammeter, its resistance need to be increased. An ammeter has resistance  $R_0$  and range  $I$ . Which of the following resistance can be connected in series with it to decreases its range to  $I/n$ ?

- a)  $\frac{R_0}{n}$                       b)  $\frac{R_0}{(n-1)}$                       c)  $\frac{R_0}{(n+1)}$                       d) None of these

342. If a current is allowed to pass through a circuit consisting of two dissimilar metals, there is either evolution or absorption of heat at the junction, depending upon the direction of the current. The effect is known as

- a) Seebeck effect                      b) Joule effect                      c) Peltier effect                      d) Thomson effect

343. Two bulbs when connected in parallel to a source take 60 W each. The total power consumed when they are connected in series with the same source is

- a) 15 W                      b) 30 W                      c) 60 W                      d) 120 W

344. In the circuit shown in figure, find the current through the branch  $BD$




- a)  $7.5 \Omega$                       b)  $45 \Omega$                       c)  $90 \Omega$                       d)  $270 \Omega$

357. Two identical cells send the same current in  $3 \Omega$  resistance, whether connected in series or in parallel. The internal resistance on the cell should be

- a)  $1 \Omega$                       b)  $3 \Omega$                       c)  $\frac{1}{2} \Omega$                       d)  $3.5 \Omega$

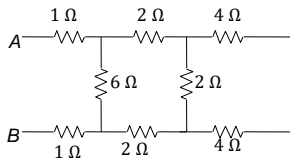358. In the adjoining figure the equivalent resistance between  $A$  and  $B$  is



- a)  $5 \Omega$                       b)  $8 \Omega$                       c)  $2.5 \Omega$                       d)  $6.8 \Omega$

359. If the ratio of the concentration of electron to that of holes in a semiconductor is  $\frac{7}{5}$  and the ratio of current is  $\frac{7}{4}$ , then what is the ratio of their drift velocities

- a)  $\frac{4}{5}$                       b)  $\frac{5}{4}$                       c)  $\frac{4}{7}$                       d)  $\frac{5}{8}$

360. Electroplating does not help in

- a) Fine finish to the surface                      b) Shining appearance  
c) Metals to become hard                      d) Protecting metal against corrosion

361. Corresponding to the resistance  $4.7 \times 10^6 \Omega \pm 5\%$ , which is order of colour coding on carbon resistors?

- a) Yellow, violet, blue, gold                      b) Yellow, violet, green, gold  
c) Orange, blue, green, gold                      d) Orange, blue, violet, gold

362. For a thermocouple, the neutral temperature is  $270^\circ\text{C}$  and the temperature of its cold junction is  $20^\circ\text{C}$ . If there is no deflection in the galvanometer, the temperature of the hot junction should be

- a)  $210^\circ\text{C}$                       b)  $540^\circ\text{C}$                       c)  $520^\circ\text{C}$                       d)  $209^\circ\text{C}$


363. Two cells  $A$  and  $B$  are connected in the secondary circuit of a potentiometer one at a time and the balancing length are respectively  $400 \text{ cm}$  and  $440 \text{ cm}$ . The emf of the cell  $A$  is  $1.08 \text{ V}$ . The emf of the second cell  $B$  is volt is

- a)  $1.08$                       b)  $1.188$                       c)  $11.88$                       d)  $12.8$

364. What determines the emf between the two metals placed in an electrolyte?

- a) Relative position of metals in the electro chemical series                      b) Distance between them  
c) Strength of electrolyte                      d) Nature of electrolyte

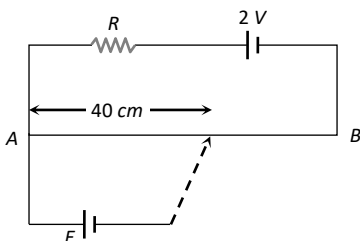365.  $AB$  is a potentiometer wire of length  $100 \text{ cm}$  and its resistance is  $10 \text{ ohm}$ . It is connected in series with a resistance  $R = 40 \text{ ohm}$  and a battery of e.m.f.  $2 \text{ V}$  and negligible internal resistance. If a source of unknown e.m.f.  $E$  is balanced by  $40 \text{ cm}$  length of the potentiometer wire, the value of  $E$  is



- a)  $0.8 \text{ V}$                       b)  $1.6 \text{ V}$                       c)  $0.08 \text{ V}$                       d)  $0.16 \text{ V}$


366. In a closed circuit, the current  $I$  (in ampere) at an instant of time  $t$  (in second) is given by  $I = 4 - 0.08t$ . The number of electrons flowing in  $50 \text{ s}$  through the cross-section of the conductor is

- a)  $1.25 \times 10^{19}$                       b)  $6.25 \times 10^{20}$                       c)  $5.25 \times 10^{19}$                       d)  $2.55 \times 10^{20}$


367. The internal resistance of a cell of emf  $2 \text{ V}$  is  $0.1 \Omega$ . It is connected to a resistance of  $3.9 \Omega$ . The potential difference across is

- a)  $0.5 \text{ V}$                       b)  $1.9 \text{ V}$                       c)  $1.95 \text{ V}$                       d)  $2 \text{ V}$

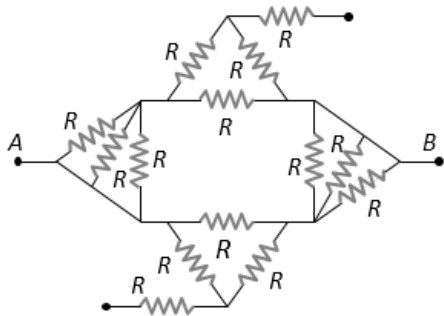
368. The accurate measurement of emf can be obtained using  
 a) Multimeter                      b) Voltmeter                      c) Voltmeter                      d) Potentiometer
369. A potential difference of  $V$  is applied at the ends of a copper wire of length  $l$  and diameter  $d$ . On doubling only  $d$ , the drift velocity,  
 a) Becomes two times              b) Becomes half                      c) Does not change                      d) Becomes one-fourth
370. Find equivalent resistance between  $A$  and  $B$



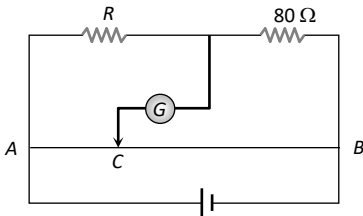
- a)  $R$                                       b)  $\frac{3R}{4}$                                       c)  $\frac{R}{2}$                                       d)  $2R$
371.  $AB$  is a wire of uniform resistance. The galvanometer  $G$  shows no current when the length  $AC = 20\text{cm}$  and  $CB = 80\text{cm}$ . The resistance  $R$  is equal to



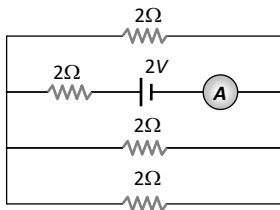- a)  $2\ \Omega$                                       b)  $8\ \Omega$                                       c)  $20\ \Omega$                                       d)  $40\ \Omega$
372. A heater coil is cut into two parts of equal length and one of them is used in the heater. The ratio of the heat produced by this half coil to that by the original coil is  
 a)  $2 : 1$                                       b)  $1 : 2$                                       c)  $1 : 4$                                       d)  $4 : 1$
373. If the cold junction of a thermocouple is kept at  $0^\circ\text{C}$  and the hot junction is kept at  $T^\circ\text{C}$ , then the relation between neutral temperature ( $T_n$ ) and temperature of inversion ( $T_i$ ) is  
 a)  $T_n = \frac{T_i}{2}$                                       b)  $T_n = 2T_i$                                       c)  $T_n = T_i - T$                                       d)  $T_n = T_i + T$
374. The reading of the ammeter as per figure shown is



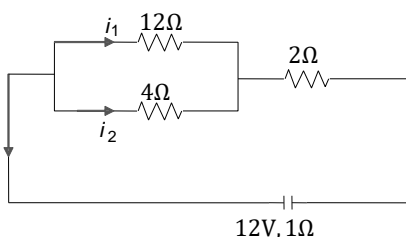- a)  $\frac{1}{8}A$                                       b)  $\frac{3}{4}A$                                       c)  $\frac{1}{2}A$                                       d)  $2A$
375. In the circuit shown, the currents  $i_1$  and  $i_2$  are



- a)  $i_1 = 3A, i_2 = 1A$                       b)  $i_1 = 1A, i_2 = 3A$                       c)  $i_1 = 0.5A, i_2 = 1.5A$                       d)  $i_1 = 1.5A, i_2 = 0.5A$
376. When a potential difference is applied across the ends of a linear metallic conductor  
 a) The free electrons are accelerated continuously from the lower potential end to the higher potential end

of the conductor

- b) The free electrons are accelerated continuously from the higher potential end to the lower potential end of the conductor
- c) The free electrons acquire a constant drift velocity from the lower potential end to the higher potential end of the conductor
- d) The free electrons are set in motion from their position of rest

377. A thermocouple of resistance  $1.6\Omega$  is connected in series with a galvanometer of  $8\Omega$  resistance. The thermocouple develops an *e.m.f.* of  $10\mu V$  per degree temperature difference between two junctions. When one junction is kept at  $0^\circ C$  and the other in a molten metal, the galvanometer reads *8 millivolt*. The temperature of molten metal, when *e.m.f.* varies linearly with temperature difference, will be

- a)  $960^\circ C$
- b)  $1050^\circ C$
- c)  $1275^\circ C$
- d)  $1545^\circ C$

378. The resistance of hot tungsten filament is about 10 times the cold resistance. What will be the resistance of 100 W and 200 lamps, when not in use?


- a)  $40\Omega$
- b)  $20\Omega$
- c)  $400\Omega$
- d)  $200\Omega$

379. The potential difference between the terminals of a cell in open circuit is  $2.2V$  with resistance of  $5\Omega$  across the terminals of a cell, the terminal potential difference is  $1.8V$ . the resistance of the cell is

- a)  $\frac{9}{10}\Omega$
- b)  $\frac{10}{9}\Omega$
- c)  $\frac{7}{12}\Omega$
- d)  $\frac{12}{7}\Omega$

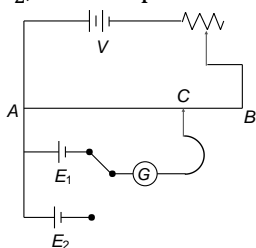380. The circuit shown here is used to compare the emf of two cells  $E_1$  and  $E_2$  ( $E_1 > E_2$ ).

The null point is at  $C$  when the galvanometer is connected to  $E_2$ . when the galvanometer is connected to  $E_1$ , the null point will be




- a) To the left of  $C$
- b) To the right of  $C$
- c) At  $C$  itself
- d) None where on  $AB$

381. A cell of constant emf first connected to a resistance  $R_1$  and then connected to a resistance  $R_2$ .

- a)  $\sqrt{R_1 R_2}$
- b)  $\sqrt{\frac{R_1}{R_2}}$
- c)  $\frac{R_1 - R_2}{2}$
- d)  $\frac{R_1 + R_2}{2}$

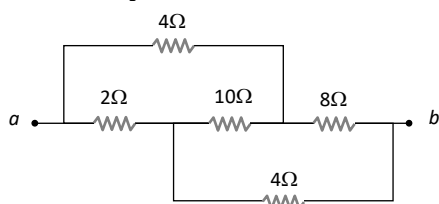382. Find the equivalent resistance between the points  $a$  and  $b$




- a)  $2\Omega$
- b)  $4\Omega$
- c)  $8\Omega$
- d)  $16\Omega$

383. An ammeter with internal resistance  $90\Omega$  reads  $1.85 A$  when connected in a circuit containing a battery and two resistors  $700\Omega$  and  $410\Omega$  in series. Actual current will be

- a)  $1.85 A$
- b) Greater than  $1.85 A$
- c) Less than  $1.85 A$
- d) None of these

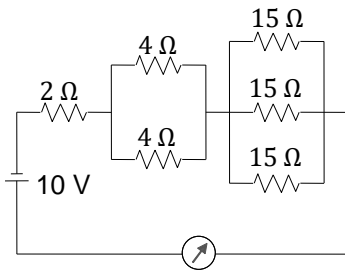384. The current through the circuit shown in figure 1A. If each of  $4\Omega$  the resistors is replaced by  $2\Omega$  resistor, the current in circuit will become nearly






- a) 1.11 A                      b) 1.25 A                      c) 1.34 A                      d) 1.67 A

385. A  $36\Omega$  galvanometer is shunted by resistance of  $4\Omega$ . The percentage of the total current, which passes through the galvanometer is

- a) 8%                      b) 9%                      c) 10%                      d) 91%

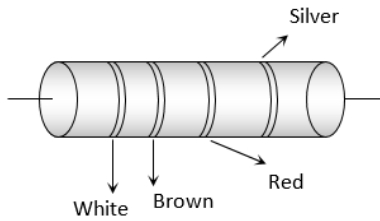386. In the figure a carbon resistor has bands of different colours on its body as mentioned in the figure. The value of the resistance is




- a)  $2.2\text{ k}\Omega$                       b)  $3.3\text{ k}\Omega$                       c)  $5.6\text{ k}\Omega$                       d)  $9.1\text{ k}\Omega$

387. In a potentiometer experiment, the galvanometer shows no deflection when a cell is connected across  $60\text{ cm}$  of the potentiometer wire. If the cell is shunted by a resistance of  $6\Omega$ , the balance is obtained across  $50\text{ cm}$  of the wire. The internal resistance of the cell is

- a)  $0.5\Omega$                       b)  $0.6\Omega$                       c)  $1.2\Omega$                       d)  $1.5\Omega$

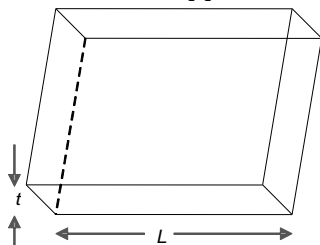388. Consider a thin square sheet of side  $L$  and thickness  $t$ , made of a material of resistivity  $\rho$ . The resistance between two opposite faces, shown by the shaded areas in the figure is



- a) Directly proportional to  $L$                       b) Directly proportional to  $t$   
 c) Independent of  $L$                       d) Independent of  $t$

389. When  $1\text{ kg}$  of hydrogen forms water,  $34 \times 10^6\text{ cal}$  of heat is liberated. If ECE of hydrogen is  $(1/96500,000)\text{kg C}^{-1}$ , then the minimum voltage required for decomposition of water is

- a)  $0.75\text{ V}$                       b)  $3.0\text{ V}$                       c)  $1.5\text{ V}$                       d)  $6.0\text{ V}$


390. The reciprocal of resistance is

- a) Conductance                      b) Resistivity                      c) Voltage                      d) None of the above

391. The resistance of a wire is  $20\text{ ohm}$ . It is so stretched that the length becomes three times, then the new resistance of the wire will be

- a)  $6.67\text{ ohm}$                       b)  $60.0\text{ ohm}$                       c)  $120\text{ ohm}$                       d)  $180.0\text{ ohm}$

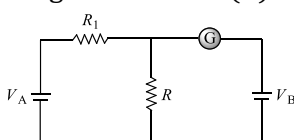392. In the circuit shown the cells  $A$  and  $B$  have negligible resistance. For  $V_A = 12\text{V}$ ,  $R_1 = 500\Omega$  and  $R = 100\Omega$  the galvanometer (G) shows no deflection. The value of  $V_B$  is



- a)  $4\text{V}$                       b)  $2\text{V}$                       c)  $12\text{V}$                       d)  $6\text{V}$

393. Under what condition will the strength of current in a wire of resistance  $R$  be the same for connection is  $n$

series or in parallel of  $n$  identical cells each of the internal resistance  $r$ , when

- a)  $R = nr$                       b)  $R = r/n$                       c)  $R = r$                       d)  $R \rightarrow \infty, r \rightarrow 0$

394. Two bulbs 40 W and 60 W and rated voltage 240 V are connected in series across a potential difference of 420 V. Which bulb will work at above its rated voltages?

- a) 40 W bulb                      b) 60 W bulb                      c) Both will work                      d) None of these


395. A thermocouple uses Bismuth and Tellurium as the dissimilar metals. The sensitivity of bismuth is  $-72\mu V/^\circ C$  and that of the tellurium is  $500\mu V/^\circ C$ . If the difference between hot and cold junction is  $100^\circ C$ , then the maximum output will be

- a) 50 mV                      b) 7.2 mV                      c) 42.8 mV                      d) 57.2 mV

396. The resistance of an ideal voltmeter is

- a) Zero                      b) Very low                      c) Very large                      d) Infinite

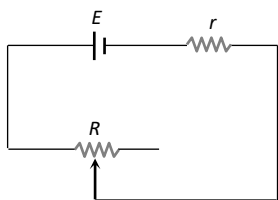397. A battery of e. m. f.  $E$  and internal resistance  $r$  is connected to a variable resistor  $R$  as shown here. Which one of the following is true



- a) Potential difference across the terminals of the battery is maximum when  $R = r$   
 b) Power delivered to the resistor is maximum when  $R = r$   
 c) Current in the circuit is maximum when  $R = r$   
 d) Current in the circuit is maximum when  $R \gg r$


398. A potential difference  $V$  is applied to a copper wire of length  $l$  and thickness  $d$ . If  $V$  is doubled, the drift velocity

- a) Is doubled                      b) Is halved                      c) Remains same                      d) Becomes zero

399. Two copper wires of lengths  $l$  and  $2l$  have radii  $r$  and  $2r$  respectively. What is ratio of their specific resistances?

- a) 1 : 2                      b) 2 : 1                      c) 1 : 1                      d) 1 : 3

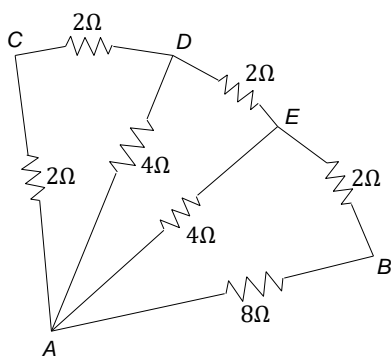400. What is the equivalent resistance between  $A$  and  $B$  in the given circuit?



- a)  $4\Omega$                       b)  $2\Omega$                       c)  $\frac{8}{3}\Omega$                       d)  $\frac{3}{8}\Omega$

401. A metal wire of specific resistance  $64 \times 10^{-6} \text{ ohm} - \text{cm}$  and length 198 cm has a resistance of 7 ohm, the radius of the wire will be


- a) 2.4 cm                      b) 0.24 cm                      c) 0.024 cm                      d) 24 cm

402. A potential difference is applied across the ends of a metallic wire. If the potential difference is doubled, the drift velocity will


- a) Be doubled                      b) Be halved                      c) Be quadrupled                      d) Remain unchanged

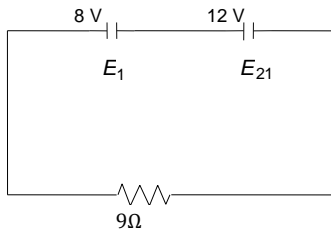403. In the figure shown below, the terminal voltage across  $E_2$  is





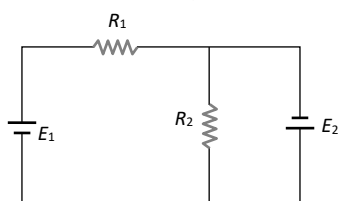- a) 12 V                      b) 12.66 V                      c) 11.34 V                      d) 11.66 V
404. A silver voltameter of resistance  $2\ \text{ohm}$  and a  $3\ \text{ohm}$  resistor are connected in series across a cell. If a resistance of  $2\ \text{ohm}$  is connected in parallel with the voltameter, then the rate of deposition of silver
- a) Decreases by 25%      b) Increases by 25%      c) Increases by 37.5%      d) Decreases by 37.5%
405. A tap supplies water at  $22^\circ\text{C}$ . A man takes 1 L of water per min at  $37^\circ\text{C}$  from the geyser. The power of the geyser is
- a) 525 W                      b) 1050 W                      c) 1575 W                      d) 2100 W
406. When a current flows through a conductor its temperature
- a) May increase or decrease      b) Remains same  
 c) Decrease                      d) Increase
407. An electric bulb is marked 100 W, 230 V. If the supply voltage drops to 115 V, what is the total energy produced by the bulb in 10 min?
- a) 30 kJ                      b) 20 kJ                      c) 15 kJ                      d) 10 kJ
408. The potentiometer is superior to a voltmeter for measuring a potential difference because
- a) The resistance of the voltmeter  
 b) The potentiometer does not draw any current from the source of the potential  
 c) The sensitivity of potentiometer is better than that of the voltmeter  
 d) The voltmeter has a dial and of small size
409. Constantan wire is used in making standard resistances because its
- a) Specific resistance is low  
 b) Density is high  
 c) Temperature coefficient of resistance is negligible  
 d) Melting point is high
410. For a given thermocouple neutral temperature
- a) Is a constant                      b) Depends on cold junction temperature  
 c) Depends on inversion temperature      d) Double that of cold junction temperature
411. An electric cable of copper has just one wire of radius 9 mm. Its resistance is  $5\ \Omega$ . This single copper wire of cable is replaced by 6 different well insulated copper wires each of radius 3 mm. The total resistance of the cable will now be equal to
- a)  $7.5\ \Omega$                       b)  $45\ \Omega$                       c)  $90\ \Omega$                       d)  $270\ \Omega$
412. Two resistance  $R_1$  and  $R_2$  are joined as shown in the figure to two batteries of e.m.f.  $E_1$  and  $E_2$ . If  $E_2$  is short-circuited, the current through  $R_1$  is



- a)  $E_1/R_1$                       b)  $E_2/R_1$                       c)  $E_2/R_2$                       d)  $E_1/(R_2 + R_1)$
413. When two resistances  $R_1$  and  $R_2$  are connected in series, they consume 12 W powers. When they are connected in parallel, they consume 50 W powers. What the ratio of the powers of  $R_1$  and  $R_2$ ?
- a) 1/4                      b) 4                      c) 3/2                      d) 3
414. The lowest resistance which can be obtained by connecting 10 resistors each of  $1/10\ \text{ohm}$  is
- a)  $1/250\ \Omega$                       b)  $1/200\ \Omega$                       c)  $1/100\ \Omega$                       d)  $1/10\ \Omega$
415. The electron of hydrogen atom is considered to be revolving round in circular orbit of radius  $h^2/me^2$  with

velocity  $e^2/h$ , where  $h = h/2\pi$ . The current  $i$  is

- a)  $\frac{4\pi^2 m e^5}{h^2}$       b)  $\frac{4\pi^2 m e^2}{h^3}$       c)  $\frac{4\pi^2 m^2 e^5}{h^3}$       d)  $\frac{4\pi^2 m e^5}{h^3}$


416. Two wires of same metal have the same length but their cross sections are in the ratio 3:1. They are joined in series. The resistance of the thicker wire is  $10\Omega$ . The total resistance of the combination is

- a)  $5/2\Omega$       b)  $40/3\Omega$       c)  $40\Omega$       d)  $100\Omega$

417. A copper wire of length  $L$  and radius  $r$  is nickel plated till its final radius become  $R$  but length remains  $L$ . If the resistivity of nickel and copper be  $\rho_n$  and  $\rho_c$  respectively, the conductance of the nickelled wire is

- a)  $\frac{\pi r^2}{L \cdot \rho_c}$       b)  $\frac{\pi(R^2 - r^2)}{L \cdot \rho_n}$       c)  $\frac{\pi}{L} \left[ \frac{r^2}{\rho_c} + \frac{(R^2 - r^2)}{\rho_n} \right]$       d)  $\frac{L \rho_c}{\pi r^2} + \frac{L \cdot \rho_n}{\pi(R^2 - r^2)}$

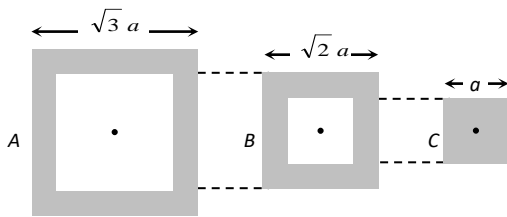418. Following figure shows cross-sections through three long conductors of the same length and material, with square cross-section of edge lengths as shown. Conductor B will fit snugly within conductor A, and conductor C will fit snugly within conductor B. Relationship between their end to end resistance is




- a)  $R_A = R_B = R_C$       b)  $R_A > R_B > R_C$   
 c)  $R_A < R_B < R_C$       d) Information is not sufficient

419. A  $100V$  voltmeter of internal resistance  $20k\Omega$  in series with a high resistance  $R$  is connected to a  $110V$  line. The voltmeter reads  $5V$ , the value of  $R$  is


- a)  $210k\Omega$       b)  $315k\Omega$       c)  $420k\Omega$       d)  $440k\Omega$

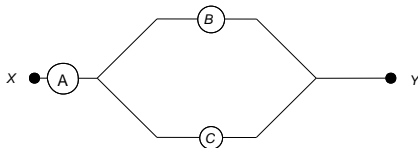420. Three voltmeters A, B and C having resistances  $R$ ,  $1.5R$  and  $3R$  respectively are used in a circuit as shown. When a potential difference is applied between X and Y, the readings of the voltmeters are  $V_1$ ,  $V_2$  and  $V_3$  respectively. Then



- a)  $V_1 = V_2 = V_3$       b)  $V_1 < V_2 = V_3$       c)  $V_1 > V_2 > V_3$       d)  $V_1 > V_2 > V_3$

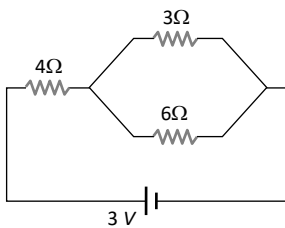421. The potential drop across the  $3\Omega$  resistor is



- a)  $1V$       b)  $1.5V$       c)  $2V$       d)  $3V$

422. A conductor wire having  $10^{29}$  free electrons/ $m^3$  carries a current of  $20A$ . If the cross-section of the wire is  $1mm^2$ , then the drift velocity of electrons will be

- a)  $6.25 \times 10^{-3}ms^{-1}$       b)  $1.25 \times 10^{-5}ms^{-1}$       c)  $1.25 \times 10^{-3}ms^{-1}$       d)  $1.25 \times 10^{-4}ms^{-1}$

423. Two wires have resistances  $R$  and  $2R$ . When both are joining in series and in parallel, then ratio of heats generated in these situations on applying the same voltage, is

- a)  $2 : 1$       b)  $1 : 2$       c)  $2 : 9$       d)  $9 : 2$

424. The potential difference in open circuit for a cell is  $2.2 volt$ . When a  $4 ohm$  resistor is connected between its two electrodes the potential difference becomes  $2 volt$ . The internal resistance of the cell will be

- a)  $1 ohm$       b)  $0.2 ohm$       c)  $2.5 ohm$       d)  $0.4 ohm$

425. The temperature of hot junction of a thermocouple changes from  $80^\circ C$  to  $100^\circ C$ , the percentage change in thermo electric power is

- a) 25%                      b) 20%                      c) 10%                      d) 8%

426. Two bulbs, one of 50 watt and another of 25 watt are connected in series to the mains. The ratio of the currents through them is

- a) 2 :1    b) 1 :2  
c) 1 :1    d) Without voltage, cannot be calculated

427. When a resistor of 11 Ω is connected in series with an electric cell, the current flowing in it is 0.5 A.

Instead, when a resistor of 5 Ω is connected to the same electric cell in series, the current increases by 0.4 A. The internal resistance of the cell is

- a) 1.5 Ω                      b) 2 Ω                      c) 2.5 Ω                      d) 3.5 Ω

428. A battery of emf 10V and internal resistance 3 Ω is connected to an external resistor. The current in the circuit is 0.5A. the terminal voltage of the battery when the circuit is close is

- a) 10V                      b) Zero                      c) 1.5 V                      d) 8.5 V

429. The relation between voltage sensitivity ( $\sigma_v$ ) and current sensitivity ( $\sigma_i$ ) of a moving coil galvanometer is (resistance of galvanometer is G).

- a)  $\frac{\sigma_i}{G} = \sigma_v$                       b)  $\frac{\sigma_v}{G} = \sigma_i$                       c)  $\frac{G}{\sigma_v} = \sigma_i$                       d)  $\frac{G}{\sigma_i} = \sigma_v$


430. An electric heater of resistances 6 Ω is run for 10 min on 120 V line. The energy librated in this period of time is?

- a)  $7.2 \times 10^5$  J                      b)  $14.4 \times 10^5$  J                      c)  $43.2 \times 10^5$  J                      d)  $28.8 \times 10^5$  J

431. A certain piece of silver of given mass is to be made like a wire. Which of the following combinations of length (L) and the area of cross-section (A) will lead to the smallest resistance

- a) L and A    b) 2L and A/2  
c) L/2 and 2 A    d) Any of the above, because volume of silver remains same

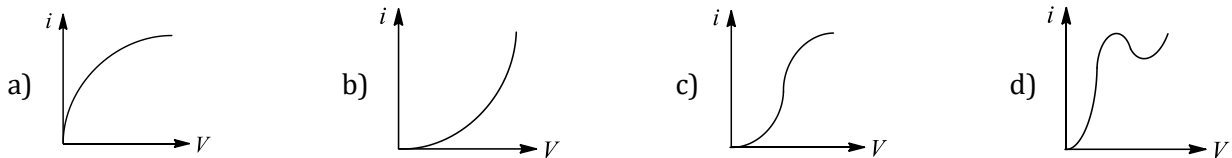432. The variation between  $V - i$  has been shown by  $V - i$  graph for heater filament.



433. Thomson coefficient of a conductor is  $10\mu V/K$ . The two ends of it are kept at  $50^\circ C$  and  $60^\circ C$  respectively. Amount of heat absorbed by the conductor when a charge of 10C flows through it is

- a) 1000 J                      b) 100 J                      c) 100 mJ                      d) 1 mJ

434. The junction of Ni-Cu thermo couple are maintained at  $0^\circ C$  and  $100^\circ C$ . The seeback emf developed in the temperature is

$$a_{Ni-Cu} = 16.3 \times 10^{-6} V^\circ C^{-1}$$


$$b_{Ni-Cu} = -0.021 \times 10^{-6} V^\circ C^{-1}$$

- a)  $2.73 \times 10^3$  V                      b)  $1.42 \times 10^{-3}$  V                      c)  $3.68 \times 10^{-3}$  V                      d)  $2.23 \times 10^3$  V

435. A source of a primary cell is 2V. what is the short circuited it provides 4A current, then the internal resistance of cell will be


- a) 8 Ω                      b) 2.0 Ω                      c) 4 Ω                      d) 0.5 Ω

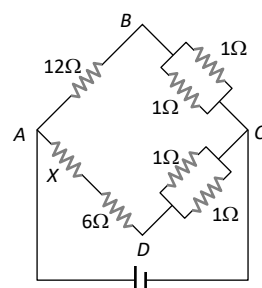436. For what value of unknown resistance X, the potential difference between B and D will be zero in the circuit shown in the figure



- a)  $4 \Omega$                                       b)  $6 \Omega$                                       c)  $2 \Omega$                                       d)  $5 \Omega$

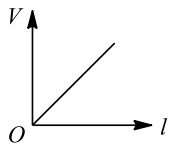437. The  $V - I$  graph for a wire of copper of length  $L$  and cross-section area  $A$  is shown in adjoining figure. The slope of the graph will be




- a) Less if the experiment is repeated at a higher temperature                                      b) More if a wire of silver having the same dimension is used  
 c) Doubled if the length of the wire is doubled                                      d) Halved if length of the wire is halved

438. The heat generated through  $2 \text{ ohm}$  and  $8 \text{ ohm}$  resistances separately, when a condenser of  $200 \mu\text{F}$  capacity charged to  $200 \text{ V}$  is discharged one by one, will be

- a)  $4 \text{ J}$  and  $16 \text{ J}$  respectively                                      b)  $16 \text{ J}$  and  $4 \text{ J}$  respectively  
 c)  $4 \text{ J}$  and  $8 \text{ J}$  respectively                                      d)  $4 \text{ J}$  and  $4 \text{ J}$  respectively

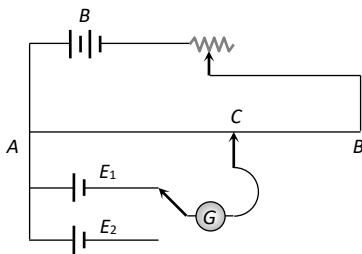439. The circuit shown here is used to compare the e.m.f.'s of two cells  $E_1$  and  $E_2$  ( $E_1 > E_2$ ). The null point is at  $C$  when the galvanometer is connected to  $E_1$ . When the galvanometer is connected to  $E_2$ , the null point will be



- a) To the left of  $C$                                       b) To the right of  $C$                                       c) At  $C$  itself                                      d) No where on  $AB$

440. The colour code for a resistor of resistance  $3.5 \text{ k}\Omega$  with  $5\%$  tolerance is

- a) Orange, green, red and gold                                      b) Red, yellow, black and gold  
 c) Orange, green, orange and silver                                      d) Orange, green, red and silver

441. The tangent galvanometer, when connected in series with a standard resistance can be used as

- a) An ammeter                                      b) A voltmeter  
 c) A wattmeter                                      d) Both ammeter and voltmeter

442. Which of the following statement is correct

- a) Both Peltier and Joule effects are reversible  
 b) Both Peltier and Joule effects are irreversible  
 c) Joule effect is reversible, whereas Peltier effect is irreversible  
 d) Joule effect is reversible, whereas Peltier effect is reversible

443. Four wires  $AB, BC, CD, DA$  of resistance  $4 \text{ ohm}$  each and a fifth wire  $BD$  of resistance  $8 \text{ ohm}$  are joined to form a rectangle  $ABCD$  of which  $BD$  is a diagonal. The effective resistance between the points  $A$  and  $B$  is

- a)  $24 \text{ ohm}$                                       b)  $16 \text{ ohm}$                                       c)  $\frac{4}{3} \text{ ohm}$                                       d)  $\frac{8}{3} \text{ ohm}$


444. Two resistors are connected (a) in series (b) in parallel. The equivalent resistance in the two cases are  $9 \text{ ohm}$  and  $2 \text{ ohm}$  respectively. Then the resistance of the component resistors are

- a)  $2 \text{ ohm}$  and  $7 \text{ ohm}$                                       b)  $3 \text{ ohm}$  and  $6 \text{ ohm}$                                       c)  $3 \text{ ohm}$  and  $9 \text{ ohm}$                                       d)  $5 \text{ ohm}$  and  $4 \text{ ohm}$

445. Two wires of the same material and equal length are joined in parallel combination. If one of them has half the thickness of the other and the thinner wire has a resistance of  $8 \text{ ohms}$ , the resistance of the combination is equal to


- a)  $\frac{5}{8} \text{ ohm}$                                       b)  $\frac{8}{5} \text{ ohm}$                                       c)  $\frac{3}{8} \text{ ohm}$                                       d)  $\frac{8}{3} \text{ ohm}$

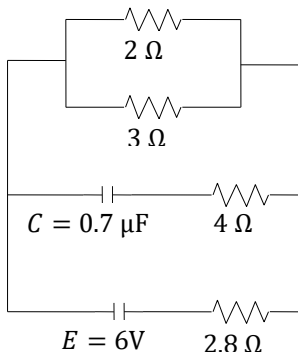446. In the circuit shown, the internal resistance of the cell is negligible. The steady state current in the  $2 \Omega$  resistance is



- a) 0.6A                      b) 1.2A                      c) 0.9A                      d) 1.5A

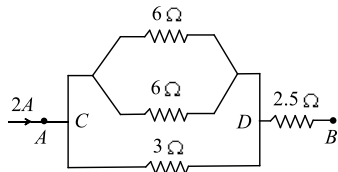447. The equivalent resistance and potential difference between *A* and *B* for the circuit is respectively



- a) 4 Ω, 8 V                      b) 8 Ω, 4 V                      c) 2 Ω, 2 V                      d) 16 Ω, 8 V


448. A wire of resistance 18Ω is divided into three equal parts. These parts are connected in side of triangle, the equivalent resistance of any two corners of triangle will be

- a) 18Ω                      b) 9Ω                      c) 6Ω                      d) 4Ω

449. The power of heater is 500 W at 800°C. What will be its power at 200°C ? (Given : temperature coefficient of resistance,  $\alpha = 4 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$ )


- a) 484 W                      b) 672 W                      c) 526 W                      d) 620 W

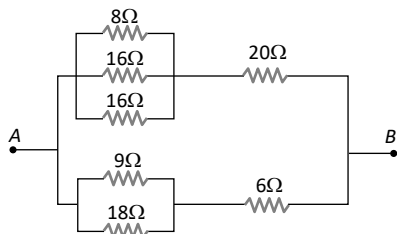450. The equivalent resistance of the arrangement of resistances shown in adjoining figure between the points *A* and *B* is



- a) 6 ohm                      b) 8 ohm                      c) 16 ohm                      d) 24 ohm

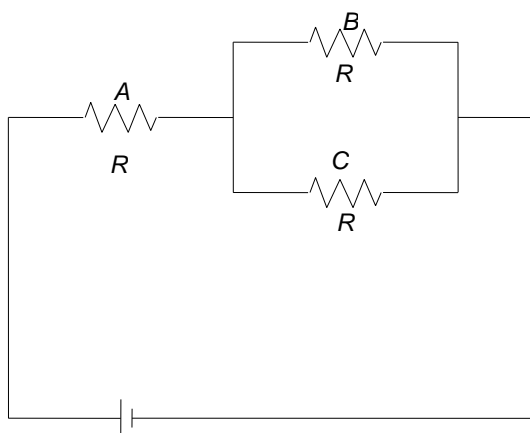451. Three identical resistances *A*, *B* and *C* are connected as shown in figure.



The heat produced will be maximum


- a) In *B*                      b) In *B* and *C*                      c) In *A*                      d) Same for *A*, *B* and *C*

452. In a conductor 4 coulomb of charge flows for 2 seconds. The value of electric current will be


- a) 4 volt                      b) 4 ampere                      c) 2 ampere                      d) 2 volt

453. The main supply voltage to a room is 120 V. The resistance of the lead wires is 6Ω. A 60 W bulb is already giving light. What is the decrease in voltage across the bulb when a 240 W heater is switched on?

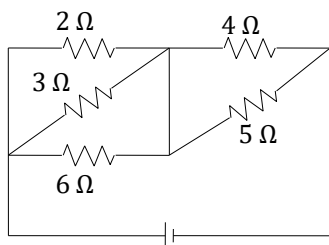
- a) No change                      b) 10 V                      c) 20 V                      d) More than 10 V
454. Two bulbs consume same power when operated at 200 V and 300 V respectively. When these bulbs are connected in series across a DC source of 400 V, then the ratio of power consumed across them is  
 a) 2/3                      b) 3/2                      c) 4/9                      d) 9/4
455. A wire is stretched so as to change its diameter by 0.25%. The percentage change in resistance is  
 a) 4.0%                      b) 2.0%                      c) 1.0%                      d) 0.5%
456. The resistor in which maximum heat will be produced is



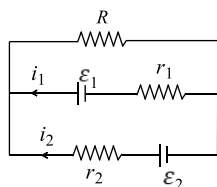- a) 2 Ω                      b) 3 Ω                      c) 4 Ω                      d) 6 Ω
457. If an ammeter is connected in parallel to a circuit, it is likely to be damaged due to excess  
 a) Current                      b) Voltage                      c) Resistance                      d) All of these
458. See the electrical circuit shown in this figure. Which of the following equations is a *correct* equation for it




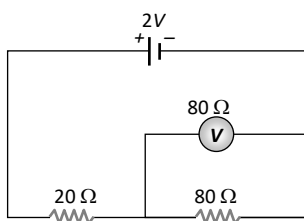- a)  $\varepsilon_1 - (i_1 + i_2)R - i_1 r_1 = 0$                       b)  $\varepsilon_2 - i_2 r_2 - \varepsilon_1 - i_1 r_1 = 0$   
 c)  $-\varepsilon_2 - (i_1 + i_2)R + i_2 r_2 = 0$                       d)  $\varepsilon_1 - (i_1 + i_2)R + i_1 r_1 = 0$
459. In the adjoining circuit, the e.m.f. of the cell is 2 volt and the internal resistance is negligible. The resistance of the voltmeter is 80 ohm. The reading of the voltmeter will be




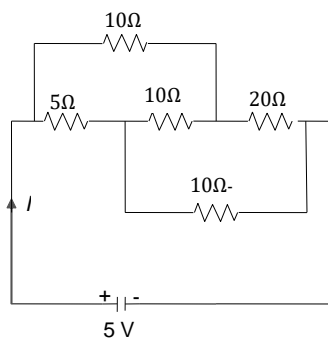- a) 0.80 volt                      b) 1.60 volt                      c) 1.33 volt                      d) 2.00 volt
460. 5 cells, each of emf 0.2V and internal resistance 1Ω are connected to an external circuit of resistance of 10Ω. Find the current through external circuit  
 a)  $\frac{1}{2.5} A$                       b)  $\frac{1}{10} A$                       c)  $\frac{1}{15} A$                       d)  $\frac{1}{2} A$
461. A 2V battery, a 990 Ω resistor and a potentiometer of 2m length, all are connected in series of the residence of potentiometer wire is 10 Ω, then the potential gradient of the potentiometer wire is  
 a)  $0.05Vm^{-1}$                       b)  $0.5Vm^{-1}$                       c)  $0.01Vm^{-1}$                       d)  $0.1 Vm^{-1}$
462. A galvanometer of resistance 36 Ω is changed into an ammeter by using a shunt of 4 Ω. The fraction  $f_0$  of total current passing through the galvanometer is  
 a)  $\frac{1}{40}$                       b)  $\frac{1}{4}$                       c)  $\frac{1}{140}$                       d)  $\frac{1}{10}$
463. Two cells of equal e. m. f. and of internal resistance  $r_1$  and  $r_2$  ( $r_1 > r_2$ ) are connected in series. On connecting this combination to an external resistance R, it is observed that the potential difference across the first cell becomes zero. The value of R will be  
 a)  $r_1 + r_2$                       b)  $r_1 - r_2$                       c)  $\frac{r_1 + r_2}{2}$                       d)  $\frac{r_1 - r_2}{2}$
464. The current I drawn from the 5 V source will be






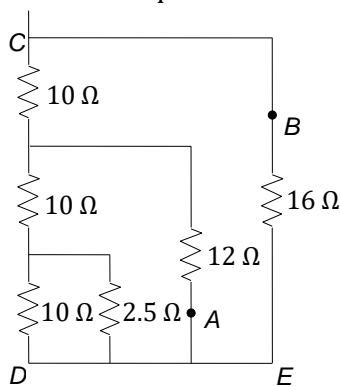- a) 0.33A                      b) 0.5A                      c) 0.67A                      d) 0.17A
465. If 2 A of current is passed through  $\text{CuSO}_4$  solution for 32 s, then the number of copper ions deposited at the cathode will be  
 a)  $4 \times 10^{20}$                       b)  $2 \times 10^{20}$                       c)  $4 \times 10^{19}$                       d)  $2 \times 10^{19}$
466. A steady current is set up in a metallic wire of non-uniform cross-section. How is the rate of flow of electrons ( $R$ ) related to the area of cross-section ( $A$ )?  
 a)  $R \propto A^{-1}$                       b)  $R \propto A$                       c)  $R \propto A^2$                       d)  $R$  is independent of  $A$
467. If 96500 *coulombs* of electricity liberates one gram equivalent of any substance, the time taken for a current of 0.15 *amperes* to deposit 20mg of copper from a solution of copper sulphate is (Chemical equivalent of copper = 32)  
 a) 5 min 20 sec                      b) 6 min 42 sec                      c) 4 min 40 sec                      d) 5 min 50 sec
468. The electron drift speed is small and the charge of the electron is also small but still, we obtain large current in a conductor. This is due to  
 a) The conducting property of the conductor  
 b) The resistance of the conductor is small  
 c) The electron number density of the conductor is small  
 d) The electron number density of the conductor is enormous
469. What is the equivalent resistance across the points  $A$  and  $B$  in the circuit given below?



- a) 8 Ω                      b) 12 Ω                      c) 16 Ω                      d) 32 Ω
470. The resistance of the filament of an electric bulb changes with temperature. If an electric bulb rated 220 volt and 100 watt is connected to  $(220 \times .8)$  volt sources, then the actual power would be  
 a)  $100 \times 0.8$  watt                      b)  $100 \times (0.8)^2$  watt  
 c) Between  $100 \times 0.8$  watt and 100 watt                      d) Between  $100 \times (0.8)^2$  watt and  $100 \times 0.8$  watt
471. Every atom makes one free electron in copper. If 1.1 A Current is flowing in the wire of copper having 1 mm diameter, then the drift velocity(approx.) will be (density of copper= $9 \times 10^3$  kg  $\text{m}^{-3}$  and atomic weight of copper=63)  
 a) 0.1  $\text{mms}^{-1}$                       b) 0.2  $\text{mms}^{-1}$                       c) 0.3  $\text{mms}^{-1}$                       d) 0.2  $\text{mms}^{-1}$
472. In a copper voltmeter , if the current ( $I$ ) and time ( $t$ ) variations of the type as shown in figure, the mass deposited in 30 min is [Atomic weight of copper is 63.5 and Faraday constant is 96500 C per g equivalent]  
 a) 0.078 g                      b) 0.054 g                      c) 0.039 g                      d) 0.0195 g

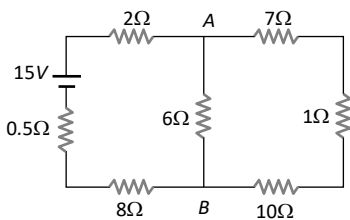473. A wire when connected to 220V mains supply has power dissipation  $P_1$ . Now the wire is cut into two equal pieces which are connected in parallel to the same supply. Power dissipation in this case is  $P_2$ . Then  $P_2 : P_1$  is  
 a) 1                                      b) 4                                      c) 2                                      d) 3
474. A source of e. m. f.  $E = 15 V$  and having negligible internal resistance is connected to a variable resistance so that the current in the circuit increases with time as  $i = 1.2 t + 3$ . Then, the total charge that will flow in first five seconds will be  
 a) 10 C                                      b) 20 C                                      c) 30 C                                      d) 40 C
475. Electric bulb 50 W-100 V glowing at full power are to be used in parallel with battery 120 V, 10  $\Omega$ . Maximum number of bulbs that can be connected so that they glow in full power is  
 a) 2                                      b) 8                                      c) 4                                      d) 6
476. 10 wires (same length, same area, same material) are connected in parallel and each has 1 $\Omega$  resistance, then the equivalent resistance will be  
 a) 10  $\Omega$                                       b) 1  $\Omega$                                       c) 0.1  $\Omega$                                       d) 0.001  $\Omega$
477. In order to pass 10% of main current through a moving coil galvanometer of 99 ohm, the resistance of the required shunt is  
 a) 9.9  $\Omega$                                       b) 10  $\Omega$                                       c) 11  $\Omega$                                       d) 9  $\Omega$
478. If the resistivity of a potentiometer wire be  $\rho$  and area of cross-section be  $A$ , then what will be potential gradient along the wire  
 a)  $\frac{I\rho}{A}$                                       b)  $\frac{I}{A\rho}$                                       c)  $\frac{IA}{\rho}$                                       d)  $IA\rho$
479. The current from the battery in circuit diagram shown is



- a) 1 A                                      b) 2 A                                      c) 1.5 A                                      d) 3 A
480. Two bulbs when connected in parallel to a source take 100 W each. The total power consumed when they are connected in series with the same source is  
 a) 25 W                                      b) 50 W                                      c) 100 W                                      d) 200 W
481. A uniform resistance  $R$  and length  $L$  is cut into four equal parts, each of length  $L/4$ , which are then connected in parallel combination. The effective resistance of the combination will be  
 a)  $R$                                       b)  $4R$                                       c)  $\frac{R}{4}$                                       d)  $\frac{R}{16}$
482. In a circuit 5 percent of total current passes through a galvanometer. If resistance of the galvanometer is  $G$  then value of the shunt is  
 a) 19  $G$                                       b) 20  $G$                                       c)  $\frac{G}{20}$                                       d)  $\frac{G}{19}$
483. An electric lamp is marked 60 W, 230 V. The cost of a 1 kWh of energy is Rs. 1.25. The cost of using this lamp 8 hrs a day for 30 days is  
 a) Rs. 10                                      b) Rs. 16                                      c) Rs. 18                                      d) Rs. 20
484. Two wires 'A' and 'B' of the same material have their lengths in the ratio 1 : 2 and radii in the ratio 2 : 1. The two wires are connected in parallel across a battery. The ratio of the heat produced in 'A' to the heat produced in 'B' for the same time is  
 a) 1 : 2                                      b) 2 : 1                                      c) 1 : 8                                      d) 8 : 1
485. (1) The product of a volt and a coulomb is a joule  
 (2) The product of a volt and an ampere is a joule/second  
 (3) The product of volt and watt is horse power  
 (4) Watt-hour can be measured in terms of electron volt


State if

- a) All four are correct  
 b) (1), (2) and (4) are correct  
 c) (1) and (3) are correct  
 d) (3) and (4) are correct

486. A copper and a chromium voltmeter are connected in series with a battery. It found that in half an hour  $0.475\text{ g}$  of copper and  $0.130\text{ g}$  of chromium have been deposited. The ECE ratio of copper and chromium is

- a) 0.274  
 b) 0.523  
 c) 3.65  
 d) 1.85

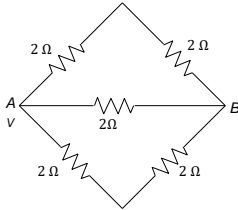487. Each resistance shown in figure is  $2\ \Omega$ . The equivalent resistance between  $A$  and  $B$  is



- a)  $2\ \Omega$   
 b)  $4\ \Omega$   
 c)  $8\ \Omega$   
 d)  $1\ \Omega$

488. If  $\sigma_1, \sigma_2$  and  $\sigma_3$  are the conductances of three conductors, then their equivalent conductance, when they are joined in series, will be

- a)  $\sigma_1 + \sigma_2 + \sigma_3$   
 b)  $\frac{1}{\sigma_1} + \frac{1}{\sigma_2} + \frac{1}{\sigma_3}$   
 c)  $\frac{\sigma_1\sigma_2\sigma_3}{\sigma_1 + \sigma_2 + \sigma_3}$   
 d) None of these

489. The resistance of a metal increases with increasing temperature because

- a) The collisions of the conducting electrons with the electrons increase  
 b) The collisions of the conducting electrons with the lattice consisting of the ions of the metal increases  
 c) The number of conduction electrons decrease  
 d) The number of conduction electrons increase

490. Two electric bulbs  $A$  and  $B$  are rated as  $60\text{ W}$  and  $100\text{ W}$ . They are connected in parallel to the same source. Then

- a)  $B$  draws more current than  $A$   
 b) Currents drawn are in the ratio of their resistances  
 c) Both draw the same current  
 d)  $A$  draws more current than  $B$


491. If an electric current is passed through a nerve of a man, then man

- a) Begins to laugh  
 b) Begins to weep  
 c) Is excited  
 d) Becomes insensitive to pain

492. An electric bulb is rated  $220\text{ V}-100\text{ W}$ . The power consumed by it when operated on  $110\text{ V}$  will be

- a)  $75\text{ W}$   
 b)  $40\text{ W}$   
 c)  $25\text{ W}$   
 d)  $50\text{ W}$

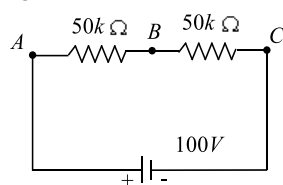493. In the adjacent shown circuit, a voltmeter of internal resistance  $R$ , when connected across  $B$  and  $C$  reads  $\frac{100}{3}\text{ V}$ . Neglecting the internal resistance of the battery, the value of  $R$  is



- a)  $100\text{ k}\Omega$   
 b)  $75\text{ k}\Omega$   
 c)  $50\text{ k}\Omega$   
 d)  $25\text{ k}\Omega$


494. A resistor  $R_1$  dissipates power  $P$  when connected to a certain generator. If the resistor  $R_2$  is put in series with  $R_1$ , the power dissipated by  $R_1$

- a) Decreases  
 b) Increases  
 c) Remains the same  
 d) Any of the above depending upon the relative values of  $R_1$  and  $R_2$


495. If two wires having resistances  $R$  and  $2R$  both are joined in series and in parallel, then ratio of heat generated in this situation, applying the same voltage is

- a)  $2 : 1$   
 b)  $1 : 2$   
 c)  $2 : 9$   
 d)  $9 : 2$

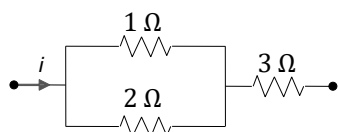496. For driving a current of  $2\text{ A}$  for  $6\text{ minutes}$  in a circuit,  $1000\text{ J}$  of work is to be done. The e.m.f. of the source in the circuit is  
 a)  $1.38\text{ V}$                       b)  $1.68\text{ V}$                       c)  $2.04\text{ V}$                       d)  $3.10\text{ V}$
497. A heater of  $220\text{ V}$  heats a volume of water in  $5\text{ min}$ . The same heater when connected to  $110\text{ V}$  heats the same volume of water in (minute)  
 a)  $5$                                   b)  $20$                                   c)  $10$                                   d)  $2.5$
498.  $50\ \Omega$  and  $100\ \Omega$  resistors are connected in series. This connection is connected with a battery of  $2.4\text{ volt}$ . When a voltmeter of  $100\ \Omega$  resistance is connected across  $100\ \Omega$  resistor, then the reading of the voltmeter will be  
 a)  $1.6\text{ V}$                               b)  $1.0\text{ V}$                               c)  $1.2\text{ V}$                               d)  $2.0\text{ V}$
499. A series combination of two resistors  $1\ \Omega$  each is connected to a  $12\text{ V}$  battery of internal resistance  $0.4\ \Omega$ . The current flowing through it will be  
 a)  $3.5\text{ A}$                               b)  $5\text{ A}$                                   c)  $6\text{ A}$                                   d)  $10\text{ A}$
500. In the circuit shown in figure, power developed across  $1\ \Omega$ ,  $2\ \Omega$ ,  $3\ \Omega$  resistance are in ratio of



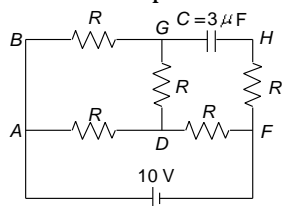- a)  $1 : 2 : 3$                               b)  $4 : 2 : 27$                               c)  $6 : 4 : 9$                               d)  $2 : 1 : 27$
501. Four resistances  $10\ \Omega$ ,  $5\ \Omega$ ,  $7\ \Omega$  and  $3\ \Omega$  are connected so that they form the sides of a rectangle  $AB$ ,  $BC$ ,  $CD$  and  $DA$  respectively. Another resistance of  $10\ \Omega$  is connected across the diagonal  $AC$ . The equivalent resistance between  $A$  and  $B$  is  
 a)  $2\ \Omega$                                   b)  $5\ \Omega$                                   c)  $7\ \Omega$                                   d)  $10\ \Omega$
502. A copper voltmeter and a silver voltmeter are connected in series in a circuit. The rate of the increase in the weight of the cathode in the two voltmeters will be in the ratio of  
 a) Atomic weights of  $\text{Cu}$  and  $\text{Ag}$                               b) Densities of  $\text{Cu}$  and  $\text{Ag}$   
 c) Half of the atomic weight of  $\text{Cu}$  to the atomic weight of  $\text{Ag}$                               d) Half of the atomic weight of  $\text{Ag}$  to half the atomic weight of  $\text{Cu}$
503. In the circuit shown, the cell is ideal, with  $\text{emf} = 10\text{ V}$ . Each resistance is of  $2\ \Omega$ . The potential difference across the capacitor is



- a)  $12\text{ V}$                                   b)  $10\text{ V}$                                   c)  $8\text{ V}$                                   d) zero
504. A current of  $16\text{ ampere}$  flows through molten  $\text{NaCl}$  for  $10\text{ minute}$ . The amount of metallic sodium that appears at the negative electrode would be  
 a)  $0.23\text{ gm}$                               b)  $1.15\text{ gm}$                               c)  $2.3\text{ gm}$                               d)  $11.5\text{ gm}$
505. A storage battery has e.m.f.  $15\text{ volt}$  and internal resistance  $0.05\text{ ohm}$ . Its terminal voltage when it is delivering  $10\text{ ampere}$  is  
 a)  $30\text{ volt}$                               b)  $1.00\text{ volt}$                               c)  $14.5\text{ volt}$                               d)  $15.5\text{ volt}$
506. There are three voltmeters of the same range but of resistances  $10000\ \Omega$ ,  $8000\ \Omega$  and  $4000\ \Omega$  respectively. The best voltmeter among these is the one whose resistance is  
 a)  $10000\ \Omega$                               b)  $8000\ \Omega$                               c)  $4000\ \Omega$                               d) All are equally good
507. In the circuit shown in the adjoining figure, the current between  $B$  and  $D$  is zero, the unknown resistance is of



a) 700°C

b) 600°C

c) 350°C

d) 670°C

518. *Ohm's* law is true

a) For metallic conductors at low temperature

b) For metallic conductors at high temperature

c) For electrolytes when current passes through them

d) For diode when current flows

519. Which of the following statements is correct

a) Liquids obey fully the *ohm's* law

b) Liquids obey partially the *ohm's* law

c) There is no relation between current and p.d. for liquids

d) None of the above

520. The range of a voltmeter of resistance  $500\ \Omega$  is 10V. the resistance to be connected to convert it into an ammeter of range 10A is

a)  $1\ \Omega$  in parallel

b)  $1\ \Omega$  in series

c)  $0.1\ \Omega$  in parallel

d)  $0.1\ \Omega$  in series

521. A uniform wire of resistance  $R$  is uniformly compressed along its length, until its radius becomes  $n$  times the original radius. Now resistance of the wire becomes

a)  $\frac{R}{n^4}$

b)  $\frac{R}{n^2}$

c)  $\frac{R}{n}$

d)  $nR$

522. The rate of increase of thermo *e.m.f.* with temperature at the neutral temperature of a thermocouple

a) Is negative

b) Is positive

c) Is zero

d) Depends upon the choice of the two materials of the thermocouple

523. What length of the wire of specific resistance  $48 \times 10^{-8}\ \Omega\ m$  is needed to make a resistance of  $4.2\ \Omega$  (diameter of wire =  $0.4\ mm$ )


a)  $4.1\ m$

b)  $3.1\ m$

c)  $2.1\ m$

d)  $1.1\ m$

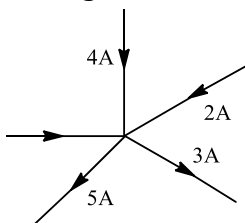524. In the given current distribution, what is the value of  $I$ ?






a) 3A



b) 8A

c) 2A

d) 5A

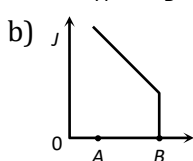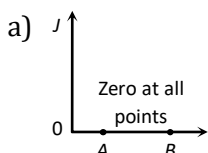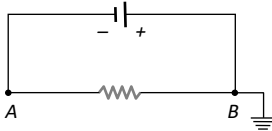525. A battery is connected to a uniform resistance wire  $AB$  and  $B$  is earthed. Which one of the graphs below shows how the current density  $J$  varies along  $AB$



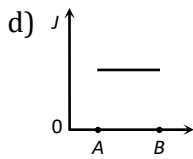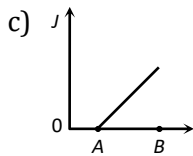


526. An ammeter and a voltmeter of resistance  $R$  are connected in series to an electric cell of negligible internal resistance. Their readings are  $A$  and  $V$  respectively. If another resistance  $R$  is connected in parallel with the voltmeter

- a) Both  $A$  and  $V$  will increase                      b) Both  $A$  and  $V$  will decrease  
 c)  $A$  will decrease and  $V$  will increase              d)  $A$  will increase and  $V$  will decrease

527. When the current  $i$  is flowing a conductor, the drift velocity is  $v$ . If  $2i$  current is flowed through the same metal but having double the area of cross-section, then the drift velocity will be

- a)  $v/4$                       b)  $v/2$                       c)  $v$                       d)  $4v$

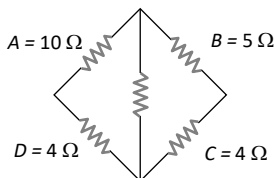528. In a typical Wheatstone network, the resistances in cycle order are  $A = 10 \Omega$ ,  $B = 5 \Omega$ ,  $C = 4 \Omega$  and  $D = 4 \Omega$ . For the bridge to be balanced



- a)  $10 \Omega$  should be connected in parallel with  $A$   
 b)  $10 \Omega$  should be connected in series with  $A$   
 c)  $5 \Omega$  should be connected in series with  $B$   
 d)  $5 \Omega$  should be connected in parallel with  $B$


529. When a resistance of  $2 \text{ ohm}$  is connected across the terminals of a cell, the current is  $0.5 \text{ ampere}$ . When the resistance is increased to  $5 \text{ ohm}$ , the current is  $0.25 \text{ ampere}$ . The internal resistance of the cell is

- a)  $0.5 \text{ ohm}$                       b)  $1.0 \text{ ohm}$                       c)  $1.5 \text{ ohm}$                       d)  $2.0 \text{ ohm}$

530. A tap supplies water at  $22^\circ\text{C}$ , a man takes of  $1 \text{ L}$  of water per min at  $37^\circ\text{C}$  from the geyser. The power of geyser is

- a)  $525 \text{ W}$                       b)  $1050 \text{ W}$                       c)  $1775 \text{ W}$                       d)  $2100 \text{ W}$

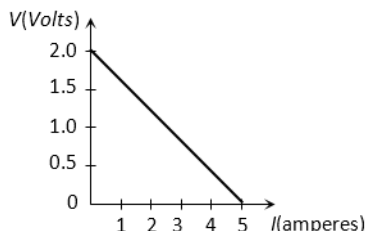531. For a cell, the graph between the potential difference ( $V$ ) across the terminals of the cell and the current ( $I$ ) drawn from the cell is shown in the figure. The e.m.f. and the internal resistance of the cell are



- a)  $2V, 0.5\Omega$                       b)  $2V, 0.4\Omega$                       c)  $> 2V, 0.5\Omega$                       d)  $> 2V, 0.4\Omega$

532. The thermistors are usually made of

- a) Metals with low temperature coefficient of resistivity  
 b) Metals with high temperature coefficient of resistivity  
 c) Metal oxides with high temperature coefficient of resistivity  
 d) Semiconducting materials having low temperature coefficient of resistivity

533. A storage cell is charged by  $5 \text{ amp D.C.}$  for  $18 \text{ hours}$ . Its strength after charging will be

- a)  $18 \text{ AH}$                       b)  $5 \text{ AH}$                       c)  $90 \text{ AH}$                       d)  $15 \text{ AH}$

534. The internal resistance of a cell of e.m.f.  $12V$  is  $5 \times 10^{-2}\Omega$ . It is connected across an unknown resistance. Voltage across the cell, when a current of  $60 \text{ A}$  is drawn from it, is


a) 15 V

b) 12 V

c) 9 V

d) 6 V

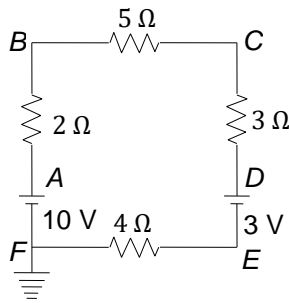535. In the circuit shown in figure, the points  $F$  is grounded. Which of the following is wrong statement?



a)  $D$  is at 5V

b)  $E$  is at zero potential

c) The current in the circuit will be 0.5 A

d) The potential at  $E$  is same whether or not  $F$  is rounded

536. Potentiometer wire of length 1m is connected in series with  $490\Omega$  resistance and 2V battery. If  $0.2\text{mVcm}^{-1}$  is the potential gradient, then resistance of the potentiometer wire is

a)  $4.9\Omega$

b)  $7.9\Omega$

c)  $5.9\Omega$

d)  $6.9\Omega$

537. The potential difference across the terminals of a battery is 50V when 11A current is drawn and 60V when 1A current is drawn. The *e. m. f.* and the internal resistance of the battery are

a) 62V,  $2\Omega$

b) 63V,  $1\Omega$

c) 61V,  $1\Omega$

d) 64V,  $2\Omega$

538. Two resistance  $R_1$  and  $R_2$  are made of different materials. The temperature coefficient of the material of  $R_1$  is  $\alpha$  and of the material of  $R_2$  is  $-\beta$ . The resistance of the series combination of  $R_1$  and  $R_2$  will not change with temperature, if  $R_1/R_2$  equals

a)  $\frac{\alpha}{\beta}$

b)  $\frac{\alpha + \beta}{\alpha - \beta}$

c)  $\frac{\alpha^2 + \beta^2}{\alpha\beta}$

d)  $\frac{\beta}{\alpha}$

539. To deposit one litre of hydrogen at 22.4 atmosphere from acidulated water, the quantity of electricity that must pass through is

a) 1 coulomb

b) 22.4 coulomb

c) 96500 coulomb

d) 193000 coulomb

540. In ballistic galvanometer, the frame in which the coil is wound is non-metallic to


a) Avoid the production of induced emf

b) Avoid the production of eddy currents

c) Increase the production of eddy currents

d) Increase the production of induced emf

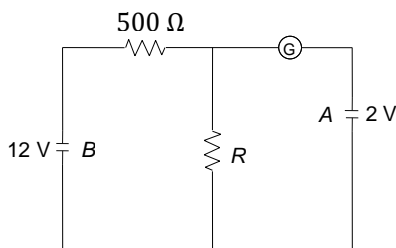541. In the circuit, the galvanometer  $G$  shows zero deflection. If the batteries  $A$  and  $B$  have negligible internal resistance, the value of the resistor  $R$  will be



a)  $200\Omega$

b)  $100\Omega$

c)  $500\Omega$

d)  $1000\Omega$

542. The resistivity of alloys =  $R_{\text{alloy}}$ ; the resistivity of constituent metals  $R_{\text{metal}}$ . Then, usually

a)  $R_{\text{alloy}} = R_{\text{metal}}$

b)  $R_{\text{alloy}} < R_{\text{metal}}$

c) There is no simple relation between  $R_{\text{alloy}}$  and  $R_{\text{metal}}$

d)  $R_{\text{alloy}} > R_{\text{metal}}$

543. The production of *e.m.f.* by maintaining a difference of temperature between the two junctions of two different metals is known as

a) Joule effect

b) Seebeck effect

c) Peltier effect

d) Thomson effect

544. An electric heater is heated respectively by *d. c.* and *a. c.* Applied voltage for both the currents is equal. The heat produced per second will be

a) More on heating by *a. c.* source

b) More on heating by *d. c.* source



- c) Same for both d) None of the above

545. A coil takes 15 min to boil a certain amount of water; another coil takes 20 min for the same process. Time taken to boil the same amount of water when both coils are connected in series

- a) 5 min b) 8.6 min c) 35 min d) 30 min


546. The electron drift speed is small and the charge of the electron is also small but still, we obtain large current in a conductor. This is due to

- a) The conducting property of the conductor  
 b) The resistance of the conductor is small  
 c) The electron number density of the conductor is small  
 d) The electron number density of the conductor is enormous

547. A small power station supplies electricity to 5000 lamps connected in parallel. Each lamp has a resistance of 220 and is operated at 220 V. The total current supplied by the station is


- a) 2500 A b) 3500 A c) 5000 A d) 10000 A

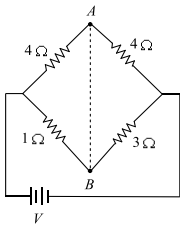548. In the circuit shown, if a conducting wire is connected between points A and B, the current in this wire will



- a) Be zero b) Flow from B to A  
 c) Flow from A to B d) Flow in the direction which will be decided by the value of V

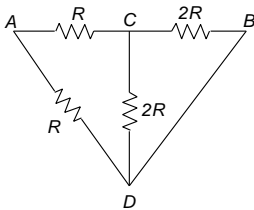549. The effective resistance between points A and B is




- a)  $R$  b)  $\frac{R}{3}$  c)  $\frac{2R}{3}$  d)  $\frac{3R}{5}$

550. A moving coil galvanometer has 150 equal divisions. Its current sensitivity is 10 divisions per milliampere and voltage sensitivity is 2 divisions per millivolt. In order that each division reads 1V, the resistance in Ohm's needed to be connected in series with the coil will be


- a)  $10^3$  b)  $10^5$  c) 99995 d) 9995

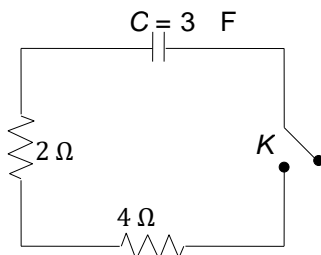551. A capacitor of capacitance  $3\mu\text{F}$  is first charged by connecting across 10 V battery, then it is allowed to get discharged through  $2\Omega$  and  $4\Omega$  resistor by closing the key K as shown in figure. The total energy dissipated in  $2\Omega$  resistor is equal to




- a) 0.15 mJ b) 0.5 mJ c) 0.05 mJ d) 1.0 mJ

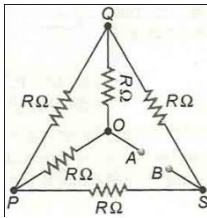
552. If each of the resistances in the network in figure.  $R$ , the equivalent resistance between terminals A and B is



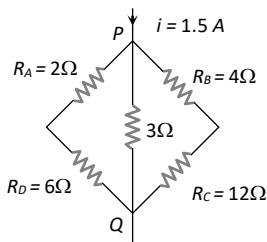- a)  $5R$                       b)  $2R$                       c)  $4R$                       d)  $R$
553. The tolerance level of a resistor with the colour code red, blue, orange, gold is  
 a)  $\pm 5\%$                       b)  $\pm 10\%$                       c)  $\pm 20\%$                       d)  $\pm 40\%$
554. A given piece of wire of length  $l$  and radius  $r$  is having a resistance  $R$ . This wire is stretched uniformly to a wire of radius  $\frac{r}{2}$ . What is the new resistance?  
 a)  $3R$                       b)  $8R$                       c)  $16R$                       d)  $2R$
555. The expression for thermo e.m.f. in a thermocouple is given by the relation  $E = 40\theta - \frac{\theta^2}{20}$ , where  $\theta$  is the temperature difference of two junctions. For this, the neutral temperature will be  
 a)  $100^\circ\text{C}$                       b)  $200^\circ\text{C}$                       c)  $300^\circ\text{C}$                       d)  $400^\circ\text{C}$
556. The steady current flows in a metallic conductor of non-uniform cross-section. The quantity/quantities constant along the length of the conductor is/are  
 a) Current, electric field and drift velocity                      b) Drift speed only  
 c) Current and drift speed                      d) Current only
557. Potential difference between the points  $P$  and  $Q$  in the electric circuit shown is




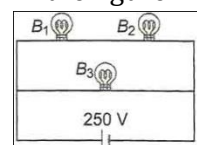- a)  $4.5V$                       b)  $1.2V$                       c)  $2.4V$                       d)  $2.88V$
558. Who among the following scientists made the statement –“Chemical change can produce electricity”  
 a) Galvani                      b) Faraday                      c) Coulomb                      d) Thomson
559. A thin wire of resistance  $4\Omega$  is bent to form a circle. The resistance across any diameter is  
 a)  $4\Omega$                       b)  $2\Omega$                       c)  $1\Omega$                       d)  $8\Omega$
560. A wire  $P$  has a resistance of  $20\Omega$ . Another wire  $Q$  of same material but length twice that of  $P$  has resistance of  $8\Omega$ . If  $r$  is the radius of cross-section of  $P$ , the radius of cross-section of  $Q$  is  
 a)  $r$                       b)  $\frac{r}{\sqrt{2}}$                       c)  $\sqrt{5}r$                       d)  $2r$
561. A  $100W$  bulb  $B_1$  and two  $60W$  bulb  $B_2$  and  $B_3$  are connected to a  $250V$  source as shown in the figure.



Now  $W_1, W_2$  and  $W_3$  are the out-put powers of the bulbs  $B_1, B_2$  and  $B_3$  respectively. Then

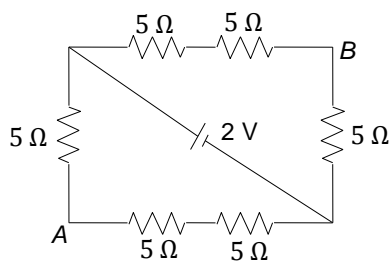- a)  $W_1 > W_2 = W_3$                       b)  $W_1 > W_2 > W_3$                       c)  $W_1 < W_2 = W_3$                       d)  $W_1 < W_2 < W_3$
562. The electric intensity  $E$ , current density  $j$  and specific resistance  $k$  are related to each other by the relation  
 a)  $E = j/k$                       b)  $E = jk$                       c)  $E = k/j$                       d)  $k = jE$
563. The kirchoff;s forst law ( $\sum i = 0$ )and second law ( $\sum iR = \sum E$ )where the symbols have their usual meanings, are respectively based on  
 a) Conservation of charge, conversion of momentum  
 b) Conservation of energy, conservation of charge  
 c) Conservation of momentum, conservation of charge  
 d) Conservation of charge, conservation of energy
564. In the circuit shown in figure the potential difference between the points  $A$  and  $B$  will be



- a)  $\frac{2}{3}V$                       b)  $\frac{8}{9}V$                       c)  $\frac{4}{3}V$                       d) 2V

565. For goldplating on a copper chain, the substance required in the form of solution is

- a) Copper sulphate                      b) Copper chloride  
c) Potassium cyanide                      d) Potassium aurocyanide

566. A milliammeter of range 10 mA has a coil of resistance 1 Ω. To use it as voltmeter of range 10 volt, the resistance that must be connected in series with it, will be

- a) 999 Ω                      b) 99 Ω                      c) 1000 Ω                      d) None of these

567. Two wires of resistance  $R_1$  and  $R_2$  have temperature coefficient of resistances  $\alpha_1$  and  $\alpha_2$  respectively. These are joined in series. The effective temperature coefficient of resistance is

- a)  $\frac{\alpha_1 + \alpha_2}{2}$                       b)  $\sqrt{\alpha_1 \alpha_2}$                       c)  $\frac{\alpha_1 R_1 + \alpha_2 R_2}{R_1 + R_2}$                       d)  $\frac{\sqrt{R_1 R_2 \alpha_1 \alpha_2}}{\sqrt{R_1^2 + R_2^2}}$

568. Conductivity increases in the order of

- a) Al, Ag, Cu                      b) Al, Cu, Ag                      c) Cu, Al, Ag                      d) Ag, Cu, Al


569. A current of 1.5 A flows through a copper voltmeter. The thickness of copper deposited on the electrode surface of area 50 cm<sup>2</sup> in 20 min is (density of Cu=9000 kgm<sup>-3</sup>; ECE of Cu =  $3.3 \times 10^{-7}$  kgC<sup>-1</sup>)

- a)  $1.3 \times 10^{-4}$  m                      b)  $1.3 \times 10^{-5}$  m                      c)  $2.6 \times 10^{-4}$  m                      d)  $2.6 \times 10^{-5}$  m

570. If resistance of the filament increases with temperature, what will be power dissipated in a 220 V- 100 W lamp when connected to 110 V power supply

- a) 25 W                      b) < 25 W                      c) > 25 W                      d) None of these

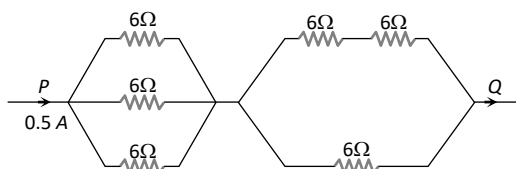571. Resistances of 6 ohm each are connected in the manner shown in adjoining figure. With the current 0.5 ampere as shown in figure, the potential difference  $V_P - V_Q$  is



- a) 3.6 V                      b) 6.0 V                      c) 3.0 V                      d) 7.2 V


572. What is the volume of hydrogen liberated at NTP by the amount of charge which liberates 0.3175 g of copper?

- a) 224 cc                      b) 112 cc                      c) 56 cc                      d) 1120 cc

573. A coil develops heat of 800 cal/sec. When 20 volts is applied across its ends. The resistance of the coil is (1 cal = 4.2 joule)

- a) 1.2 Ω                      b) 1.4 Ω                      c) 0.12 Ω                      d) 0.14 Ω

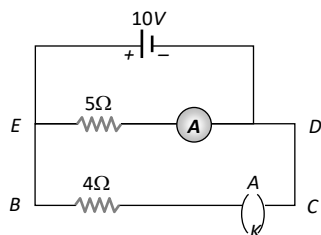574. In the given figure, when key K is opened, the reading of the ammeter A will be




- a) 50 A                      b) 2 A                      c) 0.5 A                      d)  $\frac{10}{9}$  A

575. An electric wire of length  $L$  and area of cross-section  $a$  has resistance  $R$  ohm. Another wire of the same material having same length and area of cross-section  $4a$  has a resistance of

- a)  $4R$                                       b)  $R/4$                                       c)  $R/16$                                       d)  $16R$

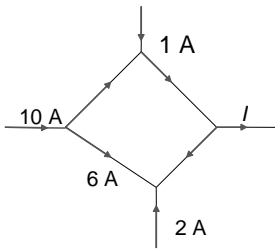576. The figure shows a network of currents. The magnitude of current is shown here. The current  $I$  will be



- a) 3A                                      b) 9A                                      c) 13A                                      d) 19A

577. An ammeter of  $5$  ohm resistance can read  $5$  mA. If it is to be used to read  $100$  volt, how much resistance is to be connected in series

- a)  $19.9995 \Omega$                                       b)  $199.995 \Omega$                                       c)  $1999.95 \Omega$                                       d)  $19995 \Omega$

578. The thermo-emf of a thermocouple is  $25 \mu V/^\circ C$  at room temperature. A galvanometer of  $40 \Omega$  resistance, capable of detecting current as low as  $10^{-5}$  A, is connected with the thermocouple. The smallest temperature difference that can be detected by this system is

- a)  $16^\circ C$                                       b)  $12^\circ C$                                       c)  $8^\circ C$                                       d)  $20^\circ C$


579. An ionization chamber with parallel conducting plates as anode and cathode has  $5 \times 10^7$  electrons and the same number of singly-charged positive ions per  $cm^3$ . The electrons are moving at  $0.4$  m/s. The current density from anode to cathode is  $4 \mu A/m^2$ . The velocity of positive ions moving towards cathode is

- a)  $0.4$  m/s                                      b)  $16$  m/s                                      c) Zero                                      d)  $0.1$  m/s

580. In a potentiometer experiment, when three cells A, B and C care connected in series the balancing length is found to be  $740$  cm. if A and B are connected in series balancing length is  $540$  cm. then the emf of  $E_A, E_B$  and  $E_C$  are respectively (in volts)

- a) 1,1.2 and 1.5                                      b) 1,2 and 3                                      c) 1.5,2 and 3                                      d) 1.5, 2.5 and 3.5

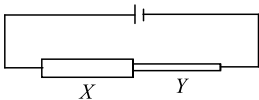581. Figure below shows a thick copper rod  $X$  and a thin copper wire  $Y$  joined in series. They carry a current which is sufficient to make  $Y$  much hotter than  $X$




Which one of the following is correct?

- |  |   |
|--|---|
| Number density of<br>Conduction<br>electrons | Mean time between<br>collisions of the<br>electrons |
| a) Same in $X$ and $Y$                       | less in $X$ than in $Y$                             |
| b) Same in $X$ and $Y$                       | same in $X$ and $Y$                                 |
| c) Same in $X$ and $Y$                       | more in $X$ than in $Y$                             |
| d) more in $X$ and $Y$                       | less in $X$ than in $Y$                             |

582. A steady current  $i$  is flowing through a conductor of uniform cross-section. Any segment of the conductor has

- a) Zero charge                                      b) Only positive charge  
c) Only negative charge                                      d) Charge proportional to current  $i$

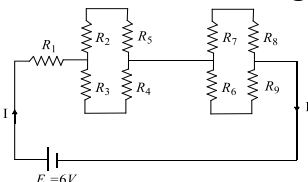583. Nine resistors each of  $1$  kΩ are conneted to a battery of  $6$  V as shown in the circuit given below. What is the total current flowing in the circuit



- a)  $3mA$                       b)  $\frac{2}{3}mA$                       c)  $\frac{3}{2}mA$                       d)  $2mA$

584. In order to increase the sensitivity of galvanometer

- a) The suspension wire should be made stiff  
 b) Area of the coil should be reduced  
 c) The magnetic field should be increased  
 d) The number of turns in the coil should be reduced


585. When the number of turns of the coil is doubled, the current sensitivity of a moving coil galvanometer is doubled whereas the voltage sensitivity of the galvanometer

- a) Remains the same      b) Is halved                      c) Is doubled                      d) Is quadrupled

586. The reading of a high resistance voltmeter when a cell is connected across it is  $2.2V$ . When the terminals of the cell are also connected to a resistance of  $5\Omega$  the voltmeter reading drops to  $1.8V$ . Find the internal resistance of the cell

- a)  $1.2\Omega$                       b)  $1.3\Omega$                       c)  $1.1\Omega$                       d)  $1.4\Omega$

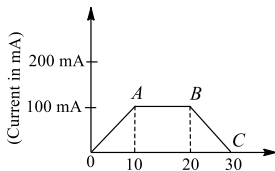587. In copper voltameter, mass deposited in 30 s is  $m$  gram. If the time current is as shown in figure, ECE of copper is



- a)  $m$                       b)  $m/2$                       c)  $0.6m$                       d)  $0.1m$


588. Two cells with the same emf  $E$  and different internal resistances  $r_1$  and  $r_2$  are connected in series to an external resistance  $R$ . the value of  $R$  so that the potential difference across the first cell be zero is

- a)  $\sqrt{r_1 r_2}$                       b)  $r_1 + r_2$                       c)  $r_1 - r_2$                       d)  $\frac{r_1 + r_2}{2}$

589. The resistivity of a wire depends on its

- a) Length                      b) Area of cross-section      c) Shape                      d) Material

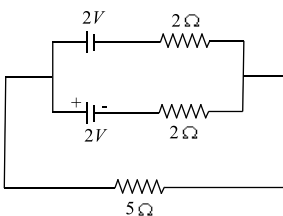590. In the circuit shown, the current through the  $5\Omega$  resistor is



- a)  $\frac{8}{3}A$                       b)  $\frac{9}{13}A$                       c)  $\frac{4}{13}A$                       d)  $\frac{1}{3}A$

591. A  $5.0A$  current is setup in an external circuit by a  $6.0$  storage battery for  $6.0$  min. The chemical energy of the battery is reduced by

- a)  $1.08 \times 10^4 J$                       b)  $1.08 \times 10^3 J$                       c)  $1.8 \times 10^4 J$                       d)  $1.8 \times 10^3 J$

592. A heater coil is cut into two equal parts and only one part is now used in the heater. The heat generated will now be

- a) Doubled                      b) Four times                      c) One-fourth                      d) Halved

593. The resistance of a galvanometer is  $90\ ohm$ . If only 10 percent of the main current may flow through the galvanometer, in which way and of what value, a resistor is to be used

- a)  $10\ ohm$  in series      b)  $10\ ohm$  in parallel      c)  $810\ ohm$  in series      d)  $810\ ohm$  in parallel

594. One junction of a certain thermo-couple is at a fixed temperature  $T_r$  and the other junction is at temperature  $T$ . The thermo electric force for this is expressed by

$$E = K(T - T_r) \left[ T_0 + \frac{1}{2}(T^2 + T_r^2) \right].$$


At temperature  $T = T_0/2$  the thermoelectric power is

- a)  $\frac{1}{2} K T_0$                       b)  $\frac{3}{2} K T_0$                       c)  $\frac{1}{2} K T_0^2$                       d)  $\frac{1}{2} K (T_0 - T_r)^2$

595. An electric lamp is marked 60 W, 230 V. The cost of kilowatt hour of power is Rs 1.25. The cost of using this lamp 8 h a day for 30 days is

- a) Rs 10                      b) Rs 16                      c) Rs 18                      d) Rs 20

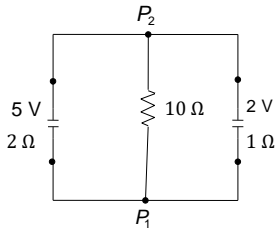
596. A 5V battery with internal resistance  $2\ \Omega$  and a 2V battery with internal resistance  $1\ \Omega$  are connected to a  $10\ \Omega$  resistor as shown in the figure



The current in the  $10\ \Omega$  resistor is


- a) 0.27A,  $P_2$  to  $P_1$                       b) 0.03A,  $P_1$  to  $P_2$                       c) 0.03A,  $P_2$  to  $P_1$                       d) 0.27A,  $P_1$  to  $P_2$

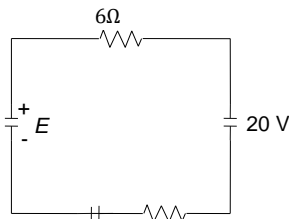597. Calculate the value E, for given circuit, when value of 2A current is either flowing in clockwise or anticlockwise direction




- a) 32 V, 8V                      b) 38V, 2V                      c) 32V, 2V                      d) 30V, 8V

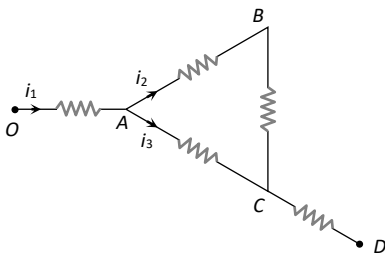598. The current in the arm CD of the circuit will be



- a)  $i_1 + i_2$                       b)  $i_2 + i_3$                       c)  $i_1 + i_3$                       d)  $i_1 - i_2 + i_3$

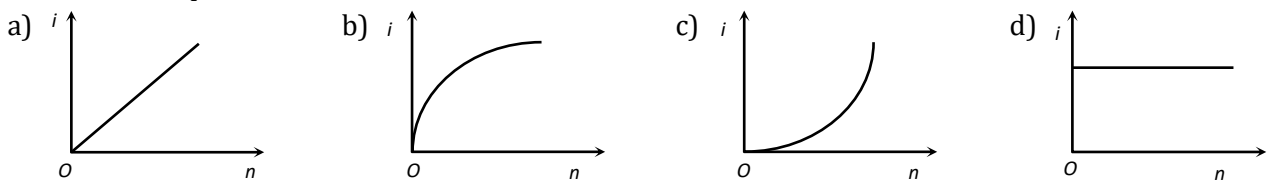599. A battery consists of a variable number 'n' of identical cells having internal resistances connected in series. The terminals of battery are short circuited and the current  $i$  is measured. Which of the graph below shows the relationship between  $i$  and  $n$



600. Assume that each atom of copper contributes one electron. If the current flowing through a copper wire of 1 mm diameter is 1.1 A, the drift velocity of electrons will be (density of Cu =  $9\ \text{g cm}^{-3}$ , atomic wt. of Cu = 63)


- a)  $0.3\ \text{mm s}^{-1}$                       b)  $0.5\ \text{mm s}^{-1}$                       c)  $0.1\ \text{mm s}^{-1}$                       d)  $0.2\ \text{mm s}^{-1}$

601. The specific resistance of a wire is  $\rho$ , its volume is  $3\ \text{m}^3$  and its resistance is  $3\ \Omega$ , then its length will be

- a)  $\sqrt{1/\rho}$                       b)  $3/\sqrt{\rho}$                       c)  $\sqrt{3}/\rho$                       d)  $\rho/\sqrt{3}$

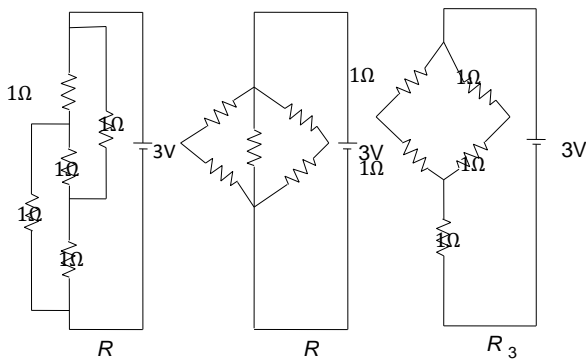
602. Two similar thermocouples, made of dissimilar metals A and B are connected as shown in figure through a key K and a sensitive galvanometer G. One of the thermocouples is dipped in a hot bath maintained at temperature  $t_2$  and the other in a cold bath at temperature  $t_1$ . When the key is pressed, a deflection is seen in the galvanometer because





- a)  $P_1 > P_2 > P_3$       b)  $P_1 > P_3 > P_2$       c)  $P_2 > P_1 > P_3$       d)  $P_3 > P_2 > P_1$

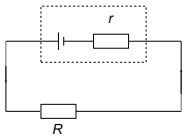613. A cell of internal resistance  $r$  is connected to a load of resistance  $R$ . Energy is dissipated in the load, but some thermal energy is also wasted in the cell. The efficiency of such an arrangement is found from the expression



$$\frac{\text{energy dissipated in the load}}{\text{energy dissipated in the complete circuit}}$$

Which of the following gives the efficiency in this case?

- a)  $\frac{r}{R}$       b)  $\frac{R}{r}$       c)  $\frac{r}{R+r}$       d)  $\frac{R}{R+r}$

614. The resistance of a wire is  $5\Omega$  at  $50^\circ\text{C}$  and  $6\Omega$  at  $100^\circ\text{C}$ . The resistance of the wire at  $0^\circ\text{C}$  will be

- a)  $2\Omega$       b)  $1\Omega$       c)  $4\Omega$       d)  $3\Omega$

615. To convert a moving coil galvanometer (MCG) into a voltmeter

- a) A high resistance  $R$  is connected in parallel with MCG      b) A low resistance  $r$  is connected in parallel with MCG  
c) A low resistance  $r$  is connected in series with MCG      d) A high resistance  $R$  is connected in series with MCG

616. A dry cell of emf  $1.5\text{ V}$  and internal resistance  $0.10\Omega$  is connected across a resistor in series with a very low resistance ammeter. When the circuit is switched on, the ammeter reading settles to a steady rate of  $2\text{ A}$ . Find (i) chemical energy consumption of the cell (ii) energy dissipation inside the cell (iii) energy dissipation inside the resistor (iv) power output of source is

- a) (i)  $3\text{ W}$  (ii)  $0.4\text{ W}$  (iii)  $2.6\text{ W}$  (iv)  $2.6\text{ W}$       b) (i)  $0.4\text{ W}$  (ii)  $3\text{ W}$  (iii)  $2.6\text{ W}$  (iv)  $2.6\text{ W}$   
c) (i)  $2.6\text{ W}$  (ii)  $0.4\text{ W}$  (iii)  $9\text{ W}$  (iv)  $1\text{ W}$       d) None of the above

617. A wire has a resistance of  $12\text{ ohm}$ . It is bent in the form of equilateral triangle. The effective resistance between any two corners of the triangle is

- a)  $9\text{ ohm}$       b)  $12\text{ ohm}$       c)  $6\text{ ohm}$       d)  $8/3\text{ ohm}$

618. One end each of a resistance  $r$  capacitor  $C$  and resistance  $2r$  are connected together. The other ends are respectively connected to the positive terminals of batteries,  $P, Q, R$  having respectively emf's  $E, E$  and  $2E$ . The negative terminals of the batteries are then connected together. In this circuit, with steady current the potential drop across the capacitor is

- a)  $\frac{E}{3}$       b)  $\frac{E}{2}$       c)  $\frac{2E}{3}$       d)  $E$

619. Two cells having the internal resistance  $0.2\Omega$  and  $0.4\Omega$  are connected in parallel. The voltage across the battery terminal is  $1.5\text{ V}$ . The emf of first cell is  $1.2\text{ V}$ . The emf of second cell is


- a)  $2.7\text{ V}$       b)  $2.1\text{ V}$       c)  $3\text{ V}$       d)  $4.2\text{ V}$

620. The equivalent resistance of  $n$  resistors each of same resistance when connected in series is  $R$ . If the same resistances are connected in parallel, the equivalent resistance will be

- a)  $R/n^2$       b)  $R/n$       c)  $n^2R$       d)  $nR$



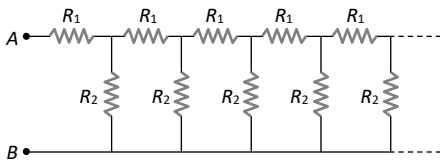621. An infinite sequence of resistances is shown in the figure. The resultant resistance between  $A$  and  $B$  will be, when  $R_1 = 1 \text{ ohm}$  and  $R_2 = 2 \text{ ohm}$




- a) Infinity                                      b)  $1 \Omega$                                       c)  $2 \Omega$                                       d)  $1.5 \Omega$

622. A  $200 \text{ W}$  and a  $100 \text{ W}$  bulb, both meant for operation at  $220 \text{ V}$  are connected in series. When connected to a  $220 \text{ V}$  supply the power consumed by the combination is


- a)  $33.3 \text{ W}$                                       b)  $66.7 \text{ W}$                                       c)  $300 \text{ W}$                                       d)  $100 \text{ W}$

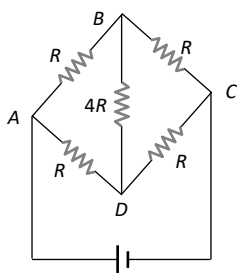623. Five resistors of given values are connected together as shown in the figure. The current in the arm  $BD$  will be



- a) Half the current in the arm  $ABC$                                       b) Zero  
c) Twice the current in the arm  $ABC$                                       d) Four times the current in the arm  $ABC$

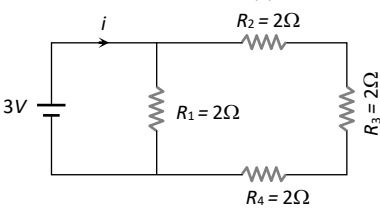624. What is the current ( $i$ ) in the circuit as shown in figure



- a)  $2 \text{ A}$                                       b)  $1.2 \text{ A}$                                       c)  $1 \text{ A}$                                       d)  $0.5 \text{ A}$

625. A galvanometer of resistance  $100\Omega$  is converted to a voltmeter of range  $10 \text{ V}$  by connecting a resistance of  $10\text{k}\Omega$ . The resistance required to convert the same galvanometer to an ammeter of range  $1 \text{ A}$  is

- a)  $0.4\Omega$                                       b)  $0.3\Omega$                                       c)  $1.2\Omega$                                       d)  $0.1\Omega$


626. The resistance of a  $10\text{m}$  long wire is  $10\Omega$ . Its length is increased by  $25\%$  by stretching the wire uniformly. Then the resistance of the wire will be

- a)  $12.5 \Omega$                                       b)  $14.5 \Omega$                                       c)  $15.6 \Omega$                                       d)  $16.6 \Omega$

627. Resistance of  $100 \text{ cm}$  long potentiometer wire is  $10\Omega$ , it is connected to a battery ( $2 \text{ volt}$ ) and a resistance  $R$  in series. A source of  $10 \text{ mV}$  gives null point at  $40 \text{ cm}$  length, then external resistance  $R$  is

- a)  $490 \Omega$                                       b)  $790 \Omega$                                       c)  $590 \Omega$                                       d)  $990 \Omega$

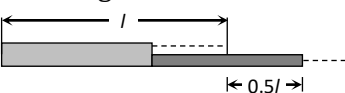628. In order to quadruple the resistance of a uniform wire, a part of its length was uniformly stretched till the final length of the entire wire was  $1.5$  times the original length, the part of the wire was fraction equal to



- a)  $1/8$                                       b)  $1/6$                                       c)  $1/10$                                       d)  $1/4$

629. A galvanometer has a resistance  $50\Omega$ . A resistance of  $5\Omega$  is connected parallel to it. Fraction of the total current flowing through galvanometer is

- a)  $\frac{1}{10}$                                       b)  $\frac{1}{11}$                                       c)  $\frac{1}{50}$                                       d)  $\frac{2}{15}$

630. The thermo emf of copper-constantan couple is  $40\mu\text{V}$  per degree. The smallest temperature difference that can be detected with this couple and a galvanometer of  $100\Omega$  resistance capable of measuring the maximum current of  $1\mu\text{A}$  is

- a)  $10^{\circ}\text{C}$                       b)  $7.5^{\circ}\text{C}$                       c)  $5.0^{\circ}\text{C}$                       d)  $2.5^{\circ}\text{C}$


631. A parallel combination of two resistors, of  $1\Omega$  each, is connected in series with a  $1.5\Omega$  resistor. The total combination is connected across a  $10\text{V}$  battery. The current flowing in the circuit is

- a)  $5\text{A}$                       b)  $20\text{A}$                       c)  $0.2\text{A}$                       d)  $0.4\text{A}$

632. Dimensions of a block are  $1\text{ cm} \times 1\text{ cm} \times 100\text{cm}$ . If specific resistance of its material is  $3 \times 10^{-7}\text{ ohm - m}$ , then the resistance between the opposite rectangular faces is


- a)  $3 \times 10^{-9}\text{ ohm}$                       b)  $3 \times 10^{-7}\text{ ohm}$                       c)  $3 \times 10^{-5}\text{ ohm}$                       d)  $3 \times 10^{-3}\text{ ohm}$

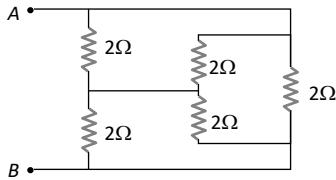633. Find the equivalent resistance across  $AB$



- a)  $1\Omega$                       b)  $2\Omega$                       c)  $3\Omega$                       d)  $4\Omega$

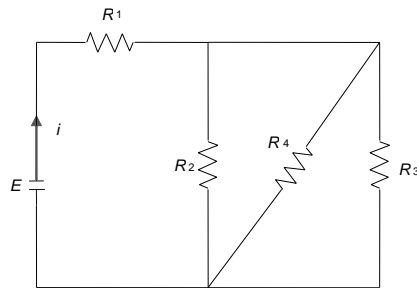634. In the circuit given  $E=0.6\text{V}$ ,  $R_1=100\Omega$ ,  $R_2 = R_3 = 50\Omega$ ,  $R_4 = 75\Omega$ . The equivalent resistance of the circuit, in ohm is



- a)  $11.875$                       b)  $26.31$                       c)  $118.75$                       d) None of these

635. Three resistances  $4\Omega$  each are connected in the form of an equilateral triangle. The effective resistance between two corners is

- a)  $8\Omega$                       b)  $12\Omega$                       c)  $\frac{3}{8}\Omega$                       d)  $\frac{8}{3}\Omega$

636. The material of wire of potentiometer is

- a) Copper                      b) Steel                      c) Manganin                      d) Aluminium

637. A Copper wire of length  $1\text{ m}$  and radius  $1\text{ mm}$  is joined in series with an iron wire of length  $2\text{ m}$  and radius  $3\text{ mm}$  and a current is passed through the wires. The ratio of the current density in the wires. The ratio of the current density in the copper and iron wires is

- a)  $2:3$                       b)  $6:1$                       c)  $9:1$                       d)  $18:1$

638. If the emf of a thermocouple, one junction of which is kept  $0^{\circ}\text{C}$  is given by  $e = at + \frac{1}{2}bt^2$ , then the neutral temperature will be

- a)  $\frac{a}{b}$                       b)  $-\frac{a}{b}$                       c)  $\frac{a}{2b}$                       d)  $-\frac{1}{ab}$

639. A given carbon resistor has the following colour code of the various strips: orange, red, yellow and gold. The value of resistance in ohm is

- a)  $32 \times 10^4 \pm 5\%$                       b)  $32 \times 10^4 \pm 10\%$                       c)  $23 \times 10^4 \pm 5\%$                       d)  $23 \times 10^4 \pm 10\%$


640. The same mass of copper is drawn into two wires  $1\text{ mm}$  and  $2\text{ mm}$  thick. Two wires are connected in series and current is passed through them. Heat produced in the wire is in the ratio

- a)  $2:1$                       b)  $1:16$                       c)  $4:1$                       d)  $16:1$

641. The resistances of a wire at temperatures  $t^{\circ}\text{C}$  and  $0^{\circ}\text{C}$  are related by

- a)  $R_t = R_0(1 + at)$                       b)  $R_t = R_0(1 - at)$                       c)  $R_t = R_0^2(1 + at)$                       d)  $R_t = R_0^2(1 - at)$

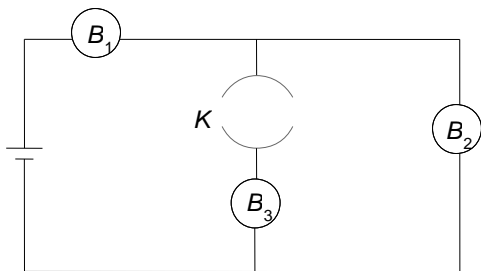642.  $B_1, B_2$  and  $B_3$  are the three identical bulbs connected to a battery of steady emf with key  $K$  closed. What happens to the brightness of the bulbs,  $B_1$  and  $B_2$  when the key is opened?




- a) Brightness of the bulb  $B_1$  increases and that of  $B_2$  decreases  
 b) Brightness of the bulbs  $B_1$  and  $B_2$  increases  
 c) Brightness of the bulb  $B_1$  decreases and  $B_2$  increases  
 d) Brightness of the bulbs  $B_1$  and  $B_2$  decreases

643. A new flashlight cell of e. m. f. 1.5 volt gives a current of 15 amp, when connected directly to an ammeter of resistance  $0.04 \Omega$ . The internal resistance of cell is


- a)  $0.04 \Omega$                       b)  $0.06 \Omega$                       c)  $0.10 \Omega$                       d)  $10 \Omega$

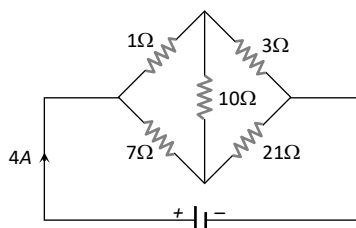644. In the circuit shown in figure, the current drawn from the battery is 4A. If  $10 \Omega$  resistor is replaced by  $20 \Omega$  resistor, then current drawn from the circuit will be



- a) 1 A                                  b) 2 A                                  c) 3 A                                  d) 0 A

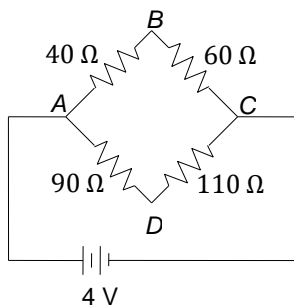645. Four resistances  $40 \Omega$ ,  $60 \Omega$ ,  $90 \Omega$  and  $110 \Omega$  make the arms of a quadrilateral  $ABCD$ . Across  $AC$  is the battery circuit, the emf of the battery being 4V and internal resistance negligible. The potential difference across  $BD$  is



- a) 1V                                  b) -1V                                  c) -0.2V                                  d) 0.2V


646. An electric current passes through a circuit containing two wires of the same material connected in parallel. If the lengths of the wires are in the ratio of  $4/3$  and radius of the wires are in the ratio of  $2/3$ , then the ratio of the current passing through the wires will be

- a) 3                                      b)  $1/3$                                       c)  $8/9$                                       d) None of these

647. In the above question if potential difference is applied, the drift velocity at temperature  $T$  is


- a) Inversely proportional to  $T$                                   b) Proportional to  $\sqrt{T}$   
 c) Zero                                      d) Finite but independent of  $T$

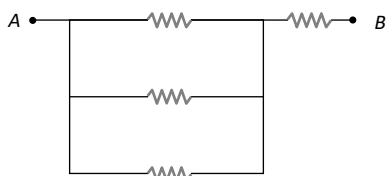648. If all the resistors shown have the value 2 ohm each, the equivalent resistance over  $AB$  is




- a) 2 ohm                                  b) 4 ohm                                  c)  $1\frac{2}{3}$  ohm                                  d)  $2\frac{2}{3}$  ohm

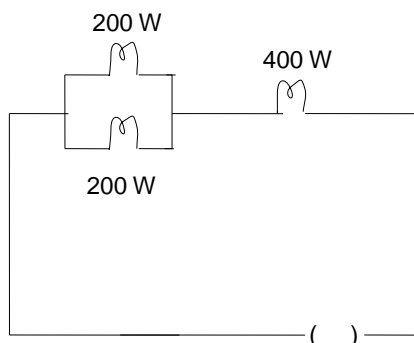649. A current through a wire depends on time  $t$  as  $i = 10 + 4t$ . The charge crossing through the section of the wire in 10 s is  
 a) 50 C                                      b) 300 C                                      c) 400 C                                      d) 4C
650. A copper and silver voltmeter are connected in parallel. If 2000 C of charge liberates the same mass of copper and silver, then charge flowing in copper voltmeter is  
 [Z(Cu) =  $3.36 \times 10^{-7} \text{ kg C}^{-1}$ , Z(Ag) =  $1.008 \times 10^{-6} \text{ kg C}^{-1}$ ]  
 a) 1250 C                                      b) 1500 C                                      c) 1750 C                                      d) 1000 C
651. Three electric bulbs of 200 W, 200 W and 400 W are shown in figure. The resultant power of the combination is




- a) 800 W                                      b) 400 W                                      c) 200 W                                      d) 600 W

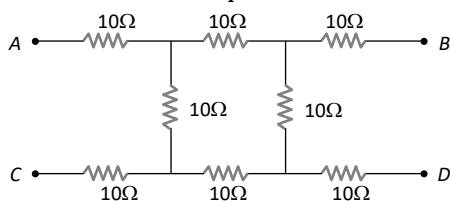652. What will be the equivalent resistance between the two points A and D




- a) 10  $\Omega$                                       b) 20  $\Omega$                                       c) 30  $\Omega$                                       d) 40  $\Omega$
653. A potentiometer wire, 10 m long, has a resistance of 40  $\Omega$ . It is connected in series with a resistance box and a 2V storage cell. If the potential gradient along the wire is ( $0.1 \text{ mVcm}^{-1}$ ), the resistance unplugged in the box is  
 a) 260  $\Omega$                                       b) 760  $\Omega$                                       c) 960  $\Omega$                                       d) 1060  $\Omega$
654. The electrolyte used in Lechlanche cell is  
 a) Copper sulphate solution                                      b) Ammonium chloride solution  
 c) Dilute sulphuric acid                                      d) Zinc sulphate
655. In a thermocouple, which of the following statements is not true  
 a) Neutral temperature depends upon the nature of materials in the thermocouple  
 b) Temperature of inversion depends upon the temperature of cold junction  
 c) When the temperature of the hot junction is equal to the temperature of inversion, the thermo emf becomes zero  
 d) When the temperature of cold junction increases, the temperature of inversion also increases
656. If current in an electric bulb changes by 1%, then the power will change by  
 a) 1%                                      b) 2%                                      c) 4%                                      d)  $\frac{1}{2}$  %
657. Neutral temperature of a thermocouple is defined as the temperature at which  
 a) The thermo e.m.f. changes sign                                      b) The thermo e.m.f. is maximum  
 c) The thermo e.m.f. is minimum                                      d) The thermo e.m.f. is zero
658. Electric power is transmitted over long distances through conducting wires at high voltage because  
 a) High voltage travels faster  
 b) Power loss is large  
 c) Power loss is less  
 d) Generator produce electrical energy at a very high voltage

659. The magnitude of  $I$  in ampere is

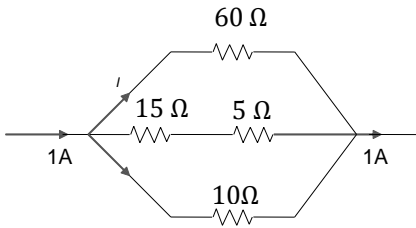


- a) 0.1                                      b) 0.3                                      c) 0.6                                      d) None of the above

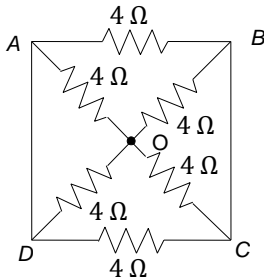660. Six equal resistances each of  $4\Omega$  are connected to form a figure. The resistance between two corners  $A$  and  $B$  is



- a)  $4\Omega$                                       b)  $4/3\Omega$                                       c)  $12\Omega$                                       d)  $2\Omega$

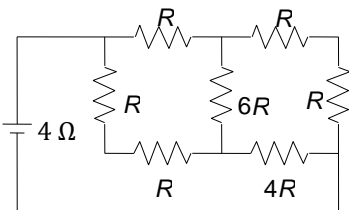661. A battery of internal resistance  $4\Omega$  is connected to the network of resistance as shown. In order to give the maximum power to the network, the value of  $R$  (in  $\Omega$ ) should be



- a)  $4/9$                                       b)  $8/9$                                       c) 2                                      d) 18

662. An electrical cable having a resistance of  $0.2\Omega$  delivers  $10\text{ kW}$  at  $200\text{ V DC}$  to a factory. What is the efficiency of transmission

- a) 65%                                      b) 75%                                      c) 85%                                      d) 95%


663. A heating coil can heat the water of a vessel from  $20^\circ\text{C}$  to  $60^\circ\text{C}$  in 30 minutes. Two such heating coils are put in series and then used to heat the same amount of water through the same temperature range. The time taken now will be (neglecting thermal capacity of the coils)

- a) 60 minutes                                      b) 30 minutes                                      c) 15 minutes                                      d) 7.5 minutes

664. What is the resistance of a carbon resistance which has bands of colours brown, black and brown

- a)  $100\Omega$                                       b)  $1000\Omega$                                       c)  $10\Omega$                                       d)  $1\Omega$

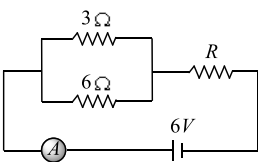665. If the ammeter in the given circuit reads  $2\text{ A}$ , the resistance  $R$  is




- a) 1 ohm                                      b) 2 ohm                                      c) 3 ohm                                      d) 4 ohm

666. Faraday's 2<sup>nd</sup> law states that mass deposited on the electrode is directly proportional to


- a) Atomic mass                                      b) Atomic mass  $\times$  Velocity  
c) Atomic mass/Valency                                      d) Valency

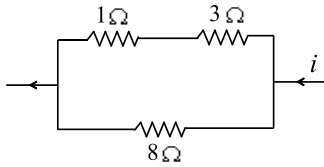667. Power dissipated across the  $8\Omega$  resistor in the circuit shown here is  $2\text{ watt}$ . The power dissipated in watt units across the  $3\Omega$  resistor is



- a) 0.5                      b) 3.0                      c) 2.0                      d) 1.0

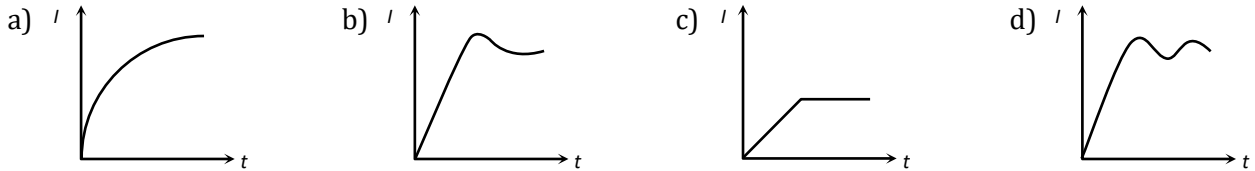668. When an electric heater is switched on, the current flowing through it ( $i$ ) is plotted against time ( $t$ ). Taking into account the variation of resistance with temperature, which of the following best represents the resulting curve




669. Which of the following are true, when the cells are connected in series?

- a) Current capacity decreases                      b) Current capacity increases  
c) The emf decreases                      d) The emf increases

670. Two wires have lengths, diameters and specific resistances all in the ratio of 1 : 2. The resistance of the first wire is 10Ω. Resistance of the second wire in ohm will be

- a) 5                      b) 10                      c) 20                      d) Infinite

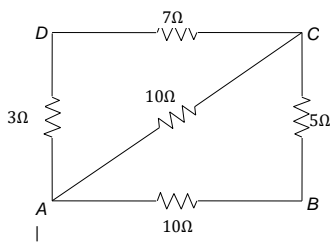671. The resistance is connected as shown in the figure below. Find the equivalent resistance between the points  $A$  and  $B$ .




- a) 205Ω                      b) 10 Ω                      c) 3.5 Ω                      d) 5 Ω

672. The  $n$  rows each containing  $m$  cells in series are joined in parallel. Maximum current is taken from this combination across an external resistance of 3 Ω. If the total number of cells used are 24 and internal resistance of each cell is 0.5 Ω, then


- a)  $m = 8, n = 3$                       b)  $m = 6, n = 4$                       c)  $m = 12, n = 2$                       d)  $m = 2, n = 12$

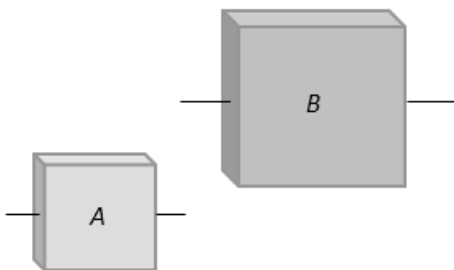673.  $A$  and  $B$  are two square plates of same metal and same thickness but length of  $B$  is twice that of  $A$ . Ratio of resistances of  $A$  and  $B$  is



- a) 4 : 1                      b) 1 : 4                      c) 1 : 1                      d) 1 : 2

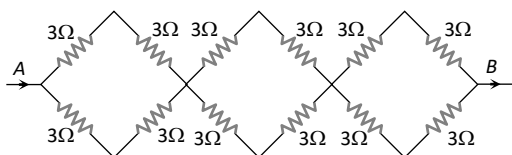
674. In the network of resistors shown in the adjoining figure, the equivalent resistance between  $A$  and  $B$  is



- a) 54 ohm                      b) 18 ohm                      c) 36 ohm                      d) 9 ohm

675. Two bars of radius  $r$  and  $2r$  are kept in contact as shown. An electric current  $i$  is passed through the bars.

Which one of the following is correct?

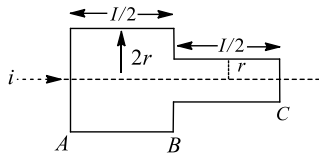


- a) Heat produced in bar  $BC$  is 4 times the heat produced in bar  $AB$
- b) Electric field in both halves is equal
- c) Current density across  $AB$  is doubled that of across  $BC$
- d) Potential difference across  $AB$  is 4 times that of across  $BC$

676. The alloys constantan and manganin are used to make standard resistance because they have

- a) Low resistivity
- b) High resistivity
- c) Low temperature coefficient of resistance
- d) Both (b) and (c)

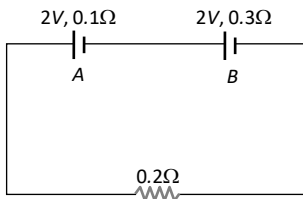677. The internal resistances of two cells shown are  $0.1 \Omega$  and  $0.3 \Omega$ . If  $R = 0.2 \Omega$ , the potential difference across the cell




- a)  $B$  will be zero
- b)  $A$  will be zero
- c)  $A$  and  $B$  will be  $2V$
- d)  $A$  will be  $> 2V$  and  $B$  will be  $< 2V$

678. In a Wheatstone's bridge, three resistances  $P$ ,  $Q$  and  $R$  connected in the three arms and the fourth arm is formed by two resistances  $S_1$  and  $S_2$  connected in parallel. The condition for the bridge to be balanced will be

- a)  $\frac{P}{Q} = \frac{2R}{S_1 + S_2}$
- b)  $\frac{P}{Q} = \frac{R(S_1 + S_2)}{S_1 S_2}$
- c)  $\frac{P}{Q} = \frac{R(S_1 + S_2)}{2S_1 S_2}$
- d)  $\frac{P}{Q} = \frac{R}{S_1 + S_2}$

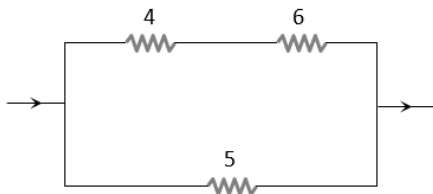679. In the circuit shown in figure, the heat produced in  $5 \text{ ohm}$  resistance is  $10 \text{ calories per second}$ . The heat produced in  $4 \text{ ohm}$  resistance is



- a)  $1 \text{ cal/sec}$
- b)  $2 \text{ cal/sec}$
- c)  $3 \text{ cal/sec}$
- d)  $4 \text{ cal/sec}$

680. In a potentiometer experiment the balancing with a cell is at length  $240 \text{ cm}$ . on shunting the cell with a resistance of  $2 \Omega$ , the balancing length becomes  $120 \text{ cm}$ . the internal resistance of cell is

- a)  $4 \Omega$
- b)  $2 \Omega$
- c)  $1 \Omega$
- d)  $0.5 \Omega$

681. A current  $I$  is passing through a wire having two sections  $P$  and  $Q$  of uniform diameters  $d$  and  $d/2$  respectively. If the mean drift velocity of electrons in sections  $P$  and  $Q$  is denoted by  $v_P$  and  $v_Q$  respectively, then

- a)  $v_P = v_Q$
- b)  $v_P = \frac{1}{2} v_Q$
- c)  $v_P = \frac{1}{4} v_Q$
- d)  $v_P = 2v_Q$


682. The relaxation time in conductors

- a) Increases with the increase of temperature
- b) Decreases with the increase of temperature
- c) It does not depend on temperature
- d) All of sudden changes at  $400 \text{ K}$


683. Two resistances  $R$  and  $2R$  are connected in parallel in an electric circuit. The thermal energy developed in  $R$  and  $2R$  are in the ratio

- a)  $1 : 2$
- b)  $2 : 1$
- c)  $1 : 4$
- d)  $4 : 1$

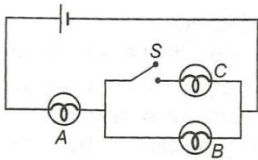
684. In the given figure.  $A$ ,  $B$  and  $C$  are three identical bulbs. When the switch  $S$  is closed



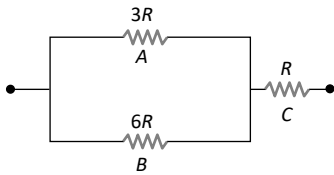- a) The brightness of bulb  $A$  does not change and that of  $B$  decreases  
 b) The brightness of bulb  $A$  increases and that of  $B$  decreases  
 c) The brightness of  $A$  increases bulb  $B$  does not glow  
 d) The brightness of both bulbs  $A$  not  $B$  decrease
685. Three resistances each of  $4\Omega$  are connected in the form of an equilateral triangle. The effective resistance between any two corners is  
 a)  $(3/8)\Omega$                       b)  $(8/3)\Omega$                       c)  $8\Omega$                       d)  $12\Omega$
686. Three resistance  $A, B$  and  $C$  have values  $3R, 6R$  and  $R$  respectively. When some potential difference is applied across the network, the thermal powers dissipated by  $A, B$  and  $C$  are in the ratio







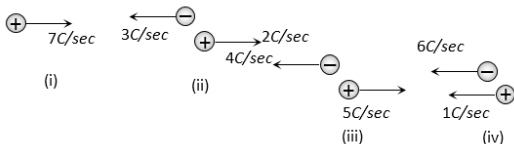- a) 2 : 3 : 4                      b) 2 : 4 : 3                      c) 4 : 2 : 3                      d) 3 : 2 : 4
687. 12 cells each having same emf are connected in series with some cells wrongly connected. The arrangement is connected in series with an ammeter and two cells which are in series. Current is 3 A when cells and battery aid each other and is 2 A when cells and battery oppose each other. The number of cells wrongly connected is  
 a) 4                      b) 1                      c) 3                      d) 2
688. Three resistance  $P, Q, R$  each of  $2\Omega$  and an unknown resistance  $S$  form the four arms of a wheatstone bridge circuit. When a resistance of  $6\Omega$  is connected in parallel to  $S$  the bridge gets balanced. What is the value of  $S$   
 a)  $2\Omega$                       b)  $3\Omega$                       c)  $6\Omega$                       d)  $1\Omega$
689. A galvanometer of  $25\Omega$  resistance can read a maximum current of  $6mA$ . It can be used as a voltmeter to measure a maximum of  $6V$  by connecting a resistance to the galvanometer. Identify the correct choice in the given answers  
 a)  $1025\Omega$  in series                      b)  $1025\Omega$  in parallel                      c)  $975\Omega$  in series                      d)  $975\Omega$  in parallel
690. The dimensions of  $\frac{1}{2}\epsilon_0 E^2$  ( $\epsilon_0$ : permittivity of free space;  $E$ : electric field) is  
 a)  $[MLT]$                       b)  $[ML^2T^{-2}]$                       c)  $[ML^{-1}T^{-2}]$                       d)  $[ML^2T^{-1}]$
691. Following figure shows four situations in which positive and negative charges move horizontally through a region and gives the rate at which each charge moves. Rank the situations according to the effective current through the region greatest first



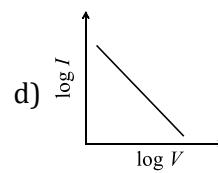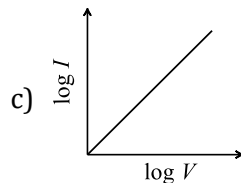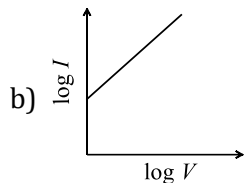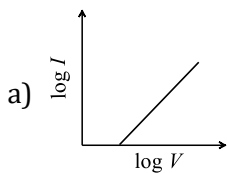- a)  $i = ii = iii = iv$                       b)  $i > ii > iii > iv$                       c)  $i = ii = iii > iv$                       d)  $i = ii = iii < iv$
692. An aluminium (resistivity  $\rho = 2.2 \times 10^{-8}\Omega - m$ ) wire of a diameter 1.4 mm is used to make a  $4\Omega$  resistor. The length of the wire is  
 a) 220 m                      b) 1000 m                      c) 280 m                      d) 1 m
693. Voltmeters  $V_1$  and  $V_2$  are connected in series across a DC line.  $V_1$  reads 80V and has a resistance of  $200\Omega V^{-1}$  and  $V_2$  has a total resistance of  $32k\Omega$ . The line voltage is  
 a) 240 V                      b) 220 V                      c) 160 V                      d) 120 V
694. When a current  $I$  is passed through a wire of constant resistance, it produces a potential difference  $V$  across its ends. The graph drawn between  $\log I$  and  $\log V$  will be






695. A galvanometer of resistance  $20\ \Omega$  shows a deflection of 10 divisions when a current of 1 mA is passed through it. If a shunt of  $4\ \Omega$  is connected and there are 50 divisions on the scale, the range of the galvanometer is

- a) 1A                                      b) 3A                                      c) 10mA                                      d) 30mA

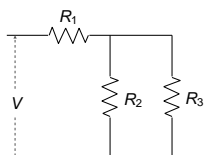696. For ensuring dissipation of same energy in all three resistors ( $R_1, R_2, R_3$ ) connected as shown in figure, their values be related as



- a)  $R_1 = R_2 = R_3$                                       b)  $R_2 = R_3$  and  $R_1 = 4R_2$   
 c)  $R_2 = R_3$  and  $R_1 = R_2/4$                                       d)  $R_1 = R_2 + R_3$


697.  $x$  g of Ag is deposited by passing 4 A of current for 1 h. How many gram of Ag will be deposited by passing 6 A for 40 min?

- a)  $2x$  g                                      b)  $4x$  g                                      c)  $x$  g                                      d)  $5x$  g

698. Resistance in the two gaps of a meter bridge are 10 ohm and 30 ohm respectively. If the resistances are interchanged the balance point shifts by

- a) 33.3 cm                                      b) 66.67 cm                                      c) 25 cm                                      d) 50 cm

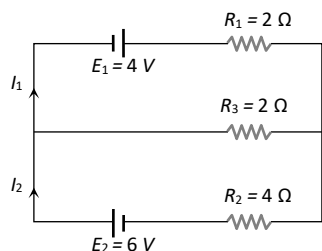699. In the circuit shown below  $E_1 = 4.0\text{ V}$ ,  $R_1 = 2\ \Omega$ ,  $E_2 = 6.0\text{ V}$ ,  $R_2 = 4\ \Omega$  and  $R_3 = 2\ \Omega$ . The current  $I_1$  is



- a) 1.6 A                                      b) 1.8 A                                      c) 1.25 A                                      d) 1.0 A

700. The amount of charge  $Q$  passed in time  $t$  through a cross-section of a wire is  $Q = 5t^2 + 3t + 1$ . The value of current at time  $t = 5$  s is

- a) 9 A                                      b) 49 A                                      c) 53 A                                      d) None of the above

701. In water voltmeter, the electrolysis of ..... takes place


- a)  $H_2O$                                       b)  $H_2SO_4$                                       c)  $H_2O$  and  $H_2SO_4$  both                                      d)  $H_2$  and  $O_2$

702. Which statement is true?

- (i) Kirchoff's law is equally applicable to both AC and DC.  
 (ii) Semiconductors have a positive temperature coefficient of resistance.  
 (iii) Meter bridge is greater sensitive when the resistance of all four arms of the bridge is of the same order.  
 (iv) The emf of a cell depends upon the size and area of electrodes.

- a) (i) and (iv)                                      b) (ii) and (iv)                                      c) (iii) and (iv)                                      d) None of these

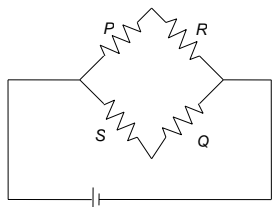703. In the circuit given, the current relation to a balanced Wheatstone's bridge is



a)  $\frac{P}{Q} = \frac{R}{S}$

b)  $\frac{P}{Q} = \frac{S}{R}$

c)  $\frac{P}{S} = \frac{Q}{R}$

d)  $\frac{P}{R} = \frac{S}{Q}$

704. A thick wire is stretched, so that its length become two times. Assuming that there is no change in its density, then what is the ratio of change in resistance of wire to the initial resistance of wire?

a) 2 : 1

b) 4 : 1

c) 3 : 1

d) 1 : 4

705. Two electric bulbs marked 40 W, 220 V and 60 W, 220 V when connected in series, across same voltage supply of 220 V, the effective power is  $P_1$  and when connected in parallel the effective power is  $P_2$ . Then  $\frac{P_1}{P_2}$

is


a) 0.5

b) 0.48

c) 0.24

d) 0.16

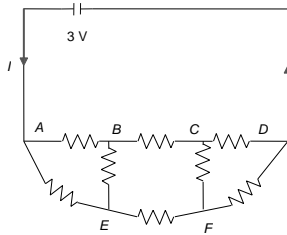706. Figure shows a network of eight resistors, each equal to  $2\ \Omega$ , connected to a 3V battery of negligible internal resistance. The current  $I$  in the circuit is



a) 0.25A

b) 0.50A

c) 0.75A

d) 1.0A

707. If the length of filament of a heater is reduced by 10%, the power of the heater will


a) Increase by about 9%

b) Increase by about 11%

c) Increase by about 19%

d) Decrease by about 10%

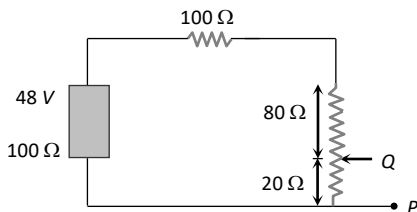708. In the circuit, the potential difference across  $PQ$  will be nearest to



a) 9.6 V

b) 6.6 V

c) 4.8 V

d) 3.2 V

709. A current of 5 A is passing through a metallic wire of cross-sectional area  $4 \times 10^{-6} \text{m}^2$ . If the density of charge carries of the wire is  $5 \times 10^{26} \text{m}^{-3}$ , the drift velocity of the electrons will be


a)  $1 \times 10^2 \text{ms}^{-1}$

b)  $1.56 \times 10^{-2} \text{ms}^{-1}$

c)  $1.56 \times 10^{-3} \text{ms}^{-1}$

d)  $1 \times 10^{-2} \text{ms}^{-1}$

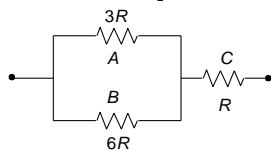710. Figure shows a network of three resistance. When some potential difference is applied across the network, the thermal powers dissipated by  $A, B$  and  $C$  in the ratio




a) 2 : 3 : 4

b) 2 : 4 : 3

c) 4 : 2 : 3

d) 3 : 2 : 4

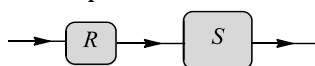711. Two plates  $R$  and  $S$  are in the form of a square and have the same thickness. A side of  $S$  is twice the side of  $R$  Compare their resistances. The direction of current is shown by an arrow head figure.



a) The resistance of  $R$  is twice that of  $S$

b) Both have the same resistance

c) The resistance of  $S$  is four times that of  $R$

d) The resistance of  $R$  is half that of  $S$

712. A resistor has a colour code of green, blue, brown and silver. What is its resistance?

a)  $5600\ \Omega \pm 10\%$

b)  $560\ \Omega \pm 5\%$

c)  $560\ \Omega \pm 10\%$

d)  $56\ \Omega \pm 5\%$


713. The electric resistance of a certain wire of iron is  $R$ . If its length and radius are both doubled, then

a) The resistance will be doubled and the specific resistance will be halved

b) The resistance will be halved and the specific resistance will remain unchanged

- c) The resistance will be halved and the specific resistance will be doubled  
 d) The resistance and the specific resistance, will both remain unchanged

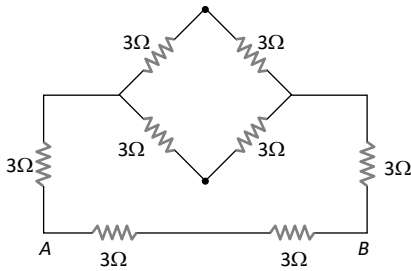714. Equivalent resistance between A and B will be



- a) 2 ohm                      b) 18 ohm                      c) 6 ohm                      d) 3.6 ohm

715. With the rise of temperature the resistivity of a semiconductor

- a) Remains unchanged                      b) Increases  
 c) Decreases                      d) First increases and then decreases

716. Two wires of the same material and having same uniform area of cross-section are connected in series in an electrical circuit. The masses of the wires are  $m$  and  $2m$ . When a current  $I$  flows in the circuit, the heats produced by them in a given time are in ratio

- a) 2 : 1                      b) 1 : 2                      c) 4 : 1                      d) 1 : 4


717. When a wire of uniform cross-section  $a$ , length  $l$  and resistance  $R$  is bent into a complete circle, resistance between any two of diametrically opposite points will be

- a)  $\frac{R}{4}$                       b)  $\frac{R}{8}$                       c)  $4R$                       d)  $\frac{R}{2}$

718. The resistance of a 5 cm long wire is 10 Ω. It is uniformly stretched so that its length becomes 20 cm. The resistance of the wire is

- a) 160 Ω                      b) 80 Ω                      c) 40 Ω                      d) 20 Ω

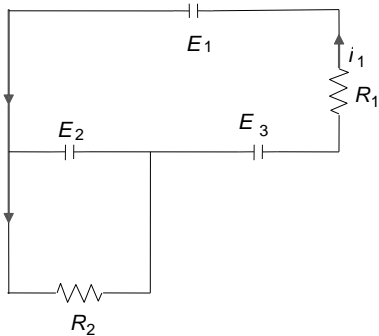719. The current  $i_1$  and  $i_2$  through the resistor  $R_1 (= 10\Omega)$  and  $R_2 (= 30\Omega)$  in the circuit diagram with  $E_1 = 3V, E_2 = 3$  and  $E_3 = 2V$  are respectively.




- a) 0.2A, 0.1A                      b) 0.4A, 0.2A                      c) 0.1A, 0.2A                      d) 0.2A, 0.4A

720. A battery has an emf of 15V and internal resistance of 1Ω. Is the terminal to terminal potential difference less than, equal to or greater than 15V if the current in the battery is (1) from negative to positive terminal, (2) from positive to negative terminal (3) zero current?

- a) Less, greater, equal                      b) Less, less, equal  
 c) Greater, greater, equal                      d) Greater, less, equal

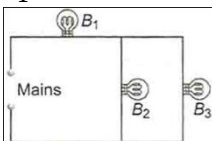721. Three bulbs  $B_1, B_2$  and  $B_3$  are connected to the main as shown in figure. How will the brightness of bulb  $B_1$  be affected if  $B_2$  or  $B_3$  are disconnected from the circuit?



- a) Bulb  $B_1$  become brighter                      b) Bulb  $B_1$  become dimmer  
 c) No change occurs in the brightness                      d) Bulb  $B_1$  becomes brighter if bulb  $B_2$  is disconnected and dimmer if bulb  $B_3$  is

disconnected.

722. Two wires of same material have length  $L$  and  $2L$  and cross-sectional areas  $4A$  and  $A$  respectively. The ratio of their specific resistances would be

- a) 1 : 2                      b) 8 : 1                      c) 1 : 8                      d) 1 : 1


723. A steady current of 5 amps is maintained for 45 mins. During this time it deposits 4.572 gm of zinc at the cathode of a voltmeter. E.C.E. of zinc is

- a)  $3.387 \times 10^{-4} \text{ gm/C}$       b)  $3.387 \times 10^{-4} \text{ C/gm}$       c)  $3.384 \times 10^{-3} \text{ gm/C}$       d)  $3.394 \times 10^{-3} \text{ C/gm}$

724. The colour sequence in a carbon resistor is red, brown, orange and silver. The resistance of the resistor is

- a)  $21 \times 10^3 \pm 10\%$       b)  $23 \times 10^1 \pm 10\%$       c)  $21 \times 10^3 \pm 5\%$       d)  $12 \times 10^3 \pm 5\%$

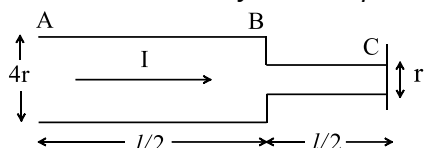725. Consider a cylindrical element as shown in the figure. Current flowing through element is  $I$  and resistivity of material of the cylinder is  $\rho$ . Choose the correct option out the following



- a) Power loss in second half is four times the power loss in first half  
 b) Voltage drop in first is twice of voltage drop in second half  
 c) Current density in both halves are equal  
 d) Electric field in both halves is equal

726. In Wheatstone's bridge  $P = 9 \text{ ohm}$ ,  $Q = 11 \text{ ohm}$ ,  $R = 4 \text{ ohm}$  and  $S = 6 \text{ ohm}$ . How much resistance must be put in parallel to the resistance  $S$  to balance the bridge

- a) 24 ohm                      b)  $\frac{44}{9} \text{ ohm}$                       c) 26.4 ohm                      d) 18.7 ohm

727. A galvanometer, having a resistance of  $50 \Omega$ , gives a full scale deflection for a current of 0.05A. The length in meter of a resistance wire of area of cross-section  $2.97 \times 10^{-2} \text{ cm}^2$  that can be used to convert the galvanometer into a ammeter which can read a maximum of 5A current is

(Specific resistance of the wire =  $5 \times 10^{-7} \Omega \text{ m}$ )

- a) 9                              b) 6                              c) 3                              d) 1.5

728. You are provided three resistances  $2 \Omega$ ,  $3 \Omega$  and  $6 \Omega$ . How will you connect them so as to obtain the equivalent resistance of  $4 \Omega$

- a)      b)      c)      d) None of these

729. A uniform wire has resistance  $24 \Omega$ . It is bent in the form of a circle. The effective resistance between the two end points on any diameter of the circle is

- a)  $6 \Omega$                       b)  $12 \Omega$                       c)  $3 \Omega$                       d)  $24 \Omega$

730. Above neutral temperature, thermo e.m.f. in a thermocouple

- a) Decreases with rise in temperature      b) Increases with rise in temperature  
 c) Remains constant      d) Changes sign

731. A galvanometer coil has a resistance of  $15 \Omega$  and gives full scale deflection for a current of 4mA. To convert it to an ammeter of range 0 to 6A

- a)  $10 \text{ m } \Omega$  resistance is to be connected in parallel to the galvanometer      b)  $10 \text{ m } \Omega$  resistance is to be connected in series with the galvanometer  
 c)  $0.1 \Omega$  resistance is to be connected in parallel to the galvanometer      d)  $0.1 \Omega$  resistance is to be connected in series with the galvanometer

732. When 1 g hydrogen (ECE =  $1.044 \times 10^6 \text{ kg C}^{-1}$ ) forms water, 34 kilo cal heat is liberated. The minimum voltage required to decompose water is

- a) 0.75 V                      b) 1.5 V                      c) 3.0 V                      d) 4.5 V

733. A current 2 A flows through a  $2 \Omega$  resistor when connected across a battery. The same battery supplies a current 0.5 A when connected across a  $9 \Omega$  resistor. The internal resistance of the battery is

- a)  $1\Omega$                                       b)  $0.5\Omega$                                       c)  $1/3\Omega$                                       d)  $1/4\Omega$


734. A cell in secondary circuit gives null deflection for  $2.5m$  length of potentiometer having  $10m$  length of wire. If the length of the potentiometer wire is increased by  $1m$  without changing the cell in the primary, the position of the null point now is

- a)  $3.5m$                                       b)  $3m$                                       c)  $2.75m$                                       d)  $2.0m$

735. Certain wire has resistance of  $10\Omega$ . If its is stretched by  $1/10$ th of its length, then its resistance is nearly

- a)  $9\Omega$                                       b)  $10\Omega$                                       c)  $11\Omega$                                       d)  $12\Omega$

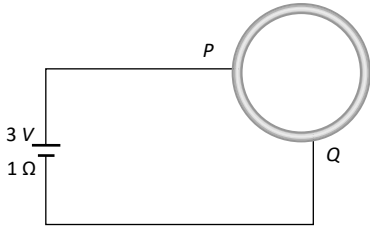736. A wire of resistance  $10\Omega$  is bent to form a circle.  $P$  and  $Q$  are points on the circumference of the circle dividing it into a quadrant and are connected to a battery of  $3V$  and internal resistance  $1\Omega$  as shown in the figure. The currents in the two parts of the circle are



- a)  $\frac{6}{23}A$  and  $\frac{18}{23}A$                                       b)  $\frac{5}{26}A$  and  $\frac{15}{26}A$                                       c)  $\frac{4}{25}A$  and  $\frac{12}{25}A$                                       d)  $\frac{3}{25}A$  and  $\frac{9}{25}A$

737. In an experiment of meter bridge, a null point is obtained at the centre of the bridge wire. When a resistance of  $10\Omega$  is connected in one gap, the value of resistance in other gap is

- a)  $10\Omega$                                       b)  $5\Omega$                                       c)  $\frac{1}{5}\Omega$                                       d)  $500\Omega$


738. A conductor wire having  $10^{29}$  free electrons/ $m^3$  carries a current of  $20A$ . If the cross-section of the wire is  $1mm^2$ , then the drift velocity of electrons will be

- a)  $6.25 \times 10^{-3}ms^{-1}$                                       b)  $1.25 \times 10^{-5}ms^{-1}$                                       c)  $1.25 \times 10^{-3}ms^{-1}$                                       d)  $1.25 \times 10^{-4}ms^{-1}$

739. Two resistances  $R$  and  $2R$  are connected in parallel in an electric circuit. The thermal energy developed in  $R$  and  $2R$  is in the ratio

- a)  $1 : 2$                                       b)  $1 : 4$                                       c)  $4 : 1$                                       d)  $2 : 1$

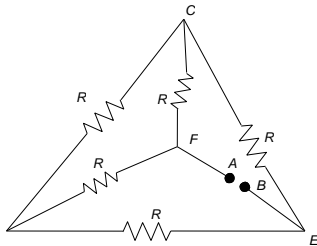740. Five equal resistances, each of resistance  $R$ , are connected as shown in figure below. A battery of  $V$  volt is connected between  $A$  and  $B$ . The current flowing in  $FC$  will be




- a)  $\frac{3V}{R}$                                       b)  $\frac{V}{R}$                                       c)  $\frac{V}{2R}$                                       d)  $\frac{2V}{R}$

741. Three moving coil galvanometers  $A$ ,  $B$  and  $C$  are made of coils of three different material having torsional constant  $1.8 \times 10^{-8}$ ,  $2.8 \times 10^{-8}$  and  $3.8 \times 10^{-8}$  respectively. If the three galvanometers are identical in all other respect, then in which of the above cases sensitivity is maximum?


- a)  $A$                                       b)  $C$                                       c)  $B$                                       d) Same in each case

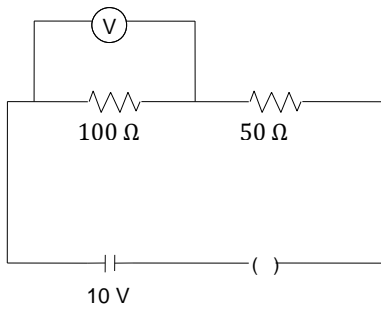742. In the given circuit, the voltmeter records  $5V$ . The resistance of the voltmeter in ohm is



- a) 200                                      b) 100                                      c) 10                                      d) 50

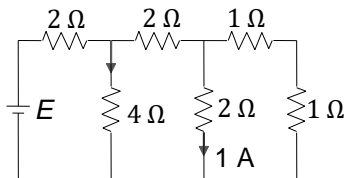743. The emf of the battery shown in figure, is



- a) 12 V                                      b) 13 V                                      c) 16 V                                      d) 18 V

744. A charge of  $2 \times 10^{-1} \text{C}$  move at 30 revolutions per second in a circle of diameter 80 cm. The current linked with the circuit is

- a) 0.02 A                                      b) 20 A                                      c) 0.60 A                                      d) 60 A


745. A capacitor of  $10 \mu\text{F}$  has a potential difference of 40 V across it. If it is discharged in 0.2 s, the average current during discharge is

- a) 2 mA                                      b) 4 mA                                      c) 1 mA                                      d) 0.5 mA

746. An electric bulb is rated 220 V – 100 W. The power consumed by it when operated on 110 V will be


- a) 75 W                                      b) 40 W                                      c) 25 W                                      d) 50 W

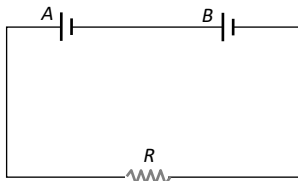747. Two batteries A and B each of e.m.f. 2 V are connected in series to an external resistance  $R = 1 \text{ ohm}$ . If the internal resistance of battery A is 1.9 ohm and that of B is 0.9 ohm, what is the potential difference between the terminals of battery A



- a) 2 V                                      b) 3.8 V                                      c) Zero                                      d) None of the above

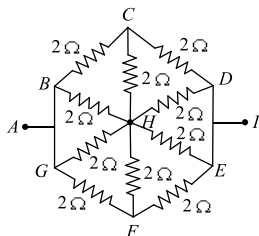748. The effective resistance across the points A and I is



- a) 2 Ω                                      b) 1 Ω                                      c) 0.5 Ω                                      d) 5 Ω

749. When the length and area of cross-section both are doubled, then its resistance

- a) Will become half                                      b) Will be doubled  
c) Will remain the same                                      d) Will become four times

750. The resistance of a conductor increases with

- a) Increase in length                                      b) Increase in temperature  
c) Decrease in cross-sectional area                                      d) All of these


751. A copper wire of resistance  $R$  is cut into ten parts of equal length. Two pieces each are joined in series and then five such combinations are joined in parallel. The new combination will have a resistance

- a)  $R$                       b)  $\frac{R}{4}$                       c)  $\frac{R}{5}$                       d)  $\frac{R}{25}$

752. Which of the following characteristics of electron determines the current in a conductor?

- a) Thermal velocity alone                      b) Drift velocity alone  
c) Both thermal velocity and drift velocity                      d) None of the above

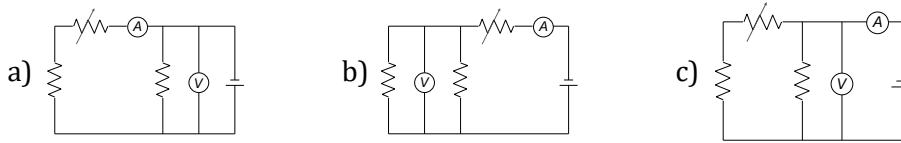753. Which of the following circuits is correct for verification of Ohm's law?



d) None of these


754. If the free electron density be  $n$  and relaxation time be  $\tau$ , the electrical conductivity of a conductor may be expressed as

- a)  $\frac{ne\tau}{m_e}$                       b)  $\frac{ne^2\tau}{m_e}$                       c)  $\frac{ne^2}{\tau m_e}$                       d)  $\frac{m_e e^2 \tau}{n}$

755. Two identical electric lamps marked  $500\text{ W}, 220\text{ V}$  are connected in series and then joined to a  $110\text{ V}$  line. The power consumed by each lamp is

- a)  $\frac{125}{4}\text{ W}$                       b)  $\frac{25}{4}\text{ W}$                       c)  $\frac{225}{4}\text{ W}$                       d)  $125\text{ W}$

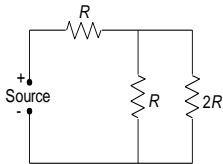756. The charge supplied by source varies with time  $t$  as  $Q = at - bt^2$ . The total heat produced in resistor  $2R$  is




- a)  $\frac{a^3 R}{6b}$                       b)  $\frac{a^3 R}{27b}$                       c)  $\frac{a^3 R}{3b}$                       d) None of these

757. A  $4\mu\text{ F}$  capacitor is charged to  $400\text{ V}$  and then its plates are joined through a resistance of  $1\text{ k}\Omega$ . The heat produced in the resistance is


- a)  $0.18\text{ J}$                       b)  $0.21\text{ J}$                       c)  $0.25\text{ J}$                       d)  $0.32\text{ J}$

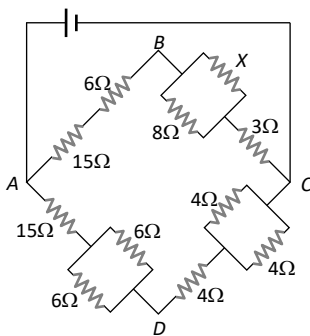758. In the figure given the value of  $X$  resistance will be, when the p.d. between  $B$  and  $D$  is zero



- a)  $4\text{ ohm}$                       b)  $6\text{ ohm}$                       c)  $8\text{ ohm}$                       d)  $9\text{ ohm}$

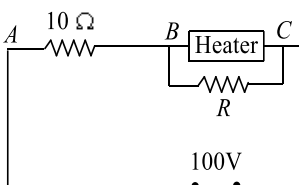759. A heater is operated with a power of  $1000\text{ W}$  in a  $100\text{ V}$  line. It is connected in combination with a resistance of  $10\Omega$  and a resistance  $R$  to a  $100\text{ V}$  line as shown in figure. What should be the value of  $R$  so, that the heater operates with a power of  $62.5\text{ W}$



- a)  $10\Omega$                       b)  $62.5\Omega$                       c)  $\frac{1}{5}\Omega$                       d)  $5\Omega$

760. The masses of three wires of copper are in the ratio  $1:3:5$  and lengths are in the ratio  $5:3:1$ . Then the ratio of their electrical resistances are


a) 1: 3: 5

b) 5: 3: 1

c) 1: 15: 25

d) 125: 15: 1

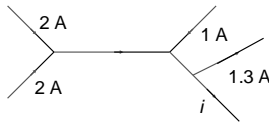761. In the figure a part of electric circuit has been shown. The value of current  $i$  is



a) 1.7 A

b) 3.7 A

c) 1.3 A

d) 1A

762. A wire of length  $L$  and 3 identical cells of negligible internal resistances are connected in series. Due to the current, the temperature of the wire due to the current, the temperature of the wire is raised by  $\Delta T$  in a time  $t$ . A number  $N$  of similar cells is now connected in series with a wire of the same material and cross-section but of length  $2L$ . The temperature of the wire is raised by the same amount  $\Delta T$  in the same time  $t$ . The value of  $N$  is

a) 4

b) 6

c) 8

d) 9

763. A milli voltmeter of 25 milli volt range is to be converted into an ammeter to 25 ampere range. The value (in ohm) of necessary shunt will be

a) 0.001

b) 0.01

c) 1

d) 0.05

764. Three bulbs of 40 W, 60 W, 100 W are arranged in series with 220 volt supply. Which bulb has minimum resistance

a) 100 W

b) 40 W

c) 60 W

d) Equal in all bulbs

765. A copper voltmeter is connected in series with a heater coil of resistance  $0.1\Omega$ . A steady current flows in the circuit for twenty minutes and mass of 0.99 g of copper is deposited at the cathode. If electrochemical equivalent of copper is  $0.00033 \text{ gm/C}$ , then heat generated in the coil is


a) 750 J

b) 650 J

c) 350 J

d) 250 J

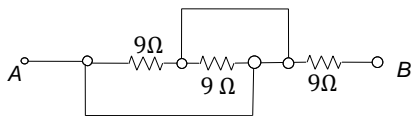766. In the circuit shown the equivalent resistance between A and B is



a) 27  $\Omega$

b) 18  $\Omega$

c) 9  $\Omega$

d) 3  $\Omega$

767. The relation between Seebeck coefficient (or thermo electric power)  $S$  and Peltier coefficient  $\pi$  is given by

a)  $S = \pi T$

b)  $S = \frac{\pi}{T}$

c)  $S = \frac{\pi^2}{T}$

d)  $S = \frac{\pi}{T^2}$

768. A thermocouple develops  $40 \mu\text{V}/\text{kelvin}$ . If hot and cold junctions are at  $40^\circ\text{C}$  and  $20^\circ\text{C}$  respectively, then emf developed by a thermopile using such 150 thermocouples in series shall be

a) 150mV

b) 80mV

c) 144mV

d) 120mV

769. The thermo emf produced in a thermo-couple is 3 microvolt per degree centigrade. If the temperature of the cold junction is  $20^\circ\text{C}$  and the thermo emf is 0.3 millivolt, the temperature of the hot junction is




a)  $80^\circ\text{C}$

b)  $100^\circ\text{C}$


c)  $120^\circ\text{C}$

d)  $140^\circ\text{C}$

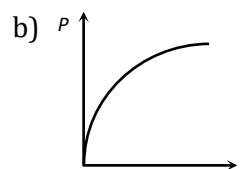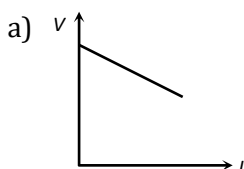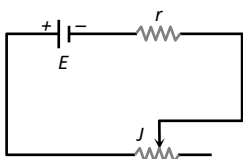770. Battery shown in figure has e.m.f.  $E$  and internal resistance  $r$ . Current in the circuit can be varied by sliding the contact  $J$ . If at any instant current flowing through the circuit is  $I$ , potential difference between terminals of the cell is  $V$ , thermal power generated in the cell is equal to  $\eta$  fraction of total electrical power generated in it.; then which of the following graphs is correct






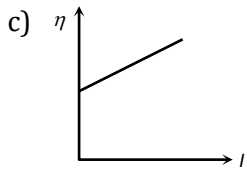

d) Both (a) and (b) are correct

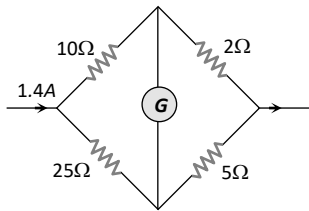771. In the circuit shown in the figure, the current flowing in  $2\ \Omega$  resistance




a)  $1.4\ A$

b)  $1.2\ A$

c)  $0.4\ A$

d)  $1.0\ A$

772. The current in the given circuit is

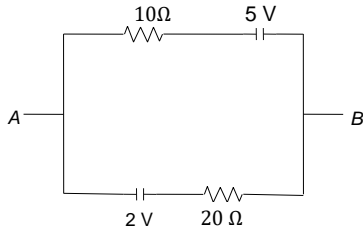

a)  $0.3\ A$

b)  $0.4\ A$

c)  $0.1\ A$

d)  $0.2\ A$

773. Given  $R_1 = 5.0 \pm 0.2\ \Omega$ ,  $R_2 = 10.0 \pm 0.1\ \Omega$ . What is total resistance in parallel with possible percentage error?


a)  $15\ \Omega \pm 2\%$

b)  $3.3\ \Omega \pm 7\%$

c)  $15\ \Omega \pm 7\%$

d)  $3.3\ \Omega \pm 2\%$

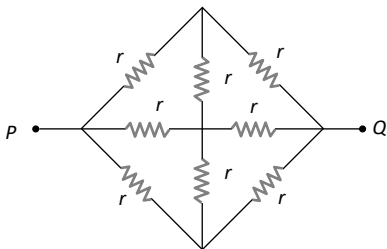774. The equivalent resistance between the points  $P$  and  $Q$  in the network given here is equal to (given  $r = \frac{3}{2}\ \Omega$ )



a)  $\frac{1}{2}\ \Omega$

b)  $1\ \Omega$

c)  $\frac{3}{2}\ \Omega$

d)  $2\ \Omega$

775. The resistance of a wire at  $300\ K$  is found to be  $0.3\ \Omega$ . If the temperature coefficient of resistance of wire is  $1.5 \times 10^{-3}\ K^{-1}$ , the temperature at which the resistance becomes  $0.6\ \Omega$  is

a)  $720\ K$

b)  $345\ K$

c)  $993\ K$

d)  $690\ K$

776. Resistance of a resistor at temperature  $t^\circ C$  is  $R_t = R_0(1 + \alpha t + \beta t^2)$ .

Here  $R_0$  is the resistance at  $0^\circ C$ . The temperature coefficient of resistance at temperature  $t^\circ C$  is

a)  $\frac{(1 + \alpha t + \beta t^2)}{\alpha + 2\beta t}$

b)  $(\alpha + 2\beta t)$

c)  $\frac{\alpha + 2\beta t}{(1 + \alpha t + \beta t^2)}$

d)  $\frac{(\alpha + 2\beta t)}{2(1 + \alpha t + \beta t^2)}$

777. If a rod has resistance  $4\ \Omega$  and if rod is turned as half circle, then the resistance along diameter is


a)  $1.56\ \Omega$

b)  $2.44\ \Omega$

c)  $4\ \Omega$

d)  $2\ \Omega$

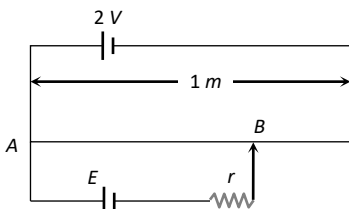778. In the given figure, battery  $E$  is balanced on  $55\ cm$  length of potentiometer wire but when a resistance of  $10\ \Omega$  is connected in parallel with the battery then it balances on  $50\ cm$  length of the potentiometer wire then internal resistance  $r$  of the battery is



- a)  $1 \Omega$                       b)  $3 \Omega$                       c)  $10 \Omega$                       d)  $5 \Omega$


779. Two wires of equal diameters, of resistivities  $\rho_1$  and  $\rho_2$  and lengths  $l_1$  and  $l_2$ , respectively, are joined in series. The equivalent resistivity of the combination is

- a)  $\frac{\rho_1 l_1 + \rho_2 l_2}{l_1 + l_2}$                       b)  $\frac{\rho_1 l_2 + \rho_2 l_1}{l_1 - l_2}$                       c)  $\frac{\rho_1 l_2 + \rho_2 l_1}{l_1 + l_2}$                       d)  $\frac{\rho_1 l_1 - \rho_2 l_2}{l_1 - l_2}$

780. If six identical cells each having an e. m. f. of  $6V$  are connected in parallel, the e.m.f. of the combination is


- a)  $1 V$                       b)  $36 V$                       c)  $\frac{1}{6} V$                       d)  $6 V$

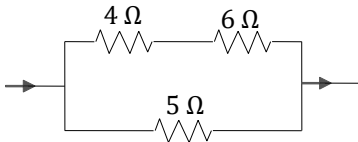781. In the circuit shown, the heat produced in the  $5\Omega$  resistor due to current flowing in it is  $10 \text{ cal} - \text{s}^{-1}$ . The heat generated in  $\Omega$  resistor is



- a)  $1 \text{ cal} - \text{s}^{-1}$                       b)  $2 \text{ cal} - \text{s}^{-1}$                       c)  $3 \text{ cal} - \text{s}^{-1}$                       d)  $4 \text{ cal} - \text{s}^{-1}$

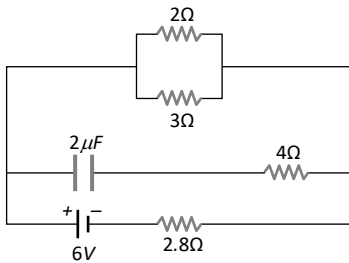782. In the figure shown, the capacity of the condenser  $C$  is  $2 \mu F$ . The current in  $2\Omega$  resistor is




- a)  $9 A$                       b)  $0.9 A$                       c)  $\frac{1}{9} A$                       d)  $\frac{1}{0.9} A$

783. To deposit one gm equivalent of an element at an electrode, the quantity of electricity needed is

- a) One ampere                      b) 96000 amperes                      c) 96500 farads                      d) 96500 coulombs

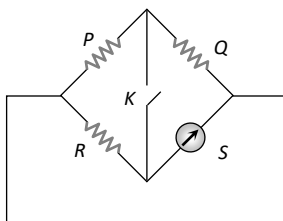784. In the following Wheatstone bridge  $P/Q = R/S$ . If key  $K$  is closed, then the galvanometer will show deflection



- a) In left side                      b) In right side                      c) No deflection                      d) In either side

785. We have two wires  $A$  and  $B$  of same mass and same material. The diameter of the wire  $A$  is half of that  $B$ . If the resistance of wire  $A$  is  $24 \text{ ohm}$  then the resistance of wire  $B$  will be

- a)  $12 \text{ Ohm}$                       b)  $3.0 \text{ Ohm}$                       c)  $1.5 \text{ Ohm}$                       d) None of the above

786. The Petlier coefficient of a thermo-couple of metals  $A$  and  $B$  at junction temperature  $T$  is given by

- a)  $T^2 \frac{dE}{dT^2}$                       b)  $T \frac{dE}{dT}$                       c)  $T^3 \frac{dE^2}{dT}$                       d)  $T^4 \frac{d^2E}{dT^2}$

787. A 30, 90 W lamps are to be operated on a 120 V DC line. For proper glow, a resistor of .....  $\Omega$  should be connected in series with the lamp.

- a) 40                      b) 10                      c) 20                      d) 30


788. The lead wires should have

- a) Larger diameter and low resistance                      b) Smaller diameter and high resistance  
c) Smaller diameter and low resistance                      d) Larger diameter and high resistance


789. A battery of emf  $2V$  and internal resistance  $0.1 \Omega$  is being charged by a current of  $5A$ . the potential difference between the terminals of the battery is

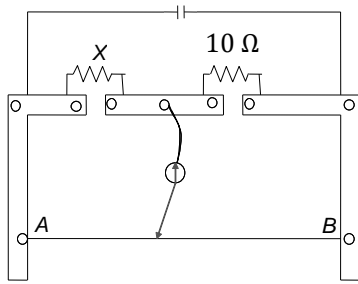- a)  $2.5 \Omega$                       b)  $1.5 \Omega$                       c)  $0.5 \Omega$                       d)  $1 \Omega$






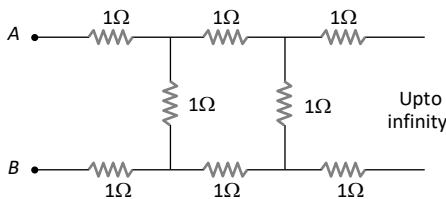798. The resistance between the terminal points *A* and *B* of the given infinitely long circuit will be
- a) 10.2 Ω                      b) 10.6 Ω                      c) 10.8 Ω                      d) 11.1 Ω




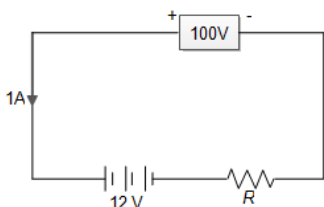- a)  $(\sqrt{3} - 1)$                       b)  $(1 - \sqrt{3})$                       c)  $(1 + \sqrt{3})$                       d)  $(2 + \sqrt{3})$
799. A 60 watt bulb carries a current of 0.5 amp. The total charge passing through it in 1 hour is
- a) 3600 coulomb                      b) 3000 coulomb                      c) 2400 coulomb                      d) 1800 coulomb
800. A bulb of 220 V and 300 W is connected across 110 V circuit, the percentage reduction in power is
- a) 100%                      b) 25%                      c) 70%                      d) 75%
801. If the temperature of cold junction of thermocouple is lowered, then the neutral temperature
- a) Increases                      b) Approaches inversion temperature  
c) Decreases                      d) Remains the same
802. The resistance of the filament of a lamp increases with the increase in temperature. A lamp rated 100 W and 200 V is connected across 220 V power supply. If the voltage drops by 10%, then the power of the lamp will be
- a) 90 W                      b) 81 W  
c) Between 90 and 100 W                      d) Between 81 and 90 W
803. Which factor is immaterial for the wire used in electric fuse?
- a) Length                      b) Radius                      c) Material                      d) Current
804. If 1 A current is passed through  $\text{CuSO}_4$  solution for 10 s, the number of copper atoms deposited at the cathode will be
- a)  $8 \times 10^{19}$                       b)  $3.1 \times 10^{19}$                       c)  $6.2 \times 10^{19}$                       d)  $1.6 \times 10^{20}$
805. All of the following statements are true except
- a) Conductance is the reciprocal of resistance and is measured in *Siemen*  
b) *Ohm's* law is not applicable at very low and very high temperatures  
c) *Ohm's* law is applicable to semiconductors  
d) *Ohm's* law is not applicable to electron tubes, discharge tubes and electrolytes
806. A galvanometer of resistance 20 Ω is to be converted into an ammeter of range 1 A. If a current of 1 mA produces full scale deflection, the shunt required for the purpose is
- a) 0.01 Ω                      b) 0.05 Ω                      c) 0.02 Ω                      d) 0.04 Ω
807. The net resistance of a voltmeter should be large to ensure that
- a) It does not get overheated  
b) It does not draw excessive current  
c) It can measure large potential difference  
d) It does not appreciably change the potential difference to be measured
808. A galvanometer of 50 ohm resistance has 25 divisions. A current of  $4 \times 10^{-4}$  ampere gives a deflection of one division. To convert this galvanometer into a voltmeter having a range of 25 volts, it should be connected with a resistance of
- a) 2500 Ω as a shunt                      b) 2450 Ω as a shunt                      c) 2550 Ω in series                      d) 2450 Ω in series






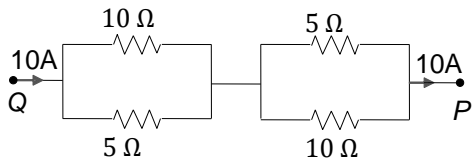- a)  $88 \Omega$                       b)  $68 \Omega$                       c)  $44 \Omega$                       d) None of these
817. Three resistances of values  $2\Omega$ ,  $3\Omega$  and  $6\Omega$  are to be connected to produce an effective resistance of  $4\Omega$ . This can be done by connecting
- a)  $6\Omega$  resistance in series with the parallel combination of  $2\Omega$  and  $3\Omega$   
 b)  $3\Omega$  resistance in series with the parallel combination of  $2\Omega$  and  $6\Omega$   
 c)  $2\Omega$  resistance in series with the parallel combination of  $3\Omega$  and  $6\Omega$   
 d)  $2\Omega$  resistance in parallel with the parallel combination of  $3\Omega$  and  $6\Omega$
818. Current provided by a battery is maximum when
- a) Internal resistance equal to external resistance  
 b) Internal resistance is greater than external resistance  
 c) Internal resistance is less than external resistance  
 d) None of these
819. Three equal resistances, each of  $R$  ohm, are connected as shown in figure. A battery of  $2V$  and internal resistance  $0.1 \Omega$  is connected across the circuit. The value of  $R$  for which the heat generated in the circuit will be maximum is
- 
- a)  $0.3\Omega$                       b)  $0.01\Omega$                       c)  $0.1\Omega$                       d)  $0.03\Omega$
820. For a certain thermocouple, if the temperature of the cold junction is  $0^\circ\text{C}$ , the neutral temperature and inversion temperature are  $285^\circ\text{C}$  and  $570^\circ\text{C}$  respectively. If the cold junction is brought to  $10^\circ\text{C}$ , then the new neutral and inversion temperatures are respectively
- a)  $285^\circ\text{C}$  and  $560^\circ\text{C}$                       b)  $285^\circ\text{C}$  and  $570^\circ\text{C}$                       c)  $295^\circ\text{C}$  and  $560^\circ\text{C}$                       d)  $275^\circ\text{C}$  and  $560^\circ\text{C}$
821. Two resistances when connected in parallel across a cell of negligible internal resistance consume 4 times the power they would consume when connected in series. If one resistance is  $5 \Omega$ , the other is
- a)  $1 \Omega$                       b)  $2.5 \Omega$                       c)  $5 \Omega$                       d)  $10 \Omega$
822. The maximum current that flows through a fuse wire before it blows out varies with its radius as
- a)  $r^{3/2}$                       b)  $r$                       c)  $r^{2/3}$                       d)  $r^{1/2}$
823. At what temperature will the resistance of a copper wire become three times its value at  $0^\circ\text{C}$  (Temperature coefficient of resistance for copper =  $4 \times 10^{-3}$  per  $^\circ\text{C}$ )
- a)  $400^\circ\text{C}$                       b)  $450^\circ\text{C}$                       c)  $500^\circ\text{C}$                       d)  $550^\circ\text{C}$
824. If  $N$  is the Avogadro's number and  $e$  is the electronic charge then the Faraday's constant  $F$  is equal to
- a)  $Ne$                       b)  $N^2e$                       c)  $Ne^2$                       d)  $\frac{1}{Ne}$
825. A current of  $1.5 A$  flows through a copper voltameter. The thickness of copper deposited on the electrode surface of size  $50 \text{ cm} \times 10 \text{ cm}$  in  $20 \text{ min}$  will be (density of copper =  $9000 \text{ kg} \cdot \text{m}^{-3}$  and ECE of copper =  $0.00033 \text{ gC}^{-1}$ )
- a)  $3.3 \times 10^{-6} \text{ m}$                       b)  $6.6 \times 10^{-6} \text{ m}$                       c)  $1.3 \times 10^{-5} \text{ m}$                       d)  $2.6 \times 10^{-5} \text{ m}$
826. Four resistances carrying a current shown in the circuit diagram are immersed in a box containing ice at  $0^\circ\text{C}$ . How much ice must be put in the box every  $10 \text{ min}$  to keep the average quantity of ice in the box constant?




- a) 5 kg                      b) 1.19 kg                      c) 3 kg                      d) 2.29 kg

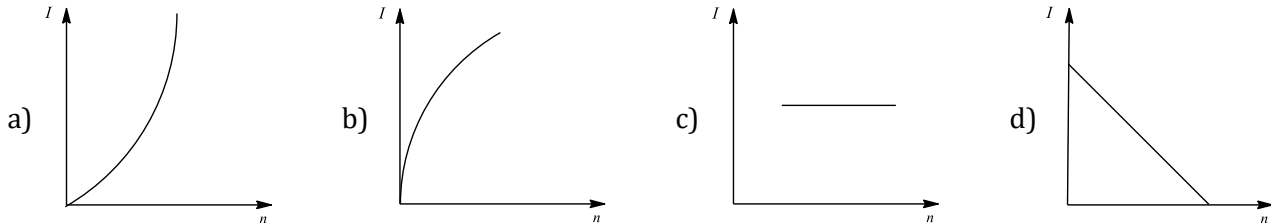827. A battery consists of a variable number ( $n$ ) of identical cells, each having an internal resistance  $r$  connected in series. The terminal of the battery is short-circuited. A graph of current *versus* the number of cells will be as shown in figure




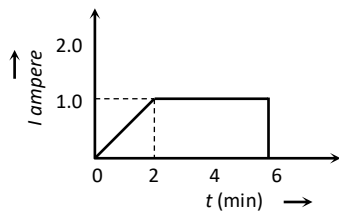828. In a copper voltameter, mass deposited in 6 minutes is  $m$  gram. If the current-time graph for the voltameter is as shown here, then the E.C.E of the copper is




- a)  $m/5$                       b)  $m/300$                       c)  $5m$                       d)  $m/18000$

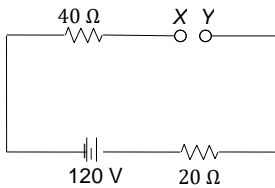829. In the circuit shown in the figure the potential difference between X and Y will be



- a) Zero                      b) 20 V                      c) 60 V                      d) 120 V

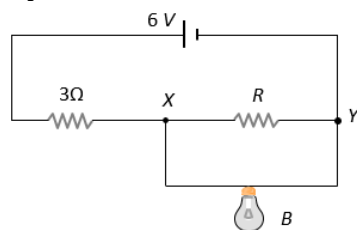830. In the following circuit, bulb rated as  $1.5\text{ V}, 0.45\text{ W}$ . If bulbs glows with full intensity then what will be the equivalent resistance between X and Y



- a)  $0.45\ \Omega$                       b)  $1\ \Omega$                       c)  $3\ \Omega$                       d)  $5\ \Omega$

831. Two wires of same dimensions but resistivities  $\rho_1$  and  $\rho_2$  are connected in series. The equivalent resistivity of the combination is

- a)  $\sqrt{\rho_1\rho_2}$                       b)  $(\rho_1 + \rho_2)$                       c)  $\frac{\rho_1 + \rho_2}{2}$                       d) None of these

832. In a balanced Wheatstone's network, the resistance in the arms Q and S are interchanged. As a result of this

- a) Network is not balanced  
 b) Network is still balanced  
 c) Galvanometer shows zero deflection  
 d) Galvanometer and the cell must be interchanged to balance

833. On passing the current in water voltmeter, hydrogen

- a) Is liberated at anode  
 c) Is not liberated
- b) Is liberated at cathode  
 d) Remains in the solution


834. Two electric bulbs have ratings respectively of 25 W, 220 V and 100 W, 220 V. If the bulbs are connected in series with a supply of 440, which bulb will fuse?

- a) 25 W bulb                      b) 100 W bulb                      c) Both of these                      d) None of these

835. A cell of internal resistance 3 ohm and emf 10 volt is connected to a uniform wire of length 500 cm and resistance 3 ohm. The potential gradient in the wire is

- a) 30 mV/cm                      b) 10 mV/cm                      c) 20 mV/m                      d) 4 mV/cm

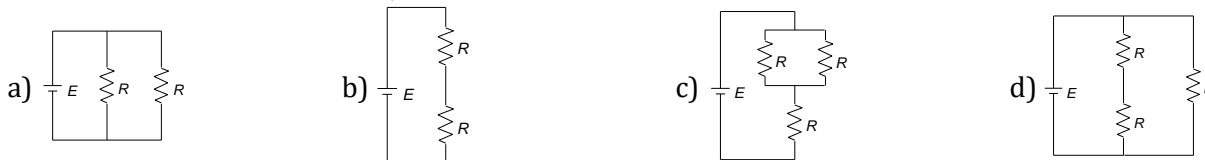836. Consider four circuits shown in figure. In which circuit power dissipated is greatest. (Neglect the internal resistance of the power supply)



837. Consider the following two statements A and B and identify the correct choice given in the answer

(A) Duddells thermo-galvanometer is suitable to measure direct current only

(B) Thermopile can measure temperature differences of the order of  $10^{-3}^{\circ}\text{C}$

- a) Both A and B are true                      b) Both A and B are false  
 c) A is true but B is false                      d) A is false but B is true

838. Three resistors 1  $\Omega$ , 2 $\Omega$  and 3 $\Omega$  are connected to form a triangle. Across 3 $\Omega$  resistor a 3V battery is connected. The current through 3  $\Omega$  resistor is

- a) 0.75A                      b) 1A                      c) 2A                      d) 1.5A

839. A silver and a zinc voltmeter are connected in series and a current  $I$  is passed through them for a time  $t$ , liberating  $w$  gram of zinc. The weight of silver deposited is nearly

- a) 1.7  $w$  g                      b) 2.4  $w$  g                      c) 3.5  $w$  g                      d) 1.2  $w$  g

840. In a meter bridge experiment, null point is obtained at 20cm from one end of the wire when resistance  $X$  is balanced against another resistance  $Y$ . If  $X < Y$ , then where will be the new position of the null point from the same end, if one decides to, balance a resistance of  $4X$  against  $Y$ ?

- a) 50 cm                      b) 80 cm                      c) 40 cm                      d) 70 cm

841. A galvanometer of resistance 240 $\Omega$  allows only 4% of the main current after connecting a shunt resistance. The value of the shunt resistance is

- a) 10  $\Omega$                       b) 20  $\Omega$                       c) 8  $\Omega$                       d) 5  $\Omega$


842. The two bulbs, one of 60W and other 200W are connected in series to a 200 volt line, then

- a) The potential drop across two bulbs in the same                      b) The potential drop across the 60 W bulb is greater than the potential drop across the 200 W bulb  
 c) The potential drop across the 200 W bulb is greater than the 60 W bulb                      d) The potential drop across both the bulbs is 200 volt

843. Electromotive force is the force, which is able to maintain a constant

- a) Current                      b) Resistance                      c) Power                      d) Potential difference

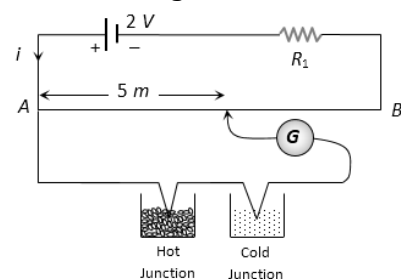
844. In the following circuit a 10 m long potentiometer wire with resistance 1.2 ohm/m, a resistance  $R_1$  and an accumulator of emf 2 V are connected in series. When the emf of thermocouple is 2.4 mV then the deflection in galvanometer is zero. The current supplied by the accumulator will be



- a)  $4 \times 10^{-4} \text{ A}$                       b)  $8 \times 10^{-4} \text{ A}$                       c)  $4 \times 10^{-3} \text{ A}$                       d)  $8 \times 10^{-3} \text{ A}$




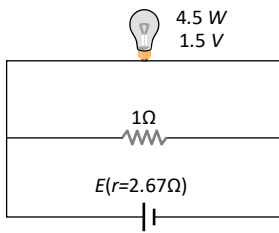845. A house wife uses a 100 W bulb 8 h a day , and an electric heater of 300 W for 4 h a day. The total cost for the month of June at the rate of 0.05 rupee per unit will be  
 a) Rs 20                                      b) Rs 25                                      c) Rs 30                                      d) Rs 30 paise 50
846. In a potentiometer, the null points are received at 7th wire. If now we have to change the null points at 9th wire, what should we do?  
 a) Attach resistance in series with battery                                      b) Increase resistance in main circuit  
 c) Decrease resistant in main circuit                                      d) Decrease applied emf
847. The effective resistance of two resistors in parallel is  $\frac{12}{7}\Omega$ . If one of the resistors is disconnected the resistance becomes 4  $\Omega$ . The resistance of the other resistor is  
 a) 4  $\Omega$                                       b) 3  $\Omega$                                       c)  $\frac{12}{7}\Omega$                                       d)  $\frac{7}{12}\Omega$
848. A torch bulb rated as 4.5 W, 1.5 V is connected as shown in the figure. The *e. m. f.* of the cell needed to make the bulb glow at full intensity is



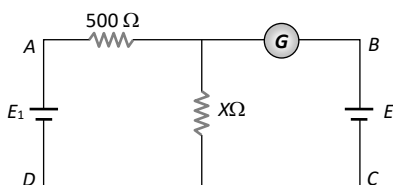- a) 4.5 V                                      b) 1.5 V                                      c) 2.67 V                                      d) 13.5 V
849. The electric current passing through a metallic wire produces heat because of  
 a) Collisions of conduction electrons with each other  
 b) Collisions of the atoms of the metal with each other  
 c) The energy released in the ionization of the atoms of the metal  
 d) Collisions of the conduction electrons with the atoms of the metallic wires
850. One junction of a thermo-couple is a particular temperature  $T_r$  and another is at  $T$ . Its thermo emf is expressed as  

$$E = K(T - T_r) \left\{ T_0 - \frac{1}{2}(T + T_r) \right\}$$
 At a temperature  $T = \frac{T_0}{2}$ , the value of thermo-electric power will be  
 a)  $\frac{1}{2}KT_0$                                       b)  $KT_0$                                       c)  $\frac{1}{2}KT_0^2$                                       d)  $\frac{1}{2}K(T_0 - T_r)^2$ .
851. Two identical heaters rated 220 volt, 1000 watt are placed in series with each other across 220 volt lines. If resistance does not change with temperature, then the combined power is  
 a) 1000 watt                                      b) 2000 watt                                      c) 500 watt                                      d) 4000 watt
852. In the adjoining circuit, the battery  $E_1$  has an *e. m. f.* of 12volt and zero internal resistance while the battery  $E$  has an *e. m. f.* of 2volt. If the galvanometer  $G$  reads zero, then the value of the resistance  $X$  in ohm is



- a) 10                                      b) 100                                      c) 500                                      d) 200
853. In a potentiometer of one metre length, an unknown *e. m. f.* voltage source is balanced at 60 cm length of potentiometer wire, while a 3 volt battery is balanced at 45 cm length. Then the *e. m. f.* of the unknown voltage source is  
 a) 3V                                      b) 2.25V                                      c) 4V                                      d) 4.5V
854. A potentiometer has uniform potential gradient across it. Two cells connected in series (i) to support each other and (ii) to oppose each other are balanced over 6m and 2m respectively on the potentiometer wire.


The e.m.f.'s of the cells are in the ratio of

- a) 1 : 2                      b) 1 : 1                      c) 3 : 1                      d) 2 : 1

855. In a thermocouple, the temperature that does not depend on the temperature of the cold junction is called


- a) Neutral temperature                      b) Temperature of inversion  
c) Both the above                      d) None of the above

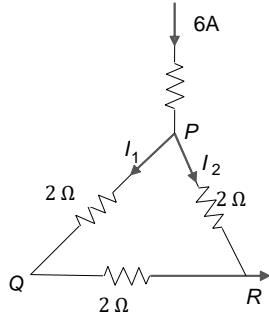856. A current of  $6A$  enters one corner one corner  $P$  of an equilateral triangle  $PQR$  having 3 wires of resistance  $2\Omega$  each and leaves by the corner  $R$ . then the current  $I_1$  and  $I_2$  are



- a) 2A, 4A                      b) 4A, 2A                      c) 1A, 2A                      d) 2A, 3A

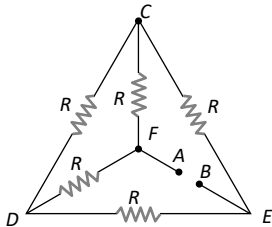857. Five equal resistances each of resistance  $R$  are connected as shown in the figure. A battery of  $V$  volts is connected between  $A$  and  $B$ . The current flowing in  $AFCEB$  will be




- a)  $\frac{3V}{R}$                       b)  $\frac{V}{R}$                       c)  $\frac{V}{2R}$                       d)  $\frac{2V}{R}$

858. The resistance of a straight conductor does not depend on its

- a) Length                      b) Temperature  
c) Material                      d) Shape of cross-section

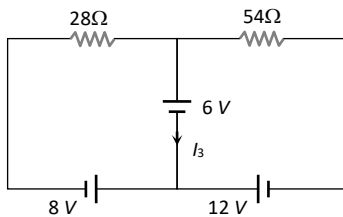859. Consider the circuit shown in the figure. The current  $I_3$  is equal to



- a) 5 amp                      b) 3 amp                      c) -3 amp                      d) -5/6 amp

860. An immersion heater with electrical resistance  $7\Omega$  is immersed in  $0.1\text{ kg}$  of water at  $20^\circ\text{C}$  for 3 min. If the flow of current is  $4\text{ A}$ , what is the final temperature of the water in ideal conditions?

(Specific heat capacity of water =  $4.2 \times 10^3 \text{ Jkg}^{-1}\text{K}^{-1}$ )

- a)  $28^\circ\text{C}$                       b)  $48^\circ\text{C}$                       c)  $52^\circ\text{C}$                       d)  $68^\circ\text{C}$

861. A cell of internal resistance  $r$  is connected to an external resistance  $R$ . The current will be maximum in  $R$ , if

- a)  $R = r$                       b)  $R < r$                       c)  $R > r$                       d)  $R = r/2$

862. If an ammeter is to be used in place of a voltmeter, then we must connect with the ammeter a

- a) Low resistance in parallel                      b) High resistance in parallel  
c) High resistance in series                      d) Low resistance in series

863. A nichrome wire  $50\text{ cm}$  long and one square millimetre cross-section carries a current of  $4\text{ A}$  when connected to a  $2\text{ V}$  battery. The resistivity of nichrome wire in ohm metre is

- a)  $1 \times 10^{-6}$                       b)  $4 \times 10^{-7}$                       c)  $3 \times 10^{-7}$                       d)  $2 \times 10^{-7}$

864. The resistance of hot tungsten filament is about 10 times the cold resistance. What will be the resistance of

100 W and 200 V lamp, when not in use?

- a) 40Ω                      b) 20Ω                      c) 400Ω                      d) 20Ω

865. In a neon gas discharge tube  $\text{Ne}^+$  ions moving through a cross-section of the tube each second to the right is  $2.9 \times 10^{18}$ , while  $1.2 \times 10^{18}$  electron move towards left in the same time; the electronic charge being  $1.6 \times 10^{-19}\text{C}$ , the net electric current is

- a) 0.27 A to the right      b) 0.66 A to the right      c) 0.66 A to the left      d) Zero

866. A battery of e.m.f. 3 volt and internal resistance 1.0 ohm is connected in series with copper voltmeter. The current flowing in the circuit is 1.5 amperes. The resistance of voltmeter will be

- a) Zero                      b) 1.0 ohm                      c) 1.5 ohm                      d) 2.0 ohm


867. If two identical heaters each rated as (1000 W-220 V) are connected in parallel to 220 V, then the total power consumed is

- a) 200 W                      b) 2500 W                      c) 250 W                      d) 2000 W

868. A voltmeter essentially consists of


- a) A high resistance, in series with a galvanometer      b) A low resistance, in series with a galvanometer  
c) A high resistance in parallel with a galvanometer      d) A low resistance in parallel with a galvanometer

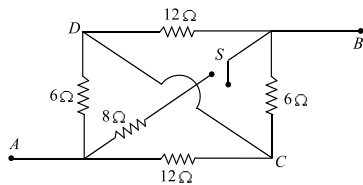869. The equivalent resistance between points A and B with switch S open and closed are respectively



- a) 4 Ω, 8 Ω                      b) 8 Ω, 4 Ω                      c) 6 Ω, 9 Ω                      d) 9 Ω, 6 Ω

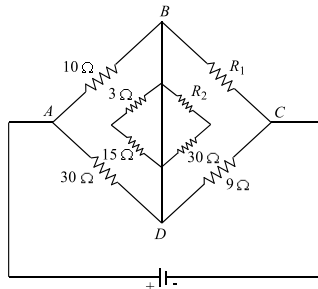870. In the Wheatstone bridge shown below, in order to balance the bridge, we must have



- a)  $R_1 = 3 \Omega ; R_2 = 3 \Omega$                       b)  $R_1 = 6 \Omega ; R_2 = 15 \Omega$   
c)  $R_1 = 1.5 \Omega ; R_2 = \text{any finite value}$                       d)  $R_1 = 3 \Omega ; R_2 = \text{any finite value}$

871. A wire of resistance  $R$  is cut into ' $n$ ' equal parts. These parts are then connected in parallel. The equivalent resistance of the combination will be

- a)  $nR$                       b)  $\frac{R}{n}$                       c)  $\frac{n}{R}$                       d)  $\frac{R}{n^2}$

872. The power dissipated across resistance  $R$  which is connected across a battery of potential  $V$  is  $P$ . If resistance is doubled, then the power becomes

- a) 1/2                      b) 2                      c) 1/4                      d) 4

873. What will happen when a 40 watt, 220 volt lamp and 100 watt, 220 volt lamp are connected in series across 40 volt supply

- a) 100 watt lamp will fuse                      b) 40 watt lamp will fuse  
c) Both lamps will fuse                      d) Neither lamp will fuse

874. If nearly  $10^5\text{C}$  liberate 1 g equivalent of aluminium, then the amount of aluminium (equivalent weight g) deposited through electrolysis in 20 min by a current of 50 A will be


- a) 0.09 g                      b) 0.6 g                      c) 5.4 g                      d) 10.8 g

875. Two cells, each of e. m. f.  $E$  and internal resistance  $r$  are connected in parallel between the resistance  $R$ . The maximum energy given to the resistor will be, only when

- a)  $R = r/2$                       b)  $R = r$                       c)  $R = 2r$                       d)  $R = 0$

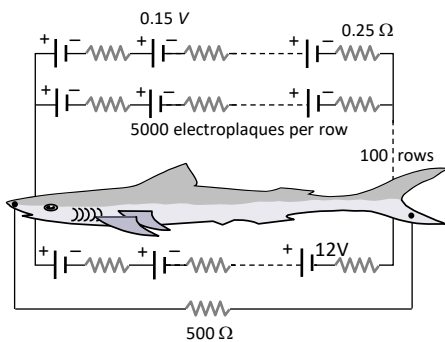876. Eels are able to generate current with biological cells called electroplaques. The electroplaques in an eel

are arranged in 100 rows, each row stretching horizontally along the body of the fish containing 5000 electroplaques. The arrangement is suggestively shown below. Each electroplaque has an emf of  $0.15\text{ V}$  and internal resistance of  $0.25\ \Omega$




The water surrounding the eel completes a circuit between the head and its tail. If the water surrounding it has a resistance of  $500\ \Omega$ , the current an eel can produce in water is about

- a)  $1.5\text{ A}$                       b)  $3.0\text{ A}$                       c)  $15\text{ A}$                       d)  $30\text{ A}$

877. Time taken by a  $836\text{ W}$  heater to heat one litre of water from  $10^\circ\text{C}$  to  $40^\circ\text{C}$  is

- a)  $50\text{ s}$                       b)  $100\text{ s}$                       c)  $150\text{ s}$                       d)  $200\text{ s}$

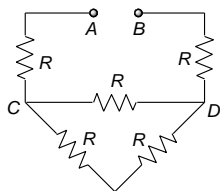878. What is the equivalent resistance between points  $A$  and  $B$  in the circuit if figure, if  $R = 3\ \Omega$ ?



- a)  $8\ \Omega$                       b)  $9\ \Omega$                       c)  $12\ \Omega$                       d)  $15\ \Omega$

879. What must be the efficiency of an electric kettle marked  $500\text{ W}$ ,  $230\text{ V}$ , if it was found to bring  $1\text{ kg}$  of water at  $15^\circ\text{C}$  to boiling point in  $15\text{ min}$ ? (Given specific heat capacity of water =  $420\text{ J/kg}^\circ\text{C}$ )

- a)  $79\%$                       b)  $81\%$                       c)  $72\%$                       d)  $69\%$

880. A metallic resistor is connected across a battery. If the number of collisions of the free electrons with the lattice is some how decreased in the resistor (for example by cooling it), the current will

- a) Remains constant                      b) Increase                      c) Decrease                      d) Become zero

881. Tap supplies water at  $20^\circ\text{C}$ . A man takes  $1\text{ L}$  of water per minute at  $35^\circ\text{C}$  from a geyser connected to the tap. The power of geyser is

- a)  $1050\text{ W}$                       b)  $2100\text{ W}$                       c)  $1500\text{ W}$                       d)  $3000\text{ W}$

882. The number of free electrons per  $100\text{ mm}$  of ordinary copper wire is  $2 \times 10^{21}$ . Average drift speed of electrons is  $0.25\text{ mms}^{-1}$ . The current flowing is

- a)  $8\text{ A}$                       b)  $0.8\text{ A}$                       c)  $80\text{ A}$                       d)  $5\text{ A}$


883. On increasing the temperature of a conductor, its resistance increases because the

- a) Relaxation time increases                      b) Mass of electron increases  
c) Electron density decreases                      d) Relaxation time decreases

884. In India electricity is supplied for domestic use at  $220\text{ V}$ . It is supplied at  $110\text{ V}$  in USA. If the resistance of a  $60\text{ W}$  bulb for use in India is  $R$ , the resistance of a  $60\text{ W}$  bulb for use in USA will be

- a)  $R$                       b)  $2R$                       c)  $R/4$                       d)  $R/2$

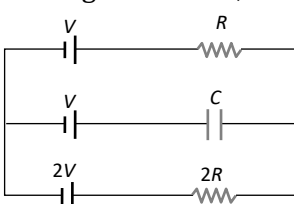885. In the given circuit, with steady current, the potential drop across the capacitor must be



- a)  $V$                       b)  $V/2$                       c)  $V/3$                       d)  $2V/3$

886. Two resistances  $R_1$  and another  $R_2$  of the same material but twice the length and half the thickness are


connected in series with a standard battery  $E$  of internal resistance  $r$ . The balancing point is

- a)  $\frac{1}{8l}$                       b)  $\frac{1}{4l}$                       c)  $8l$                       d)  $16l$

887. When a current passes through the junction of two different metals, evolution or absorption of heat at the junction is known as

- a) Joule effect                      b) Seebeck effect                      c) Peltier effect                      d) Thomson effect

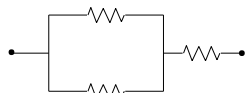888. Three equal resistors are connected as shown in figure. The maximum power consumed by each resistor is 18 W. Then maximum power consumed by the combination is



- a) 18 W                      b) 27 W                      c) 36 W                      d) 54 W

889. The length of the resistance wire is increased by 10%. What is the corresponding change in the resistance of wire?

- a) 10 %                      b) 25 %                      c) 21 %                      d) 9 %


890. The number of dry cells, each of e.m.f. 1.5 volt and internal resistance 0.5 ohm that must be joined in series with a resistance of 20 ohm so as to send a current of 0.6 ampere through the circuit is

- a) 2                      b) 8                      c) 10                      d) 12

891. A thermistor is dipped in a bath whose temperature is to be measured. When the temperature increase the current also increase, because of decreases in

- a) Capacitance                      b) Reactance                      c) Resistance                      d) Resistivity

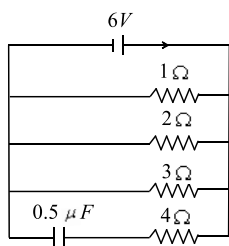892. In the given circuit diagram the current through the battery and the charge on the capacitor respectively in steady state are



- a) 1A and  $3\mu C$                       b) 17 A and  $0\mu C$                       c)  $\frac{6}{7}A$  and  $\frac{12}{7}\mu C$                       d) 11A and  $3\mu C$


893. To send 10% of main current through a moving coil galvanometer of resistance  $9\Omega$  shut required

- a)  $9\Omega$                       b)  $11\Omega$                       c)  $10\Omega$                       d)  $9.9\Omega$

894. The resistance of a wire of uniform diameter  $d$  and length  $L$  is  $R$ . The resistance of another wire of the same material but diameter  $2d$  and length  $4L$  will be

- a)  $2R$                       b)  $R$                       c)  $R/2$                       d)  $R/4$

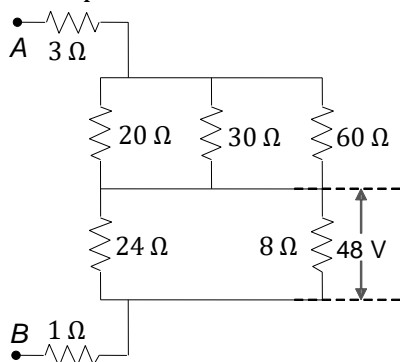895. The potential difference across  $8\Omega$  resistance is 48V as shown in figure. The value of potential difference across points A and B will be




- a) 62 V                      b) 80 V                      c) 128 V                      d) 160 V

896. For obtaining chlorine by electrolysis a current of 100 KW and 125 V is used. (Electro chemical equivalent of chlorine is  $0.367 \times 10^6 \text{kgC}^{-1}$ ). The amount of chlorine obtained in one min will be


- a) 1.7616 g                      b) 17.616 g                      c) 0.17161 kg                      d) 1.7616 kg

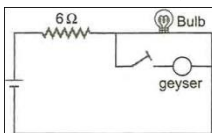897. In a meter bridge, the balancing length from the left end (standard resistance of one  $ohm$  is in the right gap) is found to be  $20\text{ cm}$ . The value of the unknown resistance is  
 a)  $0.8\ \Omega$                       b)  $0.5\ \Omega$                       c)  $0.4\ \Omega$                       d)  $0.25\ \Omega$
898. A  $25\text{ W}$  and  $100\text{ W}$  bulbs are joined in series and connected to the mains. Which bulb will glow brighter?  
 a)  $25\text{ W}$  bulb                      b)  $100\text{ W}$  bulb  
 c) Both bulb will glow brighter                      d) None will glow brighter
899. Temperature of cold junction in a thermocouple is  $270^\circ\text{C}$ , then the temperature of inversion is  
 a)  $540^\circ\text{C}$                       b)  $530^\circ\text{C}$                       c)  $280^\circ\text{C}$                       d)  $260^\circ\text{C}$
900. A galvanometer having a coil resistance of  $60\ \Omega$  shows full scale deflection when a current of  $1.0\text{ amp}$  passes through it. It can be converted into an ammeter to read currents upto  $5.0\text{ amp}$  by  
 a) Putting in parallel a resistance of  $240\ \Omega$                       b) Putting in series a resistance of  $15\ \Omega$   
 c) Putting in series a resistance of  $240\ \Omega$                       d) Putting in parallel a resistance of  $15\ \Omega$
901. A voltmeter having resistance of  $50 \times 10^3\ ohm$  is used to measure the voltage in a circuit. To increase the range of measurement 3 times the additional series resistance required is  
 a)  $10^5\ ohm$                       b)  $150\text{ k. ohm}$                       c)  $900\text{ k. ohm}$                       d)  $9 \times 10^6\ ohm$
902. The wiring of a house has resistance  $6\ \Omega$ . A  $100\text{ W}$  bulb is glowing as shown in figure. If a geyser of  $1000\text{ W}$  is switched on, the change in potential drop across the bulb is nearly




- a) Nil                      b)  $12\text{ V}$                       c)  $24\text{ V}$                       d)  $32\text{ V}$

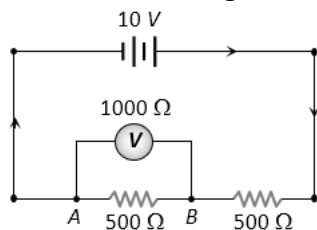903. What is the reading of voltmeter in the following figure



- a)  $3\text{ V}$                       b)  $2\text{ V}$                       c)  $5\text{ V}$                       d)  $4\text{ V}$

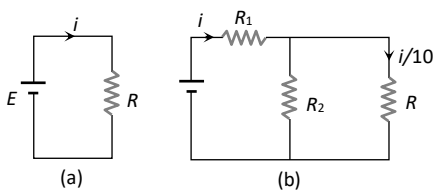904. Consider the circuits shown in the figure. Both the circuits are taking same current from battery but current through  $R$  in the second circuit is  $\frac{1}{10}$ th of current through  $R$  in the first circuit. If  $R$  is  $11\ \Omega$ , the value of  $R_1$




- a)  $9.9\ \Omega$                       b)  $11\ \Omega$                       c)  $8.8\ \Omega$                       d)  $7.7\ \Omega$

905. A given resistor has the following colour scheme of the various strips on it, brown, black, green and silver. Its value in ohm is


- a)  $1.0 \times 10^4 \pm 10\%$                       b)  $1.0 \times 10^5 \pm 10\%$                       c)  $1.0 \times 10^6 \pm 10\%$                       d)  $1.0 \times 10^7 \pm 10\%$

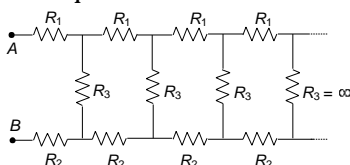906. The equivalent resistance of the figure *ie*, infinite network of resistors between the terminals  $A$  and  $B$  is



- a) Zero                      b) Infinite  
 c)  $\frac{R_1 + R_2 + R_3}{3}$                       d)  $\frac{1}{2} \left[ (R_1 + R_2) + \sqrt{(R_1 + R_2)(R_1 + R_2 + 4R_3)} \right]$

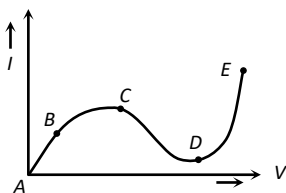907. If  $R_1$  and  $R_2$  are respectively the filament resistances of a 200 watt bulb and 100 watt bulb designed to operate on the same voltage, then  
 a)  $R_1$  is two times  $R_2$       b)  $R_2$  is two times  $R_1$       c)  $R_2$  is four times  $R_1$       d)  $R_1$  is four times  $R_2$
908. The atomic weight of silver and copper are 108 and 64. A silver voltmeter and a copper voltmeter are connected in series and when current is passed 10.8 gm of silver is deposited. The mass of copper deposited will be  
 a) 6.4 gm      b) 12.8 gm      c) 3.2 gm      d) 10.8 gm
909. An unknown resistance  $R_1$  is connected in series with a resistance of  $10\Omega$ . This combination is connected to one gap of meter bridge while a resistance  $R_2$  is connected in the other gap. The balance point is at 50 cm, Now, when the  $10\Omega$  resistance is removed the balance point shifts 40cm. The value of  $R_1$  (in ohm) is  
 a) 20      b) 10      c) 60      d) 40
910. A wire has a resistance of  $6\Omega$ . It is cut into two parts and both half values are connected in parallel. The new resistance is  
 a)  $3\Omega$       b)  $6\Omega$       c)  $12\Omega$       d)  $1.5\Omega$
911. A source of emf  $E=15V$  and having negligible internal resistance, is connected to a variable resistance, so that the current in the circuit increases with time as  $I=1.2t+3$ . Then, the total charge that will flow in first 5s will be  
 a) 10C      b) 20C      c) 30C      d) 40C
912. Two resistors of resistance  $R_1$  and  $R_2$  having  $R_1 > R_2$  are connected in parallel. For equivalent resistance  $R$ , the correct statement is  
 a)  $R > R_1 + R_2$       b)  $R_1 < R < R_2$       c)  $R_2 < R < (R_1 + R_2)$       d)  $R < R_1$
913. Identify the incorrect statement regarding a superconducting wire  
 a) Transport current flows through its surface  
 b) Transport current flows through the entire area of cross-section of the wire  
 c) It exhibits zero electrical resistivity and expels applied magnetic field  
 d) It is used to produce large magnetic field
914. By a cell a current of 0.9 A flows through 2 ohm resistor and 0.3 A through 7 ohm resistor. The internal resistance of the cell is  
 a)  $0.5\Omega$       b)  $1.0\Omega$       c)  $1.2\Omega$       d)  $2.0\Omega$
915. The value of current required to deposit 0.972 gm of chromium in 3 hours if the E.C.E. of chromium is 0.00018 gm per coulomb, is  
 a) 1 amp      b) 1.5 amp      c) 0.5 amp      d) 2 amp
916. If for a thermocouple  $T_n$  is the neutral temperature,  $T_c$  is the temperature of the cold junction and  $T_i$  is the temperature of inversion, then  
 a)  $T_i = 2T_n - T_c$       b)  $T_n = T_i - 2T_c$       c)  $T_i = T_n - T_c$       d) None of these
917. The temperature of the cold junction of a thermocouple is  $0^\circ C$  and the temperature of the hot junction is  $T^\circ C$ . The emf is  $E = 16T - 0.04T^2 \mu V$ . The inversion temperature  $T_i$  is  
 a)  $200^\circ C$       b)  $400^\circ C$       c)  $100^\circ C$       d)  $300^\circ C$
918. From the graph between current  $I$  and voltage  $V$  shown below, identify the portion corresponding to negative resistance




- a) AB      b) BC      c) CD      d) DE
919. A thermocouple is formed by two metals X and Y, metal X comes earlier to Y in Seebeck series. If temperature of hot junction increases beyond the temperature of inversion, then direction of current in thermocouple will be from  
 a) X to Y through cold junction      b) X to Y through hot junction

c) Y to X through cold junction

d) Both (b) and (c)

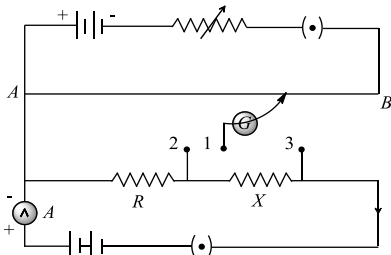920. A potentiometer circuit is set up as shown. The potential gradient, across the potentiometer wire, is  $k$  volt/cm and the ammeter, present in the circuit, reads  $1.0\text{ A}$  when two way key is switched off. The balance points, when the key between the terminals (i) 1 and 2 (ii) 1 and 3, is plugged in, are found to be at lengths  $l_1\text{ cm}$  and  $l_2\text{ cm}$  respectively. The magnitudes, of the resistors  $R$  and  $X$ , in ohms, are then, equal, respectively, to




a)  $kl_1$  and  $kl_2$

b)  $k(l_2 - l_1)$  and  $kl_2$

c)  $kl_1$  and  $k(l_2 - l_1)$

d)  $k(l_2 - l_1)$  and  $kl_1$

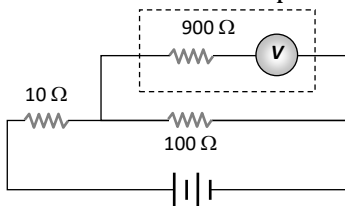921. The potential difference across the  $100\Omega$  resistance in the following circuit is measured by a voltmeter of  $900\Omega$  resistance. The percentage error made in reading the potential difference is



a)  $\frac{10}{9}$

b) 0.1

c) 1.0

d) 10.0

922. A heater coil cut into two equal parts and one part is connected with heater. Now heat generated in heater will be

a) Twice

b) Half

c) One-fourth

d) Four times

923. Some electric bulbs are connected in series across a  $220\text{V}$  supply in a room. If one bulb is fused, then remaining bulbs are connected again in series across the same supply. The illumination in the room will be

a) Increase

b) Decrease

c) Remain the same

d) Not continuous

924. A moving coil galvanometer has a resistance of  $50\Omega$  and gives full scale deflection for  $10\text{ mA}$ . How could it be converted into an ammeter with a full scale deflection for  $1\text{ A}$

a)  $50/99\Omega$  in series

b)  $50/99\Omega$  in parallel

c)  $0.01\Omega$  in series

d)  $0.01\Omega$  in parallel

925. An ammeter reads upto  $1\text{ A}$ . Its internal resistance is  $0.81\Omega$ . To increase the range to  $10\text{ A}$  the value of the required shunt is

a)  $0.03\Omega$

b)  $0.3\Omega$

c)  $0.9\Omega$

d)  $0.09\Omega$

926. There are two concentric spheres of radius  $a$  and  $b$  respectively. If the space between them is filled with medium of resistivity  $\rho$ , then the resistance of the inter gap between the two spheres will be


a)  $\frac{\rho}{4\pi(b+a)}$

b)  $\frac{\rho}{4\pi}\left(\frac{1}{b} - \frac{1}{a}\right)$

c)  $\frac{\rho}{4\pi}\left(\frac{1}{a^2} - \frac{1}{b^2}\right)$

d)  $\frac{\rho}{4\pi}\left(\frac{1}{a} - \frac{1}{b}\right)$

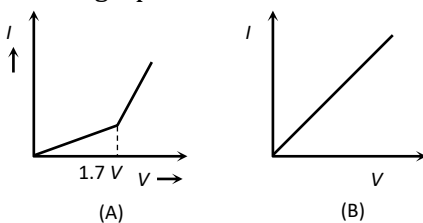927. The  $V-i$  graphs A and B are drawn for two voltmeters. Identify each graph



a) A for water voltmeter and B for Cu voltmeter


b) A for Cu voltmeter and B for water voltmeter

c) Both A and B represents Cu voltmeter


d) None of these



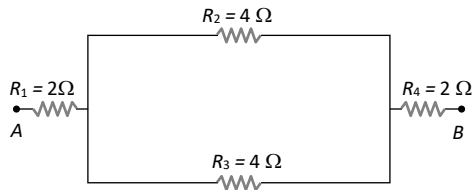
928. A certain electrical conductor has a square cross-section, 2.0 mm on side, and is 12 m long. The resistance between its ends is  $0.072\Omega$ . The resistivity of its material is equal to  
 a)  $2.4 \times 10^{-6}\Omega\text{m}$       b)  $1.2 \times 10^{-6}\Omega\text{m}$       c)  $1.2 \times 10^{-8}\Omega\text{m}$       d)  $2.4 \times 10^{-8}\Omega\text{m}$
929. A galvanometer has a resistance of  $3663\Omega$ . A shunt  $S$  is connected across it such that  $(1/34)$  of the total current passes through the galvanometer. Then the value of shunt is  
 a)  $3663\Omega$       b)  $111\Omega$       c)  $107.7\Omega$       d)  $3555.3\Omega$
930. In the given figure, the equivalent resistance between the points  $A$  and  $B$  is



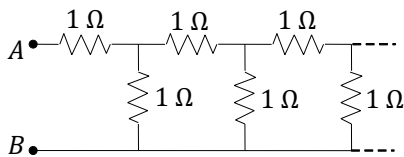
- a)  $8\Omega$       b)  $6\Omega$       c)  $4\Omega$       d)  $2\Omega$
931. Three resistances of  $4\Omega$ ,  $6\Omega$  and  $12\Omega$  are connected in parallel and the combination is connected in series with  $4\text{ V}$  battery with internal resistance of  $2\Omega$ . The battery current is  
 a)  $1\text{ A}$       b)  $10\text{ A}$       c)  $2\text{ A}$       d)  $0.5\text{ A}$
932. The equivalent resistance between points  $A$  and  $B$  of an infinite network of resistances each of  $1\Omega$  connected as shown in figure, is



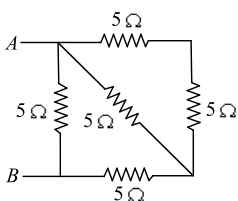- a) Infinite      b) Zero      c)  $2\Omega$       d)  $(1 + \sqrt{5})/2\Omega$
933. An electric iron draws  $5\text{ amp}$ , a TV set draws  $3\text{ amp}$  and refrigerator draws  $2\text{ amp}$  from a  $220\text{ volt}$  main line. The three appliances are connected in parallel. If all the three are operating at the same time, the fuse used may be of  
 a)  $20\text{ amp}$       b)  $5\text{ amp}$       c)  $15\text{ amp}$       d)  $10\text{ amp}$
934. The equivalent resistance between the points  $A$  and  $B$  in the following circuit is




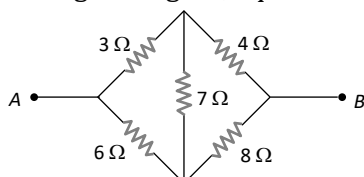- a)  $3.12\Omega$       b)  $1.56\Omega$       c)  $6.24\Omega$       d)  $12.48\Omega$
935. A  $3^\circ\text{C}$  rise in temperature is observed in a conductor by passing certain current. When the current is doubled, the rise in temperature will be  
 a)  $15^\circ\text{C}$       b)  $12^\circ\text{C}$       c)  $9^\circ\text{C}$       d)  $3^\circ\text{C}$
936. In the given figure, equivalent resistance between  $A$  and  $B$  will be



- a)  $\frac{14}{3}\Omega$       b)  $\frac{3}{14}\Omega$       c)  $\frac{9}{14}\Omega$       d)  $\frac{14}{9}\Omega$
937. If  $\theta_i$  is the inversion temperature,  $\theta_n$  is the natural temperature,  $\theta_c$  is the temperature of the cold junction then  
 a)  $\theta_i + \theta_c = \theta_n$       b)  $\theta_i - \theta_c = 2\theta_n$       c)  $\frac{\theta_i + \theta_c}{2} = \theta_n$       d)  $\theta_c - \theta_i = 2\theta_n$
938. Potential difference across the terminals of the battery shown in figure is ( $r$  = internal resistance of

battery)

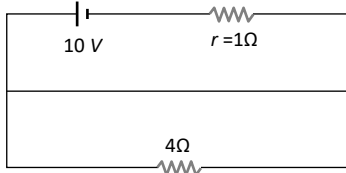

- a) 8 V                      b) 10 V                      c) 6 V                      d) Zero


939. Potentiometer measures the potential difference more accurately than a voltmeter because

- a) It has a wire of high resistance                      b) It has a wire of low resistance  
c) It does not draw current from external circuit                      d) It draws a heavy current from external circuit

940. To get maximum current through a resistance of  $2.5 \Omega$ , one can use  $m$  rows of cells, each row having  $n$  cells. The internal resistance of each cell is  $0.5 \Omega$ . What are the values of  $n$  and  $m$ , if the total number of cell is 45?

- a)  $m = 3, n = 15$                       b)  $m = 5, n = 9$                       c)  $m = 9, n = 5$                       d)  $m = 15, n = 3$

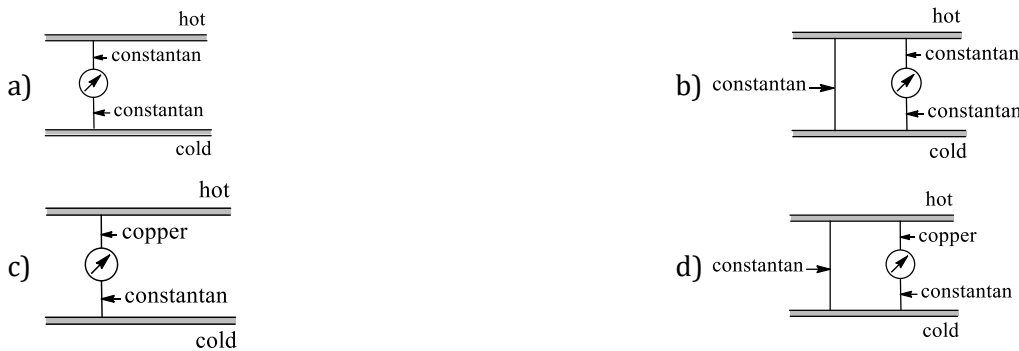941. A cold-water pipe and a hot-water pipe are both made of copper and are initially electrically isolated. In which one of the following arrangements will the galvanometer indicate a thermo-electric current?



942. The emf of a thermocouple, cold junction of which is kept at  $-300^\circ\text{C}$  is given by  $E = 40t + \frac{1}{10}t^2$ . The temperature of inversion of thermocouple will be

- a)  $200^\circ\text{C}$                       b)  $400^\circ\text{C}$                       c)  $-200^\circ\text{C}$                       d)  $-100^\circ\text{C}$

943. How much current should be passed through acidified water for 100s to liberate 0.224 L of hydrogen?

- a) 22.4 A                      b) 19.3 A                      c) 9.65 A                      d) 1 A

944. The speed at which the current travels, in a conductor, is nearly

- a)  $3 \times 10^{-4} \text{ ms}^{-1}$                       b)  $3 \times 10^{-5} \text{ ms}^{-1}$                       c)  $4 \times 10^6 \text{ ms}^{-1}$                       d)  $3 \times 10^8 \text{ ms}^{-1}$


945. A uniform wire of resistance  $9 \Omega$  is cut into 3 equal parts. They are connected in the form of equilateral triangle  $ABC$ . A cell of e. m. f.  $2 \text{ V}$  and negligible internal resistance is connected across  $B$  and  $C$ . Potential difference across  $AB$  is

- a) 1 V                      b) 2 V                      c) 3 V                      d) 0.5 V

946. A bulb rated at  $(100\text{W} - 200\text{V})$  is used on a  $100\text{V}$  line. The current in the bulb is

- a)  $\frac{1}{4} \text{ amp}$                       b) 4 amp                      c)  $\frac{1}{2} \text{ amp}$                       d) 2 amp

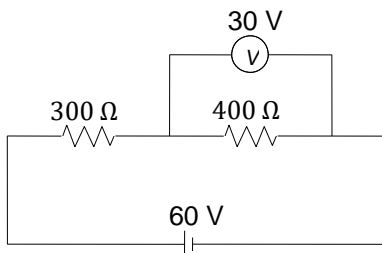947. In the circuit figure, the voltmeter reads 30 V. what is the resistance of the voltmeter?



- a)  $1200 \Omega$                       b)  $700 \Omega$                       c)  $400 \Omega$                       d)  $300 \Omega$


948. Forty electric bulbs are connected in series across a  $220 \text{ V}$  supply. After one bulb is fused, the remaining 39 are connected again in series the same supply. The illumination will be

- a) More with 40 bulbs than with 39                      b) More with 39 bulbs than with 40

c) Equal in both the cases

d) In the ratio of  $49^2 : 39^2$

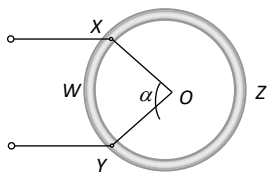949. A wire of resistor  $R$  is bent into a circular ring of radius  $r$ . Equivalent resistance between two points  $X$  and  $Y$  on its circumference, when angle  $XOY$  is  $\alpha$ , can be given by



a)  $\frac{R\alpha}{4\pi^2}(2\pi - \alpha)$

b)  $\frac{R}{2\pi}(2\pi - \alpha)$

c)  $R(2\pi - \alpha)$

d)  $\frac{4\pi}{R\alpha}(2\pi - \alpha)$

950. Ampere hour is the unit of


a) Quantity of charges

b) Potential

c) Energy

d) Current

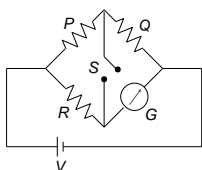951. In the circuit shown as  $P \neq R$  and the reading of the galvanometer  $G$  is same with switch open or closed. Then



a)  $I_R = R_G$

b)  $I_P = I_G$

c)  $I_Q = I_G$

d)  $I_Q = I_R$

952. A bulb of 220 V and 300 W is connected across 110 V circuit. The percentage reduction in power is

a) 100%

b) 25%

c) 70%

d) 75%

953. Peltier coefficient for the junction of a pair of metals is proportional to

a) Absolute temperature of junction  $T$

b) Square of absolute temperature of junction

c)  $1/T$

d)  $1/T^2$

954. The following four wires are made of the same material and are at the same temperature. Which one of them has the highest electrical resistance?


a) Length=50 cm, diameter=0.5 mm

b) Length=100 cm, diameter=1 mm

c) Length=200 cm, diameter=2 mm

d) Length=300 cm, diameter=3 mm

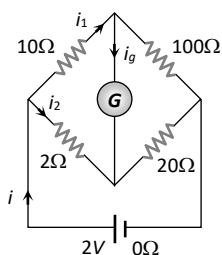955. In the circuit shown below the resistance of the galvanometer is  $20 \Omega$ . In which of the following alternative are the currents arranged strictly in the decreasing order



a)  $i, i_1, i_2, i_g$

b)  $i, i_2, i_1, i_g$

c)  $i, i_2, i_g, i_1$

d)  $i, i_1, i_g, i_2$

956. A potentiometer having the potential gradient of  $2 \text{ mV/cm}$  is used to measure the difference of potential across a resistance of  $10 \text{ ohm}$ . If a length of  $50 \text{ cm}$  of the potentiometer wire is required to get the null point, the current passing through the  $10 \text{ ohm}$  resistor is (in  $\text{mA}$ )


a) 1

b) 2

c) 5

d) 10

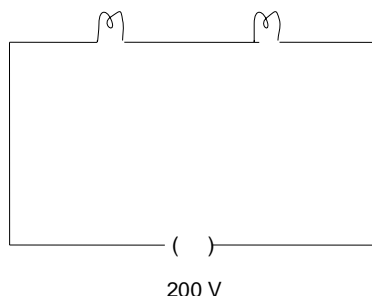957. Two bulbs marked  $200 \text{ V} - 100 \text{ W}$  and  $200 \text{ V} - 200 \text{ W}$  are joined in series and connected to a power supply of



200 V


200 V. The total power consumed by the two will be near to

- a) 35 W                      b) 66 W                      c) 100 W                      d) 300 W

958. A colour coded carbon resistor has the colours orange, blue, green and silver. Its resistance value and tolerance percentage respectively are

- a)  $36 \times 10^5 \Omega$  and 10%    b)  $36 \times 10^4 \Omega$  and 5%    c)  $63 \times 10^5 \Omega$  and 10%    d)  $35 \times 10^6 \Omega$  and 5%

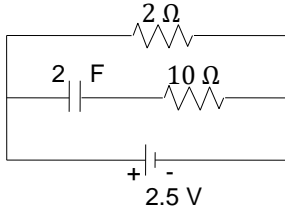959. A capacitor of capacitance  $2\mu\text{F}$  is connected as shown in figure. The internal resistance of the cell is  $0.5\Omega$ . The amount of charge on the capacitor plates is



- a) Zero                      b)  $2\mu\text{C}$                       c)  $4\mu\text{C}$                       d)  $6\mu\text{C}$

960. A wire of a certain material is stretched slowly by ten percent. Its new resistance and specific resistance become respectively

- a) Both remain the same    b) 1.1 times, 1.1 times    c) 1.2 times, 1.1 times    d) 1.21 times, same

961. Two conductors are made of the same material and have the same length. Conductor *A* is a solid wire of diameter  $1.0\text{ mm}$ . Conductor *B* is a hollow tube of outside diameter  $2.0\text{ mm}$  and inside diameter  $1.0\text{ mm}$ . The resistance ratio  $R_A/R_B$  will be

- a) 1                      b) 2                      c) 3                      d) 4

962. A certain current passing through a galvanometer produces a deflection of 100 divisions. When a shunt of one ohm is connected, the deflection reduces to 1 division. The galvanometer resistance is

- a)  $100\Omega$                       b)  $99\Omega$                       c)  $10\Omega$                       d)  $9.9\Omega$


963. An expression for rate of heat generated, if a current of  $I$  ampere flows through a resistance of  $R\Omega$ , is

- a)  $I^2 R t$                       b)  $I^2 R$                       c)  $V^2 R$                       d)  $I R$

964. If a  $2\text{ kW}$  boiler is used everyday for 1 hour, then electrical energy consumed by boiler in thirty days is


- a) 15 unit                      b) 60 unit                      c) 120 unit                      d) 240 unit

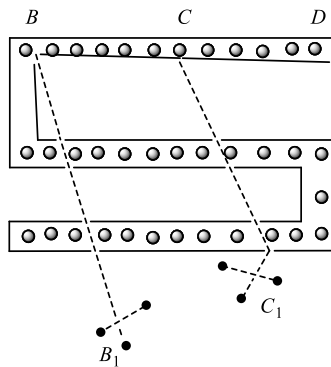965. For the post office box arrangement to determine the value of unknown resistance, the unknown resistance should be connected between







- a) *B* and *C*                      b) *C* and *D*                      c) *A* and *D*                      d) *B*<sub>1</sub> and *C*<sub>1</sub>

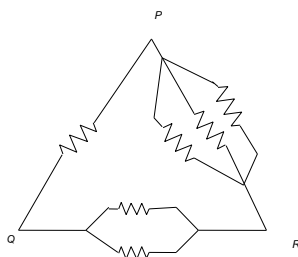966. Six equal resistances are connected between points *P*, *Q* and *R* as shown in the figure. Then the net resistance will be maximum between



- a) *P* and *Q*                      b) *Q* and *R*                      c) *P* and *R*                      d) Only two points

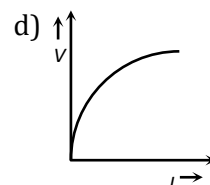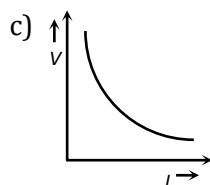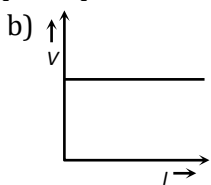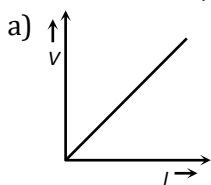967. Which of the adjoining graphs represents *ohmic* resistance



968. A lead acid accumulatory (storage battery) is connected to a battery charge for over night charging. Which of the following observations will indicate that the battery was partly charged during the next morning

- a) The density of acid has decreased                      b) The density of acid has increased  
 c) The acid has changed colour                              d) The acid level has dropped

969. How much current should be passed through a silver voltmeter to deposit 200 gm of silver per hour on the cathode? (Faraday constant =  $96500 \text{ C/mol}$  and relative atomic mass of silver is 108)

- a) 50 mA                      b) 50 A                      c) 15 mA                      d) 15 A

970. All the edges of a block with parallel faces are unequal. Its tangent edge is twice its shortest edge. The ratio of the maximum to minimum resistance between parallel faces is

- a) 8                      b) 4                      c) 2                      d) None of these

971. A battery has e.m.f.  $4 \text{ V}$  and internal resistance  $r$ . When this battery is connected to an external resistance of  $2 \text{ ohm}$ , a current of  $1 \text{ amp}$ . flows in the circuit. How much current will flow if the terminals of the battery are connected directly

- a)  $1 \text{ amp}$                       b)  $2 \text{ amp}$                       c)  $4 \text{ amp}$                       d) Infinite


972. A cell of emf  $6 \text{ V}$  and resistance  $0.5 \text{ ohm}$  is short circuited. The current in the cell is

- a)  $3 \text{ amp}$                       b)  $12 \text{ amp}$                       c)  $24 \text{ amp}$                       d)  $6 \text{ amp}$

973. It is easier to start a car engine on a hot day than on a cold day. This is because the internal resistance of the car battery

- a) Decreases with rise in temperature                      b) Increases with rise in temperature  
 c) Decreases with a fall in temperature                      d) Does not change with a change in temperature

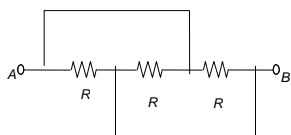974. The resistance across  $A$  and  $B$  in the figure below will be




- a)  $3R$                       b)  $R$                       c)  $\frac{R}{3}$                       d) None of these

975. With a potentiometer null point were obtained at  $140 \text{ cm}$  and  $180 \text{ cm}$  with cells of emf  $1.1 \text{ V}$  and one unknown  $X$  volt. Unknown emf is

- a)  $1.1 \text{ V}$                       b)  $1.8 \text{ V}$                       c)  $2.4 \text{ V}$                       d)  $1.41 \text{ V}$

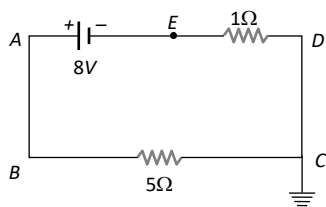976. In the given circuit, the potential of the point  $E$  is




- a) Zero                      b)  $-8 \text{ V}$                       c)  $-4/3 \text{ V}$                       d)  $4/3 \text{ V}$

977. Two resistors  $400 \Omega$  and  $800 \Omega$  are connected in series with  $6 \text{ V}$  battery. The potential difference measured by voltmeter of  $10 \text{ k} \Omega$  across  $400 \Omega$  resistor is


- a)  $2 \text{ V}$                       b)  $1.95 \text{ V}$                       c)  $3.8 \text{ V}$                       d)  $4 \text{ V}$

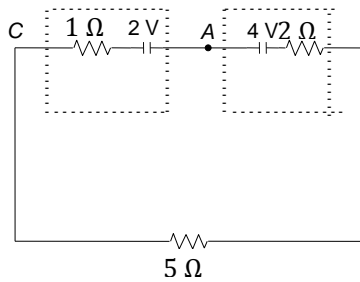978. What is the potential drop between points  $A$  and  $C$  in the following circuit? Resistances  $1 \Omega$  and  $2 \Omega$  represent the internal resistance of the respective cells




- a) 1.75V                      b) 2.25V                      c)  $\frac{5}{4}V$                       d)  $\frac{4}{5}V$

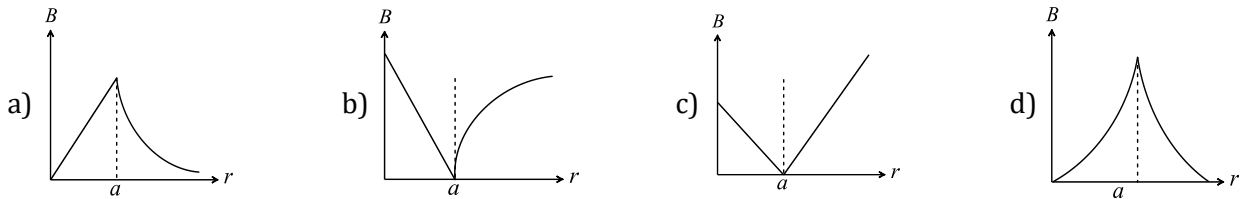979. A long straight wire of a circular cross section (radius  $a$ ) carries a steady current  $I$  and the current  $I$  is uniformly distributed across this cross-section. Which of the following plots represents the variation of magnitude of magnetic field  $B$  with distance  $r$  from the centre of the wire



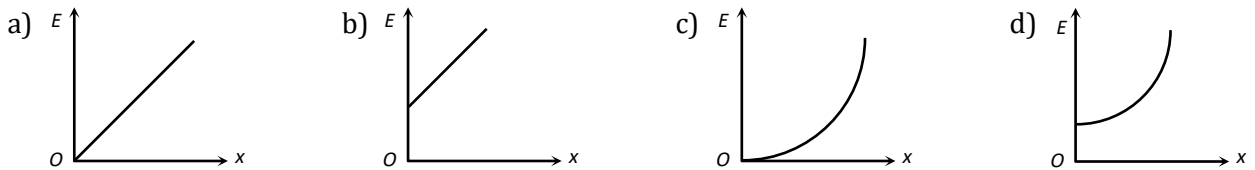980. A cylindrical conductor has uniform cross-section. Resistivity of its material increases linearly from left end to right end. If a constant current is flowing through it and at a section distance  $x$  from left end, magnitude of electric field intensity is  $E$ , which of the following graphs is correct



981. The *emf* of a battery is 2 V and its internal resistance is 0.5 Ω. The maximum power which it can deliver to any external circuit will be

- a) 8 Watt                      b) 4 Watt                      c) 2 Watt                      d) None of the above


982. An electric bulb of 100 watt is connected to a supply of electricity of 220 V. Resistance of the filament is

- a) 484 Ω                      b) 100 Ω                      c) 22000 Ω                      d) 242 Ω

983.  $n$  identical bulbs, each designed to draw a power  $p$  from a certain voltage supply, are joined in series across that supply. The total power which they will draw is

- a)  $p/n^2$                       b)  $p/n$                       c)  $p$                       d)  $np$

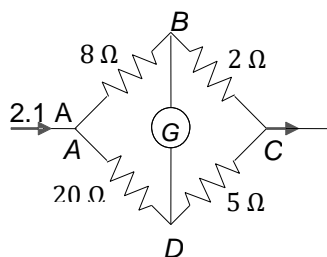984. In the given figure when galvanometer shows no deflection current flowing through 5Ω resistance will be




- a) 0.5 A                      b) 0.6 A                      c) 1.5 A                      d) 2.0 A

985. If voltage across a bulb rated 220 Volt-100 Watt drops by 2.5% of its rated value, the percentage of the rated value by which the power would decrease is

- a) 20%                      b) 2.5%                      c) 5%                      d) 10%

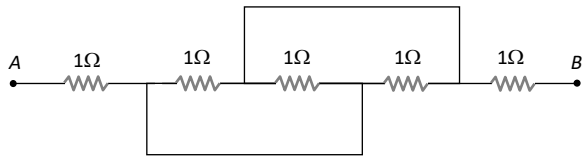986. Equivalent resistance between the points A and B is (in Ω)



- a)  $\frac{1}{5}$                       b)  $1\frac{1}{4}$                       c)  $2\frac{1}{3}$                       d)  $3\frac{1}{2}$

987. A fuse wire with radius 1 mm blows at 1.5 A. The radius of the fuse wire of the same material to blow at 3 A will be

- a)  $3^{1/4}$  mm                      b)  $4^{1/3}$  mm                      c)  $3^{1/2}$  mm                      d)  $2^{1/3}$  mm

988. A galvanometer of resistance  $G$  can measure 1 A current. If a shunt  $S$  is used to convert it into an ammeter to measure 10 A current. The ratio of  $\frac{G}{S}$  is

- a)  $\frac{1}{9}$                       b)  $\frac{9}{1}$                       c) 10                      d)  $\frac{1}{10}$

989. Calculate the amount of charge flowing in 2 minutes in a wire of resistance  $10\Omega$  when a potential difference of 20 V is applied between its ends

- a) 120 C                      b) 240 C                      c) 20 C                      d) 4 C

990. An electric wire is connected across a cell of e.m.f.  $E$ . The current  $I$  is measured by an ammeter of resistance  $R$ . According to ohm's law

- a)  $E = I^2 R$                       b)  $E = IR$                       c)  $E = R/I$                       d)  $E = I/R$


991. Drift velocity  $v_d$  varies with the intensity of electric field as per the relation

- a)  $v_d \propto E$                       b)  $v_d \propto \frac{1}{E}$                       c)  $v_d = \text{constant}$                       d)  $v_d \propto E^2$

992. An immersion heater is rated 418 W. It should heat a litre of water from  $10^\circ\text{C}$  to  $30^\circ\text{C}$  in nearly


- a) 44 s                      b) 100 s                      c) 200 s                      d) 400 s

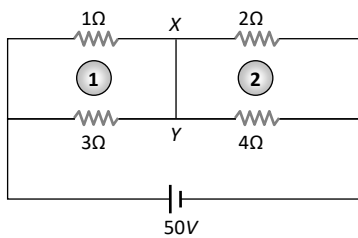993. Current through wire  $XY$  of circuit shown is




- a) 1 A                      b) 4 A                      c) 2 A                      d) 3 A

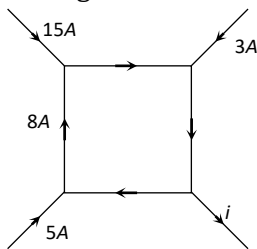994. The figure shows a network of currents. The magnitude of currents is shown here. The current  $i$  will be



- a) 3 A                      b) 13 A                      c) 23 A                      d) -3 A

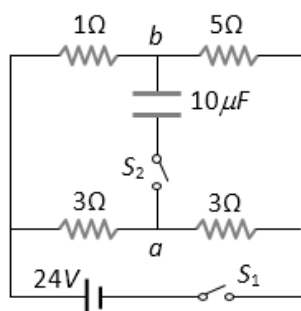
995. In the circuit shown in the figure, switch  $S_1$  is initially closed and  $S_2$  is open. Find  $V_a - V_b$



- a) 4 V                                      b) 8 V                                      c) 12 V                                      d) 16 V
996.  $62.5 \times 10^{18}$  electrons per second are flowing through a wire of area of cross-section  $0.1 \text{ m}^2$ , the value of current flowing will be  
 a) 1 A                                      b) 0.1 A                                      c) 10 A                                      d) 0.11 A
997. If three bulbs 60W, 100W and 200 W are connected in parallel, then  
 a) 200 W bulb will glow more                                      b) 60 W bulb will glow more  
 c) 100 W bulb will glow more                                      d) All the bulbs will glow equally
998. Four resistances of  $100 \Omega$  each are connected in the form of square. Then, the effective resistance along the diagonal points is  
 a)  $200 \Omega$                                       b)  $400 \Omega$                                       c)  $100 \Omega$                                       d)  $150 \Omega$
999. Water of volume 2 litre in a container is heated with a coil of 1 kW at  $27^\circ\text{C}$ . The lid of the container is open and energy dissipates at rate of  $160 \text{ J/s}$ . In how much time temperature will rise from  $27^\circ\text{C}$  to  $77^\circ\text{C}$  [Given specific heat of water is  $4.2 \text{ kJ/kg}$ ]  
 a) 8 min 20 s                                      b) 6 min 2 s                                      c) 7 min                                      d) 14 min
- 100 Flash light equipped with a new set of batteries, produces bright white light. As the batteries wear out  
 0.

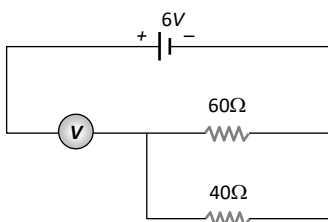
- a) The light intensity gets reduced with no change in its colour  
 b) Light colour changes first to yellow and then red with no change in intensity  
 c) It stops working suddenly while giving white light  
 d) Colour changes to red and also intensity gets reduced
- 100 A potentiometer has uniform potential gradient. The specific resistance of the material of the  
 1. potentiometer wire is  $10^{-7} \text{ ohm - meter}$  and the current passing through it is  $0.1 \text{ ampere}$ ; cross-section of the wire is  $10^{-6} \text{ m}^2$ . The potential gradient along the potentiometer wire is  
 a)  $10^{-4} \text{ V/m}$                                       b)  $10^{-6} \text{ V/m}$                                       c)  $10^{-2} \text{ V/m}$                                       d)  $10^{-8} \text{ V/m}$
- 100 A hot electric iron has a resistance of  $80 \Omega$  and is used on a  $200 \text{ V}$  source. The electrical energy spent, if it is  
 2. used for two hours, will be  
 a)  $8000 \text{ Wh}$                                       b)  $2000 \text{ Wh}$                                       c)  $1000 \text{ Wh}$                                       d)  $800 \text{ Wh}$
- 100 The thermocouple is based on the principle of  
 3.
- a) Seebeck effect                                      b) Thomson effect                                      c) Peltier effect                                      d) Joule effect

- 100 The measurement of voltmeter in the following circuit is  
 4.



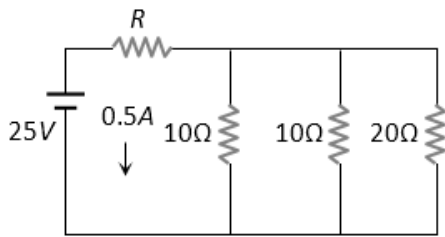- a) 2.4 V                                      b) 3.4 V                                      c) 4.0 V                                      d) 6.0 V
- 100 In the circuit given, the correct relation to a balanced Wheatstone bridge is  
 5.
- 
- a)  $\frac{P}{Q} = \frac{R}{S}$                                       b)  $\frac{P}{Q} = \frac{S}{R}$                                       c)  $\frac{P}{R} = \frac{S}{Q}$                                       d) None of these
- 100 In the circuit as shown in figure the  
 6.





- a) Resistance  $R = 46 \Omega$
- b) Current through  $20 \Omega$  resistance is  $0.1 A$
- c) Potential difference across the middle resistance is  $2 V$
- d) All option are correct

100 Two electric bulbs, each designed to operate with a power of  $500 W$  in  $220 V$  line are connected in series in a  $110 V$  line. The power generated by each bulb will be

- a)  $31.25 W$
- b)  $40 W$
- c)  $60 W$
- d)  $3.125 W$

100 A heater draws a current of  $2A$  when connected to a  $250 V$  source. The rate of energy dissipation is


- a)  $500 W$
- b)  $1000 W$
- c)  $250 W$
- d)  $125 W$

100 A  $100 \text{ ohm}$  galvanometer gives full scale deflection at  $10 \text{ mA}$ . How much shunt is required to read  $100 \text{ mA}$

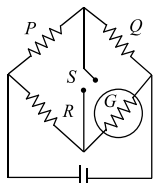- a)  $11.11 \text{ ohm}$
- b)  $9.9 \text{ ohm}$
- c)  $1.1 \text{ ohm}$
- d)  $4.4 \text{ ohm}$


101 The figure shows a circuit diagram of a 'Wheatstone Bridge' to measure the resistance  $G$  of the

galvanometer. The relation  $\frac{P}{Q} = \frac{R}{G}$  will be satisfied only when



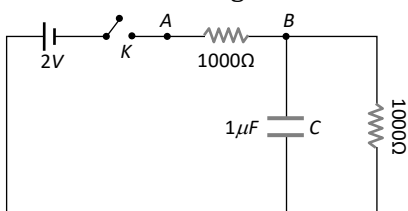
- a) The galvanometer shows a deflection when switch  $S$  is closed
- b) The galvanometer shows a deflection when switch  $S$  is open
- c) The galvanometer shows no change in deflection whether  $S$  is open or closed
- d) The galvanometer shows no deflection

101 When the key  $K$  is pressed at time  $t = 0$ , which of the following statements about the current  $I$  in the resistor  $AB$  of the given circuit is true



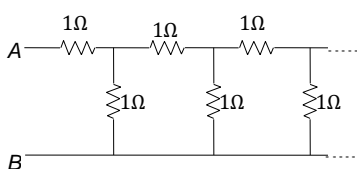- a)  $I = 2 \text{ mA}$  at all  $t$
- b)  $I$  oscillates between  $1 \text{ mA}$  and  $2 \text{ mA}$
- c)  $I = 1 \text{ mA}$  at all  $t$
- d) At  $t = 0, I = 2 \text{ mA}$  and with time it goes to  $1 \text{ mA}$

101 The equivalent resistance between points  $A$  and  $B$  of an infinite network of resistances, each of  $1 \Omega$ , connected as shown is



a) Infinite

b)  $2\ \Omega$

c)  $\frac{1 + \sqrt{5}}{2}\ \Omega$

d) zero

101 If 100 kWh of energy is consumed at 66 V in a copper voltmeter, then the mass of copper liberated will be

3. (Given, ECE of Cu =  $0.33 \times 10^{-6}\ \text{kg C}^{-1}$ )

a) 1.65 kg


b) 1.8 kg

c) 3.3 kg

d) 3.6 kg

101 In the circuit shown in the figure, if the potential at point A is taken to be zero, the potential at point B is

4.

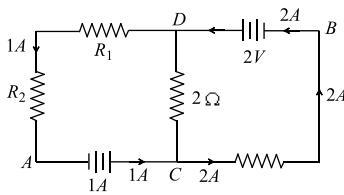

a)  $-2V$

b)  $+1V$

c)  $-1V$

d)  $+2V$

101 When a current is passed through water, acidified with a dilute sulphuric acid, the gases formed at the

5. platinum electrodes are

a) 1 vol. hydrogen (cathode) and 2 vol. oxygen (anode)

b) 2 vol. hydrogen (cathode) and 1 vol. oxygen (anode)

c) 1 vol. hydrogen (cathode) and 1 vol. oxygen (anode)

d) 1 vol. oxygen (cathode) and 2 vol. hydrogen (anode)

101 The temperature at which thermo emf is zero, is

6.

a) Temperature of inversion

b) Temperature of cold junction

c) Neutral temperature

d) None of the above

101 An emf of 0.9 V is generated when the temperature difference hot and cold junction of thermocouple is 75

7. K. Assuming that the thermo emf is directly proportional to the temperature difference, the extent to which the thermo emf will change when the cold junction is heated up by 15 K is

a) 10%

b) 20%

c) 40%

d) 60%

101  $n$  identical cells, each of emf  $E$  and internal resistance  $r$ , are connected in series a cell  $A$  is joined with

8. reverse polarity. The potential difference across each cell, except  $A$  is

a)  $\frac{2nE}{n-2}$


b)  $\frac{(n-2)E}{n}$

c)  $\frac{(n-1)E}{n}$

d)  $\frac{2E}{n}$

101 The ammeter  $A$  reads 2 A and the voltmeter  $V$  reads 20 V. The value of resistance  $R$  is (Assuming finite

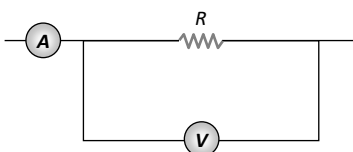9. resistance's of ammeter and voltmeter)



a) Exactly 10 ohm

b) Less than 10 ohm

c) More than 10 ohm

d) We cannot definitely say

102 An electric heater kept in vacuum is heated continuously by passing electric current. Its temperature

0.

a) Will go on rising with time

b) Will stop after sometime as it will loose heat to the surroundings by conduction

c) Will rise for sometime and there after will start falling

d) Will become constant after sometime because of loss of heat due to radiation

102 Two identical batteries each emf  $E = 2V$  and internal resistance  $r = 1\ \Omega$  are available to produce heat in an

1. external resistance by passing a current through it. The maximum Joulean power that can be developed across  $R$  using these batteries is

a) 1.28 W

b) 2.0 W

c)  $\frac{8}{9}$  W

d) 3.2 W

102 One junction of thermocouple is at  $0^\circ\text{C}$  and the other is at  $T^\circ\text{C}$ . The thermo emf (in volts) is given by

2.  $E = 20 \times 10^{-6}T - 0.02 \times 10^{-6}T^2$


The maximum value of  $E$  is

- a) 5 mV                      b) 1 mV                      c) 10 mV                      d) Zero

102 If  $t_1$  and  $t_2$  are the times taken by two different coils for producing same heat with same supply, then the time taken by them to produce the same heat when connected in parallel will be

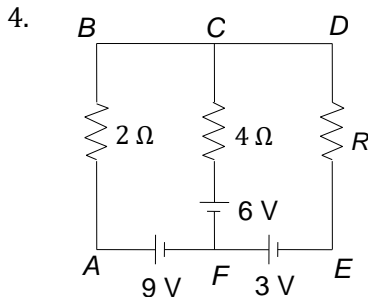
- a)  $t_1 + t_2$                       b)  $\frac{t_1 t_2}{t_1 + t_2}$                       c)  $\frac{2t_1 t_2}{t_1 + t_2}$                       d)  $t_1 t_2$

102 For what value of  $R$  in the circuit as shown in figure, current passing through  $4\Omega$  resistance will be zero.



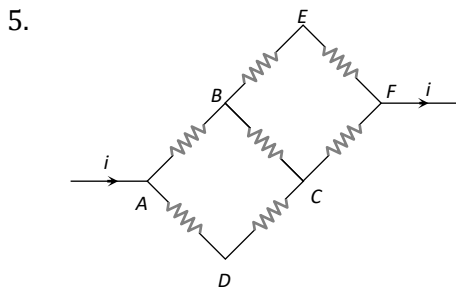- a) 1  $\Omega$                       b) 2  $\Omega$                       c) 3  $\Omega$                       d) 4  $\Omega$

102 In the adjoining circuit diagram each resistance is of  $10\Omega$ . The current in the arm AD will be




- a)  $\frac{2i}{5}$                       b)  $\frac{3i}{5}$                       c)  $\frac{4i}{5}$                       d)  $\frac{i}{5}$

102 An electric fan and a heater are marked as 100 watt, 220 volt and 1000 watt, 220 volt respectively. The resistance of the heater is

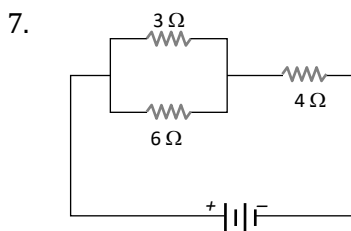- a) Zero                      b) Greater than that of the fan  
c) Less than that of the fan                      d) Equal to that of the fan

102 In the figure, current through the  $3\Omega$  resistor is 0.8 ampere, then potential drop through  $4\Omega$  resistor is



- a) 9.6 V                      b) 2.6 V                      c) 4.8 V                      d) 1.2 V

102 In a potentiometer experiment two cells of e.m.f.'s  $E_1$  and  $E_2$  are used in series and in conjunction and the balancing length is found to be 58 cm of the wire. If the polarity of  $E_2$  is reversed, then the balancing length becomes 29 cm. The ratio  $\frac{E_1}{E_2}$  of the e.m.f. of the two cells is

- a) 1 : 1                      b) 2 : 1                      c) 3 : 1                      d) 4 : 1

102 An energy source will supply a constant current into, the load, if its internal resistance is


9.  
a) Equal to the resistance of the load  
b) Very large as compared to the load resistance  
c) Zero  
d) Non-zero but less than the resistance of the load

103 The electric bulbs have tungsten filaments of same length. If one of them gives 60 watt and other 100 watt,

0. then
- 100 watt bulb has thicker filament
  - 60 watt bulb has thicker filament
  - Both filaments are of same thickness
  - It is possible to get different wattage unless the lengths are different


103 The value of current I in figure is

1.

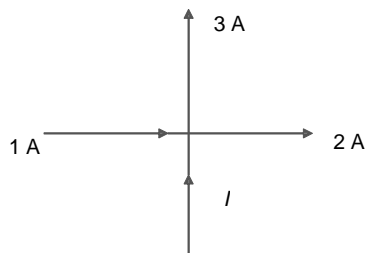

- 4A
- 6A
- 3A
- 5A

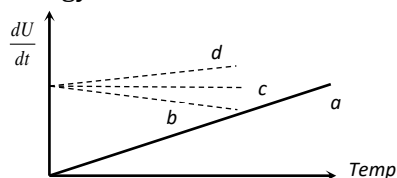103 A constant current  $i$  is passed through a resistor. Taking the temperature coefficient of resistance into account, indicate which of the plots shown in figure best represents the rate of production of thermal energy in the resistor



- a
- b
- c
- d

103 A torch battery consists of two cells of 1.45 volt and an internal resistance 0.15  $\Omega$ . If each cell sends current through the filament of the lamps having resistance 1.5 ohm, the value of current will be

- 16.11 amp
- 1.611 amp
- 0.1611 amp
- 2.6 amp

103 Thermoelectric constant of a thermocouple are  $\alpha$  and  $\beta$ . Thermoelectric power at inversion temperature is

- $\alpha$
- $-\alpha$
- $\frac{\alpha}{\beta}$
- $-\frac{\alpha}{\beta}$

103 A galvanometer whose resistance is  $120\Omega$  gives full scale deflection with a current of 0.005 A so that it can read a maximum current of 10 A. A shunt resistance is added in parallel with it. The resistance of the ammeter so formed is

- 0.06  $\Omega$
- 0.006  $\Omega$
- 0.6  $\Omega$
- 6  $\Omega$

103 An electron revolves  $6 \times 10^{15}$  times/sec in circular loop. The current in the loop is

- 0.96 mA
- 0.96  $\mu$ A
- 28.8 A
- None of these

103 A galvanometer of resistance 25  $\Omega$  measures  $10^{-3}$ A. shunt required to increase range upto 2A is

- 12.5  $\Omega$
- 0.125  $\Omega$
- 0.125  $\Omega$
- 1.25  $\Omega$

103 The maximum current that can be measured by a galvanometer of resistance 40 $\Omega$  is 10mA. It is converted into a voltmeter that can read upto 50V. The resistance to be connected in series with the galvanometer (in ohm) is

- 2010
- 4050
- 5040
- 4960

103 A student has 10 resistors of resistance ' $r$ '. The minimum resistance made by him from given resistors is

- 10 r
- $\frac{r}{10}$
- $\frac{r}{100}$
- $\frac{r}{5}$

104  $n$  identical cells each of e. m. f.  $E$  and internal resistance  $r$  are connected in series. An external resistance  $R$  is connected in series to this combination. The current through  $R$  is

- $\frac{nE}{R + nr}$
- $\frac{nE}{nR + r}$
- $\frac{E}{R + nr}$
- $\frac{nE}{R + r}$

104 A thermoelectric refrigerator works on

1. a) Joule effect                      b) Seebeck effect                      c) Peltier effect                      d) Thermionic emission

104 A wire of length 100 cm is connected to a cell of *emf* 2 V and negligible internal resistance. The resistance

2. of the wire is 3 Ω. The additional resistance required to produce a potential drop of 1 milli volt per cm is


- a) 60 Ω                      b) 47 Ω                      c) 57 Ω                      d) 35 Ω

104 An electric bulb is rated 60W, 220V. The resistance of its filament is

3. a) 708 Ω                      b) 870 Ω                      c) 807 Ω                      d) 780 Ω

104 In a Ag voltmeter 2.68 g of silver is deposited in 10 min. The heat developed in 20Ω resistor during the

4. same period will be

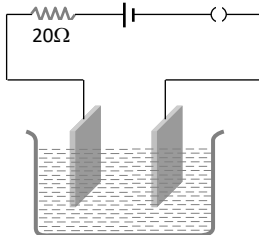

- a) 192 kJ                      b) 192 J                      c) 200 J                      d) 132 kJ

104 A railway compartment is lit up by thirteen lamps each taking 2.1 A at 15 V. The heat generated per

5. second in each lamp will be

- a) 4.35 cal                      b) 5.73 cal                      c) 7.5 cal                      d) 2.5 cal

104 If  $R_1$  and  $R_2$  be the resistances of the filaments of 200 W and 100 W electric bulbs operation at 220 V, then

6.  $\left(\frac{R_1}{R_2}\right)$  is

- a) 1                      b) 2                      c) 0.5                      d) 4

104 In voltaic air cell if 5g zinc is consumed, how many ampere hours shall we get?

7. a) 2.05                      b) 8.2                      c) 4.1                      d)  $5 \times 5.38 \times 10^{-3}$

104 A house, served by 220 V supply line, is protected by a 9 A fuse. The maximum number of 60 W bulbs in

8. parallel that can be turned on is

- a) 11                      b) 22                      c) 33                      d) 44

104 The temperature coefficient of resistance for a wire is  $0.00125^\circ \text{C}^{-1}$ . At 300 K its resistance is 1 Ω. The

9. temperature at which the resistance becomes 1.5 Ω is?

- a) 450 K                      b) 727 K                      c) 454 K                      d) 900 K

105 A 10 μF capacitor is charged to 500 V and then its plates are joined together through a resistance of 10 Ω.

0. The heat produced in the resistance is

- a) 500 J                      b) 250 J                      c) 125 J                      d) 1.25 J

105 The ratio of the amounts of heat developed in the four arms of a balanced Wheatstone bridge, when the

1. arms have resistance  $P = 100 \Omega$ ;  $Q = 10 \Omega$ ;  $R = 300 \Omega$  and  $S = 30 \Omega$  respectively is

- a) 3 : 30 : 1 : 10                      b) 30 : 3 : 10 : 1                      c) 30 : 10 : 1 : 3                      d) 30 : 1 : 3 : 10

105 If the resistivity of an alloy of  $\rho'$  and that of constituent metals is  $\rho$ , then

2. a)  $\rho' > \rho$                       b)  $\rho' < \rho$   
c)  $\rho' = \rho$                       d) There is no simple relation between  $\rho$  and  $\rho'$

105 The electrochemical equivalent of a material in an electrolyte depends on

3. a) The nature of the material  
b) The current through the electrolyte  
c) The amount of charge passed through electrolyte  
d) The amount of material present in electrolyte


105 A current passing through a copper voltmeter deposits 0.002 kg of copper on cathode plate in 100 min. If

4. there are  $10^{25}$  copper atoms in one kg of copper, the electric charge delivered to cathode by  $\text{Cu}^{++}$  ions per second will be
- a) 0.53 C                      b) 0.71 C                      c) 1.06 C                      d) 10.06 C

105 Resistance of a wire at  $20^\circ\text{C}$  is  $20\Omega$  and at  $500^\circ\text{C}$  is  $60\Omega$ . At what temperature its resistance is  $25\Omega$ ?

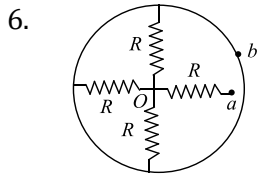
5. a)  $160^\circ\text{C}$                       b)  $250^\circ\text{C}$                       c)  $100^\circ\text{C}$                       d)  $80^\circ\text{C}$

105 The equivalent resistance between points  $a$  and  $b$  of a network shown in the figure is given by



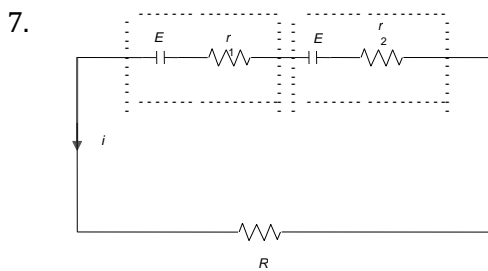- a)  $\frac{3}{4}R$                       b)  $\frac{4}{3}R$                       c)  $\frac{5}{4}R$                       d)  $\frac{4}{5}R$

105 If the potential difference across the internal resistance  $r_1$  is equal to the emf  $E$  of the battery, then




- a)  $R = r_1 + r_2$                       b)  $R = \frac{r_1}{r_2}$                       c)  $R = r_1 - r_2$                       d)  $R = \frac{r_2}{r_1}$

105 In an electric heater 4 amp current passes for 1 minute at potential difference of 250 volt, the power of heater and energy consumed will be respectively

- a) 1 kW, 60 kJ                      b) 0.5 kW, 30 kJ                      c) 10 kW, 600 kJ                      d) None of these

105 In a metre bridge experiment, resistances are connected as shown in figure. The balancing length  $l_1$  is

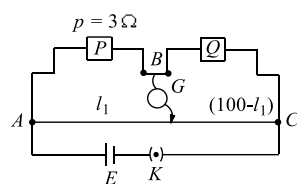9. 55 cm. Now an unknown resistance  $x$  is connected in series with  $P$  and the new balancing length is found to be 75 cm. The value of  $x$  is




- a)  $\frac{54}{12}\Omega$                       b)  $\frac{20}{11}\Omega$                       c)  $\frac{48}{11}\Omega$                       d)  $\frac{11}{48}\Omega$

106 The plates of a charged condenser is connected to a voltmeter. If the plates are moved apart, the reading of voltmeter will

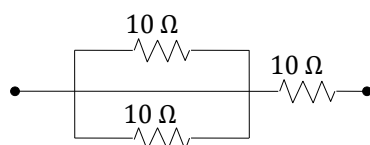- a) Increase                      b) Decrease  
c) Remain unchanged                      d) Information is insufficient

106 Three equal resistances, each of  $10\Omega$  are connected as shown in figure. The maximum power consumed by each resistance is 20 W. What is maximum power that can be consumed by the combination?



- a) 5 W                      b) 15 W                      c) 30 W                      d) 60 W

106 Two resistance wires on joining in parallel the resultant resistance is  $\frac{6}{5}$  ohms. One of the wire breaks, the effective resistance is 2 ohms. The resistance of the broken wire is

a)  $\frac{3}{5} \text{ ohm}$


b)  $2 \text{ ohm}$

c)  $\frac{6}{5} \text{ ohm}$

d)  $3 \text{ ohm}$

106 For the circuit shown in the figure the potential difference between  $A$  and  $B$  will be (in volt)

3.

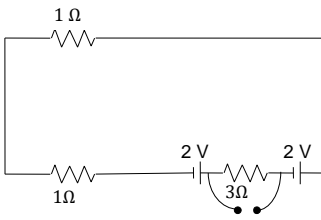

a) 2


b) 1.5

c) 1.0

d) Zero

106 Shown in the figure adjacent is a meter-bridge set up with null deflection in the galvanometer. The value of

4. the unknown resistor  $R$  is

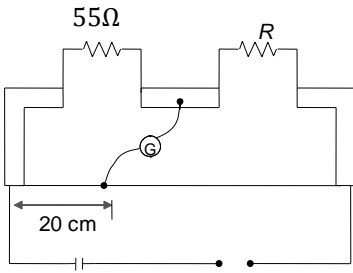

a)  $13.75 \Omega$


b)  $220 \Omega$

c)  $110 \Omega$

d)  $55 \Omega$

106 The heat produced in  $4 \Omega$  resistance is 10 cal. The heat produced in  $10 \Omega$  resistance will be

5.

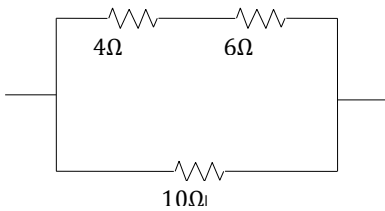

a) 25 cal

b) 14 cal

c) 10 cal

d) 20 cal

106 To liberate two litres of hydrogen at 222.4 atmosphere from acidulated water the quantity of electricity

6. that must pass through is

a) 44.8 C


b) 96500 C

c) 193000 C

d) 386000 C

106 In the circuit shown, the reading of ammeter when switch  $S$  is open and when switch  $S$  is closed

7. respectively are

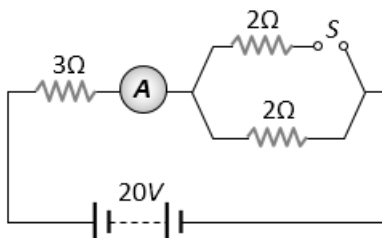

a) 3 A and 4 A

b) 4 A and 5 A

c) 5 A and 6 A

d) 6 A and 7 A

106 In the process of electrolysis, the current is carried out inside the electrolyte by

8.

a) Electrons

b) Atoms


c) Positive and negative ions

d) All the above

106 The resistance of an ammeter is  $3 \Omega$  and its scale is graduated for a current upto 100A. After an additional

9. shunt has been connected to this ammeter it becomes possible to measure currents upto 750A by this meter. The value of shunt resistance is

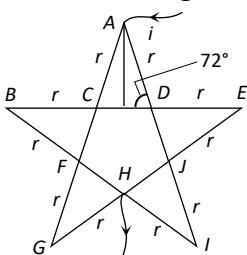- a)  $20\ \Omega$                       b)  $2\ \Omega$                       c)  $0.2\ \Omega$                       d)  $2\text{K}\ \Omega$
- 107 The relation between Faraday's constant  $F$ , electron charge  $e$  and avogadro number  $N$  is 0.
- a)  $F = N/e$                       b)  $F = Ne$                       c)  $N = F^2$                       d)  $F = N^2e$
- 107 The resistance of a wire is  $10\ \Omega$ . Its length is increased by 10% by stretching. The new resistance will now 1. be
- a)  $12\ \Omega$                       b)  $1.2\ \Omega$                       c)  $13\ \Omega$                       d)  $11\ \Omega$
- 107 The length of a given cylindrical wire is increased by 100%. Due to the consequent decrease in diameter 2. the change in the resistance of the wire will be
- a) 200 %                      b) 100 %                      c) 50 %                      d) 300 %
- 107 The power of heater is 750 W at  $1000^\circ\text{C}$ . What will be its power at  $200^\circ\text{C}$  if  $\alpha = 4 \times 10^{-4}$  per $^\circ\text{C}$ ? 3.
- a) 400 W                      b) 990 W                      c) 250 W                      d) 1500 W
- 107 Masses of the three wires of same material are in the ratio of 1: 2: 3 and their lengths in the ratio of 3: 2: 1. 4. Electrical resistance of these wires will be in the ratio of
- a) 1: 1: 1                      b) 1: 2: 3                      c) 9: 4: 1                      d) 27: 6: 1
- 107 A wire of diameter 0.02 metre contains  $10^{28}$  free electrons per cubic metre. For an electrical current of 5. 100 A, the drift velocity of the free electrons in the wire is nearly
- a)  $1 \times 10^{-19}\text{m/s}$                       b)  $5 \times 10^{-10}\text{m/s}$                       c)  $2 \times 10^{-4}\text{m/s}$                       d)  $8 \times 10^3\text{m/s}$
- 107 Two uniform wires A and B are of the same metal and have equal masses. The radius of wire A is twice 6. that of wire B. The total resistance of A and B when connected in parallel is
- a)  $4\ \Omega$  when the resistance of wire A is  $4.25\ \Omega$   
b)  $5\ \Omega$  when the resistance of wire A is  $4.25\ \Omega$   
c)  $4\ \Omega$  when the resistance of wire B is  $4.25\ \Omega$   
d)  $5\ \Omega$  when the resistance of wire B is  $4.25\ \Omega$
- 107 A piece of fuse wire melts when a current of 15 ampere flows through it. With this current, if it dissipates 7. 22.5 W, the resistance of fuse wire will be
- a) Zero                      b)  $10\ \Omega$                       c)  $1\ \Omega$                       d)  $0.10\ \Omega$
- 107 A current of 2.0 ampere passes through a cell of e.m.f. 1.5 volt having internal resistance of 0.15 ohm. The 8. potential difference measured, in volt, across both the ends of the cell will be
- a) 1.35                      b) 1.50                      c) 1.00                      d) 1.20
- 107 To draw maximum current from a combination of cells, how should the cells be grouped? 9.
- a) Parallel                      b) Series  
c) Mixed grouped                      d) Depends upon the relative values of internal and external resistances
- 108 Watt-hour meter measures 0.
- a) Electric energy                      b) Current                      c) Voltage                      d) Power
- 108 A 12 HP motor has to be operated 8 h/day. How much will it cost at the rate of 50 paise/kWh in 10 days? 1.
- a) Rs 347                      b) Rs 358                      c) Rs 375                      d) Rs 397
- 108 In the following star circuit diagram (figure), the equivalent resistance between the points A and H will be 2.



- a)  $1.944\ r$                       b)  $0.973\ r$                       c)  $0.486\ r$                       d)  $0.243\ r$




108 A voltmeter has resistance of  $2000\ \text{ohm}$  and it can measure upto  $2V$ . If we want to increase its range to  $10\ V$ , then the required resistance in series will be

- a)  $2000\ \Omega$                       b)  $4000\ \Omega$                       c)  $6000\ \Omega$                       d)  $8000\ \Omega$

108 The thermocouple among the following that can produce maximum thermo-emf for the same temperature difference between the junction is

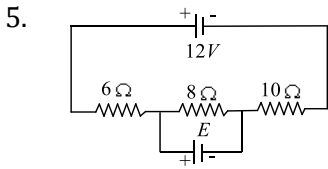- a) Fe-Cu                      b) Ag-Au                      c) Sb-Bi                      d) Cu-Pb

108 In the circuit shown, the current through  $8\ \text{ohm}$  is same before and after connecting  $E$ . The value of  $E$  is




- a)  $12\ V$                       b)  $6\ V$                       c)  $4\ V$                       d)  $2\ V$

108 Heat produced in a wire of resistance  $R$  due to current flowing at constant potential difference is proportional to

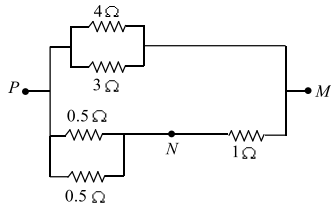- a)  $\frac{1}{R^2}$                       b)  $\frac{1}{R}$                       c)  $R$                       d)  $R^2$

108 In the circuit shown, the current through the  $4\ \Omega$  resistor is  $1\ \text{amp}$  when the points  $P$  and  $M$  are connected to a d.c. voltage source. The potential difference between the points  $M$  and  $N$  is



- a)  $0.5\ V$                       b)  $3.2\ V$                       c)  $1.5\ V$                       d)  $1.0\ V$

108 The thermo emf of a thermo-couple is found to depend on temperature  $T$  (in degree Celsius) as  $E = 4T -$


8.  $\frac{T^2}{200}$ , where  $T^\circ\text{C}$  is the temperature of the hot junction. The neutral and inversion temperature of the thermocouple are (in degree celsius)

- a)  $100, 200$                       b)  $200, 400$                       c)  $300, 600$                       d)  $400, 800$

108 In the above question, the resistance between the square faces is

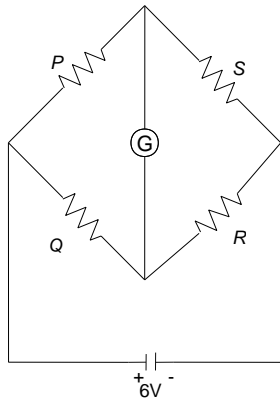9. a)  $3 \times 10^{-9}\ \text{ohm}$                       b)  $3 \times 10^{-7}\ \text{ohm}$                       c)  $3 \times 10^{-5}\ \text{ohm}$                       d)  $3 \times 10^{-3}\ \text{ohm}$

109 In the Wheatstone's network given,  $P=10\ \Omega, Q = 20\ \Omega, R=15\ \Omega, S=30\ \Omega$ , the current passing through the battery (of negligible internal resistance) is



- a)  $0.36A$                       b) Zero                      c)  $0.18A$                       d)  $0.72A$

109 When a current is passed in a conductor,  $3^\circ\text{C}$  rise in temperature is observed. If the strength of current is increased by two times, then rise in temperature will approximately be


- a)  $36^\circ\text{C}$                       b)  $27^\circ\text{C}$                       c)  $18^\circ\text{C}$                       d)  $9^\circ\text{C}$

109 To get a maximum current through a resistance of  $2.5\ \Omega$ , one can use  $m$  rows of cells each row having  $n$

2. cells. The internal resistance of each cell is  $0.5\Omega$ . What are the values of  $m$  and  $n$  if the total number of cells are 20?
- a)  $m = 2, n = 10$                       b)  $m = 4, n = 5$                       c)  $m = 5, n = 4$                       d)  $n = 2, m = 10$

109 If an ammeter is joined in parallel through a circuit, it can be damaged due to excess  
3.

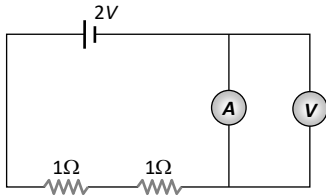
- a) Resistance                      b) Current                      c) Voltage                      d) None of these
- 109 In the circuit shown,  $A$  and  $V$  are ideal ammeter and voltmeter respectively. Reading of the voltmeter will  
4. be



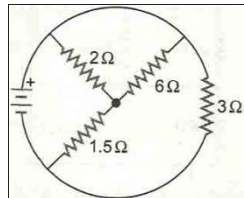- a) 2 V                      b) 1 V                      c) 0.5 V                      d) Zero
- 109 Two identical batteries each of emf 2 V and internal resistance  $1\Omega$  are available to produce heat in an  
5. external resistance by passing current through it. The maximum Joulean power that can be developed across the resistance using these batteries is.
- a) 2W                      b) 3.2 W                      c) 1.28 W                      d)  $8/9$  W
- 109 When the temperature difference between hot and cold junctions of a thermo-couple is 100 K an emf of 1  
6. V is generated. Assume the cold junction is heated by 20 K, the percentage change in thermo emf is
- a) 20%                      b) 30%                      c) 40%                      d) 25%


- 109 There are  $n$  similar conductors each of resistance  $R$ . The resultant resistance comes out to be  $x$  when  
7. connected in parallel. If they are connected in series, the resistance comes out to be
- a)  $x/n^2$                       b)  $n^2x$                       c)  $x/n$                       d)  $nx$

109 The total current supplied to the circuit by the battery as shown figure is  
8.



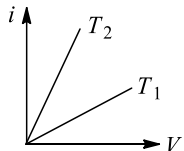
- a) 1A                      b) 6A                      c) 4A                      d) 2A
- 109 A galvanometer has a resistance of  $25\text{ ohm}$  and a maximum of  $0.01\text{ A}$  current can be passed through it. In  
9. order to change it into an ammeter of range  $10\text{ A}$ , the shunt resistance required is
- a)  $5/999\text{ ohm}$                       b)  $10/999\text{ ohm}$                       c)  $20/999\text{ ohm}$                       d)  $25/999\text{ ohm}$
- 110 In cosmic rays  $0.15\text{ protons cm}^{-2}\text{ sec}^{-1}$  are entering the earth's atmosphere. If the radius of the earth is  
0.  $6400\text{ km}$ , the current received by the earth in the form of cosmic rays is nearly.
- a) 0.12 A                      b) 1.2 A                      c) 12 A                      d) 120 A

110 The current  $i$  and voltage  $V$  graphs for a given metallic wire at two different temperatures  $T_1$  and  $T_2$  are  
1. shown in the figure. It is concluded that



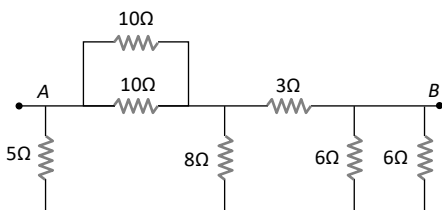- a)  $T_1 > T_2$                       b)  $T_1 < T_2$                       c)  $T_1 = T_2$                       d)  $T_1 = 2T_2$
- 110 In a region  $10^{19}\alpha$  -particles and  $10^{19}$  protons move to the left, while  $10^{19}$  electrons move to the right  
2. per second. The current is
- a) 3.2 A towards left                      b) 3.2 A towards right                      c) 6.4 A towards left                      d) 6.4 A towards right
- 110 An electric heater rated 220 V and 550 W is connected to AC mains. The current drawn by it is  
3.
- a) 0.8 A                      b) 2.5 A                      c) 0.4 A                      d) 1.25 A

- 110 A galvanometer has 30 divisions and a sensitivity  $16 \mu A/\text{div}$ . It can be converted into a voltmeter to read 4.  $3 V$  by connecting
- Resistance nearly  $6 k \Omega$  in series
  - $6 k \Omega$  in parallel
  - $500 \Omega$  in series
  - It cannot be converted
- 110 Three resistors are connected to form the sides of a triangle  $ABC$ , the resistance of the sides  $AB, BC$  and 5.  $CA$  are  $40 \text{ ohm}, 60 \text{ ohm}$  and  $100 \text{ ohm}$  respectively. The effective resistance between the points  $A$  and  $B$  in  $\text{ohm}$  will be
- 32
  - 64
  - 50
  - 200
- 110 A potentiometer wire of length  $1m$  and resistance  $10 \Omega$  is connected in series with a cell of  $\text{emf } 2V$  with 6. internal resistance  $1 \Omega$  and a resistance box including a resistance  $R$ . If potential difference between the ends of the wire is  $1 mV$ , the value of  $R$  is
- $20000 \Omega$
  - $19989 \Omega$
  - $10000 \Omega$
  - $9989 \Omega$
- 110 An external resistance  $R$  is connected to a battery of  $e. m. f. V$  and internal resistance  $r$ . The joule heat 7. produced in resistor  $R$  is maximum when  $R$  is equal to
- $r$
  - $\frac{r}{2}$
  - $2r$
  - Infinitely large
- 110 Two bulbs of  $500 W$  and  $200 W$  are manufactured to operate on  $220 V$  line. The ratio of heat produced in 8.  $500 W$  and  $200 W$ , in two cases, when firstly they are connected in parallel and secondly in series will be
- $\frac{5}{2} : \frac{2}{5}$
  - $\frac{5}{2} : \frac{5}{2}$
  - $\frac{2}{5} : \frac{5}{2}$
  - $\frac{2}{5} : \frac{2}{5}$
- 110 The current in a simple series circuit is  $5.0 A$ . when an additional resistance of  $2.0 \Omega$  is inserted, the 9. current drops to  $4.0 A$ . the original resistance of the circuit in  $\text{ohm}$  was
- 1.25
  - 8
  - 10
  - 20
- 111 When connected across the terminals of a cell, a voltmeter measures  $5V$  and a connected ammeter 0. measures  $10 A$  of current. A resistance of  $2 \text{ ohm}$  is connected across the terminals of the cell. The current flowing through this resistance will be
- $2.5 A$
  - $2.0 A$
  - $5.0 A$
  - $7.5 A$
- 111 In a potentiometer experiment for measuring the  $\text{emf}$  of a cell, the null point is at  $480 \text{ cm}$  when we have a 1.  $400 \Omega$  resistor in series with the cell and galvanometer. If the series resistances is reduced to half, the null point will be at
- $120 \text{ cm}$
  - $240 \text{ cm}$
  - $480 \text{ cm}$
  - $600 \text{ cm}$
- 111 An aluminium (Al) rod with area of cross-section  $4 \times 10^{-6} \text{ m}^2$  has a current of  $5 A$  flowing through it. Find 2. the drift velocity of electron in the rod. Density of Al =  $2.7 \times 10^3 \text{ kgm}^{-3}$  and atomic wt. =  $27u$ . Assume that each Al atom provides one electron.
- $8.6 \times 10^{-4} \text{ ms}^{-1}$
  - $1.3 \times 10^{-4} \text{ ms}^{-1}$
  - $2.8 \times 10^{-2} \text{ ms}^{-1}$
  - $3.8 \times 10^{-3} \text{ ms}^{-1}$
- 111 Seven resistance are connected as shown in the figure. The equivalent resistance between  $A$  and  $B$  is 3.




- $3 \Omega$
- $4 \Omega$
- $4.5 \Omega$
- $5 \Omega$

- 111 In a conductor if  $3000 \text{ coulomb}$  of charge enters and  $3000 \text{ coulomb}$  of charge exits in time  $10 \text{ minutes}$ , 4. then the current is
- $5 \text{ ampere}$
  - $10 \text{ ampere}$
  - $2.5 \text{ ampere}$
  - Zero
- 111 There are  $8$  equal resistance  $R$ . Two are connected in parallel, such four groups are connected in series, the 5. total resistance of the system will be
- $R/2$
  - $2 R$
  - $4 R$
  - $8 R$
- 111 Fifty electric bulbs, all identical, are connected in series across the mains of a  $220 V$  supply. After one bulb 6. is fused, the remaining  $49$  bulbs connected in series across the same mains. The illumination will be
- More with  $50$  bulbs than with  $48$  bulbs
  - More with  $49$  bulbs than with  $50$  bulbs

c) Equal in both cases

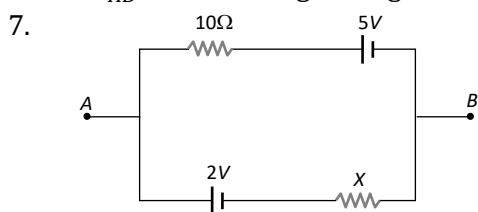d) In the ratio  $(50)^2 : (49)^2$  in the first and second case respectively

111 If  $V_{AB} = 4V$  in the given figure, then resistance  $X$  will be



- a) 5 Ω                                      b) 10 Ω                                      c) 15 Ω                                      d) 20 Ω

111 A current  $i$  passes through a wire of length  $l$ , radius of cross-section  $r$  and resistivity  $\rho$ . The rate of heat generation is

8. a)  $\frac{i^2 l \rho}{\pi r^2}$                                       b)  $i^2 \left(\frac{l \rho}{\pi r^2}\right)^2$                                       c)  $i^2 l \rho / r$                                       d)  $il \rho / r$

111 Two wires that are made up of two different materials whose specific resistance are in the ratio 2 : 3, length 3 : 4 and area 4 : 5. The ratio of their resistances is

9. a) 6 : 5                                      b) 6 : 8                                      c) 5 : 8                                      d) 1 : 2

112 Two electric bulbs (60W and 100W respectively) are connected in series. The current passing through them is

10. a) More in 100W bulb                      b) More in 60W bulb                      c) Same in both                      d) None of these


112 Twelve wires of equal resistance  $R$  are connected to form a cube. The effective resistance between two opposite diagonal ends will be

11. a)  $(5/6)R$                                       b)  $(6/5)R$                                       c)  $3R$                                       d)  $12R$

112 E.C.E. of Cu and Ag are  $7 \times 10^{-6}$  and  $1.2 \times 10^{-6}$ . A certain current deposits 14 gm of Cu. Amount of Ag deposited is

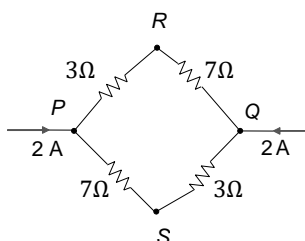12. a) 1.2 gm                                      b) 1.6 gm                                      c) 2.4 gm                                      d) 1.8 gm

112 A current of 2A flows in an electric circuit as shown in figure. The potential difference ( $V_R - V_S$ ), in volts (3.  $V_R - V_S$  are potentials at R and S respectively) is




- a) -4                                      b) +2                                      c) +4                                      d) -2

112 Two wires of the same dimensions but resistivities  $\rho_1$  and  $\rho_2$  are connected in series. The equivalent resistivity of the combination is

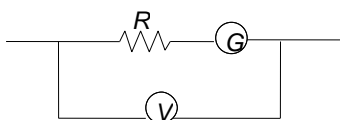4. a)  $\frac{\rho_1 + \rho_2}{2}$                                       b)  $\rho_1 + \rho_2$                                       c)  $2(\rho_1 + \rho_2)$                                       d)  $\sqrt{\rho_1 \rho_2}$

112 If resistance of voltmeter is  $10000\Omega$  and resistance of galvanometer is  $2\Omega$ , then find  $R$  when voltmeter reads 12V and galvanometer reads 0.1A.




- a)  $118\Omega$                                       b)  $120\Omega$                                       c)  $124\Omega$                                       d)  $114\Omega$


112 A 25 W, 220 V bulb and a 100 W, 220 V bulb are connected in parallel across a 440 V line.

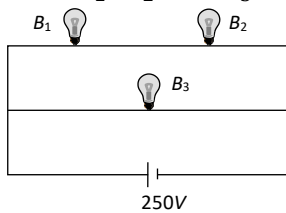6. a) Only 100 watt bulb will fuse                      b) Only 25 watt bulb will fuse  
c) Both bulbs will fuse                      d) None of the bulbs will fuse

- 112 A battery is made by connecting 6 cells each having capacity 5 Ah at 1.5V. The battery will have capacity  
7. equal to  
a) 20 Ah at 9 V                      b) 30 Ah at 1.5 V                      c) 5 Ah at 9 V                      d) 5 Ah at 1.5 V
- 112 If a wire of resistance  $20\Omega$  is covered with ice and a voltage of  $210\text{ V}$  is applied across the wire, then the  
8. rate of melting of ice is  
a)  $0.85\text{g/s}$                       b)  $1.92\text{g/s}$                       c)  $6.56\text{g/s}$                       d) All of these
- 112 A voltmeter of resistance  $1000\Omega$  gives full scale deflection when a current of  $100\text{ mA}$  flows through it. The  
9. shunt resistance required across it to enable it to be used as an ammeter reading  $1\text{ A}$  at full scale deflection is  
a)  $10000\Omega$                       b)  $9000\Omega$                       c)  $222\Omega$                       d)  $111\Omega$
- 113 A certain wire has a resistance  $R$ . The resistance of another wire identical with the first except having  
0. twice its diameter is  
a)  $2R$                       b)  $0.25R$                       c)  $4R$                       d)  $0.5R$
- 113 As the temperature of hot junction increases, the thermo *e.m.f*  
1.  
a) Always increases                      b) Always decreases  
c) May increase or decrease                      d) Always remains constant
- 113 A uniform wire of  $16\Omega$  is made into the form of square. Two opposite corners of the square are connected  
2. by a wire of resistance  $16\Omega$ . The effective resistance between the other two opposite corners is  
a)  $32\Omega$                       b)  $20\Omega$                       c)  $8\Omega$                       d)  $4\Omega$
- 113 A  $100\text{ W}$  bulb  $B_1$ , and two  $60\text{-W}$  bulbs  $B_2$  and  $B_3$ , are connected to a  $250\text{ V}$  source, as shown in the figure.  
3. Now  $W_1, W_2$  and  $W_3$  are the output powers of the bulbs  $B_1, B_2$  and  $B_3$ , respectively. Then



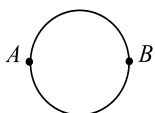- a)  $W_1 > W_2 = W_3$                       b)  $W_1 > W_2 > W_3$                       c)  $W_1 < W_2 = W_3$                       d)  $W_1 < W_2 < W_3$
- 113 What is the equivalent resistance of the circuit  
4.  
a)  $6\Omega$                       b)  $7\Omega$                       c)  $8\Omega$                       d)  $9\Omega$
- 113 An immersion heater is rated  $836\text{ watt}$ . It should heat  $1\text{ litre}$  of water from  $10^\circ\text{C}$  to  $40^\circ\text{C}$  in about  
5.  
a)  $200\text{ sec}$                       b)  $150\text{ sec}$                       c)  $836\text{ sec}$                       d)  $418\text{ sec}$
- 113 A resistance of  $2\Omega$  is connected across one gap of a meter-bridge (the length of the wire is  $100\text{cm}$ ) and an  
6. unknown resistance, greater than  $2\Omega$  is connected across the other gap. When these resistances are interchanged, the unknown resistance is  
a)  $3\Omega$                       b)  $2\Omega$                       c)  $4\Omega$                       d)  $6\Omega$
- 113 A wire of resistance  $12\text{ ohms per meter}$  is bent to form a complete circle of radius  $10\text{ cm}$ . The resistance  
7. between its two diametrically opposite points  $A$  and  $B$  as shown in the figure, is



- a)  $0.6\pi\Omega$                       b)  $3\Omega$                       c)  $6\pi\Omega$                       d)  $6\Omega$
- 113 Metals have

8. a) Zero resistivity                      b) High resistivity                      c) Low resistivity                      d) Infinite resistivity

113 A galvanometer acting as a voltmeter should have  
9.

- a) Low resistance in series with its coil                      b) Low resistance in parallel with its coil  
c) High resistance in series with its coil                      d) High resistance in parallel with its coil


114 The electromotive force of a primary cell is 2 volt. When it is short-circuited it gives a current of 4 ampere.

0. Its internal resistance in ohm is

- a) 0.5                      b) 5.0                      c) 2.0                      d) 8.0

114 In the circuit given here, the points A, B and C are 70V, zero, 10 V respectively. Then

1.

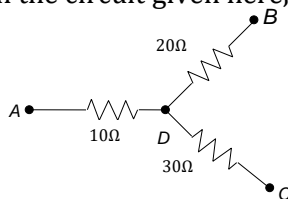

- a) The point D will be at a potential of 60V  
b) The point D will be at a potential of 20V  
c) Currents in the path AD, DB and DC are in the ratio of 1:2:3  
d) Currents in the path AD, DB and DC are in the ratio of 3 : 2 : 1

114 A 500 W heating unit is designed to operate from a 115 volt line. If the line voltage drops to 110 volt, the

2. percentage drop in heat output will be

- a) 10.20%                      b) 8.1%                      c) 8.6%                      d) 7.6%

114 Resistors P and Q are connected in the gaps of the meter bridge. The balancing point is obtained  $\frac{1}{3}$  m from

3. the zero end. If a 6 Ω resistance is connected in series with P the balance point shifts to  $\frac{2}{3}$  m from the same end. P and Q are

- a) 4,2                      b) 2,4  
c) Both (a) and (b)                      d) Neither (a) nor (b)


114 4 cells each of emf 2 V and internal resistance of 1Ω are connected in parallel to a load resistor of 2Ω. Then

4. the current through the load resistor is

- a) 2 A                      b) 1.5 A                      c) 1 A                      d) 0.888 A

114 A potential divider is used to give outputs of 4 V and 8 V from a 12 V source. Which combination of

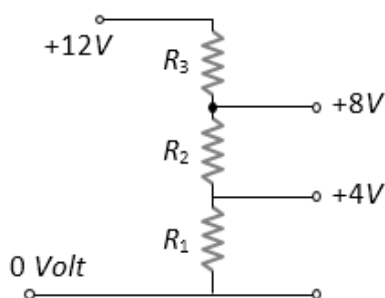5. resistances, ( $R_1 : R_2 : R_3$ ) gives the correct voltages?



- a) 2 : 1 : 2                      b) 1 : 1 : 1                      c) 2 : 2 : 1                      d) 1 : 1 : 2

114 Two identical heaters of 220V, 1000 W are placed in parallel with each other across 220V line, then the

6. combined power is

- a) 1000 W                      b) 2000 W                      c) 500 W                      d) 4000 W




114 Length of a hollow tube is 5m, it's outer diameter is 10 cm and thickness of it's wall is 5 mm. If resistivity

7. of the material of the tube is  $1.7 \times 10^{-8} \Omega \times m$  then resistance of tube will be

- a)  $5.6 \times 10^{-5} \Omega$                       b)  $2 \times 10^{-5} \Omega$                       c)  $4 \times 10^{-5} \Omega$                       d) None of these


114 The mass of ions deposited during a given interval of time in the process of electrolysis depends on

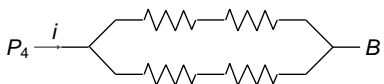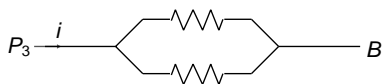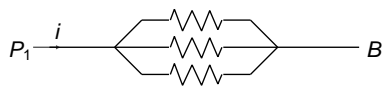8. a) The current                      b) The resistance                      c) The temperature                      d) The electric power
- 114 A current of  $0.01\text{mA}$  passes through the potentiometer wire of a resistivity of  $10^9 \Omega\text{-cm}$  and area of cross-section  $10^{-2}\text{cm}^2$ . The potential gradient is
9. a)  $10^9\text{Vm}^{-1}$                       b)  $10^{11}\text{Vm}^{-1}$                       c)  $10^{10}\text{Vm}^{-1}$                       d)  $10^8\text{Vm}^{-1}$
- 115 A galvanometer of resistance  $25\Omega$  giving full scale deflection for a current of  $10\text{ milliampere}$ , is to be changed into a voltmeter of range  $100\text{ V}$  by connecting a resistance of ' $R$ ' in series with galvanometer. The value of resistance  $R$  in  $\Omega$  is
- 115  $n$  conducting wires of same dimensions but having resistivities  $1,2,3,\dots,n$  are connected in series. The equivalent resistivity of the combinations is
1. a)  $\frac{n(n+1)}{2}$                       b)  $\frac{n+1}{2}$                       c)  $\frac{n+2}{2n}$                       d)  $\frac{2n}{n+1}$
- 115 Arrange the order of power dissipated in the given circuits, if the same current is passing through all the circuits. The resistance of each resistor is  $r$ .



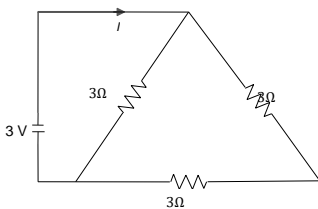
- a)  $P_1 > P_2 > P_3 > P_4$                       b)  $P_2 > P_3 > P_4 > P_1$   
c)  $P_4 > P_3 > P_2 > P_1$                       d)  $P_1 = P_2 = P_3 = P_4$
- 115 Three electric bulbs of rating  $60\text{W}$  each are joined in series and then connected to electric mains. The power consumed by these three bulbs will be
3. a)  $180\text{ W}$                       b)  $60\text{ W}$                       c)  $20\text{ W}$                       d)  $\frac{20}{3}\text{ W}$

- 115 A  $3\text{ V}$  battery with negligible internal resistance is connected in a circuit as shown in the figure. The current  $I$ , in the circuit will be



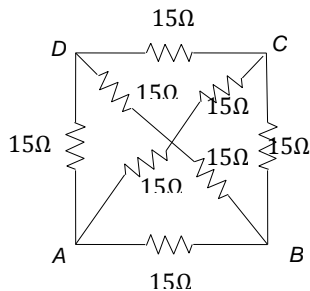
- a)  $1\text{ A}$                       b)  $1.5\text{ A}$                       c)  $2\text{ A}$                       d)  $\frac{1}{3}\text{ A}$
- 115 Two conductors of the same material have their diameters in the ratio  $1 : 2$  and their lengths in the ratio  $2 : 1$ . If the temperature difference between their ends is the same, then the ratio of amounts of heat conducted per second through them will be
5. a)  $4 : 1$                       b)  $1 : 4$                       c)  $8 : 1$                       d)  $1 : 8$
- 115 An electric kettle boils some water in  $16\text{ min}$ . Due to some defect, it becomes necessary to remove  $10\%$  turns of heating coil of the kettle. Now, how much time will it take to boil the same of water?
6. a)  $17.7\text{ min}$                       b)  $14.4\text{ min}$                       c)  $20.9\text{ min}$                       d)  $13.7\text{ min}$
- 115 A rod of a certain metal is  $1.0\text{ m}$  long and  $0.6\text{ cm}$  in diameter. Its resistance is  $3.0 \times 10^{-3}\Omega$ . Another disc made of the same metal is  $2.0\text{ cm}$  in diameter and  $1.0\text{ mm}$  thick. What is the resistance between the round faces of the disc?
7. a)  $1.35 \times 10^{-8}\Omega$                       b)  $2.70 \times 10^{-7}\Omega$                       c)  $4.05 \times 10^{-6}\Omega$                       d)  $8.10 \times 10^{-5}\Omega$

- 115 The equivalent resistance between the points  $A$  and  $B$  will be (each resistance is  $15\ \Omega$ )




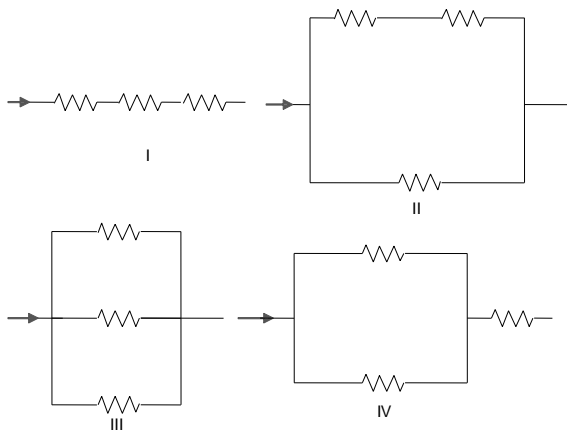- a)  $30\ \Omega$                       b)  $8\ \Omega$                       c)  $10\ \Omega$                       d)  $40\ \Omega$
- 115 An ammeter, suspected to give inaccurate reading, is connected in series with a *silver* voltmeter. The ammeter indicates  $0.54\ A$ . A steady current passed for one hour deposits  $2.0124\ g$  of *silver*. If the E.C.E. of *silver* is  $1.118 \times 10^{-3}\ g/C^{-1}$ , then the error in ammeter reading is
9. a)  $+0.04\ A$                       b)  $+0.02\ A$                       c)  $-0.03\ A$                       d)  $-0.01\ A$
- 116 The cell has an emf of  $2V$  and the internal resistance of  $3.9\ \Omega$ , the voltage across the cell will be
0. a)  $1.95\ V$                       b)  $1.5V$                       c)  $2V$                       d)  $1.8V$
- 116 Two bulbs of  $100\ W$  and  $200\ W$  working at  $220\ V$  are joined in series with  $220\ V$  supply. Total power consumed will be
1. a)  $65\ W$                       b)  $33\ W$                       c)  $300\ W$                       d)  $100\ W$
- 116 A current of  $1\ mA$  is flowing through a copper wire. How many electrons will pass a given point in one second
2.  $[e = 1.6 \times 10^{-19}\ Coulomb]$
- a)  $6.25 \times 10^{19}$                       b)  $6.25 \times 10^{15}$                       c)  $6.25 \times 10^{31}$                       d)  $6.25 \times 10^8$
- 116 A wire of resistance  $R$  is elongated  $n$  – fold to make a new uniform wire. The resistance of new wire
3. a)  $nR$                       b)  $n^2R$                       c)  $2nR$                       d)  $2n^2R$
- 116 Three unequal resistors in parallel are equivalent to a resistance  $1\ \Omega$ . If two of them are in the ratio  $1:2$  and if no resistance value is fractional, the largest of the three resistance in ohm is
4. a)  $4$                       b)  $6$                       c)  $8$                       d)  $12$
- 116 An electric kettle has two heating coils. When one coil is used, water in the kettle boils in  $5$  minutes, while when second coil is used, same water boils in  $10$  minutes. If the two coils, connected in parallel are used simultaneously, the same water will boil in time
5. a)  $3\ min\ 20\ sec$                       b)  $5\ min$                       c)  $7\ min\ 30\ sec$                       d)  $2\ min\ 30\ sec$
- 116 An electric kettle takes  $4\ A$  current at  $220\ V$ . How much time will it take to boil  $1\ kg$  of water from room temperature  $20^\circ C$ ? The temperature of boiling water is  $100^\circ C$
6. a)  $0.63\ minutes$                       b)  $6.3\ minutes$                       c)  $12.6\ minutes$                       d)  $12.8\ minutes$
- 116 The three resistances of equal value are arranged in the different combinations shown below. Arrange them in increasing order of power dissipation
- 7.






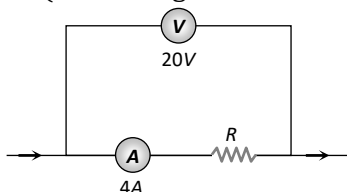- a) III < II < IV < I      b) II < III < IV < I      c) I < IV < III < II      d) I < III < II < IV
- 116 When a metal conductor connected to the left gap of a meter bridge is heated, the balancing point
8. a) Shifts towards right      b) Shifts towards left  
c) Remains unchanged      d) Remains at zero
- 116 The electro chemical equivalent of metal is  $3.3 \times 10^{-7} \text{ kgC}^{-1}$ . The mass of the metal liberated at the
9. cathode when a 3 A current is passed for 2 s, will be  
a)  $19.8 \times 10^{-7} \text{ kg}$       b)  $9.9 \times 10^{-7} \text{ kg}$       c)  $6.6 \times 10^{-7} \text{ kg}$       d)  $1.1 \times 10^{-7} \text{ kg}$
- 117 The resistance of a wire of iron is 10 ohm and temp. coefficient of resistance is  $5 \times 10^{-3}/^\circ\text{C}$ . At  $20^\circ\text{C}$  it
0. carries 30 milliampere of current. Keeping constant potential difference between its ends, the temperature of the wire is raised to  $120^\circ\text{C}$ . The current in milliampere that flows in the wire is  
a) 20      b) 15      c) 10      d) 40
- 117 One kilowatt hour is equal to
1. a)  $36 \times 10^5 \text{ joules}$       b)  $36 \times 10^3 \text{ joules}$       c)  $10^3 \text{ joules}$       d)  $10^5 \text{ joules}$
- 117 A battery of 6 volts is connected to the terminals of a three metre long wire of uniform thickness and
2. resistance of the order of  $100\Omega$ . The difference of potential between two points separated by 50 cm on the wire will be  
a) 1 V      b) 1.5 V      c) 2 V      d) 3 V
- 117 Two resistances of  $400\Omega$  and  $800\Omega$  are connected in series with 6 volt battery of negligible internal
3. resistance. A voltmeter of resistance  $10,000\Omega$  is used to measure the potential difference across  $400\Omega$ . The error in the measurement of potential difference in volt approximately is  
a) 0.01      b) 0.02      c) 0.03      d) 0.05
- 117 If potential  $V = 100 \pm 0.5 \text{ Volt}$  and current  $I = 10 \pm 0.2 \text{ amp}$  are given to us, then what will be the value
4. of resistance  
a)  $10 \pm 0.7 \text{ ohm}$       b)  $5 \pm 2 \text{ ohm}$       c)  $0.1 \pm 0.2 \text{ ohm}$       d) None of these
- 117 An electric bulb rated for 500 W at 100V is used in a circuit having a 200 V supply. The resistance R that
5. must be put in series with the bulb, so that the bulb drawn 500 W is  
a)  $18\Omega$       b)  $20\Omega$       c)  $40\Omega$       d)  $700\Omega$
- 117 In the diagram shown, the reading of voltmeter is 20 V and that of ammeter is 4 A. The value of R should
6. be (Consider given ammeter and voltmeter are not ideal)



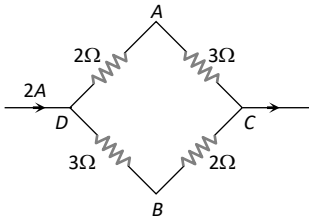- a) Equal to  $5\Omega$       b) Greater than  $5\Omega$   
c) Less than  $5\Omega$       d) Greater or less than  $5\Omega$  depending on the material of R

117 A current of 2 A flows in a system of conductors as shown. The potential difference ( $V_A - V_B$ ) will be



- a) +2V                      b) +1V                      c) -1V                      d) -2V


117 A bulb has specification of one kilowatt and 250 volts, the resistance of bulb is

- a) 125 Ω                      b) 62.5 Ω                      c) 0.25 Ω                      d) 625 Ω

117 The direction of current in an iron-copper thermocouple is

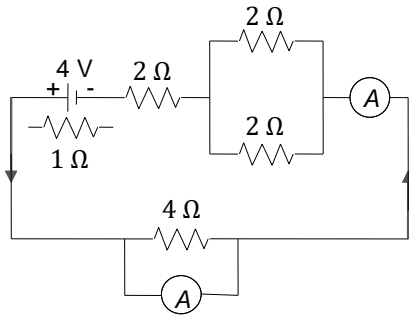
- a) From copper to iron at the hot junction                      b) From iron to copper at the hot junction  
c) From copper to iron at cold junction                      d) No current will flow

118 What is the total resistance of the circuit?



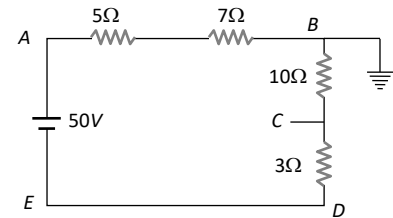
- a) 6 Ω                      b) 7 Ω                      c) 8 Ω                      d) 9 Ω

118 In the circuit shown, the point 'B' is earthed. The potential at the point 'A' is



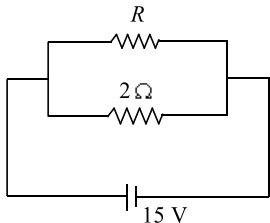
- a) 14 V                      b) 24 V                      c) 26 V                      d) 50 V

118 If in the circuit, power dissipation is 150 W, then R is



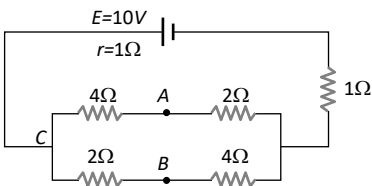- a) 2 Ω                      b) 6 Ω                      c) 5 Ω                      d) 4 Ω

118 In the circuit shown below, the cell has an e.m.f. of 10 V and internal resistance of 1 ohm. The other resistances are shown in the figure. The potential difference  $V_A - V_B$  is




- a) 6 V                      b) 4 V                      c) 2 V                      d) -2 V


118 A Daniel cell is balanced on 125cm length of a potentiometer wire. Now the cell is short-circuited by a

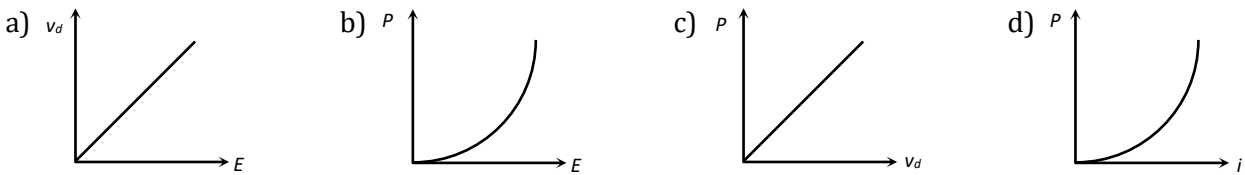4. resistance  $2\ \text{ohm}$  and the balance is obtained at  $100\ \text{cm}$ . The internal resistance of the Daniel cell is  
 a)  $0.5\ \text{ohm}$                       b)  $1.5\ \text{ohm}$                       c)  $1.25\ \text{ohm}$                       d)  $4/5\ \text{ohm}$
- 118 Charge  $Q$  is divided into two parts which are then kept some distance apart. The force between them will  
 5. be maximum if the two parts are having the charge  
 a)  $Q/2$  each                                      b)  $Q/4$  and  $3Q/4$   
 c)  $Q/3$  and  $2Q/3$                                       d)  $e$  and  $(Q - e)$ , where  $e$  = electronic charge
- 118 When  $1\ \text{g}$  hydrogen ( $\text{ECE} = 1.044 \times 10^{-8}\ \text{kg C}^{-1}$ ) forms water,  $34\ \text{kcal}$  heat is liberated. The minimum  
 6. voltage required to decompose water is  
 a)  $0.75\ \text{V}$                                       b)  $3\ \text{V}$                                       c)  $1.5\ \text{V}$                                       d)  $4.5\ \text{V}$


118  $E$  denotes electric field in a uniform conductor,  $I$  corresponding current through it,  $v_d$  drift velocity of  
 7. electrons and  $P$  denotes thermal power produced in the conductor, then which of the following graph is incorrect



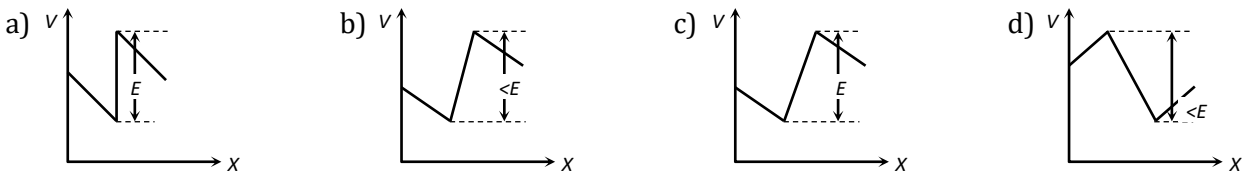118 The two ends of a uniform conductor are joined to a cell of e.m.f.  $E$  and some internal resistance. Starting  
 8. from the midpoint  $P$  of the conductor, we move in the direction of current and return to  $P$ . The potential  $V$  at every point on the path is plotted against the distance covered ( $x$ ). Which of the following graphs best represents the resulting curve




118 Three wires of copper, iron and nickel are joined to form three junctions as shown in Fig. When the  
 9. temperature of junction 1 is kept  $50^\circ\text{C}$  with the other two junctions at  $0^\circ\text{C}$ , the sensitive galvanometer gives a deflection of 14 divisions. When the temperature of junction 3 is kept  $50^\circ\text{C}$ , with the other two junctions at  $0^\circ\text{C}$ , the galvanometer gives a deflection of 11 divisions. Then the deflection given by the galvanometer, when temperature of the junction 2 is kept at  $50^\circ\text{C}$ , with the other two junctions at  $0^\circ\text{C}$ , will be

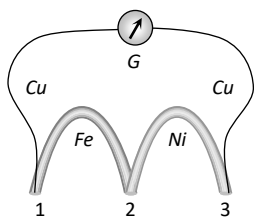

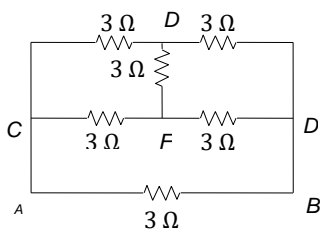- a) 3 div                                      b) 11 div                                      c) 14 div                                      d) 25 div

119 Six resistors, each of value  $3\ \Omega$  are connected as shown in the figure. A cell of emf  $3\text{V}$  is connected across  
 0.  $AB$ . The effective resistance across  $AB$  and the current through the arm  $AB$  will be




- a)  $0.6\ \Omega, 1\ \text{A}$                                       b)  $1.5\ \Omega, 2\ \text{A}$                                       c)  $0.6\ \Omega, 2\ \text{A}$                                       d)  $1.5\ \Omega, 1\ \text{A}$

119 In Seebeck series  $Sb$  appears before  $Bi$ . In a  $Sb - Bi$  thermocouple current flows from  
 1.

- a)  $Sb$  to  $Bi$  at the hot junction  
 c)  $Bi$  to  $Sb$  at the cold junction

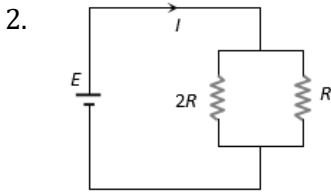- b)  $Sb$  to  $Bi$  at the cold junction  
 d) None of the above

119 What is the ratio of heat generated in  $R$  and  $2R$




- a) 2 :1                                      b) 1 :2                                      c) 4 :1                                      d) 1 :4

119 Which of the following statement is correct

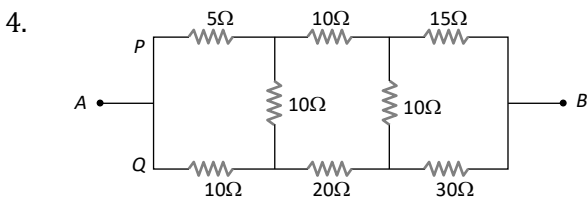- 3.
- a) Electric field is zero on the surface of current carrying wire  
 b) Electric field is non-zero on the axis of hollow current carrying wire  
 c) Surface integral of magnetic field for any closed surface is equal to  $\mu_0$  times of total algebraic sum of current which are crossing through the closed surface  
 d) None

119 In the arrangement of resistance shown below, the effective resistance between points  $A$  and  $B$  is



- a) 20  $\Omega$                                       b) 30  $\Omega$                                       c) 90  $\Omega$                                       d) 110  $\Omega$

119 If 10 A deposits 10.8 g of silver in 25 min, how much copper would deposit when 9 A current flows for 20 min.?

- 5.
- a) 3.81 g                                      b) 6.35 g                                      c) 10.1 g                                      d) 12.7 g

119 The relation between Faraday constant ( $F$ ), chemical equivalent ( $E$ ) and electrochemical equivalent ( $Z$ ) is

- 6.
- a)  $F = EZ$                                       b)  $F = \frac{Z}{E}$                                       c)  $F = \frac{E}{Z}$                                       d)  $F = \frac{E}{Z^2}$

119 Two resistances are joined in parallel whose resistance is  $\frac{3}{5}\Omega$ . One of the resistance wire is broken and the effective resistance become  $3\Omega$ . The resistance in ohm of the wire that got broken was

- 7.
- a)  $\frac{4}{3}$                                       b) 2                                      c)  $\frac{6}{5}$                                       d)  $\frac{3}{4}$

119 A moving coil galvanometer has a resistance of  $10\Omega$  and full scale deflection of  $0.01A$ . It can be converted into voltmeter of  $10V$  full scale by connecting into resistance of

- 8.
- a)  $9.90\Omega$  is series                                      b)  $10\Omega$  in series                                      c)  $990\Omega$  in series                                      d)  $0.10\Omega$  in series

119 If a high power heater is connected to electric mains, then the bulbs in the house become dim, because there is a

- 9.
- a) Current drop                                      b) Potential drop                                      c) No current drop                                      d) No potential drop

120 A  $10\text{ m}$  long wire of  $20\Omega$  resistance is connected with a battery of  $3\text{ volt}$  e.m.f. (negligible internal resistance) and a  $10\Omega$  resistance is joined to it is series. Potential gradient along wire in volt per meter is

- 0.
- a) 0.02                                      b) 0.3                                      c) 0.2                                      d) 1.3

120 A certain charge liberates  $0.8\text{ gm}$  of  $O_2$ . The same charge will liberate how many  $\text{gm}$  of silver

- 1.
- a)  $108\text{ gm}$                                       b)  $10.8\text{ gm}$                                       c)  $0.8\text{ gm}$                                       d)  $\frac{108}{0.8}\text{ gm}$

120 A student measures the terminal potential difference ( $V$ ) of a cell (of  $\text{emf } E$  and internal resistance  $r$ ) as a function of the current ( $I$ ) flowing through it. The slope, and intercept, of the graph between  $V$  and  $I$ , then, respectively, equal


- 2.
- a)  $E$  and  $-r$                                       b)  $-r$  and  $E$                                       c)  $r$  and  $-E$                                       d)  $-E$  and  $r$

120 The charge on the capacitor of capacitance  $C$  shown in the figure below will be





0.

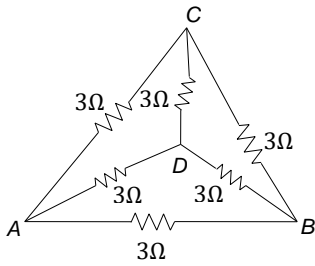

- a)  $3\Omega$                       b)  $6\Omega$                       c)  $12\Omega$                       d)  $1.5\Omega$

122 The material of fuse wire should have

1.

- a) A high specific resistance and high melting point  
 b) A low specific resistance and low melting point  
 c) A high specific resistance and low melting point  
 d) A low specific resistance and a high melting point

122 Resistance of a voltmeter is  $2\Omega$ , it is connected in series to a battery of  $10\text{ V}$  through a resistance of  $3\Omega$ . In

2. a certain time mass deposited on cathode is  $1\text{ g}$ . Now the voltmeter and the  $3\Omega$  resistance are connected in parallel with the battery. Increase in the deposited mass on cathode in the same time will be

- a) 0                      b)  $1.5\text{ g}$                       c)  $2.5\text{ g}$                       d)  $2\text{ g}$

122 The length of a wire of a potentiometer is  $100\text{ cm}$ , and the emf of its stand and cell is  $E$  volt. It is employed

3. to measure the emf of a battery whose internal resistance is  $0.5\Omega$ . If the balance point is obtained at  $l = 30\text{ cm}$  from the positive end, the emf of the battery is

- a)  $\frac{30E}{100.5}$                       b)  $\frac{30E}{100 - 0.5}$   
 c)  $\frac{30(E - 0.5i)}{100}$ , Where  $i$  is the current in the potentiometer wire.                      d)  $\frac{30E}{100}$

122 Resistance of tungsten wire at  $150^\circ\text{C}$  is  $133\Omega$ . Its resistance temperature coefficient is  $0.0045/^\circ\text{C}$ . The





4. resistance of this wire at  $500^\circ\text{C}$  will be

- a)  $180\Omega$                       b)  $225\Omega$                       c)  $258\Omega$                       d)  $317\Omega$

122 Resistors of resistance  $20\Omega$  and  $30\Omega$  are joined in series with a battery of emf  $3\text{ V}$ . It is desired to measure





5. current and voltage across the  $20\Omega$  resistor with the help of an ammeter and voltmeter. Identify the correct arrangement of ammeter ( $A$ ) and voltmeter ( $V$ ) out of four possible arrangements shown in figure.

Given below

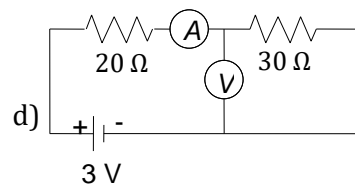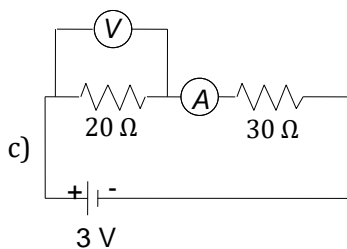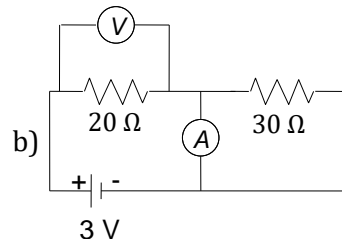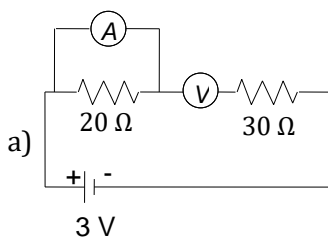

122 Which arrangement of four identical resistance should be used to draw maximum energy from a cell of voltage  $V$

6.

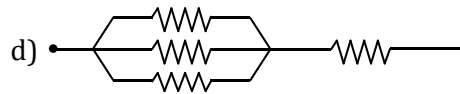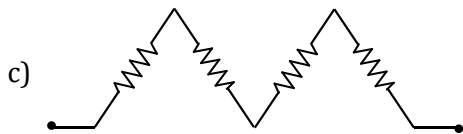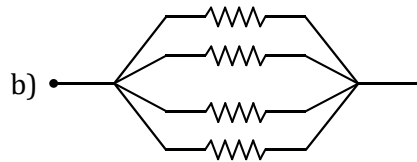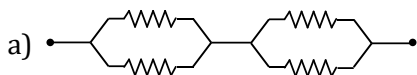

122 A capacitor is connected to a cell of emf  $E$  having some internal resistance  $r$ . The potential difference across the

- a) Cell is  $< E$                       b) Cell is  $E$                       c) Capacitor is  $> E$                       d) Capacitor is  $< E$

122 A wire of resistance 5.5 ohm is drawn out uniformly so that its length is increased twice. Then its new resistance is

- a) 44Ω                      b) 42Ω                      c) 40Ω                      d) 22Ω

122 Silver and copper voltameters are connected in parallel with a battery of emf 12 V. In 30 min 1 g of silver and 1.8 g of copper are liberated. The energy supplied by the battery is

- a) 720 J                      b) 2.41 J                      c) 24.12 J                      d)  $4.34 \times 10^4$  J


123 Two bulbs of 250 V and 100 W are first connected in series and then in parallel with a supply of 250 V. Total power in each of the case will be respectively

- a) 100 W, 50 W                      b) 50 W, 100 W                      c) 200 W, 150 W                      d) 50 W, 200 W

123 An ammeter gives full scale deflection when a current of 2A flows through it. The resistance of ammeter is 12 Ω. If the same ammeter is to be used for measuring a maximum current of 5A, then ammeter must be connected with a resistance of

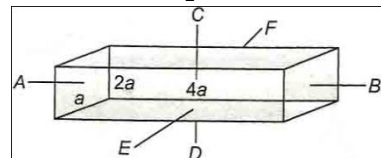- a) 18 Ω in parallel                      b) 8 Ω in parallel                      c) 18 Ω in series                      d) 8 Ω in series

123 A conductor with rectangular cross-section has dimensions ( $a \times 2a \times 4a$ ) as shown in figure. Resistance across  $AB$  is  $R_1$ , across  $CD$  is  $R_2$  and across  $EF$  is  $R_3$ . Then



- a)  $R_1 = R_2 = R_3$                       b)  $R_1 > R_2 > R_3$                       c)  $R_2 > R_3 > R_1$                       d)  $R_1 > R_3 > R_2$


123 The current flowing in a coil of resistance 90 Ω is to be reduced by 90%. What value of resistance should be connected in parallel with it

- a) 9 Ω                      b) 90 Ω                      c) 1000 Ω                      d) 10 Ω

123 In the absence of applied potential, the electric current flowing through a metallic wire is zero because

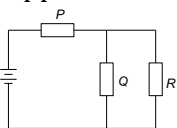- a) The electrons remain stationary  
 b) The electrons are drifted in random direction with a speed of the order of  $10^{-2}$  cm s $^{-1}$   
 c) The electrons move in random direction with a speed of the order close to that of velocity of light  
 d) Electrons and ions move in opposite direction

123 The resistors  $P, Q$  and  $R$  in the circuit have equal resistance. The battery, of negligible internal resistance, supplies a total power of 12 W. What is the power dissipated by heating in resistor  $R$ ?



- a) 2 W                      b) 4 W                      c) 3 W                      d) 6 W

123 The temperature coefficient of resistance of a wire is  $0.00125$  K $^{-1}$ . At 300K, its resistance is 1Ω. The resistance of the wire will be 2Ω at

- a) 1154 K                      b) 1100 K                      c) 1400 K                      d) 1127 K

123 The resistance of a heater coil is 110 ohm. A resistance  $R$  is connected in parallel with it and the






0. wiring circuit
- They have equal currents through them
  - The resistance of the filaments in both the bulbs is same
  - The resistance of the filament in 40 watt bulb is more than the resistance in 100 watt bulb
  - The resistance of the filament in 100 watt bulb is more than the resistance in 40 watt bulb

125 In which of the following substances does resistance decrease with increase in temperature?

- 1.
- Copper
  - Carbon
  - Constantan
  - Silver

125 Thirteen resistances each of resistance  $R\Omega$  are connected in the circuit as shown in the figure. The effective

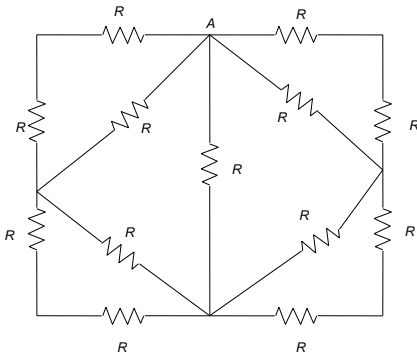2. resistance between points  $A$  and  $B$  is



- $\frac{4R}{3}\Omega$
- $2R\Omega$
- $R\Omega$
- $\frac{2}{3}R\Omega$

125 The resistance of a 10 m long wire is  $10\Omega$ . Its length is increased by 25% by stretching the wire uniformly.

3. The resistance of wire will change to (approximately)

- $12.5\Omega$
- $14.5\Omega$
- $15.6\Omega$
- $16.6\Omega$

125 The masses of the three wires of copper are in the ratio  $5 : 3 : 1$  and their lengths are in the ratio  $1 : 3 : 5$

4. the ratio of their electrical resistance is

- $5 : 3 : 1$
- $\sqrt{125} : 15 : 1$
- $1 : 15 : 125$
- $1 : 3 : 5$


125 A milliammeter of range  $0-30\text{mA}$  has internal resistance of  $20\Omega$ . The resistance to be connected in series

5. to convert it into a voltmeter of maximum reading  $3\text{V}$  is

- $49\Omega$
- $80\Omega$
- $40\Omega$
- $30\Omega$

125 Given figure shows a rectangular block with dimensions  $x$ ,  $2x$  and  $4x$ . Electrical contacts can be made to

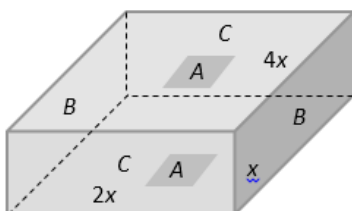
6. the block between opposite pairs of faces (for example, between the faces labelled  $A - A$ ,  $B - B$  and  $C - C$ ). Between which two faces would the maximum electrical resistance be obtained ( $A - A$  : Top and bottom faces,  $B - B$  : Left and right faces,  $C - C$  : Front and rear faces)



- $A - A$
- $B - B$
- $C - C$
- Same for all three pairs


125 Resistance as shown in figure is negative at

7.

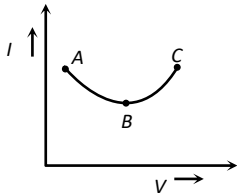

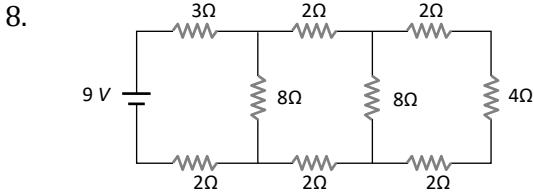- a) A    b) B    c) C    d) None of these

125 In the circuit shown in the figure, the current through



- a) The 3Ω resistor is 0.50 A    b) The 3Ω resistor is 0.25 A  
 c) The 4Ω resistor is 0.50 A    d) The 4Ω resistor is 0.25 A

125 The potential gradient along the length of a uniform wire is 10 volt/metre. B and C are the two points at 9.

- 30 cm and 60 cm point on a meter scale fitted along the wire. The potential difference between B and C will be  
 a) 3 volt    b) 0.4 volt    c) 7 volt    d) 4 volt

126 Current is flowing with a current density  $J = 480 \text{ A cm}^{-2}$  in a copper wire. Assuming that each copper atom 0.

- contributes one free electron and given that  
 Avogadro number =  $6.0 \times 10^{23} \text{ atoms mol}^{-1}$   
 Density of copper =  $9.0 \text{ g cm}^{-3}$   
 Atomic weight of copper =  $64 \text{ g mol}^{-1}$   
 The drift velocity of electrons is

- a) 1 mm s<sup>-1</sup>    b) 2 mm s<sup>-1</sup>    c) 0.5 mm s<sup>-1</sup>    d) 0.36 mm s<sup>-1</sup>

126 Two wires of the same material but of different diameters carry the same current  $i$ . If ratio of their 1.

- diameters is 1:2, then the corresponding ratio of their mean drift velocities will be  
 a) 4:1    b) 1:1    c) 1:2    d) 1:4

126 How much work is required to carry a  $6 \mu\text{C}$  charge from the negative terminal to the positive terminal of a 2.

- 9 V battery  
 a)  $54 \times 10^{-3} \text{ J}$     b)  $54 \times 10^{-6} \text{ J}$     c)  $54 \times 10^{-9} \text{ J}$     d)  $54 \times 10^{-12} \text{ J}$


126 An electric bulb rated 220 V, 100 W is connected in series with another bulb rated 220 V, 60 W. If the 3.

- voltage across the combination is 220 V, the power consumed by the 100 W bulb will be about  
 a) 25 W    b) 14 W    c) 60 W    d) 100 W

126 When a current of 1 ampere is passed through a conductor whose ends are maintained at temperature 4.

- difference of 1°C, the amount of heat evolved or absorbed is called  
 a) Peltier coefficient    b) Thomson coefficient  
 c) Thermoelectric power    d) Thermo e.m.f.

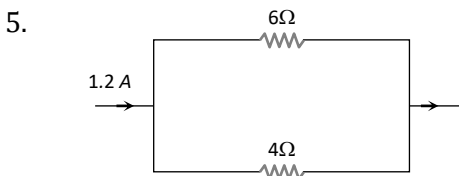126 In the figure given below, the current passing through 6Ω resistor is



- a) 0.40 ampere    b) 0.48 ampere    c) 0.72 ampere    d) 0.80 ampere

126 For a given temperature difference which of the following pairs will generate maximum thermo-emf? 6.

- a) Lead-nickel    b) Copper-iron    c) Gold-silver    d) Antimony-bismuth

126 The resistance of ideal voltmeter is

7.

- a) Zero  
c) Infinite
- b) Greater than zero but finite value  
d)  $5000 \Omega$

126 A 100 watt bulb working on 200 volt and a 200 watt bulb working on 100 volt have 8.

- a) Resistances in the ratio of 4 : 1  
b) Maximum current ratings in the ratio of 1 : 4  
c) Resistances in the ratio of 2 : 1  
d) Maximum current ratings in the ratio of 1 : 2

126 The graph between resistivity and temperature, for a limited range of temperatures, is a straight line for a 9. material like

- a) Copper  
b) Nichrome  
c) Silicon  
d) Mercury

127 The emf of a generator is 6 V and internal resistance is  $0.5 \text{ k}\Omega$ . The reading of a voltmeter having an 0. internal resistance of  $2.5 \text{ k}\Omega$  is

- a)  $10^{-3} \text{ V}$   
b) 10 V  
c) 5 V  
d) 0.5 V

127 A metallic block has no potential difference applied across it, then the mean velocity of free electrons at 1. absolute temperature  $T$  is

- a) Proportional to  $T$   
b) Proportional to  $\sqrt{T}$   
c) Zero  
d) Finite but independent of  $T$


127 An ammeter reads 0.90 A when connected in series with a silver voltmeter that deposits 2.60 g of silver in 2. 40 min. By what percentage is the ammeter reading is correct? Atomic weight of silver = 108 and  $1 \text{ F} = 96500 \text{ C}$ ?

- a) 5%  
b) 7%  
c) -5%  
d) -7%

127 A thermo-emf  $V$  appears across a conductor maintained at a temperature difference  $T$ . The thomson 3. coefficient is then given by

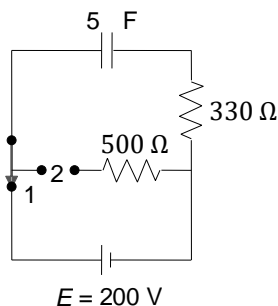
- a)  $-T^2 \frac{d^2V}{dT^2}$   
b)  $T^2 \frac{dV}{dT}$   
c)  $-T \frac{d^2V}{dT^2}$   
d)  $-\frac{1}{T^2} \frac{dV}{dT}$

127 The amount of heat generated in  $500 \Omega$  resistance, when the key is thrown over from contact 1 to 2, as 4. shown in figure is



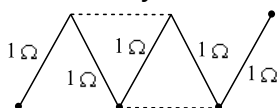
- a)  $10^\circ \text{C}$   
b)  $7.5^\circ \text{C}$   
c)  $5.0^\circ \text{C}$   
d)  $2.5^\circ \text{C}$

127 A circuit consists of five identical conductors as shown in figure. The two similar conductors are added as 5. indicated by the dotted lines. The ratio of resistances before and after addition will be



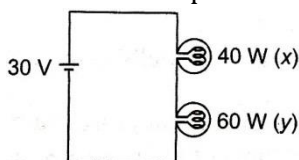- a)  $7/5$   
b)  $3/5$   
c)  $5/3$   
d)  $6/5$


127 Two bulbs X and Y having same voltage rating and of power 40 W and 60 W respectively are connected in 6. series across a potential difference of 300 V, then



- a) X will glow brighter  
b) Resistance of Y will be greater than X

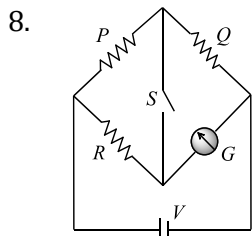- c) Heat produced in  $Y$  will be greater than  $X$                       d) Voltage drop in  $X$  will be greater than  $Y$
- 127 Two voltmeters, one of copper and another of silver, are joined in parallel. When a total charge  $q$  flows through the voltmeters, equal amount of metals are deposited. If the electrochemical equivalents of copper and silver are  $z_1$  and  $z_2$  respectively, the charge which flows through the silver voltmeter is
7. a)  $\frac{q}{1 + \frac{z_1}{z_2}}$                       b)  $\frac{q}{1 + \frac{z_2}{z_1}}$                       c)  $q \frac{z_1}{z_2}$                       d)  $q \frac{z_2}{z_1}$

127 In the circuit shown  $P \neq R$ , the reading of the galvanometer is same with switch  $S$  open or closed. Then



- a)  $I_R = I_G$                       b)  $I_P = I_G$                       c)  $I_Q = I_G$                       d)  $I_Q = I_R$
- 127 The density of copper is  $9 \times 10^3 \text{ kg/m}^3$  and its atomic mass is 63.5 u. Each copper atom provides one free electron. Estimate the number of free electrons per cubic metre in copper.
9. a)  $10^{19}$                       b)  $10^{23}$                       c)  $10^{25}$                       d)  $10^{29}$

128 Find the true statements

- 0.
- a) Ohm's law is applicable to all conductors of electricity  
 b) In an electrolyte solution, the electric current is mainly due to the movement of electrons  
 c) The resistance of an incandescent lamp is lesser when the lamp is switched on  
 d) Specific resistance of a wire depends upon its dimension

128 A galvanometer can be converted into a voltmeter by connecting

- 1.
- a) Low resistance in parallel                      b) Low resistance in series  
 c) High resistance in parallel                      d) High resistance in series

128 By mistake a voltmeter is connected in series and an ammeter is connected in parallel with a resistance in an electrical circuit. What will happen to the instrument?

- 2.
- a) Voltmeter is damaged                      b) Ammeter is damaged  
 c) Both are damaged                      d) None is damaged

128 In a thermocouple, the neutral temperature is  $270^\circ\text{C}$  and the temperature of inversion is

3.  $525^\circ\text{C}$ . The temperature of cold junction would be
- a)  $30^\circ\text{C}$                       b)  $255^\circ\text{C}$                       c)  $15^\circ\text{C}$                       d)  $25^\circ\text{C}$

128 Two electric lamps of 40 watt each are connected in parallel. The power consumed by the combination


4. will be
- a) 20 watt                      b) 60 watt                      c) 80 watt                      d) 100 watt

128 Consider the following two statements  $A$  and  $B$ , and identify the correct choice out of given answers

5. A. Thermo e.m.f. is minimum at neutral temperature of a thermocouple  
 B. When two junctions made of two different metallic wires are maintained at different temperatures, an electric current is generated in the circuit
- a)  $A$  is false and  $B$  is true                      b)  $A$  is true and  $B$  is false  
 c) Both  $A$  and  $B$  are false                      d) Both  $A$  and  $B$  are true


128 Variation of current passing through a conductor as the voltage applied across its ends is varied as shown

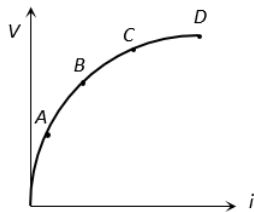6. in the adjoining diagram. If the resistance ( $R$ ) is determined at the points  $A, B, C$  and  $D$ , we will find that



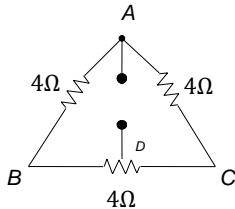- a)  $R_C = R_D$                       b)  $R_B > R_A$                       c)  $R_C > R_B$                       d) None of these

128 There resistances of  $4\ \Omega$  each are connected as shown in figure. If the point  $D$  divides the resistance into two equal halves, the resistance between points  $A$  and  $D$  will be



- a)  $12\ \Omega$                       b)  $6\ \Omega$                       c)  $3\ \Omega$                       d)  $\frac{1}{3}\ \Omega$

128 A copper wire of cross-sectional area  $2.0\ \text{mm}^2$ , resistivity  $=1.7 \times 10^{-8}\ \Omega\text{m}$ , carries a current of  $1\text{A}$ . The electric field in the copper wire is

- a)  $8.5 \times 10^{-5}\ \text{Vm}^{-1}$                       b)  $8.5 \times 10^{-4}\ \text{Vm}^{-1}$                       c)  $8.5 \times 10^{-3}\ \text{Vm}^{-1}$                       d)  $8.5 \times 10^{-2}\ \text{Vm}^{-1}$

128 The thermo-emf of a thermocouple varies with the temperature  $\theta$  of the hot junction as  $E = a\theta + b\theta^2$  in

9. volts where the ratio  $a/b$  is  $700^\circ\text{C}$ . If the cold junction is kept at  $0^\circ\text{C}$ , then the neutral temperature is  
 a)  $700^\circ\text{C}$ .                      b)  $350^\circ\text{C}$ .  
 c)  $1400^\circ\text{C}$ .                      d) No neutral temperature is possible for this thermocouple


129  $2, 4$  and  $6\ \text{S}$  are the conductance of three conductors. When they are joined in parallel, their equivalent conductance will be

- a)  $12\ \text{S}$                       b)  $(1/12)\ \text{S}$                       c)  $(12/11)\ \text{S}$                       d)  $(11/12)\ \text{S}$

129 Two resistances are connected in two gaps of a meter bridge. The balance point is  $20\text{cm}$  from the zero end.

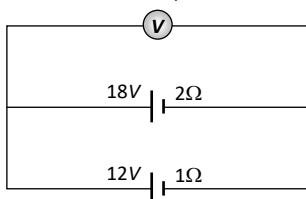1. A resistance of  $15\ \Omega$  is connected in series with the smaller of the two. The null point shifts to  $40\text{cm}$ . The value of the smaller resistance in ohm is  
 a)  $3$                       b)  $6$                       c)  $9$                       d)  $12$

129 Two batteries, one of emf  $18\ \text{volt}$  and internal resistance  $2\ \Omega$  and the other of emf  $12\ \text{volt}$  and internal resistance  $1\ \Omega$ , are connected as shown. The voltmeter  $V$  will record a reading of



- a)  $15\ \text{volt}$                       b)  $30\ \text{volt}$                       c)  $14\ \text{volt}$                       d)  $18\ \text{volt}$

129 The drift velocity does not depend upon

3. a) Cross-section of the wire                      b) Length of the wire  
 c) Number of free electrons                      d) Magnitude of the current

129 The emf of a thermocouple, one junction of which is kept at  $0^\circ\text{C}$ , is given by  $e = at + bt^2$ . The Peltier coefficient will be

4. a)  $(t + 273)(a + 2bt)$                       b)  $(t + 273)(a - 2bt)$                       c)  $(t - 273)(a - 2bt)$                       d)  $(t - 273)(a + 2bt)$

129 For electroplating a spoon, it is placed in the voltmeter at


5. a) The position of anode  
 b) The position of cathode

- c) Exactly in the middle of anode and the cathode  
 d) Anywhere in the electrolyte

129 Two resistors of  $6\ \Omega$  and  $9\ \Omega$  are connected in series to a  $120\ \text{volt}$  source. The power consumed by the  $6\ \Omega$  resistor is

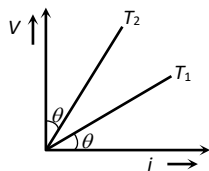- a)  $384\ \text{W}$                       b)  $576\ \text{W}$                       c)  $1500\ \text{W}$                       d)  $1200\ \text{W}$

129 The  $V - i$  graph for a conductor at temperatures  $T_1$  and  $T_2$  are as shown in the figure.  $(T_2 - T_1)$  is proportional to




- a)  $\cos 2\theta$                       b)  $\sin \theta$                       c)  $\cot 2\theta$                       d)  $\tan \theta$

129 For a thermocouple, the inversion temperature is  $600^\circ\text{C}$  and the neutral temperature is  $320^\circ\text{C}$ . Find the temperature of the cold junction?

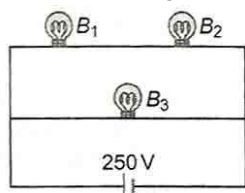- a)  $40^\circ\text{C}$                       b)  $20^\circ\text{C}$                       c)  $80^\circ\text{C}$                       d)  $60^\circ\text{C}$

129 A  $100\ \text{W}$  bulb  $B_1$  and two  $60\ \text{W}$  bulbs  $B_2$  and  $B_3$  are connected to a  $250\ \text{V}$  source as shown in figure. Now  $W_1, W_2$  and  $W_3$  are the output powers of the bulbs  $B_1, B_2$  and  $B_3$  respectively, then



- a)  $W_1 > W_2 = W_3$                       b)  $W_1 > W_2 > W_3$                       c)  $W_1 < W_2 = W_3$                       d)  $W_1 < W_2 < W_3$

130 A resistor is constructed as hollow cylinder of dimensions  $r_a = 0.5\ \text{cm}$  and  $r_b = 1.0\ \text{cm}$  and  $\rho = 3.5 \times 10^{-5}\ \Omega\text{m}$ . The resistance of the configuration for the length of  $5\ \text{cm}$  cylinder is  $\dots \times 10^{-3}\ \Omega$ .

- a) 7.42                      b) 10.56                      c) 14.38                      d) 16.48

130 The  $V - i$  graph for a conductor makes an angle  $\theta$  with  $V$ -axis. Here  $V$  denotes the voltage and  $i$  denotes current. The resistance of conductor is given by

- a)  $\sin \theta$                       b)  $\cos \theta$                       c)  $\tan \theta$                       d)  $\cot \theta$

130 If a wire is stretched to make it  $0.1\%$  longer, its resistance will

- a) Increase by  $0.2\%$                       b) Decrease by  $0.2\%$                       c) Decrease  $0.05\%$                       d) Increase by  $0.05\%$

130 Two filaments of same length are connected first in series and then in parallel. For the same amount of main current flowing the ratio of the heat produced is

- a)  $2 : 1$                       b)  $1 : 2$                       c)  $4 : 1$                       d)  $1 : 4$

130 Water boils in an electric kettle in  $15\ \text{minutes}$  after switching on. If the length of the heating wire is decreased to  $2/3$  of its initial value, then the same amount of water will boil with the same supply voltage in

- a)  $15\ \text{minutes}$                       b)  $12\ \text{minutes}$                       c)  $10\ \text{minutes}$                       d)  $8\ \text{minutes}$


130 Antimony and bismuth are usually used in a thermocouple, because



- a) Negative thermal  $e.m.f.$  is produced                      b) Constant thermal  $e.m.f.$  is produced  
 c) Lower thermal  $e.m.f.$  is produced                      d) Higher thermal  $e.m.f.$  is produced

130 Specific resistance of copper, constantan and silver are  $1.78 \times 10^{-8}$ ,  $39.1 \times 10^{-8}$  and  $10^{-8}\ \Omega\text{-m}$  respectively. Which of these is the best conductor of heat and electricity?

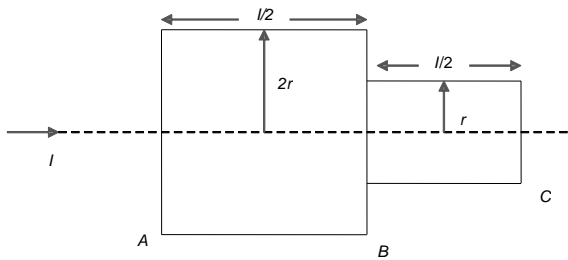- a) Copper                      b) Constantan                      c) Silver                      d) All of them


130 Two bars of radius  $r$  and  $2r$  are kept in contact as shown. An electric current  $I$  is passed through the bars. Which one of following is correct?



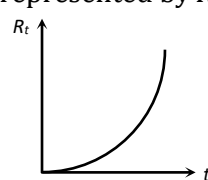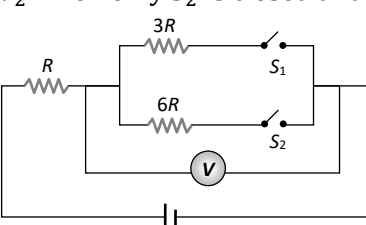
- a) Heat produced in bar  $BC$  is 4 times the heat produced in bar  $AB$
- b) Electric field in both halves is equal
- c) Current density across  $AB$  is double that of across  $BC$
- d) Potential difference across  $AB$  is 4 times that of across  $BC$
- 130 In producing chlorine through electrolysis 100 watt power at 125 V is being consumed. How much chlorine per minute is liberated? E.C.E. chlorine is  $0.367 \times 10^{-6} \text{ kg/coulomb}$
8. a) 24.3 mg                      b) 16.6 mg                      c) 17.6 mg                      d) 21.3 mg
- 130 The amount of heat produced in a resistor when a current is passed through it can be found using
9. a) Faraday's Law                      b) Kirchoff's Law                      c) Laplace's Law                      d) Joule's Law
- 131 A beam contains  $2 \times 10^8$  doubly charged positive ions per cubic centimeter, all of which are moving with a speed of  $10^5 \text{ m/s}$ . The current density is
0. a)  $6.4 \text{ A/m}^2$                       b)  $3.2 \text{ A/m}^2$                       c)  $1.6 \text{ A/m}^2$                       d) None of these
- 131 Three equal resistors connected in series across a source of e.m.f. together dissipate 10 watt. If the same resistors are connected in parallel across the same e.m.f., then the power dissipated will be
1. a) 10 watt                      b) 30 watt                      c)  $10/3$  watt                      d) 90 watt
- 131 When a current passes through a wire whose different parts are maintained at different temperatures, evolution or absorption of heat all along the length of wire is known as
2. a) Joule effect                      b) Seebeck effect                      c) Peltier effect                      d) Thomson effect
- 131 To get the maximum current from a parallel combination of  $n$  identical cells each of internal resistance  $r$  and external resistance  $R$ , when
3. a)  $R \gg r$                       b)  $R \ll r$                       c)  $R = r$                       d) None of these
- 131 Which of the following is vector quantity
4. a) Current density                      b) Current                      c) Wattless current                      d) Power
- 131 The resistance  $R_t$  of a conductor varies with temperature  $t$  as shown in the figure. If the variation is represented by  $R_t = R_0[1 + \alpha t + \beta t^2]$ , then
5. 
- a)  $\alpha$  and  $\beta$  are both negative                      b)  $\alpha$  and  $\beta$  are both positive
- c)  $\alpha$  is positive and  $\beta$  is negative                      d)  $\alpha$  is negative and  $\beta$  are positive
- 131 In the circuit shown in the figure reading of voltmeter is  $V_1$  when only  $S_1$  is closed, reading of voltmeter is  $V_2$  when only  $S_2$  is closed and reading of voltmeter is  $V_3$  when both  $S_1$  and  $S_2$  are closed. Then
6. 
- a)  $V_3 > V_2 > V_1$                       b)  $V_2 > V_1 > V_3$                       c)  $V_3 > V_1 > V_2$                       d)  $V_1 > V_2 > V_3$
- 131 Two batteries of e.m.f. 4 V and 8 V with internal resistances 1  $\Omega$  and 2  $\Omega$  are connected in a circuit with a



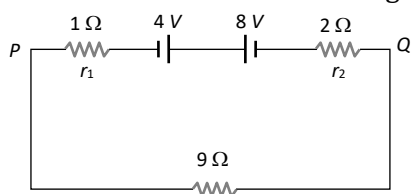7. resistance of  $9\ \Omega$  as shown in figure. The current and potential difference between the points  $P$  and  $Q$  are



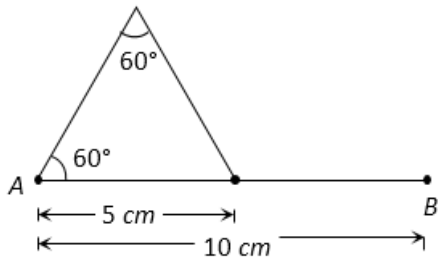- a)  $\frac{1}{3}\text{ A}$  and  $3\text{ V}$       b)  $\frac{1}{6}\text{ A}$  and  $4\text{ V}$       c)  $\frac{1}{9}\text{ A}$  and  $9\text{ V}$       d)  $\frac{1}{2}\text{ A}$  and  $12\text{ V}$
- 131 Assume that each atom of copper contributes one free electron. What is the average drift velocity of conduction electrons in a copper wire of cross-sectional area  $10^{-7}\text{ m}^2$ , carrying a current of  $1.5\text{ A}$ ? (Given density of copper  $=9 \times 10^{-3}\text{ kgm}^{-3}$ ; atomic mass of copper  $=63.5$ ; Avogadro's number  $=6.023 \times 10^{23}$  per gram atom)
- a)  $1.1 \times 10^{-2}\text{ ms}^{-1}$       b)  $1.1 \times 10^{-3}\text{ ms}^{-1}$       c)  $2.2 \times 10^{-2}\text{ ms}^{-1}$       d)  $2.2 \times 10^{-3}\text{ ms}^{-1}$
- 131 The internal resistance of a primary cell is  $4\ \Omega$ . It generates a current of  $0.2\text{ A}$  in an external resistance of  $21\ \Omega$ . The rate at which chemical energy is consumed in providing the current is
- a)  $0.42\text{ J s}^{-1}$       b)  $0.84\text{ J s}^{-1}$       c)  $1\text{ J s}^{-1}$       d)  $5\text{ J s}^{-1}$
- 132 The current in the primary circuit of a potentiometer is  $0.2\text{ A}$ . the specific resistance and cross-section of the potentiometer wire are  $4 \times 10^{-7}\ \Omega\text{ m}$  and  $8 \times 10^{-7}\text{ m}^2$  respectively. Potential gradient will be equal to
- a)  $0.2\text{ V/m}$       b)  $1\text{ V/m}$       c)  $0.3\text{ V/m}$       d)  $0.1\text{ V/m}$
- 132 A cell of e. m. f.  $E$  connected with an external resistance  $R$ , then p.d. across cell is  $V$ . The internal resistance of cell will be
- a)  $\frac{(E - V)R}{E}$       b)  $\frac{(E - V)R}{V}$       c)  $\frac{(V - E)R}{V}$       d)  $\frac{(V - E)R}{E}$
- 132 The current flowing in a copper voltmeter is  $1.6\text{ A}$ . The number of  $\text{Cu}^{++}$  ions deposited at the cathode per minute are
- a)  $1.5 \times 10^{20}$       b)  $3 \times 10^{20}$       c)  $6 \times 10^{20}$       d)  $1 \times 10^{19}$
- 132 There are three resistance coils of equal resistance. The maximum number of resistances you can obtain by connecting them in any manner you choose, being free to use any number of the coils in any way is
- a) 3      b) 4      c) 6      d) 5
- 132 A galvanometer of resistance  $22.8\ \Omega$  measures  $1\text{ A}$ . How much shunt should be used, so that it can be used to measure  $20\text{ A}$ ?
- a)  $1\ \Omega$       b)  $2\ \Omega$       c)  $1.2\ \Omega$       d)  $2.2\ \Omega$
- 132 If two electric bulbs have  $40\text{ W}$  and  $60\text{ W}$  rating at  $220\text{ V}$ , then the ratio of their resistances will be
- a) 9 : 4      b) 4 : 3      c) 3 : 8      d) 3 : 2
- 132 The negative Zn pole of Daniell cell, sending a constant current through a circuit, decreases in mass by  $0.13\text{ g}$  in  $30\text{ min}$ . If the electrochemical equivalent of Zn and Cu are  $32.5$  and  $31.5$  respectively, the increase in the mass of the positive Cu pole in this time is
- a)  $0.180\text{ g}$       b)  $0.141\text{ g}$       c)  $0.126\text{ g}$       d)  $0.242\text{ g}$
- 132 A lead-acid battery of a car has an emf of  $12\text{ V}$ . If the internal resistance of the battery is  $0.5\ \Omega$ , the maximum current that can be drawn from the battery will be
- a)  $30\text{ A}$       b)  $20\text{ A}$       c)  $6\text{ A}$       d)  $24\text{ A}$
- 132 When an electrical appliance is switched on, it responds almost immediately, because
- a) The electrons in the connecting wires move with the speed of light  
 b) The electrical signal is carried by electromagnetic waves moving with the speed of light  
 c) The electrons move with speed which is close to but less than speed of light  
 d) The electron are stagnant
- 132 A wire has resistance of  $24\ \Omega$  is bent in the following shape. The effective resistance between  $A$  and  $B$  is



a)  $24 \Omega$

b)  $10 \Omega$

c)  $\frac{16}{3} \Omega$

d) None of these

3.CURRENT ELECTRICITY

**: ANSWER KEY :**

1)	d	2)	b	3)	a	4)	a	189)	d	190)	c	191)	c	192)	a
5)	a	6)	c	7)	b	8)	b	193)	b	194)	d	195)	d	196)	c
9)	b	10)	c	11)	b	12)	c	197)	b	198)	b	199)	c	200)	d
13)	d	14)	b	15)	a	16)	c	201)	c	202)	a	203)	b	204)	a
17)	b	18)	d	19)	a	20)	d	205)	a	206)	c	207)	a	208)	b
21)	a	22)	a	23)	a	24)	c	209)	b	210)	a	211)	b	212)	b
25)	b	26)	a	27)	d	28)	d	213)	c	214)	a	215)	d	216)	a
29)	b	30)	d	31)	a	32)	a	217)	a	218)	b	219)	a	220)	b
33)	a	34)	c	35)	b	36)	a	221)	b	222)	d	223)	b	224)	d
37)	a	38)	d	39)	b	40)	a	225)	c	226)	d	227)	c	228)	a
41)	c	42)	b	43)	d	44)	a	229)	c	230)	b	231)	b	232)	c
45)	c	46)	d	47)	d	48)	a	233)	a	234)	b	235)	c	236)	b
49)	d	50)	c	51)	d	52)	c	237)	d	238)	b	239)	d	240)	a
53)	b	54)	c	55)	b	56)	c	241)	a	242)	c	243)	b	244)	c
57)	d	58)	a	59)	a	60)	b	245)	b	246)	b	247)	b	248)	d
61)	a	62)	d	63)	d	64)	d	249)	b	250)	d	251)	d	252)	d
65)	c	66)	a	67)	c	68)	b	253)	d	254)	d	255)	d	256)	c
69)	b	70)	d	71)	d	72)	d	257)	c	258)	c	259)	d	260)	d
73)	d	74)	c	75)	c	76)	d	261)	c	262)	a	263)	a	264)	d
77)	b	78)	d	79)	a	80)	a	265)	c	266)	a	267)	d	268)	a
81)	a	82)	d	83)	a	84)	c	269)	a	270)	d	271)	c	272)	a
85)	a	86)	c	87)	c	88)	a	273)	d	274)	a	275)	b	276)	c
89)	b	90)	a	91)	c	92)	b	277)	a	278)	a	279)	a	280)	b
93)	a	94)	b	95)	b	96)	a	281)	c	282)	b	283)	c	284)	d
97)	a	98)	b	99)	a	100)	b	285)	a	286)	d	287)	c	288)	c
101)	a	102)	d	103)	a	104)	d	289)	c	290)	d	291)	c	292)	b
105)	d	106)	b	107)	c	108)	b	293)	d	294)	d	295)	b	296)	c
109)	b	110)	a	111)	d	112)	c	297)	b	298)	c	299)	c	300)	a
113)	c	114)	b	115)	d	116)	c	301)	d	302)	a	303)	b	304)	d
117)	c	118)	b	119)	b	120)	b	305)	b	306)	c	307)	b	308)	b
121)	a	122)	d	123)	b	124)	b	309)	a	310)	a	311)	a	312)	c
125)	b	126)	a	127)	a	128)	b	313)	a	314)	a	315)	c	316)	a
129)	b	130)	c	131)	c	132)	c	317)	b	318)	b	319)	b	320)	b
133)	b	134)	d	135)	d	136)	d	321)	a	322)	c	323)	d	324)	a
137)	a	138)	b	139)	b	140)	c	325)	a	326)	a	327)	d	328)	d
141)	b	142)	a	143)	a	144)	b	329)	a	330)	c	331)	a	332)	a
145)	a	146)	d	147)	b	148)	a	333)	b	334)	b	335)	a	336)	c
149)	c	150)	c	151)	c	152)	b	337)	a	338)	d	339)	c	340)	c
153)	a	154)	c	155)	c	156)	c	341)	d	342)	c	343)	b	344)	a
157)	c	158)	b	159)	c	160)	b	345)	a	346)	c	347)	a	348)	b
161)	c	162)	c	163)	b	164)	c	349)	d	350)	c	351)	d	352)	b
165)	d	166)	a	167)	b	168)	a	353)	b	354)	c	355)	d	356)	a
169)	c	170)	c	171)	b	172)	d	357)	b	358)	a	359)	b	360)	c
173)	d	174)	b	175)	c	176)	a	361)	b	362)	c	363)	b	364)	a
177)	c	178)	c	179)	d	180)	b	365)	d	366)	b	367)	c	368)	d
181)	d	182)	b	183)	d	184)	c	369)	c	370)	c	371)	c	372)	a
185)	a	186)	c	187)	b	188)	b	373)	a	374)	b	375)	c	376)	c

377) a	378) a	379) b	380) a	581) c	582) a	583) d	584) c
381) a	382) b	383) b	384) a	585) a	586) c	587) b	588) c
385) c	386) d	387) c	388) c	589) d	590) d	591) a	592) a
389) c	390) a	391) d	392) b	593) b	594) b	595) c	596) c
393) c	394) b	395) d	396) d	597) a	598) b	599) d	600) c
397) b	398) a	399) c	400) c	601) b	602) a	603) a	604) d
401) c	402) a	403) c	404) d	605) d	606) a	607) c	608) d
405) b	406) d	407) c	408) b	609) b	610) a	611) c	612) c
409) c	410) a	411) a	412) a	613) d	614) c	615) d	616) a
413) c	414) c	415) d	416) c	617) d	618) a	619) a	620) a
417) c	418) a	419) c	420) a	621) c	622) b	623) b	624) a
421) a	422) c	423) c	424) d	625) d	626) c	627) b	628) a
425) a	426) c	427) c	428) d	629) b	630) d	631) a	632) b
429) a	430) b	431) c	432) a	633) a	634) c	635) d	636) c
433) d	434) b	435) d	436) b	637) c	638) b	639) a	640) d
437) c	438) d	439) a	440) a	641) a	642) c	643) b	644) d
441) b	442) d	443) d	444) b	645) d	646) b	647) a	648) d
445) b	446) c	447) a	448) d	649) b	650) b	651) c	652) c
449) d	450) b	451) c	452) c	653) b	654) b	655) d	656) b
453) d	454) c	455) c	456) c	657) b	658) c	659) a	660) b
457) a	458) a	459) c	460) c	661) c	662) d	663) a	664) a
461) c	462) d	463) b	464) b	665) a	666) c	667) b	668) b
465) b	466) a	467) b	468) d	669) d	670) b	671) d	672) c
469) a	470) d	471) a	472) c	673) c	674) d	675) a	676) d
473) b	474) c	475) c	476) c	677) a	678) b	679) b	680) b
477) c	478) a	479) a	480) b	681) c	682) b	683) b	684) b
481) d	482) d	483) c	484) d	685) b	686) c	687) b	688) b
485) b	486) c	487) a	488) d	689) c	690) c	691) c	692) c
489) b	490) a	491) c	492) c	693) a	694) a	695) d	696) c
493) c	494) a	495) c	496) a	697) c	698) d	699) b	700) c
497) b	498) c	499) b	500) b	701) a	702) c	703) d	704) c
501) b	502) c	503) c	504) c	705) c	706) d	707) b	708) d
505) c	506) a	507) b	508) a	709) b	710) c	711) c	712) c
509) b	510) d	511) c	512) a	713) b	714) d	715) c	716) b
513) d	514) a	515) a	516) c	717) a	718) a	719) a	720) a
517) d	518) a	519) b	520) c	721) b	722) d	723) a	724) a
521) a	522) c	523) d	524) c	725) a	726) c	727) c	728) c
525) d	526) d	527) c	528) a	729) a	730) a	731) a	732) b
529) b	530) b	531) b	532) c	733) c	734) c	735) d	736) a
533) c	534) c	535) b	536) a	737) a	738) c	739) d	740) c
537) c	538) d	539) d	540) b	741) a	742) b	743) b	744) c
541) b	542) d	543) b	544) c	745) a	746) c	747) c	748) b
545) c	546) d	547) c	548) b	749) c	750) d	751) d	752) b
549) c	550) d	551) c	552) d	753) b	754) b	755) a	756) b
553) a	554) c	555) d	556) d	757) d	758) c	759) d	760) d
557) d	558) a	559) c	560) c	761) b	762) b	763) a	764) a
561) d	562) b	563) d	564) a	765) a	766) d	767) b	768) d
565) d	566) a	567) c	568) b	769) c	770) d	771) d	772) c
569) b	570) c	571) c	572) b	773) b	774) b	775) c	776) c
573) c	574) b	575) b	576) c	777) c	778) a	779) a	780) d
577) d	578) a	579) d	580) a	781) b	782) b	783) d	784) d

785) c	786) b	787) d	788) a	989) b	990) b	991) a	992) c
789) a	790) a	791) b	792) d	993) c	994) c	995) b	996) c
793) d	794) a	795) c	796) a	997) a	998) c	999) a	1000) d
797) b	798) c	799) d	800) d	1001) c	1002) c	1003) a	1004) d
801) d	802) d	803) a	804) b	1005) c	1006) d	1007) a	1008) a
805) c	806) c	807) d	808) d	1009) a	1010) c	1011) d	1012) c
809) a	810) d	811) c	812) d	1013) b	1014) b	1015) b	1016) a
813) c	814) b	815) d	816) a	1017) b	1018) d	1019) c	1020) d
817) c	818) a	819) a	820) a	1021) b	1022) a	1023) b	1024) b
821) c	822) a	823) c	824) a	1025) a	1026) c	1027) c	1028) c
825) b	826) b	827) c	828) b	1029) c	1030) a	1031) a	1032) d
829) d	830) b	831) c	832) a	1033) b	1034) b	1035) c	1036) a
833) b	834) a	835) b	836) a	1037) a	1038) d	1039) b	1040) a
837) d	838) b	839) c	840) a	1041) c	1042) c	1043) c	1044) a
841) a	842) b	843) d	844) a	1045) c	1046) c	1047) c	1048) c
845) c	846) b	847) b	848) d	1049) b	1050) d	1051) b	1052) a
849) d	850) a	851) c	852) b	1053) a	1054) c	1055) d	1056) b
853) c	854) d	855) a	856) a	1057) c	1058) a	1059) c	1060) a
857) b	858) d	859) d	860) d	1061) c	1062) d	1063) d	1064) b
861) a	862) c	863) a	864) a	1065) a	1066) d	1067) b	1068) c
865) b	866) b	867) d	868) a	1069) b	1070) b	1071) a	1072) d
869) b	870) d	871) d	872) a	1073) b	1074) d	1075) c	1076) a
873) d	874) c	875) a	876) a	1077) d	1078) d	1079) d	1080) a
877) c	878) a	879) a	880) b	1081) a	1082) b	1083) d	1084) c
881) a	882) b	883) d	884) c	1085) c	1086) b	1087) b	1088) d
885) c	886) c	887) c	888) b	1089) d	1090) a	1091) b	1092) a
889) c	890) c	891) d	892) d	1093) b	1094) d	1095) a	1096) a
893) b	894) b	895) d	896) b	1097) b	1098) c	1099) d	1100) a
897) d	898) a	899) b	900) d	1101) a	1102) c	1103) b	1104) a
901) a	902) c	903) d	904) a	1105) a	1106) b	1107) a	1108) a
905) c	906) d	907) b	908) d	1109) b	1110) b	1111) c	1112) b
909) a	910) d	911) c	912) d	1113) b	1114) a	1115) b	1116) d
913) b	914) a	915) c	916) a	1117) d	1118) a	1119) c	1120) c
917) b	918) c	919) d	920) c	1121) a	1122) c	1123) c	1124) a
921) c	922) b	923) a	924) b	1125) a	1126) c	1127) c	1128) c
925) d	926) d	927) a	928) d	1129) d	1130) b	1131) c	1132) d
929) b	930) b	931) a	932) d	1133) d	1134) c	1135) b	1136) a
933) c	934) a	935) b	936) a	1137) a	1138) c	1139) c	1140) a
937) c	938) d	939) c	940) a	1141) d	1142) c	1143) b	1144) d
941) d	942) c	943) b	944) d	1145) b	1146) b	1147) a	1148) a
945) a	946) a	947) a	948) b	1149) d	1150) d	1151) a	1152) b
949) a	950) a	951) a	952) d	1153) c	1154) b	1155) d	1156) b
953) a	954) a	955) b	956) d	1157) b	1158) b	1159) a	1160) a
957) b	958) a	959) c	960) d	1161) a	1162) b	1163) b	1164) b
961) c	962) b	963) b	964) b	1165) a	1166) b	1167) a	1168) a
965) c	966) a	967) a	968) b	1169) a	1170) a	1171) a	1172) a
969) a	970) b	971) b	972) b	1173) d	1174) d	1175) b	1176) c
973) a	974) c	975) d	976) c	1177) b	1178) b	1179) a	1180) c
977) b	978) b	979) a	980) b	1181) b	1182) b	1183) d	1184) a
981) c	982) a	983) b	984) b	1185) a	1186) c	1187) c	1188) b
985) c	986) c	987) b	988) b	1189) d	1190) d	1191) b	1192) a

1193) c	1194) a	1195) a	1196) c	1265) b	1266) d	1267) c	1268) b
1197) d	1198) c	1199) b	1200) c	1269) b	1270) c	1271) c	1272) d
1201) b	1202) b	1203) c	1204) c	1273) c	1274) c	1275) c	1276) a
1205) b	1206) a	1207) a	1208) c	1277) b	1278) a	1279) d	1280) c
1209) c	1210) b	1211) b	1212) b	1281) d	1282) d	1283) c	1284) c
1213) d	1214) b	1215) d	1216) d	1285) a	1286) d	1287) c	1288) c
1217) a	1218) b	1219) b	1220) d	1289) d	1290) a	1291) c	1292) c
1221) c	1222) b	1223) d	1224) c	1293) b	1294) a	1295) b	1296) a
1225) c	1226) b	1227) b	1228) d	1297) c	1298) a	1299) d	1300) a
1229) d	1230) d	1231) b	1232) d	1301) d	1302) a	1303) c	1304) c
1233) d	1234) c	1235) a	1236) c	1305) d	1306) c	1307) a	1308) c
1237) a	1238) b	1239) b	1240) b	1309) d	1310) a	1311) d	1312) d
1241) c	1242) d	1243) a	1244) d	1313) b	1314) a	1315) b	1316) b
1245) b	1246) b	1247) b	1248) a	1317) a	1318) b	1319) c	1320) d
1249) c	1250) c	1251) b	1252) d	1321) b	1322) b	1323) b	1324) b
1253) c	1254) c	1255) b	1256) c	1325) d	1326) c	1327) d	1328) b
1257) a	1258) d	1259) a	1260) d	1329) b			
1261) d	1262) b	1263) b	1264) b				

## : HINTS AND SOLUTIONS :

1 (d)

$$\text{Current} = \frac{\text{net emf}}{\text{net resistance}}$$

$$\text{or } I = \frac{2+2+2}{1+1+1+2} = \frac{6}{5} = 1.2A$$

2 (b)

The bridge will be balanced when the shunted resistance of value  $2\Omega$  i.e.,  $2 = \frac{3 \times S}{3+S}$ . On solving  $S = 6\Omega$

4 (a)

$$\text{Using Wheatstone principle } \frac{P}{Q} = \frac{R}{S} = \frac{R}{100-l}$$

$$= \frac{35}{100-35} = \frac{35}{65} = \frac{7}{13}$$

5 (a)

If resistances of bulbs are  $R_1$  and  $R_2$  respectively then in parallel

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow \frac{1}{\left(\frac{V^2}{P_p}\right)} = \frac{1}{\left(\frac{V^2}{P_1}\right)} + \frac{1}{\left(\frac{V^2}{P_2}\right)}$$

$$\Rightarrow P_p = P_1 + P_2$$

6 (c)

Ist case

$$\frac{30}{P+Q} = \frac{l}{(100-l)}$$

$$\frac{30}{30+Q} = \frac{37.5}{100-37.5}$$

$$\frac{30}{P+Q} = \frac{37.5}{62.5}$$

$$P+Q = \frac{30 \times 62.5}{37.5}$$

$$P+Q = 50 \quad \dots(i)$$

IInd case

$$\frac{30}{\frac{PQ}{P+Q}} = \frac{l}{(100-l)}$$

$$\frac{30(P+Q)}{PQ} = \frac{71.4}{(100-71.4)}$$

$$\frac{30 \times 50}{PQ} = \frac{71.4}{28.6}$$

$$PQ = \frac{30 \times 50 \times 28.6}{71.4}$$

$$P \approx 600 \quad \dots(ii)$$

So, from Eqs. (i) and (ii)

$$P = 30\Omega \text{ and } Q = 20\Omega$$

7 (b)

$$r = \left(\frac{l_1-l_2}{l_2}\right) \times R' = \left(\frac{l_1-2}{2}\right) \times 5 \quad \dots(i)$$

$$\text{and } r = \left(\frac{l_1-3}{3}\right) \times 10 \quad \dots(ii)$$

on solving (i) and (ii),  $r = 10\Omega$ 

8 (b)

$$\text{No. of ions liberated } (n) = \frac{I \times t}{e \times \text{Valency}(p)}$$

$$\text{i.e., } n \propto \frac{1}{P}$$

$$\therefore \frac{n_{Ag}}{n_{Al}} = \frac{P_{Al}}{P_{Ag}} = \frac{3}{1}$$

9 (b)

$$\text{Heat produced} = \frac{V^2 t}{4.2 R} = mL$$

$$\text{or } m = \frac{V^2}{4.2 R L} = \frac{(210)^2 \times 1}{4.2 \times 50 \times 80} = 2.62 \text{ g}$$

10 (c)

$$S = \frac{i_g G}{(i - i_g)} = \frac{1 \times 0.018}{10 - 1} = \frac{0.018}{9} = 0.002\Omega$$

11 (b)

$$\text{Order of drift velocity} = 10^{-4} \text{ m/sec} = 10^{-2} \text{ cm/sec}$$

12 (c)

Ammeter is always connected in series with circuit

13 (d)

Let  $(\rho_A, l_A, r_A, A_A)$  and  $(\rho_B, l_B, r_B, A_B)$  are specific resistances, lengths, radii and areas of wires  $A$  and  $B$  respectively.

Resistance of

$$A = R_A = \frac{\rho_A l_A}{A_A} = \frac{\rho_A l_A}{\pi R_A^2}$$

Resistance of

$$B = R_B = \frac{\rho_B l_B}{A_B} = \frac{\rho_B l_B}{\pi r_B^2}$$

For given information

$$\rho_B = 2\rho_A$$

$$r_B = 2r_A$$

$$\text{And } R_A = R_B$$

$$\therefore \frac{\rho_A l_A}{\pi r_A^2} = \frac{\rho_B l_B}{\pi r_B^2}$$

$$\Rightarrow \frac{\rho_A l_A}{\pi r_A^2} = \frac{2\rho_A \times l_B}{\pi (2r_A)^2}$$

$$\Rightarrow \frac{l_B}{l_A} = \frac{2}{1} = 2:1$$

14 (b)

$$P = \frac{V^2}{R} \Rightarrow \frac{P_1}{P_2} = \frac{R_2}{R_1} \Rightarrow \frac{6}{P_2} = \frac{4}{6} = \frac{2}{3} \Rightarrow P_2 = 9W$$

15 (a)

An ideal cell has zero resistance

16 (c)

$$i = q/t = ne/t$$

$$\text{or } n = it/e = \frac{2 \times 1}{1.6 \times 10^{-19}} = 1.25 \times 10^{19}$$

17 (b)

In parallel  $P_{\text{consumed}} \propto \text{Brightness} \propto \frac{1}{R}$

$$P_A > P_B \text{ [Given]} \therefore R_A < R_B$$

18 (d)

$$I = \frac{P}{V} = \frac{10^5}{200} = 500 \text{ A}$$


$$\text{and } W = zlt = 0.367 \times 10^{-3} \times 500 \times 1 = 0.1835$$

g

19 (a)

Equivalent resistance of the combination
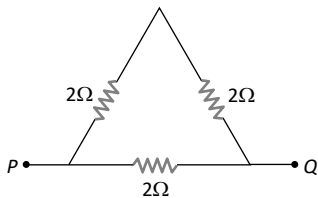
$$= \frac{(2+2) \times 2}{2+2+2} = \frac{8}{6} = \frac{4}{3} \Omega$$



20 (d)

Resistance of a conductor varies linearly with temperature as

$$R_t = R_0(1 + \alpha t)$$

For the first conductor

$$R_{t_1} = R_0(1 + \alpha_1 t_1)$$

$$\text{or } \alpha_1 = \frac{R_{t_1} - R_0}{t} \dots (i)$$

Similarly, for second conductor

$$\alpha_2 = \frac{R_{t_2} - R_0}{t_2} \dots (ii)$$

From Eq. (i) and Eq. (ii), we get

$$\frac{\alpha_1}{\alpha_2} = \frac{t_2}{t_1}$$

21 (a)

Ammeter is always connected in series and voltmeter in parallel.

22 (a)

$$S = \frac{G}{\frac{i}{i_g} - 1} = \frac{25}{\frac{5}{50 \times 10^{-6}} - 1} = \frac{25}{10^5 - 1} = \frac{25}{10^5} = 2.5 \times 10^{-4} \Omega$$


23 (a)

$$\text{Potential gradient} = \frac{V}{L} = \frac{iR}{L} = \frac{i\rho L}{AL} = \frac{i\rho}{A}$$

$$= \frac{0.2 \times 40 \times 10^{-8}}{8 \times 10^{-6}} = 10^{-2} \text{ V/m}$$

24 (c)

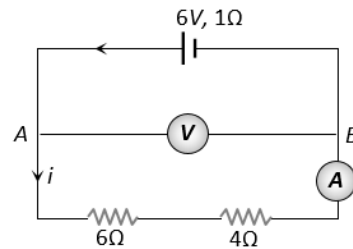The given circuit can be redrawn as follows



$$\text{Current } i = \frac{6}{6+4+1} = \frac{6}{11} \text{ A}$$

$$\text{P.D. between A and B, } V = \frac{6}{11} \times 10 = \frac{60}{11} \text{ V}$$

25 (b)

$$1 \text{ division} = 1 \mu\text{A}$$

$$\text{Current for } 1^\circ\text{C} = \frac{40 \mu\text{V}}{10} = 4 \mu\text{A}$$

$$1 \mu\text{A} = \frac{1}{4} ^\circ\text{C} = 0.25^\circ\text{C}$$

26 (a)

Two resistances of each side of triangle are connected in parallel. Therefore, the effective resistance of each arm of the triangle would be =  $\frac{r \times r}{r+r} = \frac{r}{2}$ . The two arms AB

and AC are in series and they together are in parallel with third one.

$$\therefore R'(r/2) + (r/2) = r$$

Total resistance

$$\frac{1}{R} = \frac{1}{r} + \frac{2}{r} = \frac{3}{r}$$

$$R = r/3$$

27 (d)

$$I = neAv_d$$

$$\text{or } v_d = \frac{1}{neA}$$

$$\text{or } v_d \propto \frac{I}{A}$$

$$\therefore \frac{v'd}{vd} = \frac{I'/A'}{I/A} = \frac{2I/2A}{I/A} = 1$$

$$\text{or } v'd = v_d = v$$

28 (d)

Let the resistance of the wire be  $R$ , then we know that resistance is proportional to the length of the wire. So each of the four wires will have  $R/4$  resistance and they are connected in parallel. So the effective resistance will be

$$\frac{1}{R_1} = \left(\frac{4}{R}\right)^4 \Rightarrow R_1 = \frac{R}{16}$$

29 (b)

By Faraday's law,  $m \propto it$

$$\therefore \frac{m_1}{m_2} = \frac{i_1 t_1}{i_2 t_2} \Rightarrow \frac{m}{m_2} = \frac{4 \times 120}{6 \times 40} \Rightarrow m_2 = \frac{m}{2}$$



30 (d)

$$1 \text{ coulomb} \times 1 \text{ volt} = 1 \text{ joule}$$

Hence, option (d) is incorrect.

31 (a)

$$\frac{i}{i_g} = 1 + \frac{G}{S} \Rightarrow \frac{i \cdot G}{V_g} = 1 + \frac{G}{S} \Rightarrow \frac{100 \times 10^{-3} \times 40}{800 \times 10^{-3}} = 1 + \frac{40}{S}$$

$$\Rightarrow S = 10\Omega$$

32 (a)

This is a balanced Wheatstone bridge. Therefore no current will flow from the diagonal resistance  $10\Omega$

$$\therefore \text{Equivalent resistance} = \frac{(10+10) \times (10+10)}{(10+10) + (10+10)} = 10\Omega$$

33 (a)

$$E = at + \frac{1}{2}bt^2 \quad \dots (i)$$

Differentiating Eq. (i), w.r.t, t

We have

$$\frac{dE}{dt} = a + bt$$

When  $t = t_n$ , ie, neutral temperature, then

$$\frac{dE}{dt} = 0$$

$$\therefore 0 = a + bt_n \text{ or } t_n = -\frac{a}{b}$$

The temperature of inversion

$$t_i = 2t_n = t_0$$

$$= 2t_n - 0 = -\frac{2a}{b}$$

Thermoelectric power

$$P = \frac{dE}{dt} = a + bt$$

34 (c)

Since, charge ( $q$ ) = current ( $i$ )  $\times$  times ( $t$ )  
Therefore, charge is equal to area under the curve.

$$\therefore \text{Ist rectangle} = q = lb = 2$$

$$\text{IInd rectangle} = q = lb = 2$$

$$\text{IIIrd triangle} = q = \frac{1}{2}lb = 2$$

Hence, ratio is 1:1:1.

35 (b)

The internal resistance of battery is given by

$$r = \left(\frac{E}{V} - 1\right)R = \left(\frac{40}{30} - 1\right) \times 9 = \frac{9 \times 10}{30} = 3\Omega$$

36 (a)

$$\text{Conductivity } \sigma = \frac{1}{\rho} \quad \dots (i)$$

$$\text{and conductance } G = \frac{1}{R}$$

$$\Rightarrow GR = 1 \quad \dots (ii)$$

$$\text{From equation (i) and (ii) } \sigma = \frac{GR}{\rho}$$

38 (d)

Let the current in  $12\Omega$  resistance is  $i$

Applying loop theorem in closed mesh  $AEFCA$

$$12i = -E + E = 0$$

$$\therefore i = 0$$

39 (b)

$$P \propto V^2 \Rightarrow \frac{P}{P_0} = \left(\frac{V}{V_0}\right)^2 \Rightarrow P = \left(\frac{V}{V_0}\right)^2 P_0$$

40 (a)

$$P = \frac{V^2}{R} \Rightarrow \frac{P_P}{P_S} = \frac{R_S}{R_P} = \frac{(R_1 + R_2)}{R_1 R_2 / (R_1 + R_2)} = \frac{(R_1 + R_2)^2}{R_1 R_2}$$


$$\Rightarrow \frac{100}{25} = \frac{(R_1 + R_2)^2}{R_1 R_2} \Rightarrow \frac{R_1}{R_2} = \frac{1}{1}$$

41 (c)

For semiconductors, resistance decreases on increasing the temperature

42 (b)

Given circuit is equivalent to

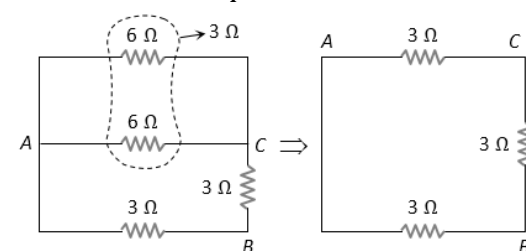

So the equivalent resistance between points A and B is equal to

$$R = \frac{6 \times 3}{6 + 3} = 2\Omega$$

43 (d)

$$\text{Energy consumed in } kWh = \frac{\text{watt} \times \text{hour}}{1000}$$

$$\Rightarrow \text{For 30 days, } P = \frac{10 \times 50 \times 10}{1000} \times 30 = 150kWh$$

44 (a)

Ammeter is always connected in series and Voltmeter is always connected in parallel

45 (c)

$$It = \frac{m}{z} = \frac{5 \times 10^{-3}}{3.387 \times 10^{-7}} = \frac{5 \times 10^4}{3.387 \times 60 \times 60} \text{ Ah} = 4.1 \text{ Ah}$$

46 (d)


$$\frac{R_1}{R_2} = \frac{(1 + \alpha t_1)}{(1 + \alpha t_2)} \Rightarrow \frac{5}{6} = \frac{(1 + \alpha \times 50)}{(1 + \alpha \times 100)} \Rightarrow \alpha = \frac{1}{200} \text{ per } ^\circ\text{C}$$

$$\text{Again by } R_t = R_0(1 + \alpha t)$$

$$\Rightarrow 5 = R_0 \left( 1 + \frac{1}{200} \times 50 \right) \Rightarrow R_0 = 4\Omega$$


47 (d)

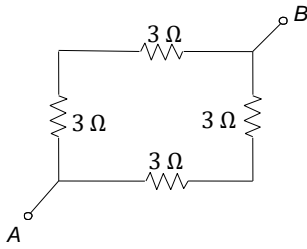Given, the resistance of wire  $R=12\Omega$ . The wire is bent in square form



$$R_1 = 3 + 3 = 6\Omega$$

$$R_2 = 3 + 3 = 6\Omega$$

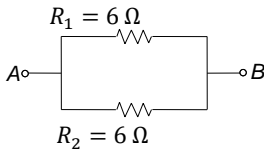

$$\frac{1}{R'} = \frac{1}{6} + \frac{1}{6}$$

$$\text{or } \frac{1}{R'} = \frac{2}{6}$$

$$\text{or } R' = 3\Omega$$

48 (a)

Chemical equivalent of gold =  $\frac{197.1}{3} = 65.7$

Gold to be deposited =  $\frac{200 \times 5}{100} = 10\text{g}$

Electrochemical equivalent of gold

$$z_2 = \frac{W_2}{W_1} z_1 \quad z_2 = \frac{65.7}{1.008} \times 0.1044 \times 10^{-4} \text{gC}^{-1}$$

$$\text{Also } m = zlt, t = \frac{m}{zl}$$

$$\Rightarrow = \frac{10}{\left( \frac{65.7}{1.008} \times 0.1044 \times 10^{-4} \times 2 \right)}$$

$$= 7347.9\text{s}$$


49 (d)

$$I^2 \times 6 = 60 \text{ or } I = \sqrt{10} \text{ A}$$

Current through upper branch =  $2\sqrt{10}\text{A}$ . Heat produced per second  $3\Omega =$

$$(2\sqrt{10})^2 \times 3 \text{ cal} = 120 \text{ cal.}$$

50 (c)

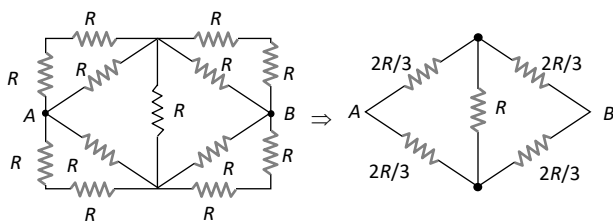

Hence  $R_{eq} = \frac{2R}{3}$  [Since it's a balanced Wheatstone bridge]

51 (d)

Because cell is in open circuit

54 (c)

$$v_d = \frac{I}{nAe} = \frac{20}{10^{29} \times 10^{-6} \times 1.6 \times 10^{-19}} = 1.25 \times 10^{-3} \text{ m/s}$$

55 (b)

Let  $R$  be the resistance of each lamp and  $V$  be the voltage supplied to the circuit. Current in the circuit is

$$I_1 = \frac{V}{R + \frac{R \times R}{R+R}} = \frac{2V}{3R}$$

Current flowing through  $B$  or  $C$ ,

$$I_2 = \frac{I_1}{2} = \frac{1}{2} \left( \frac{2V}{3R} \right) = \frac{V}{3R}$$

When  $C$  is fused, the whole current flows through  $A$  and  $B$ .

Then,  $I'_2 = V/2R$

So current through  $A$  decreases and current through  $B$  increases. Therefore brilliance of  $A$  decreases and that of  $B$  increase.

56 (c)

As for an electric appliance  $R = \frac{V^2}{P}$ .

For first bulb, its resistance

$$R_2 = \frac{V^2}{P_1} = \frac{250 \times 250}{100} = 625 \Omega$$

For second bulb, its resistance

$$R_2 = \frac{V_2^2}{P_2} = \frac{200 \times 200}{100} = 400 \Omega$$

Now, in series potential divides in proportion to resistance.

$$\text{So, } V_2 = \frac{R_2}{(R_1 + R_2)} V$$

Where  $V$  is supply voltage.

$\therefore$  Potential drop across bulb  $B_2$ .

$$V_2 = \frac{400}{(625 + 400)} \times 250 = 97.56 \text{ V} = 98 \text{ V}$$

57 (d)


Equivalent weight of aluminium =  $\frac{27}{3} = 9$

So 1 faraday = 96500 C are required to liberate 9 gm of Al

58 (a)

In the following circuit potential difference between
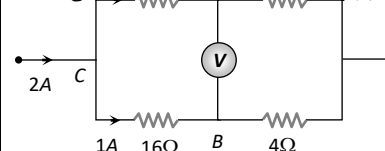
$$C \text{ and } A \text{ is } V^A - V^C = 1 \times 4 = 4 \dots (i)$$




C and B is  $V_C - V_B = 1 \times 16 = 16 \dots(ii)$

On solving equations (i) and (ii) we get

$$V_A - V_B = 12V$$

59 (a)

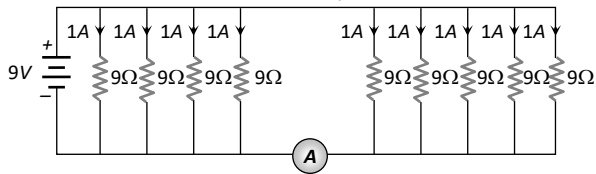Equivalent resistance  $R = \frac{9}{9} = 1\Omega$



Current  $i = \frac{9}{1} = 9A$

Current passing through the ammeter = 5A

60 (b)

Power,  $P = \frac{V^2}{R}$

$$R = \frac{V^2}{P} = \frac{(60)^2}{160} = 22.5\Omega$$

Now, according to Ohm's law

$$V = IR$$

$$\therefore I = \frac{60}{22.5}$$

$$\Rightarrow I = 2.6A$$

Here,  $t = 60s$

$$\text{As } I = \frac{ne}{t}$$

$$\Rightarrow n = \frac{I \times t}{e} = \frac{2.6 \times 60}{1.6 \times 10^{-19}} \approx 10^{21}$$


61 (a)

$$i = \frac{e}{R} \Rightarrow 3 \times 10^{-7} = \frac{(30 \times 10^{-6}) \times \theta}{50} \Rightarrow \theta = 0.5^\circ$$

62 (d)

Since  $E_1(10V) > E_2(4V)$

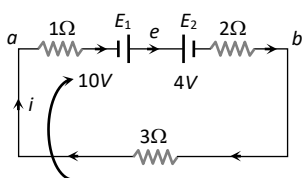So current in the circuit will be clockwise



Applying Kirchhoff's voltage law

$$-1 \times i + 10 - 4 - 2 \times i - 3i = 0 \Rightarrow i = 1A(a \text{ to } b \text{ via } e)$$

$$\therefore \text{Current} = \frac{V}{R} = \frac{10-4}{6} = 1.0 \text{ ampere}$$

63 (d)

$$\text{Given, } V = 10 \times 10^{-6}t - \frac{1}{40} \times 10^{-6}t^2$$

At neutral temperature

$$\frac{dV}{dt} = 0$$

$$\therefore 10 \times 10^{-6} - \frac{1}{20} \times 10^{-6} t_n = 0$$

or  $t_n = 200^\circ C$

Also at neutral temperature, thermo-emf is maximum.

Thus,

$$V_{max} = 10 \times 10^{-6}(200) - \frac{1}{40} \times 10^{-6}(200)^2 = 2 \times 10^{-3} - 1 \times 10^{-3} = 1 \text{ mv}$$

64 (d)

For conversion of galvanometer (of resistance) into voltmeter, a resistance  $R$  is connected in series

$$\therefore i_g = \frac{V_1}{R+G} \text{ and } i_g = \frac{V_2}{2R+G}$$

$$\Rightarrow \frac{V_1}{R+G} = \frac{V_2}{2R+G} \Rightarrow \frac{V_2}{V_1} = \frac{2R+G}{R+G} = \frac{2(R+G)-G}{(R+G)}$$

$$= 2 - \frac{G}{(R+G)} \Rightarrow V_2 = 2V_1 - \frac{V_1 G}{(R+G)} \Rightarrow V_2 < 2V_1$$

65 (c)

$$I = \frac{E}{R_T} = \frac{2.5}{10+R} \text{ and } V = I.R = \frac{2.5 \times 10}{10+R} = \frac{25}{10+R}$$

$$x = \frac{V}{L} = \frac{25}{(10+R)L}$$

$$E = x.l_1$$

$$\Rightarrow 1 = \frac{25}{(10+R)L} \times \frac{L}{2} \Rightarrow 25 = 20 + 2R$$

$$\Rightarrow 2R = 5 \Rightarrow R = \frac{5}{2}$$

$\therefore$  Now the resistance is doubled

$$R^1 = \frac{5}{2} \times 2 = 5\Omega$$

$$\therefore x = \frac{25}{(10+5)L} = \frac{25}{15.L} = \frac{5}{3L}$$

$$E = x.l_2$$

$$\Rightarrow 1 = \frac{5}{3L} . l_2 \Rightarrow l_2 = \frac{3L}{2} = 0.6L$$

66 (a)

$$\text{Voltage sensitivity} = \frac{Q}{V}$$

$$\text{Current sensitivity} = \frac{Q}{I}$$

Also, potential difference


$$V = IG$$

$$\text{Hence, } \frac{V_s}{I_s} = \frac{Q/V}{Q/I} = \frac{I}{V} = \frac{I}{IG}$$

$$\therefore \frac{V_s}{I_s} = \frac{1}{G}$$

67 (c)

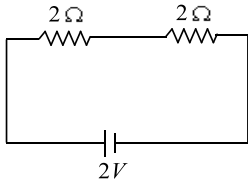In steady state the branch containing capacitors, can be neglected. So reduced circuit is as follows




$$\text{Power } P = \frac{V^2}{R} = \frac{(2)^2}{4} = 1W$$

68 (b)

According to Kirchoff's first law

$$(5A) + (4A) + (-3A) + (-5A) + I = 0$$

$$\text{Or } I = -1A$$

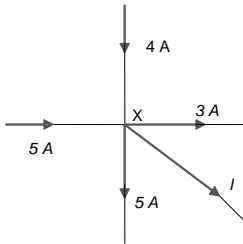

69 (b)

When the heating coil is cut into two equal parts and these parts are joined in parallel, the resistance of coil is reduced to one fourth, so power consumed will become 4 times *i.e.*  $400 \text{ Js}^{-1}$

70 (d)

The emf of the standard cell must be greater than that of experimental cells, otherwise balance point is not obtained

71 (d)

$E = at + \frac{1}{2}\beta t^2$ , graph between  $E$  and  $t$  will be a parabola, such that first emf increases and then decreases

72 (d)

Potential difference between A and B

$$V_A - V_B = 1 \times 1.5$$

$$\Rightarrow V_A - 0 = 1.5V \Rightarrow V_A = 1.5V$$

Potential difference between B and C

$$V_B - V_C = 1 \times 2.5 = 2.5V$$

$$\Rightarrow 0 - V_C = 2.5V \Rightarrow V_C = -2.5V$$


Potential difference between C and D

$$V_C - V_D = -2V \Rightarrow -2.5 - V_D = -2 \Rightarrow V_D = -0.5V$$

73 (d)

$$R_{eq} = \frac{5}{2} \Omega$$
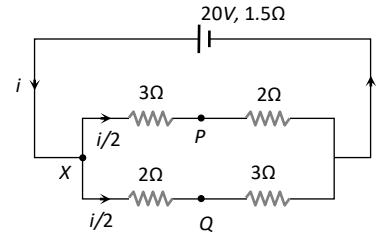
$$i = \frac{20}{\frac{5}{2} + 1.5} = 5A$$



Potential difference between X and P,

$$V_X - V_P = \left(\frac{5}{2}\right) \times 3 = 7.5V \quad \dots(i)$$

$$V_X - V_Q = \frac{5}{2} \times 2 = 5V \quad \dots(ii)$$

On solving (i) and (ii)  $V_P - V_Q = -2.5 \text{ volt}; V_Q > V_P$

$$\text{Short Trick: } (V_P - V_Q) = \frac{i}{2}(R_2 - R_1) =$$

$$\frac{5}{2}(2 - 3) = -2.5$$

$$\Rightarrow V_Q > V_P$$


74 (c)

Initially the inductance will oppose the current which tries to flow through the inductance. But  $10\Omega$  and  $20\Omega$  can conduct. The current will be

$$\frac{2V}{30\Omega} = \frac{1}{15} A$$

75 (c)

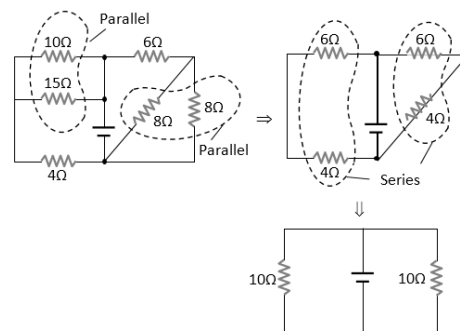Given circuit can be reduced to a simple circuit as shown in figures below




76 (d)

Let polarity of  $m$  cells in a 12 cells battery is reversed, then equivalent emf of the battery =  $(12 - 2m)E$

Now the circuit can be drawn as

$$(12 - 2m)E$$

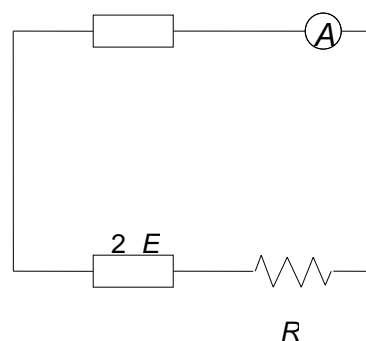

When 12-cell battery and 2-cell battery aid each

other, then current through the circuit

$$i_1 = \frac{(12 - 2m)E + 2E}{R}$$

$$\text{or } 3 = \frac{(14 - 2m)E}{R} \dots (i)$$

When they oppose each other, the current through the circuit.

$$i_2 = \frac{(12 - 2m)E - 2E}{R}$$

$$\text{or } 2 = \frac{(10 - 2m)E}{R} \dots (ii)$$

Dividing Eq. (i) by Eq. (ii), we have

$$\frac{3}{2} = \frac{14 - 2m}{10 - 2m}$$

$$\text{or } 30 - 6m = 28 - 4m$$

$$\text{or } 2m = 2$$

$$\text{or } m = 1$$

77 (b)

$$i = qv = 1.6 \times 10^{-19} \times 6.6 \times 10^{15} \\ = 10.56 \times 10^{-4} A = 1mA$$

78 (d)

$$R = \rho \frac{l}{A} \text{ and } P \propto \frac{1}{R} \Rightarrow P \propto \frac{A}{l} \Rightarrow P \propto \frac{d^2}{l} \Rightarrow P_A = 2P_B$$

79 (a)

Let the resistance of each heater wire is  $R$ . When two wires are connected in series, the heat developed is

$$H_1 = \frac{V^2 t}{2R} \dots (i)$$

When two heater wires are connected in parallel, the heat developed is

$$H_2 = \frac{V^2 t}{R/2} = \frac{2V^2 t}{R} \dots (ii)$$

Dividing Eq. (i) by Eq. (ii), we get

$$\frac{H_1}{H_2} = \frac{1}{4} \text{ or } H_1 : H_2 = 1 : 4$$

80 (a)

$$R_{\text{eff}} = \frac{(P + Q)(R + S)}{(P + Q + R + S)} = \frac{4}{3} R$$

81 (a)

In the first case,  $Zit = m$

In the second case,  $Z \times \frac{i}{4} \times 4t = m$

82 (d)

For conductors, resistance  $\propto$  Temperature and for semiconductor, resistance  $\propto \frac{1}{\text{Temperature}}$

83 (a)

Since resistance connected in arms  $CE, ED, CF$

and  $FD$  will form a balanced Wheatstone bridge, therefore, the resistance of arm  $EF$  becomes ineffective. Now resistance of arm  $CED$  or  $CFD = 2 + 2 = 4\Omega$ . Effective resistance of these two parallel arm =  $\frac{4 \times 4}{4+4} = 2\Omega$

Now resistance of arm  $ACDB = 2 + 2 + 2 = 6\Omega$ , is in parallel with resistance arm  $AB = 2\Omega$ . Thus, effective resistance between  $A$  and  $B$

$$= \frac{6 \times 2}{6 + 2} = \frac{3}{2} \Omega$$

84 (c)

$$i = \frac{dQ}{dt} = \frac{d}{dt} (5t^2 + 3t + 1) = 10t + 3$$

When  $t = 5s, i = 10 \times 5 + 3 = 53 A$

85 (a)

The current taken by the silver voltmeter

$$I_1 = \frac{n}{Zt} = \frac{1}{11.2 \times 10^{-4} \times 30 \times 60} = 0.496 A$$

and by copper voltmeter

$$I_2 = \frac{1.8}{6.6 \times 10^{-4} \times 30 \times 60} = 1.515 A$$

The current  $I = (I_1 + I_2) = 2.011 A$

Power  $P = IV = 2.011 \times 12 = 24.132 J/sec$

86 (c)

Average current

$$i = \frac{50+100+50}{3} = \frac{200}{3} \text{ mA}$$

$$z = \frac{m}{it} = \frac{3m}{200 \times 10^{-3} \times 30} = \frac{m}{2}$$

87 (c)

The equivalent current due to motion of electrons is given by

$$I = \frac{e}{t} = \frac{1.6 \times 10^{-19}}{1.594 \times 10^{-18}}$$


$$= 1.0037 \times 10^{-1}$$

$$= 100.37 \times 10^{-3} A$$

$$= 100.37 \text{ mA}$$

88 (a)

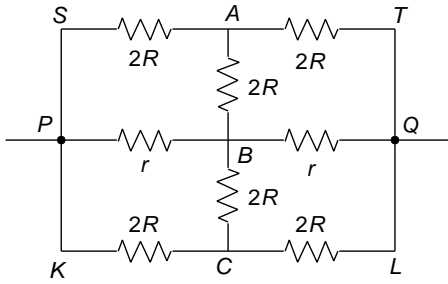In the circuit arrangement  $PSTQ$  is a balanced Wheatstone bridge, hence resistance  $2R$  joined in arm  $AB$  be omitted. Similarly, resistance  $2R$  joined in arm  $BC$  may also be omitted.



$$\therefore \frac{1}{R_{eq}} = \frac{1}{4R} + \frac{1}{2r} + \frac{1}{4R} = \frac{\mu + 2R + \mu}{4\mu R} = \frac{(R+r)}{2Rr}$$

$$\Rightarrow R_{eq} = \frac{2Rr}{R+r}$$

89 (b)

$$\frac{dT}{dt} = \frac{d}{dt}(at^2 - bt^3) = 2at - 3bt^2$$

When  $t = t_n$  (ie, neutral temperature),  $\frac{dE}{dt} = 0$


$$\therefore 0 = 2at_n - 3bt_n^2 \text{ or } t_n = \frac{2a}{3b}$$

90 (a)

The circuit may be redrawn as shown in the adjacent figure

$$\text{Here } E_{eq} = 12V, r_{eq} = \frac{2 \times 2}{2+2} = 1\Omega$$
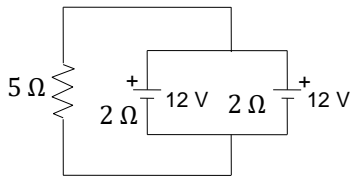
$$i = \frac{E_{eq}}{R + r_{eq}} = \frac{12}{5 + 1} = \frac{12}{6} = 2\Omega$$



91 (c)

$$i = nAev_d$$

$$\text{or } v_d = \frac{i}{nAe}$$

Total number of free electrons in the unit length of conductor,  $N = nA \times 1$ .

Total linear momentum of all free electrons per unit length

$$= (Nm)v_d = nAm \times \frac{i}{nAe} = \frac{i}{(e/m)} = \frac{i}{s}$$

92 (b)


$$\text{As } m = z l t = z \left(\frac{V}{R}\right) t \text{ ie, } m \propto Vt$$

$$\therefore \frac{m_2}{m_1} = \frac{V_2 t_2}{V_1 t_1}$$

$$\text{or } m_2 = \frac{V_2 t_2}{V_1 t_1} \times m_1 = \frac{6 \times 45 \times 2}{12 \times 30} = 1.5g.$$

93 (a)

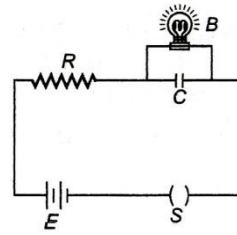Neon bulb is filled with gas, so the resistance is infinite; hence no current flows through it.



$$\text{Now, } V_c = E(1 - e^{-t/RC})$$

$$\Rightarrow 120 = 200(1 - e^{-t/RC})$$

$$\Rightarrow e^{-t/RC} = \frac{2}{5}$$

$$\Rightarrow t = RC \ln 2.5$$


$$\Rightarrow R = \frac{t}{C \ln 2.5} = \frac{5}{2.303 \times 2 \times 10^6 \log 2.5} = 2.7 \times 10^6 \Omega$$

94 (b)

$v_d \propto 1/l$ . Therefore, drift velocity is halved

95 (b)
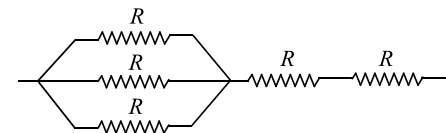
$$\frac{1}{R_p} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} = \frac{3}{R}$$



$$\Rightarrow R_p = \frac{R}{3}\Omega$$

$$\Rightarrow R_s = R + R = 2R\Omega$$

$$\Rightarrow R_{net} = R_p + R_s = 2R + \frac{R}{3} = \frac{7R}{3}\Omega$$

96 (a)

The resistivity of metal increases when it is converted into an alloy

$$\therefore \rho' > \rho$$

98 (b)

This is because of secondary ionisation which is possible in the gas filled in it

99 (a)


$$\text{Using } R_{T_2} = R_{T_1} [1 + \alpha(T_2 - T_1)]$$

$$\Rightarrow R_{100} = R_{50} [1 + \alpha(100 - 50)]$$

$$\Rightarrow 7 = 5 [1 + (\alpha \times 50)] \Rightarrow \alpha = \frac{(7 - 5)}{250} = 0.008/^\circ C$$

100 (b)

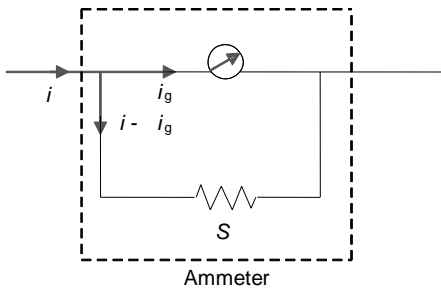Ammeter is made by connecting a low resistance shunt  $S$  in parallel with galvanometer  $G$ . since  $G$  and  $S$  are in parallel, the potential difference across them is same.



$$i_g \times G = (i - i_g) \times S$$

Given,  $G = R, i = 4i_g$

$$S = \frac{i_g}{4i_g - i_g} \times R = \frac{i_g}{3i_g} \times R = \frac{R}{3}$$

101 (a)

Maximum current flows through bulb (1)

Therefore, it will lights brightly.

102 (d)

$$S = \frac{i_g G}{(i - i_g)} \Rightarrow \frac{G}{S} = \frac{i - i_g}{i_g} = \frac{10 - 1}{1} = \frac{9}{1}$$


104 (d)

Potentiometer works on null deflection method.

In balance condition no current flows in secondary circuit.

106 (b)

The circuit can be simplified as follows

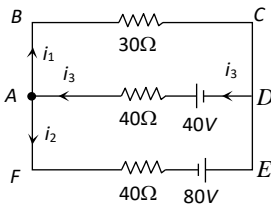

Applying KCL at junction A

$$i_3 = i_1 + i_2 \quad \dots(i)$$

Applying Kirchoff's voltage law for the loop ABCDA

$$\begin{aligned} -30i_1 - 40i_3 + 40 &= 0 \\ \Rightarrow -30i_1 - 40(i_1 + i_2) + 40 &= 0 \\ \Rightarrow 7i_1 + 4i_2 &= 4 \quad \dots(ii) \end{aligned}$$

Applying Kirchoff's voltage law for the loop ADEFA

$$\begin{aligned} -40i_2 - 40i_3 + 80 + 40 &= 0 \\ \Rightarrow -40i_2 - 40(i_1 + i_2) &= -120 \\ \Rightarrow i_1 + 2i_2 &= 3 \quad \dots(iii) \end{aligned}$$

On solving equation (ii) and (iii)  $i_1 = -0.4A$

107 (c)

From Faraday's law,  $m/E = \text{constant}$   
where  $m = \text{mass of substance deposited}$ ,  $E = \text{chemical equivalent}$

$$\therefore \frac{m_2}{m_1} = \frac{E_2}{E_1} \Rightarrow m_2 = \frac{108}{32} \times 1.6 = 5.4g$$

108 (b)

Based on Peltier effect

109 (b)

The current through the voltmeter is same as drawn from the battery outside it

110 (a)

Slope of graph

$$= \frac{I}{V} = \frac{1}{R}$$

If experiment is performed at higher temperature then resistance increase and hence slope decrease, choice (a) is wrong.

Similarly in choice (b) and (c) resistance increase.

But for choice (d) resistance  $R$  increases, so slope decreases

111 (d)

Heat produced,  $H = \frac{V^2 t}{R}$ . When voltage is halved, the heat produced becomes one-fourth. Hence time taken to heat the water becomes four time.

112 (c)

$$H = \frac{V^2}{R} t \Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = \frac{4}{2} = \frac{2}{1}$$

113 (c)

Given that

$$\text{emf } E_N = 1.5r_N$$

Where  $r_N$  is the internal resistance of  $n$ th cell.

$$\text{Total emf } E = E_1 + E_2 + E_3 + \dots + E_n$$

$$= 1.5[r_1 + r_2 + r_3 + \dots + r_n]$$

Total internal resistance

$$r = r_1 + r_2 + r_3 + \dots + r_n$$

$$\therefore \text{Current } i = \frac{E_{\text{total}}}{r_{\text{total}}}$$

$$i = \frac{1.5[r_1 + r_2 + r_3 + \dots + r_n]}{[r_1 + r_2 + r_3 + \dots + r_n]}$$

Hence,  $i = 1.5A$

114 (b)

The given network is a balanced Wheatstone bridge. It's equivalent resistance will be  $R = \frac{18}{5} \Omega$

So current from the battery  $i = \frac{V}{R} = \frac{V}{18/5} = \frac{5V}{18}$

115 (d)

The resistance of 40 W bulb will be more and 60 W bulb will be less

116 (c)

$$E = aT + bT^2$$


At temperature of inversion,  $E = 0$ ,

$$\therefore aT_i + bT_i^2 = 0$$

$$\Rightarrow T_i = -\frac{a}{b}$$

$$\Rightarrow T_i = -\frac{10 \times 10^{-6}}{(0.02 \times 10^{-6})} = 500^\circ\text{C}$$

117 (c)

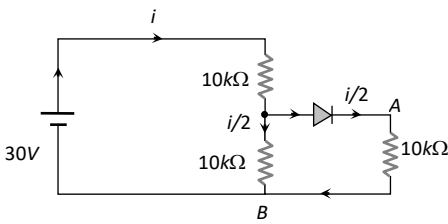

Equivalent resistance  $R = 10 + \frac{10}{2} = 15 \text{ k}\Omega$

$$\text{Current } i = \frac{30}{15} = 2 \times 10^{-3} \text{ A}$$

Hence, potential difference between A and B

$$V = \left(\frac{2 \times 10^{-3}}{2}\right) \times 10 \times 10^3 = 10 \text{ Volt}$$

118 (b)

Let the potential difference across battery is  $V$  and internal resistance of the cell is  $r$ , then

$$E = V + ir \quad \dots (i)$$

$$V = iR \quad \dots \dots (ii)$$

Now, from Eqs. (i) and (ii) we have

$$E = iR + ir = i(R + r) \quad \dots (iii)$$

Now, dividing Eq. (iii) by Eq. (ii), we get

$$\frac{E}{V} = \frac{R + r}{R} = 1 + \frac{r}{R}$$

$$\frac{E}{V} - 1 = \frac{r}{R}$$

$$\text{or } \left(\frac{E - V}{V}\right)R = r$$


Hence, internal resistance

$$r = \left(\frac{E - V}{V}\right)R$$

120 (b)

In the given circuit, resistors  $4R$  and  $2R$  are connected in parallel while resistance  $R$  is connected in series to it.

Hence, equivalent resistance is

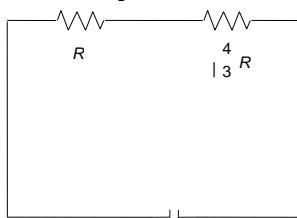

$$\frac{1}{R'} = \frac{1}{4R} + \frac{1}{2R}$$

$$= \frac{6R}{8R^2}$$


$$R' = \frac{8}{6}R$$

$$= \frac{4}{3}R$$

$$\Rightarrow R'' = R + \frac{4}{3}R = \frac{7R}{3}$$

Given, emf is  $E$  Volts, therefore

$$i = \frac{E}{R} = \frac{3E}{7R}$$

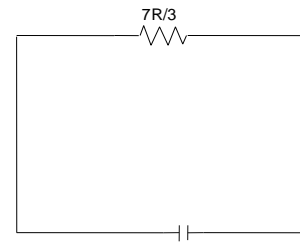

Potential difference across  $R$  is

$$V = ir = \frac{3R}{7R} \times R = \frac{3E}{7}$$

Potential difference across  $2R$  is

$$V' = E - \frac{3E}{7} = \frac{4E}{7}$$

121 (a)

$$\text{Drift velocity, } v_d = \frac{e\tau V}{mL} \left[ \because E = \frac{V}{L} \right]$$

Where the symbols have their usual meaning

If the temperature are not same,  $\tau$  cannot be same. Then none of the given options is correct

If temperatures are same, then  $\frac{v_{d1}}{v_{d2}} = \frac{V_1}{V_2} = \frac{1}{2}$

122 (d)

The light from bulb spread out uniformly in all directions.

For a 100 W bulb, intensity at a distance of 3 m is

$$I = \frac{\text{Power}}{\text{Area}} = \frac{100}{4\pi(3)^2}$$

$$\text{As } I = \epsilon_0 c E_{rms}^2 \Rightarrow E_{rms}^2 = \frac{I}{\epsilon_0 c} \quad \dots (i)$$

For a 400 W bulb, intensity at the same point is

$$I' = \frac{400}{4\pi(3)^2} \Rightarrow E_{rms}'^2 = \frac{I'}{\epsilon_0 c}$$

$$\frac{E_{rms}'^2}{E_{rms}^2} = \frac{I'}{I} = \frac{400}{4\pi(3)^2} \times \frac{4\pi(3)^2}{100}$$

$$E_{rms}'^2 = E_{rms}^2 \times 4 = (2.9)^2 \times 4 \left[ \because E_{rms} = 2.9 \text{ Vm}^{-1} (\text{Given}) \right]$$

$$\text{or } E_{rms}' = 2.9 \times 2 \text{ Vm}^{-1} = 5.8 \text{ Vm}^{-1}$$

123 (b)

$$\text{Neutral temperature, } t_n = \frac{t_i + t_c}{2}$$

$$\Rightarrow 285^\circ = \frac{t_i + 10^\circ}{2}$$

$$570^\circ = t_i + 10^\circ$$

$$\text{or } t_i = 560^\circ$$

124 (b)

Here,  $V < E$

$$\therefore E = V + Ir$$

For first case



$$E = 12 + \frac{12}{16}r \quad \dots (i)$$

**For second case**

$$E = 11 + \frac{11}{10}r \quad \dots (ii)$$

From Eqs. (i) and (ii),

$$12 + \frac{12}{16}r = 11 + \frac{11}{10}r$$

$$\Rightarrow r = \frac{20}{7} \Omega$$

125 (b)

The amount of chlorine

$$\begin{aligned} m &= zlt = z \left( \frac{P}{V} \right) t \quad [\because P = VI] \\ &= 0.367 \times 10^{-6} \times \left( \frac{100 \times 1000}{125} \right) \times 60 \\ &= 0.017616 \text{ kg} = 17.616 \text{ g} \end{aligned}$$

126 (a)

$R_{\text{Parallel}} < R_{\text{Series}}$ . From graph it is clear that slope of the line A is lower than the slope of the line B. Also slope = resistance, so line A represents the graph for parallel combination

127 (a)

Near room temperature, the electric resistance of a typical metal conductor increases linearly with temperature.

$$R = R_0(1 + \alpha T)$$

Where  $\alpha$  is the thermal resistance coefficient.

128 (b)

$$R = \frac{\rho L}{A} \Rightarrow 0.7 = \frac{\rho \times 1}{\frac{22}{7} (1 \times 10^{-3})^2}$$

$$\rho = 2.2 \times 10^{-6} \text{ ohm-m}$$

129 (b)

In the part c b d,

$$V_c - V_b = V_b - V_d \Rightarrow V_b = \frac{V_c + V_d}{2}$$

In the part c a d

$$V_c - V_a > V_a - V_d \Rightarrow \frac{V_c + V_d}{2} > V_a \Rightarrow V_b > V_a$$

130 (c)

$$\begin{aligned} m &= Zi \Rightarrow t = \frac{m}{Zi} = \frac{m \times F}{E \times i} \quad [\because Z = \frac{E}{F}] \\ t &= \frac{27 \times 96500}{108 \times 2} = 12062.5 \text{ sec} = \frac{12062.5}{3600} \text{ hr} \\ &= 3.35 \text{ hr} \end{aligned}$$

132 (c)

$$\text{We know that } \frac{P_1}{P_2} = \frac{R_2}{R_1} = \frac{2}{1}$$


133 (b)

As both cells are in series, the circuit current

$$i = \frac{E + E}{r_1 + r_2 + R} = \frac{2E}{r_1 + r_2 + R}$$

As terminal potential drop across 1st cell is zero, hence
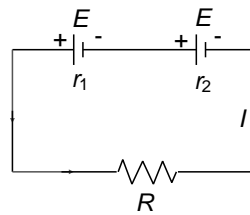
$$V_1 = E - ir_1 = E - \frac{2E}{(r_1 + r_2 + R)} r_1 = 0$$



$$\begin{aligned} \Rightarrow E &= \frac{2Er_1}{(r_1 + r_2 + R)} \text{ or } r_1 + r_2 + R = 2r_1 = R \\ &= (r_1 - r_2) \end{aligned}$$

134 (d)

When a circuit is made up on any two metals in thermoelectric series, the current flows across the cold junction from the later occurring metal in the series to the one occurring earlier. In thermoelectric series Bismuth comes earlier than Antimony. So, at cold junction current flows from Antimony to Bismuth and at hot junction it flows from bismuth to Antimony.

135 (d)

Resistivity is the property of the material. It does not depend upon size and shape

136 (d)

As circuit is open, therefore no current flows through circuit. Hence potential difference across X and Y = EMF of battery = 120V

137 (a)

$$H = \frac{I^2 R t}{J} = \frac{I^2 R t}{4.2} \text{ cal}$$

138 (b)

Kirchhoff's second law is  $\sum V = 0$

It states that the algebraic sum of the potential differences in any loop including those associated emf's and those of resistive elements, must equal zero.

This law represents 'conservation of energy'.

139 (b)


When length and radius both are doubled, in accordance with relation  $R = \frac{\rho L}{A}$  the resistance of wire is reduced to 1/2 of its initial value. As at constant voltage the heat produced  $H \propto 1/R$ , hence heat produced is doubled

140 (c)

Approximate change in resistance =  $2 \times$  % change in length by stretching

141 (b)

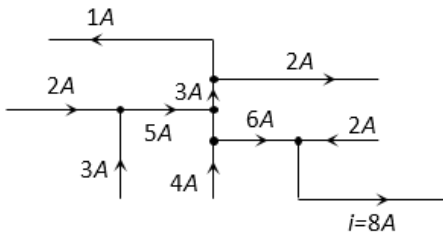By using Kirchoff's junction law as shown below



We get  $i = 8A$

142 (a)

$$I = \frac{dq}{dt} = 3t^2 + 2t + 5$$

$$\therefore dq = (3t^2 + 2t + 5)dt$$

$$\therefore q = \int_{t=0}^{t=2} (3t^2 + 2t + 5)dt$$

$$= \frac{3t^3}{3} + \frac{2t^2}{2} + 5t \Big|_0^2 = t^3 + t^2 + 5t \Big|_0^2 = 22 C$$

143 (a)

$$\frac{i}{i_g} = \frac{G + S}{S} \Rightarrow \frac{i_g}{i} = \frac{S}{G + S} = \frac{2.5}{27.5} = \frac{1}{11}$$


144 (b)

Current flowing through  $2\Omega$  resistance is  $3A$ , so P.D. across it is  $3 \times 2 = 6V$

Current through the bottom line =  $\frac{6}{1+5} = 1A$

$\therefore$  Power dissipated in  $5\Omega$  resistance is

$$P = i^2 R = (1)^2 \times 5 = 5W$$

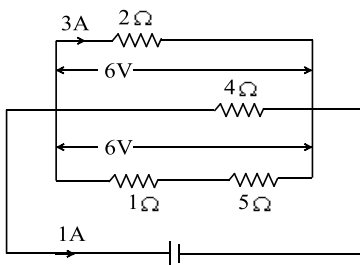

145 (a)

We know that thermoelectric power

$$S = \frac{dE}{dT}$$

$$\text{Given, } E = K(T - T_r) \left[ T_0 - \frac{1}{2}(T + T_r) \right]$$

By differentiating the above equation w.r.t.  $T$  and

putting  $T = \frac{1}{2} T_0$ , we get  $S = \frac{1}{2} kT_0$

146 (d)

Three resistances are in parallel,

$$\therefore \frac{1}{R'} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} = \frac{3}{R}$$

The equivalent resistance

$$R' = \frac{R}{3} \Omega = \frac{6}{3} = 2\Omega$$

148 (a)

Internal resistance of the cell

$$r = \left[ \frac{E}{V} - 1 \right] R$$

$$r = \left[ \frac{1.5}{1.4} - 1 \right] 14 = 1\Omega$$

149 (c)

From Kirchoff's second law

$$V = \sum ir \quad (\text{for closed mesh})$$

Where  $V$  is potential difference,  $i$  the current and  $r$  the resistance.

$$\therefore E + E = Ir + Ir = 2Ir$$

$$\text{or } I = \frac{E}{r} \quad \dots (i)$$

$$V_x - V_y = E - Ir$$

Putting the value of  $I$  from Eq (i), we get

$$V_x - V_y = E - \frac{E}{r} \times V = 0$$

150 (c)

$$\text{Here, } \frac{P}{Q} = \frac{2}{3}$$

we know

$$\frac{P}{Q} = \frac{l}{100 - l}$$

$$\Rightarrow \frac{2}{3} = \frac{l}{100 - l}$$

$$\Rightarrow l = 40 \text{ cm}$$

151 (c)

$$v_d = \frac{I}{nAe} = \frac{20}{10^{29} \times 10^{-6} \times 1.6 \times 10^{-19}} = 1.25 \times 10^{-3} \text{ m/s}$$

152 (b)

Total resistance

$$\text{Or } R = 20 + 40$$

$$R = 60\Omega$$

Given  $G = 15V$

$$\text{Current } I = \frac{V}{R} = \frac{15}{60}$$

$$I = 0.25A$$

$$\text{Potential gradient} = \frac{V}{l}$$

$$= \frac{20 \times 0.25}{10} = 0.5 \text{ Vm}^{-1}$$

PD across  $240 \text{ cm}$

$$E = 0.5 \times 2.4$$

$$E = 1.2V$$

153 (a)



Equivalent resistance of the given network

$$R_{\text{eq}} = 75\Omega$$

$\therefore$  Total current through battery,

$$i = \frac{3}{75}$$
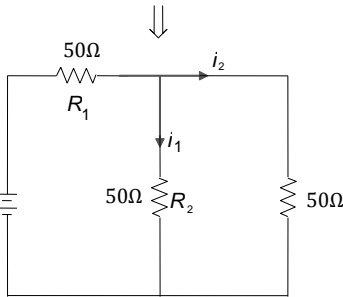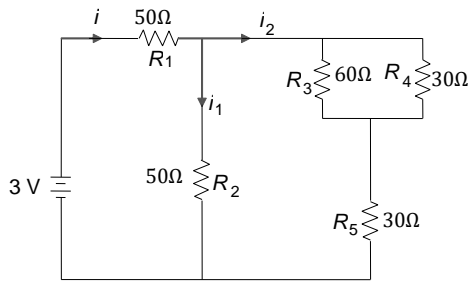
$$i_1 = i_2 = \frac{3}{75 \times 2} = \frac{3}{150}$$



Current through resistance

$$R_4 = \frac{3}{150} \times \frac{60}{(30 + 60)}$$

$$= \frac{3}{150} \times \frac{60}{90}$$

$$= \frac{2}{150} \text{ A}$$

$$V_4 = i_4 \times R_4$$

$$= \frac{2}{150} \times 30$$

$$= \frac{2}{5} = 0.4 \text{ volt}$$

154 (c)

Current through a conductor is constant at even cross-section of the conductor

155 (c)

Mass deposited = density  $\times$  volume of the metal

$$m = p \times A \times X \quad \dots(i)$$

$$\text{Hence from Faraday's first law } m = Zit \quad \dots(ii)$$

So from equation (i) and (ii)


$$Zit = \rho \times Ax \Rightarrow x = \frac{Zit}{\rho A}$$

$$= \frac{3.04 \times 10^{-4} \times 10^{-3} \times 1 \times 3600}{9000 \times 0.05} = 2.4 \times 10^{-6} \text{ m}$$

$$= 2.4 \mu\text{m}$$

157 (c)

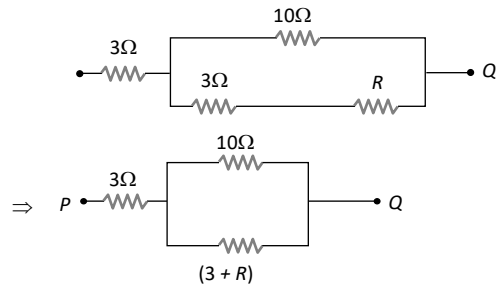The given circuit can be simplified as follows



$$R = 3 + \frac{10 \times (3 + R)}{10 + 3 + R} = 3 + \frac{30 + 10R}{13 + R}$$

$$R = \frac{39 + 3R + 30 + 10R}{13 + R} = \frac{69 + 13R}{13 + R}$$

$$13R + R^2 = 69 + 13R \Rightarrow R = \sqrt{69} \Omega$$

158 (b)

$R \propto l^2 \Rightarrow$  If  $l$  doubled then  $R$  becomes 4 times

159 (c)

Ammeter is used to measure the current through the circuit

160 (b)

$$i = \frac{E}{r + R} \Rightarrow P = i^2 R \Rightarrow P = \frac{E^2 R}{(r + R)^2}$$

Power is maximum when  $r = R \Rightarrow P_{\max} = E^2/4r$


161 (c)

$$\theta_0 = 2\theta_n - \theta_i = 2 \times 210 - (600 - 273)$$

$$= 420 - 327 = 93^\circ \text{C}$$

162 (c)

Let the circuit be as shown

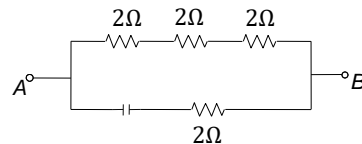

Equivalent resistance between A and B is

$$\frac{1}{R} = \frac{1}{2} + \frac{1}{(2 + 2 + 2)} = \frac{2}{3}$$

$$R = \frac{3}{2} = 1.5 \Omega$$

Therefore, 4 resistances are required.

163 (b)

$$\frac{r_{\text{iron}}}{r_{\text{copper}}} = \sqrt{\frac{\rho_{\text{iron}}}{\rho_{\text{copper}}}} = \sqrt{\frac{1 \times 10^{-7}}{1.7 \times 10^{-8}}} = 2.4$$

164 (c)

For a fuse  $I^2 \propto r^3$

$$\therefore \frac{I_1^2}{I_2^2} = \frac{r_1^3}{r_2^2}$$

$$\frac{3^2}{I_2^2} = \left(\frac{0.02}{0.03}\right)^3$$

$$I_2 = 3 \times \left(\frac{3}{2}\right)^{3/2} \text{ A}$$

165 (d)

Let  $n$  cells be in series and  $m$  in parallel, then

$$\frac{nE}{R + nr} = \frac{E}{R + \frac{r}{m}}$$

$$\Rightarrow n \left[ R + \frac{r}{m} \right] = R + nr$$

$$\Rightarrow nRm + nr = Rm + mnr$$

$$\Rightarrow 6 + 2r = 3 + 4r$$

$$\Rightarrow 2r = 3$$

$$\Rightarrow r = 1.5\Omega$$

166 (a)

The ratio  $\frac{AC}{CB}$  will remain unchanged.

167 (b)

$$V_2 - V_1 = E - ir = 5 - 2 \times 0.5 = 4 \text{ volt}$$

$$\Rightarrow V_2 = 4 + V_1 = 4 + 10 = 14 \text{ volt}$$

168 (a)

Power in electric bulb

$$P = \frac{V^2}{R}$$

So, resistance of electric bulb

$$R = \frac{V^2}{P}$$

Given,  $P_1 = 25 \text{ W}$ ,  $P_2 = 100 \text{ W}$ ,

$$V_1 = V_2 = 220 \text{ volt}$$

Therefore, for same potential difference  $V$

$$R \propto \frac{1}{P}$$

Thus, we observe that for minimum power, resistance will be maximum and *vice - versa*.

Hence, resistance of 25 W bulb is maximum and 100 W bulb is minimum.

169 (c)

Let temperature of cold junction be  $0^\circ\text{C}$  and that of hot junction be  $T^\circ\text{C}$ . The relation for thermo-emf is given by

$$E = AT - \frac{1}{2} BT^2$$

Given,  $A = 16$ ,  $B = 0.08$

$$\therefore E = 16T - \frac{1}{2} \times 0.08 \times T^2$$


Since, at temperature of inversion emf is zero, we have

$$0 = 16T - 0.04 T^2$$

$$\Rightarrow T = \frac{16}{0.04} = 400^\circ\text{C}$$

170 (c)

The equivalent circuit can be redrawn as

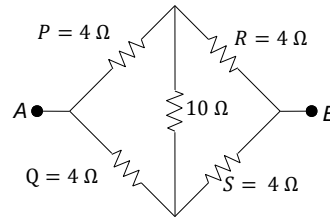

we have,  $\frac{P}{Q} = \frac{R}{S}$

$$\text{ie, } \frac{4}{4} = \frac{4}{4}$$

So, the given circuit is a balanced Wheatstone's bridge.

Hence, the equivalent resistance

$$R_{AB} = \frac{(4 + 4) \times (4 + 4)}{(4 + 4) + (4 + 4)}$$

$$= \frac{8 \times 8}{8 + 8} = \frac{64}{16} = 4\Omega$$

171 (b)

Force = Electric intensity  $\times$  charge

$$= \frac{\text{Potential difference}}{\text{distance}} \times \text{charge}$$

$$\therefore 4.8 \times 10^{-19} = \frac{V}{5} \times 1.6 \times 10^{-19}$$

or  $V = 15 \text{ volt}$

172 (d)

In stretching of wire  $R \propto \frac{1}{d^4}$ , where  $d$  = Diameter of wire

173 (d)

Total current through the circuit

$$i = \frac{10}{\frac{1000}{3} + 500} = \frac{3}{250} \text{ A}$$

$$\text{Now voltmeter reading} = i_v \times R_V = \frac{2}{3} \times \frac{3}{250} \times 500 = 4V$$

174 (b)

$$E = xl = \frac{V}{l} = \frac{iR}{L} \times l \Rightarrow E = \frac{r}{(R + R_h + r)} \times \frac{R}{L} \times l$$

$$\Rightarrow E = \frac{10}{(5 + 4 + 1)} \times \frac{5}{5} \times 3 = 3V$$

175 (c)

$$i = nAev_d$$

$$\text{or } v_d = \frac{i}{nAe} \text{ ie, } v_d \propto \frac{1}{A}$$

As  $A$  increases  $v_d$  decreases, because  $i$  remains constant

176 (a)

$R = \rho l/A$  or  $R \propto l/A$ . Thus, resistance is least in a

wire of length  $L/2$  and area of cross-section  $2A$

177 (c)

$$V_d = \frac{i}{nAe} = \frac{5.4}{8.4 \times 10^{28} \times 10^{-6} \times 1.6 \times 10^{-19}} = 0.4 \times 10^{-3} \text{ m/sec} = 0.4 \text{ mm/sec}$$

178 (c)

The power of the battery, when charged, is given by

$$P_1 = V_1 I_1$$

The electrical energy dissipated is given by  $E_1 = P_1 t_1$

$$\text{i.e., } E_1 = V_1 I_1 t_1 = 15 \times 10 \times 8 = 1200 \text{ Wh}$$

Similarly, the electrical energy dissipated during the discharge a battery is given by,

$$E_2 = V_2 I_2 t_2 = 14 \times 5 \times 15 = 1050 \text{ Wh}$$

Hence, watt-hour efficiency of the battery is given by

$$\eta = \frac{E_2}{E_1} \times 100 = 0.875 \times 100 = 87.5\%$$

179 (d)

Total power spend across two resistors connected

$$\text{in parallel to battery} = \frac{V^2}{R_1} + \frac{V^2}{R_2}$$


$$= \frac{3 \times 3}{2} + \frac{3 \times 3}{2/3} = \frac{36}{2} = 18$$

$$= 3 \times 3 \times 2 \text{ J}$$

180 (b)

$$\text{Conductance } C = \frac{1}{R} = \frac{A}{\rho l} \Rightarrow C \propto \frac{1}{l}$$

181 (d)

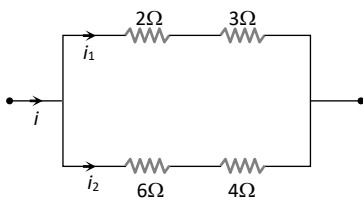

Resistance of upper branch  $R_1 = 2 + 3 = 5\Omega$

Resistance of lower branch  $R_2 = 4 + 6 = 10\Omega$

$$\text{Hence } \frac{i_1}{i_2} = \frac{R_2}{R_1} = \frac{10}{5} = 2$$

$$\frac{\text{Heat generated across } 3\Omega (H_1)}{\text{Heat generated across } 6\Omega (H_2)} = \frac{i_1^2 \times 3}{i_2^2 \times 6} = \frac{4}{2} = 2$$

$$\therefore \text{Heat generated across } 3\Omega = 120 \text{ cal/sec}$$

182 (b)

At resonance both bulbs will glow with same brightness. At resonance,

$$X_L = X_C$$

$$\text{Or } 2\pi fL = \frac{1}{2\pi fC}$$

$$\text{Or } f = \frac{1}{2\pi\sqrt{LC}}$$

183 (d)


$$R \propto \frac{1}{r^2} \Rightarrow \frac{R_1}{R_2} = \frac{l_1}{l_2} \times \frac{r_2^2}{r_1^2} \Rightarrow \frac{1}{1} = \frac{5}{l_2} \times \left(\frac{2}{1}\right)^2 \Rightarrow l_2 = 20m$$

184 (c)

If an identical battery is connected in opposition, net emf =  $E - E = 0$  and the current through circuit will be zero, although each one of them has constant emf.

185 (a)

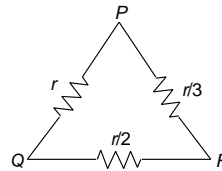The circuit given in figure can be redrawn as shown here. Here two resistances are joined in series and the combination is joined in parallel with the third resistance. Since in parallel grouping effective resistance is even less than the smallest individual resistance, hence net resistance will be maximum between the points  $P$  and  $Q$



186 (c)

$$i_g = \frac{iS}{S+G} \Rightarrow 10 = \frac{50 \times 12}{12+G} \Rightarrow 12+G = 60 \Rightarrow G = 48\Omega$$


187 (b)

$$i_g S = (i - i_g)G \Rightarrow i_g(S+G) = iG$$

$$\Rightarrow \frac{i_g}{i} = \frac{G}{S+G} = \frac{8}{2+8} = 0.8$$

188 (b)
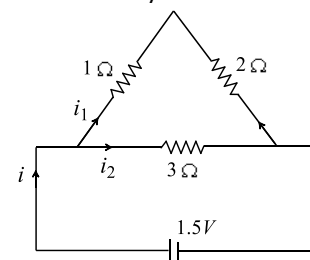
$$i_1 + i_2 = \frac{1.5}{3/2} = 1 \text{ amp}$$



$$\frac{i_1}{i_2} = \frac{3}{3} \Rightarrow i_1 = i_2 \therefore i_2 = 0.5A = i_1$$

189 (d)


Current through the galvanometer

$$I = \frac{3}{(50+2950)} = 10^{-3}A$$

Current for 30 divisions =  $10^{-3}A$

Current for 20 divisions
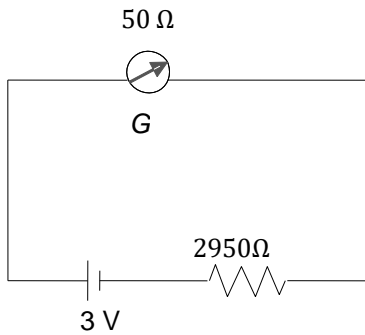
$$= \frac{10^{-3}}{30} \times 20 = \frac{2}{3} \times 10^{-3}A$$



For the same deflection to obtain for 20 divisions, let resistance added be  $R$


$$\therefore \frac{2}{3} \times 10^{-3} = \frac{3}{(50 + 1R)}$$

or  $R = 4450\Omega$

190 (c)

Suppose resistance  $R$  is corrected in series with bulb

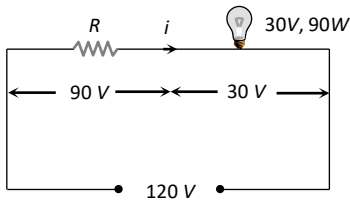Current through the bulb  $i = \frac{90}{30} = 3 A$



Hence for resistance  $V = iR \Rightarrow 90 = 3 \times R \Rightarrow R = 30\Omega$

191 (c)

$$R_{\max} = nR \text{ and } R_{\min} = R/n \Rightarrow \frac{R_{\max}}{R_{\min}} = n^2$$

192 (a)

The voltage per unit length of the metre wire  $PQ$  is  $\left(\frac{6.00 \text{ mV}}{0.600 \text{ m}}\right)$  i.e.  $10 \text{ mV/m}$ . Hence potential difference across the metre wire is  $10 \text{ mV/m} \times 1 \text{ m} = 10 \text{ mV}$ . The current drawn from the driver cell is  $i = \frac{10 \text{ mV}}{5 \Omega} = 2 \text{ mA}$

$$\text{The resistance } R = \frac{(2V - 10 \text{ mV})}{2 \text{ mA}} = \frac{1990 \text{ mV}}{2 \text{ mA}} = 995 \Omega$$

193 (b)


To make range  $n$  times, the galvanometer resistance should be  $G/n$ , where  $G$  is initial resistance

194 (d)

Let a resistance  $r$  ohm be shunted with resistance  $S$ , so that the bridge is balanced.

If  $S'$  is the resultant resistance of  $S$  and  $r$ , then

In balanced position

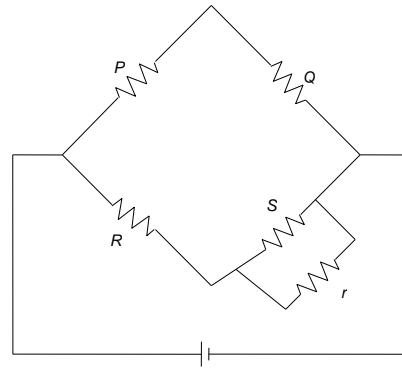

$$\frac{P}{Q} = \frac{R}{S'}$$

$$\frac{2}{2} = \frac{2}{S'}$$

$$\therefore S' = 2\Omega$$

Now,

$$\frac{1}{S'} = \frac{1}{S} + \frac{1}{r}$$

$$\text{or } \frac{1}{r} = \frac{1}{S'} - \frac{1}{S} = \frac{1}{2} - \frac{1}{3} = \frac{3-2}{6}$$

$$\frac{1}{r} = \frac{1}{6}$$

$$r = 6\Omega$$

195 (d)

Let the value of shunt be  $r$ . Hence the equivalent resistance of branch containing  $S$  will be  $\frac{Sr}{S+r}$

In balance condition,  $\frac{P}{Q} = \frac{Sr/(S+r)}{R}$ . This gives  $r = 8\Omega$

197 (b)

$$P = Vi \Rightarrow i = \frac{2.2 \times 10^3}{22000} = \frac{1}{10} A$$

$$\text{Now loss of power} = i^2 R = \left(\frac{1}{10}\right)^2 \times 100 = 1 W$$

198 (b)

Let resistance for bulb filament at  $0^\circ\text{C}$  be  $R_0$  and at a temperature  $\theta^\circ\text{C}$  its value be  $200 \Omega$ . Then,  $100 = R_0(1 + \alpha \times 100) = R_0(1 + 0.005 \times 100)$

$$= R_0(1.5) \dots(i)$$

$$\text{and } 200 = R_0(1 + \alpha \times \theta) = R_0(1 + 0.005 \times \theta)$$

$$= R_0(1.005\theta) \dots(ii)$$

$$\text{Dividing Eq. (ii) by Eq.(i), we get } 2 = \frac{1+0.005\theta}{1.5}$$

$$3 = 1 + 0.005\theta$$

$$\Rightarrow \theta = \frac{2}{0.005} = 400^\circ\text{C}$$

199 (c)

Since the current coming out from the positive

terminal is equal to the current entering the negative terminal, therefore, current in the respective loop will remain confined in the loop itself

∴ Current through  $2\Omega$  resistor = 0

200 (d)

Graph (d) represents the thermal energy produced in a resistor.


201 (c)

Potential difference across  $1\text{ M}\Omega$  resistor is

$$V_P - V_B = \frac{18V \times 1 \times 10^6 \Omega}{(0.2 + 1) \times 10^6 \Omega} = \frac{18V \times 1 \times 10^6 \Omega}{1.2 \times 10^6 \Omega} = 15V$$

$$V_B = -15V \text{ [Given]}$$
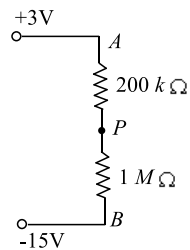
$$\therefore V_P - V_B = 15V \text{ or } V_P = 15V + V_B = 15V - 15V = 0V$$



Potential difference across  $200\text{ k}\Omega$  resistor is

$$V_A - V_P = \frac{18V \times 0.2 \times 10^6 \Omega}{(0.2 + 1) \times 10^6 \Omega} = \frac{18V \times 0.2 \times 10^6 \Omega}{1.2 \times 10^6 \Omega} = 3V$$

$$V_A = +3V \text{ [Given]}$$

$$\therefore V_A - V_P = 3V \text{ or } V_P = V_A - 3V = +3V - 3V = 0V$$

202 (a)

Current through resistance  $P$  and  $Q$ ,

$$i_1 = \frac{4}{90 + 110} = \frac{1}{50} \text{ A}$$

$$V_A - V_B = P i_1 = 90 \times \frac{1}{50} = 1.8 \text{ V}$$

Current through resistance  $R$  and  $S$ ,

$$i_2 = \frac{4}{40 + 60} = \frac{1}{25} \text{ A}$$

$$V_A - V_D = R i_2 = 40 \times \frac{1}{25} = 1.6 \text{ V}$$

$$V_B - V_D = (V_A - V_D) - (V_A - V_B)$$

$$= 1.6 - 1.8 = -0.2V$$

203 (b)

$$\text{By using } e_0^{100} = e_0^{32} + e_{32}^{70} + e_{70}^{100}$$

$$\Rightarrow 200 = 64 + 76 + e_{70}^{100} \Rightarrow e_{70}^{100} = 60 \mu V$$

204 (a)

$$\text{Given, } E_1 = 1.5V, l_1 = 27 \text{ cm,}$$

$$l_2 = 54 \text{ cm, } E_2 = ?$$

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

$$\text{or } E_2 = \frac{E_1 l_2}{l_1}$$

$$\text{or } E_2 = \frac{1.5 \times 54}{27}$$


$$E_2 = 3V$$

205 (a)

Joule effect is not reversible

206 (c)

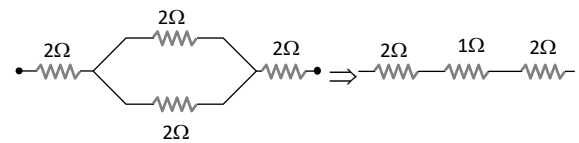The given circuit can be redrawn as follows



$$\Rightarrow R_{eq} = 5\Omega$$

207 (a)

$$i = \frac{E}{R + r} = \frac{5}{4.5 + 0.5} = 1A$$

$$V = E - ir = 5 - 1 \times 0.5 = 4.5 \text{ Volt}$$

208 (b)

$$\text{Current } I = \frac{ne}{l}$$

$$3.2 = \frac{n \times 1.6 \times 10^{-19}}{1}$$

$$n = \frac{3.2}{1.6 \times 10^{-19}} = 2 \times 10^{19}$$

209 (b)

As the current and the other factors are same for both the galvanometers

$$N \propto \tan \theta$$

$$\frac{N_1}{N_2} = \frac{\tan 60^\circ}{\tan 30^\circ} = \frac{\sqrt{3}}{1/\sqrt{3}}$$

$$\Rightarrow \frac{N_1}{N_2} = 3$$

210 (a)

$$\text{Resistance} = \frac{\text{Potential difference}}{\text{Current}}$$

211 (b)

$$i_g = i \frac{S}{G + S} \Rightarrow \frac{0.01}{10} = \frac{S}{50 + S} \Rightarrow S = \frac{50}{999} = 0.05\Omega$$


212 (b)

The sensitivity of potentiometer can be increased by decreasing the potential gradient *i. e.* by increasing the length of potentiometer wire

$$[\text{Sensitivity} \propto \frac{1}{P.G.} \propto \text{Length}]$$

213 (c)

We can simplify the network as shown

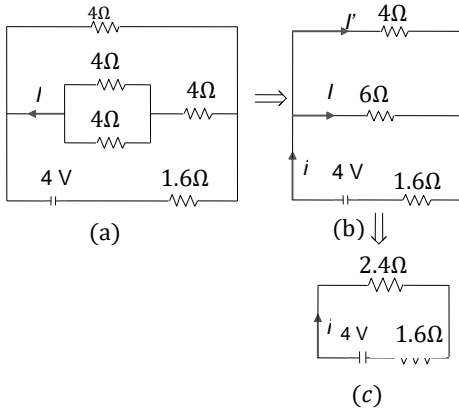

So, net resistance,

$$R = 2.4 + 1.6 = 4.0\Omega$$

Therefore, current from the battery.

$$i = \frac{V}{R} = \frac{4}{4} = 1A$$

Now, from the circuit (b),

$$4I' = 6I$$

$$\Rightarrow I' = \frac{3}{2}I$$

But  $i = I + I'$


$$= I + \frac{3}{2}I = \frac{5}{2}I$$

$$\therefore 1 = \frac{5}{2}I$$

$$\Rightarrow I = \frac{2}{5} = 0.4A$$

214 (a)

$$V_{ab} = i_g \cdot G = (i - i_g)S$$

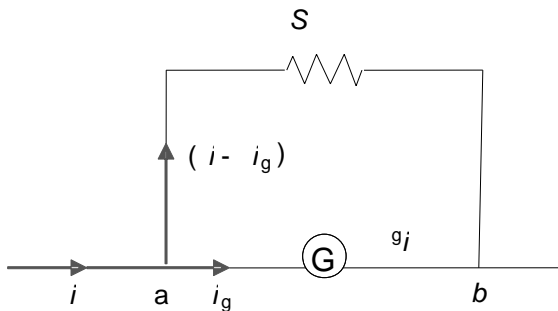

$$\therefore i = \left(1 + \frac{G}{S}\right) i_g$$

Substituting the values we get,

$$i = 100.1mA$$

215 (d)

$$\text{In series } i = \frac{2E}{2+R}$$

$$\therefore J_1 = i^2 R = \left(\frac{2E}{2+R}\right)^2 \cdot R$$

In parallel

$$i = \frac{E}{0.5+R}$$

$$J_2 = i^2 R = \left(\frac{E}{0.5+R}\right)^2 \cdot R$$

$$\frac{J_1}{J_2} = 2.25 = \frac{4(0.5+R)^2}{(2+R)^2}$$

Solving we get,  $R = 4\Omega$

216 (a)

With rise in temperature the thermal velocity of the electron increases. Relaxation time and hence drift velocity will decrease.

217 (a)

$$I_1 = \frac{2}{2+4} \times 6 = 2A$$

$$I_2 = 4 \text{ amp}$$

218 (b)

$$v_d = i/nAe$$

$$= 0.21 / (8.4 \times 10^{28} \times 10^{-6} \times 1.6 \times 10^{-19})$$

$$= 1.56 \times 10^{-5} \text{ms}^{-1}$$

219 (a)

For power transmission power loss in line  $P_L = i^2 R$

If power of electricity is  $P$  and it is transmitted at voltage  $V$ , then  $P = Vi \Rightarrow i = \frac{P}{V}$

$$P_L = \left(\frac{P}{V}\right)^2 R = \frac{P^2 R}{V^2} = \frac{2.2 \times 10^3 \times 2.2 \times 10^3 \times 10}{22000 \times 22000} = 0.1W$$

220 (b)

As  $5\Omega$  resistor is joined in parallel to series combination of  $4\Omega$  and  $6\Omega$  ( $i.e.$ , total resistance  $10\Omega$ ),  $V = \text{constant}$ .

$$\text{and } \frac{i_1}{i_2} = \frac{R_2}{R_1} = \frac{10}{5} = 2$$

$$\text{or } i_2 = \frac{i_1}{2}$$

Now heat produced per second in  $5\Omega$  resistor

$$H_1 = i_1^2 R_1 = i_1^2 \times 5 = 100 \text{Js}^{-1} \dots(i)$$

and for  $4\Omega$  resistor

$$H_2 = i_2^2 R_2 = \left(\frac{i_1}{2}\right)^2 \times 4 = i_1^2 \dots(ii)$$

Simplifying Eqs. (i) and (ii), we get

$$\frac{H_2}{100} = \frac{1}{5} \text{ or } H_2 = \frac{1}{5} \times 100 = 20 \text{Js}^{-1}$$

221 (b)



The resistance of one wire

$$R_1 = \rho \frac{l_1}{A_1}$$

and the resistance of second wire

$$R_2 = \rho \frac{l_2}{A_2}$$

Ratio of their resistance

$$\frac{R_1}{R_2} = \frac{l_1}{A_1} \times \frac{A_2}{l_2}$$

∴ Mass = density × volume

∴ Mass = density × area × length

$$\text{Or } \frac{R_1}{R_2} = \left(\frac{l_1}{l_2}\right)^2 \times \frac{\rho A_2 l_2}{\rho A_1 l_1}$$

$$\text{Or } \frac{R_1}{R_2} = \left(\frac{l_1}{l_2}\right)^2 \times \frac{m_2}{m_1}$$

$$\text{Or } \frac{R_1}{R_2} = \frac{9}{16} \times \frac{3}{2} \text{ Or } \frac{R_1}{R_2} = \frac{27}{32}$$

$$R_1 : R_2 = 27 : 32$$

222 (d)

We know that the current in the circuit

$$I = \frac{E}{R + r}$$

and power delivered to the resistance  $R$  is

$$P = I^2 R = \frac{E^2 R}{(R + r)^2}$$

It is maximum when  $\frac{dP}{dR} = 0$

$$\frac{dP}{dR} = E^2 \left[ \frac{(r + R)^2 - 2R(r + R)}{(r + R)^4} \right] = 0$$

$$\text{Or } (r + R)^2 = 2R(r + R)$$

$$\text{Or } R = r$$

223 (b)

$$T_n = \frac{T_i + T_c}{2} = \frac{10 + 530}{2} = 270^\circ\text{C}$$

224 (d)

Let  $R_1$  and  $R_2$  be the resistances of the coils

$$H = \frac{V^2 t_1}{R_1} \text{ and } H = \frac{V^2 t_2}{R_2}$$

$$\Rightarrow \frac{t_1}{R_1} = \frac{t_2}{R_2}, \text{ i.e., } \frac{R_2}{R_1} = \frac{t_2}{t_1} \quad \dots (i)$$

Now in parallel

$$R' = \frac{R_1 R_2}{R_1 + R_2} = R_1$$

$$\therefore H = \frac{V^2 t}{R'} \quad \dots (ii)$$

$$\text{Now, } \frac{V^2 t}{R'} = \frac{V^2 t_1}{R_1}$$

$$\Rightarrow \frac{t \times (R_1 + R_2)}{R_1 R_2} = \frac{t_1}{R_1} \quad \dots (iii)$$


On using Eqs. (i) and (iii), we get

$$t = \frac{t_1 t_2}{t_1 + t_2}$$

225 (c)

Error in measurement = Actual value - Measured value

Actual value =  $2V$

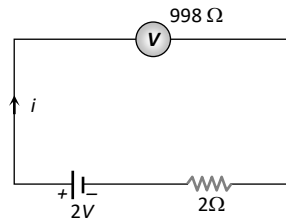

$$i = \frac{2}{998 + 2}$$

$$= \frac{1}{500} \text{ A}$$

Since  $E = V + ir$

$$\Rightarrow V = E - ir = 2 - \frac{1}{500} \times 2 = \frac{998}{500} \text{ V}$$

$$\therefore \text{Measured value} = \frac{998}{500} \text{ V}$$

$$\Rightarrow \text{Error} = 2 - \frac{998}{500} = 4 \times 10^{-3} \text{ volt}$$

226 (d)

The circuit shown is a balanced Wheatstone bridge. So, there is no current flowing through  $10\Omega$  resistance. Therefore, by replacing  $10\Omega$  resistance by  $20\Omega$  resistance, current in the circuit will be as such i.e.,  $4A$ .

227 (c)

$$r = R \left( \frac{l_1}{l_2} - 1 \right) = 10 \left( \frac{75}{65} - 1 \right) \\ = 10 \times 0.0154 = 1.54\Omega$$

228 (a)

Suppose  $m$  rows are connected in parallel and each row contains  $n$  identical cells (each cell having  $E = 15V$  and  $r = 2\Omega$ )

For maximum current in the external resistance

$R$ , the necessary condition is  $R = \frac{nr}{m}$

$$\Rightarrow 12 = \frac{n \times 2}{m} \Rightarrow n = 6m \quad \dots (i)$$

$$\text{Total cells} = 24 = n \times m \quad \dots (ii)$$

On solving equations (i) and (ii)  $n = 12$  and  $m = 2$  i.e. 2 rows of 12 cells are connected in parallel

229 (c)

Current drawn from the cell in resistance  $R_1$  will be  $I = E/(R_1 + r)$

Therefore, heat produced in  $R_1$  i.e.,

$$H_1 = \frac{E^2 R_1 t}{(R_1 + r)^2}$$

$$\text{Heat produced in } R_2 \text{ i.e., } H_2 = \frac{E^2 R_2 t}{(R_2 + r)^2}$$

As per question  $H_1 = H_2$

$$\text{or } \frac{E^2 R_1 t}{(R_1 + r)^2} = \frac{E^2 R_2 t}{(R_2 + r)^2}$$

On solving we get;

$$r = \sqrt{R_1 R_2} \\ = \sqrt{100 \times 40} = 63.25 \Omega$$

230 (b)

$$R = \frac{V^2}{P}$$

$$\text{or } R \propto \frac{1}{P}$$

$$\therefore \frac{1}{R_{100}} > \frac{1}{R_{60}} > \frac{1}{R_{70}}$$

Hence, the correct option is (d)

231 (b)

$$\text{Potential gradient } x = \frac{V}{L} = \frac{iR}{L}$$

$$\Rightarrow x = \frac{2}{(15 + 5)} \times \frac{15}{10} = \frac{3}{2000} \text{ volt/cm}$$

232 (c)

$$\text{Resistance, } R = \rho \frac{l}{A}$$

$$R \propto l \propto \frac{1}{A}$$

$\therefore R$  is maximum when

$$\text{length} = 2L \text{ and area} = \frac{A}{2}$$

233 (a)

$$22.4 \text{ litre } H_2 = 1 \text{ mole of } H_2 = N \text{ molecules of } H_2 \\ = 2N \text{ atoms of } H$$

$$\text{So charge required to liberate } 22.4 \text{ litre of } H_2 = 2Ne = 2F$$

$$\text{Hence charge required to liberate } 11.2 \text{ litre of } H_2 = F$$

234 (b)

Current through external resistance,

$$i = \frac{nE}{nr + R} = \frac{5 \times 2}{5 \times 0.2 + 4} = 2A$$

235 (c)

$$\text{When bulbs are connected in series, } P = \frac{V^2}{R'} = \frac{V^2}{3R}$$

When bulbs are connected in parallel

$$P' = \frac{V^2}{R''} = \frac{V^2 \times 3}{R} = 3 \times 3P = 9P$$

236 (b)

11.2 L of  $H_2$  is liberated by 96500 C 22.4 L of  $H_2$  is

liberated by

$$96500 \times 2 = 193000 \text{ C.}$$

237 (d)

$$\text{Case (i) } E + E = (r + r + 5) \times 1.0$$

$$\text{or } 2E = 2r + 5 \dots (i)$$

$$\text{Case (ii) } E = \left(\frac{r \times r}{r+r} + 5\right) \times 0.8$$

$$\text{or } E = \left(\frac{r}{2} + 5\right) 0.8 \text{ or } E = 0.4r + 4.0 \dots (ii)$$

Multiplying Eq.(ii) by 2 and equating with Eq.(i), we get

$$2r + 5 = 0.8r + 8$$

$$\text{or } 1.2 = 3 \text{ or } r = \frac{3}{1.2} = 2.5 \Omega$$

239 (d)

$6\Omega$  and  $6\Omega$  are in series, so effective resistance is  $12\Omega$  which is in parallel with  $3\Omega$ , so

$$\frac{1}{R} = \frac{1}{3} + \frac{1}{12} = \frac{15}{36}$$

$$\Rightarrow R = \frac{36}{15}$$

$$\therefore I = \frac{V}{R} = \frac{4.8 \times 15}{36} = 2A$$

240 (a)

Let  $R_0$  = resistance of filament at room temperature

$R_t$  = resistance of filament at  $2500^\circ\text{C}$

Similarly powers,  $P_0$  and  $P_t$ .

Here, voltage remains the same.

$$P_0 = \frac{V^2}{R_0}$$

$$\text{or } R_0 = \frac{V^2}{P_0}, \quad R_t = \frac{V^2}{P_t}$$

$$\text{also } R_t = R_0 [1 + \alpha(2500 - 20)]$$

$$\text{and } P_0 = P_t [1 + \alpha(2500 - 20)] \\ = 50 [1 + 4.5 \times 10^{-3} (2500 - 20)] \\ = 608W$$

241 (a)


Each part will have a resistance  $r = R/10$

Let equivalent resistance be  $r_R$ , then

$$\frac{1}{r_R} = \frac{1}{r} + \frac{1}{r} + \frac{1}{r} \dots \dots 10 \text{ times}$$

$$\therefore \frac{1}{r_R} = \frac{10}{r} = \frac{10}{R/10} = \frac{100}{R} \Rightarrow r_R = \frac{R}{100} = 0.01R$$

242 (c)

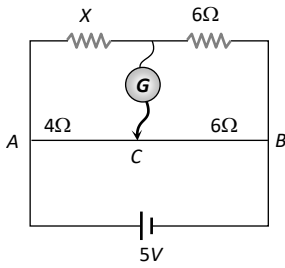

Resistance of the part AC

$$R_{AC} = 0.1 \times 40 = 4\Omega \text{ and } R_{CB} = 0.1 \times 60 = 6\Omega$$

$$\text{In balanced condition } \frac{X}{6} = \frac{4}{6} \Rightarrow X = 4\Omega$$

Equivalent resistance  $R_{eq} = 5\Omega$  so current drawn from battery

$$i = \frac{5}{5} = 1A$$

244 (c)

$$i = ev = 1.6 \times 10^{-19} \times 6.8 \times 10^{15} = 1.1 \times 10^{-3} \text{ amp}$$

245 (b)

$$v_d = \frac{i}{ne\pi r^2} \Rightarrow v_d \propto \frac{i}{r^2} \Rightarrow \frac{v}{v'} = \frac{i_1}{i_2} \times \left(\frac{r_2}{r_1}\right)^2 \Rightarrow v' = \frac{v}{2}$$

246 (b)

$$m = z = \frac{E}{F} It = \frac{(M/P)}{F} It$$

$$\text{or } t = \frac{mF_P}{MI} = \frac{(0.254 \times 10^3) \times 96500 \times 2}{63.5 \times 100} = 7720 \text{ s.}$$

247 (b)

In series, current,

$$i_1 = \frac{2E}{2 + 2r}$$

In parallel, current,


$$i_2 = \frac{E}{2 + \frac{r}{2}} = \frac{2E}{4 + r}$$

According to the question

$$\begin{aligned} i_1 &= i_2 \\ \Rightarrow \frac{2E}{4 + r} &= \frac{2E}{2 + 2r} \\ \Rightarrow r &= 2\Omega \end{aligned}$$

248 (d)

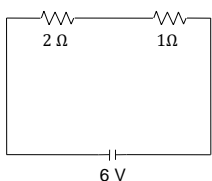In the given circuit  $4\Omega$  resistors are connected in parallel, this combination is connected in series with  $1\Omega$  resistance.



$$\therefore \frac{1}{R'} = \frac{1}{4} + \frac{1}{4} = \frac{2}{4} = \frac{1}{2}$$

$$\Rightarrow R' = 2\Omega$$

$$\text{Also, } R'' = 2\Omega + 1\Omega = 3\Omega$$

From Ohm's law,  $V = iR$

$$\therefore i = \frac{V}{R} = \frac{6}{3} = 2A$$

249 (b)

$$\text{Heat produced by heater per second} = 1.08 \times 10^3 \text{ J}$$

Heat taken by water to form steam  $mL$

$$= 100 \times 540 \text{ cal}$$

$$= 100 \times 540 \times 4.2 \text{ J}$$

$$\therefore 1.08 \times 10^3 \times t = 100 \times 540 \times 4.2$$

$$\text{or } t = \frac{100 \times 540 \times 4.2}{1.08 \times 10^3} = 210 \text{ s}$$

250 (d)

Heat developed by 210 W electric bulb in 5 min is given by

$$H = \frac{W}{J} = \frac{210 \times 5 \times 60}{4.2} = 15000 \text{ cal}$$

251 (d)

$$\text{Equivalent resistance} = \frac{4 \times 4}{4 + 4} + \frac{6 \times 6}{6 + 6} = 5 \text{ ohm}$$

So the current in the circuit =  $\frac{20}{5} = 4 \text{ ampere}$

Hence the current flowing through each resistance =

$2 \text{ ampere}$

252 (d)

Here,  $2\Omega$  and  $2\Omega$  are in parallel

$$\therefore \frac{1}{R} = \frac{1}{2} + \frac{1}{2}$$

$$R = \frac{2 \times 2}{2 + 2} = 1\Omega$$

Now, internal resistance ( $1\Omega$ ),  $2\Omega$ ,  $4\Omega$  and resistance  $R$  in series.

$$\therefore R_{\text{net}} = 1\Omega + 2\Omega + 4\Omega + 1\Omega = 8\Omega$$

Hence, current

$$I = \frac{V}{R} = \frac{4}{8} = 0.5A$$

253 (d)

The given circuit is a balanced wheatstone bridge circuit. Hence potential difference between A and B is zero

254 (d)

$$P = \frac{V^2}{R} \text{ but } R = \frac{\rho l}{A} \Rightarrow P = \frac{V^2}{\rho l / A} = \frac{AV^2}{\rho l}. \text{ Since } \frac{AV^2}{l} \text{ is constant as per given condition so } P \propto \frac{1}{\rho}$$

255 (d)

Current in  $9\Omega$  is  $2A$ , so that in  $6\Omega$  is  $3A$ . Total current is  $2 + 3 = 5A$ . Potential drop  $5 \times 2 = 10V$

256 (c)

$$H = \frac{V^2}{R}$$

$$\Rightarrow R = \frac{V^2}{H}$$

$$= \frac{(25)^2}{25} = 25 \Omega$$

257 (c)

If a cell is connected between points *A* and *C*, no current will flow in arms *BE* and *ED*. Therefore, the resistance of arms *BE* and *ED* can be removed. Now resistance between points *A* and *C* will be the resistance of three parallel arms, each of resistance =  $R + R = 2R$

$\therefore$  Total resistance  $R_p$  will be

$$\frac{1}{R_p} = \frac{1}{2R} + \frac{1}{2R} + \frac{1}{2R} = \frac{3}{2R} \text{ or } R_p = \frac{2R}{3}$$

258 (c)

$$I \propto Q$$

$$\frac{I_g}{I} = \frac{1}{2}$$

$$\frac{S}{G + S} = \frac{1}{2}$$

$$\frac{40}{G + 40} = \frac{1}{2} \Rightarrow G = 40 \Omega$$

259 (d)

The resistance of the cell is independent of *e.m.f*

260 (d)

In the given circuit the resistors of  $2\Omega$  and  $3\Omega$  are connected in parallel hence, equivalent resistance is


$$\frac{1}{R'} = \frac{1}{2} + \frac{1}{3} = \frac{5}{6}$$

$$\therefore R' = \frac{6}{5} \Omega$$

Also in steady state, the circuit is shown as.

Resistor's of

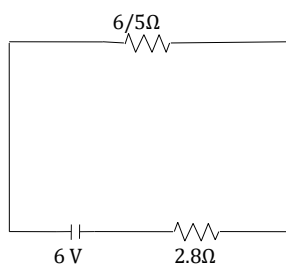$\frac{6}{5} \Omega$  and  $2.8\Omega$  are connected in series.



$$\text{Hence, } R'' = \frac{6}{5} \Omega + 2.8\Omega$$


$$= 1.2\Omega + 2.8\Omega = 4.0\Omega$$

From Ohm's law,

$$\text{Current } i = \frac{V}{R} = \frac{6}{4.0} = 1.5A$$

261 (c)

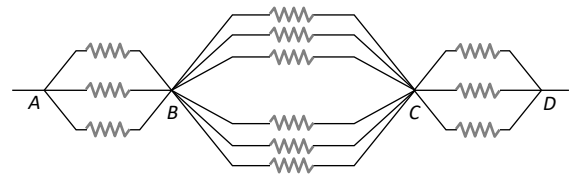The given circuit can be simplified as follows



$$\therefore R_{AD} = \frac{5R}{6}$$

262 (a)

Specific resistance is independent of dimensions of conductor but depends on nature of conductor.

263 (a)

Here three resistance of  $4\Omega$  each are connected in parallel so that their combined resistance =  $\frac{4}{3}\Omega$ . It is in series with ammeter, battery and last  $4\Omega$  resistance.

$$\therefore \text{Net resistances } R = \frac{4}{3} + 4 = \frac{16}{3} \Omega$$

$\therefore$  Current in main circuit = ammeter reading

$$i = \frac{E}{R} = \frac{2V}{\frac{16}{3}\Omega} = \frac{3}{8} A$$

264 (d)


Slope of  $V - i$  curve = resistance. Hence  $R = \frac{1}{1} = 1\Omega$

265 (c)

When rod is bent in the form of square, then each side has resistance of

$\frac{1}{4}\Omega$ . As shown  $R_1, R_2$  and  $R_3$  are connected in

series, so their equivalent resistance

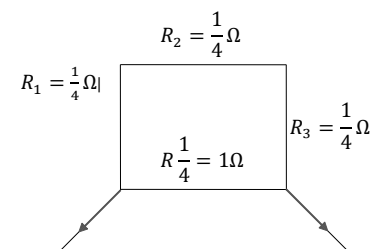

$$R' = R_1 + R_2 + R_3$$

$$= \frac{1}{4} + \frac{1}{4} + \frac{1}{4} = \frac{3}{4} \Omega$$

Now,  $R'$  and  $R_4$  are connected in parallel, so equivalent resistance of the circuit is

$$R = \frac{R' \times R_4}{R' + R_4}$$

$$= \frac{\left(\frac{3}{4}\right) \left(\frac{1}{4}\right)}{\left(\frac{3}{4}\right) + \left(\frac{1}{4}\right)}$$


$$= \frac{\left(\frac{3}{16}\right)}{1} = \frac{3}{16} \Omega$$

266 (a)

$$F = Ne = 6 \times 10^{23} \times 1.6 \times 10^{-19}$$

267 (d)

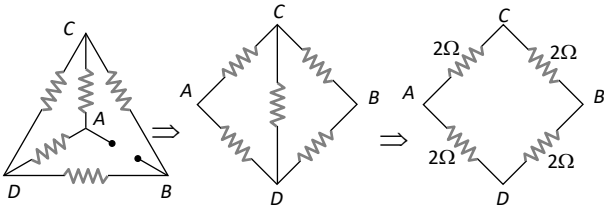The equivalent circuits are as shown below



Clearly, the circuit is a balanced Wheatstone bridge. So effective resistance between A and B is  $2\Omega$

268 (a)

$$T_n = \frac{T_i + T_c}{2}$$

$$T_i = 2T_n - T_c = 540^\circ\text{C}$$

270 (d)

The last two resistances are out of circuit. Now  $8\Omega$  is in parallel with  $(1 + 1 + 4 + 1 + 1)\Omega$


$$\therefore R = 8\Omega \parallel 8\Omega = \frac{8}{2} = 4\Omega \Rightarrow R_{AB} = 4 + 2 + 2 = 8\Omega$$

271 (c)

As  $3\Omega$  and  $6\Omega$  resistances are

In parallel their equivalent resistance will be  $2\Omega$ .

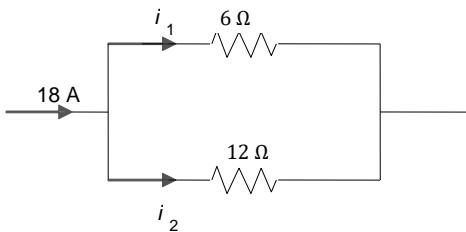
Here  $2\Omega$  and  $4\Omega$  are in series, their equivalent resistance will be  $6\Omega$ . From current distribution law



$$i_1 = \frac{12 \times 18}{18} = 12A$$

$$i_2 = \frac{6 \times 18}{18} = 6A$$

$3\Omega$

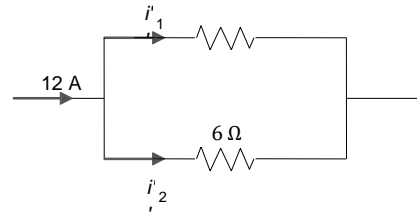

Now,  $12A$  current is entering in parallel combination of  $3\Omega$  and  $6\Omega$  again from current distribution law

$$i'_1 = \frac{6 \times 12}{9} = 8A$$

$$i'_2 = \frac{3 \times 12}{9} = 4A.$$

$\therefore$  Potential difference across  $3\Omega$  resistance  $= 8 \times 3 = 24V$


272 (a)

$$R = \rho \frac{l}{A} = \frac{m}{ne^2\tau} \cdot \frac{l}{A}$$

273 (d)

Let  $x$  is the resistance per unit length then

Equivalent resistance

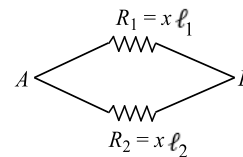

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$\Rightarrow \frac{8}{3} = \frac{(x\ell_1)(x\ell_2)}{x\ell_1 + x\ell_2} \Rightarrow \frac{8}{3} = x \frac{\ell_1 \ell_2}{\ell_1 + \ell_2}$$

$$\Rightarrow \frac{8}{3} = x \frac{\ell_1}{\frac{\ell_1}{\ell_2} + 1} \dots (i)$$

$$\text{Also } R_0 = x\ell_1 + x\ell_2 \Rightarrow 12 = x(\ell_1 + \ell_2)$$

$$\Rightarrow 12 = x\ell_2 \left( \frac{\ell_1}{\ell_2} + 1 \right) \dots (ii)$$

Dividing eq. (i) by eq. (ii)

$$\frac{\frac{8}{3}}{\frac{12}{1}} = \frac{\frac{x\ell_1}{\left(\frac{\ell_1}{\ell_2} + 1\right)}}{x\ell_2 \left(\frac{\ell_1}{\ell_2} + 1\right)} = \frac{\ell_1}{\ell_2 \left(\frac{\ell_1}{\ell_2} + 1\right)^2}$$

$$\Rightarrow \left(\frac{\ell_1}{\ell_2} + 1\right)^2 \times \frac{8}{36} = \frac{\ell_1}{\ell_2}$$

$$\Rightarrow (y^2 + 1 + 2y) \times \frac{8}{36} = y \quad [\text{Where } y = \frac{\ell_1}{\ell_2}]$$

$$\Rightarrow 8y^2 + 8 + 16y = 36y$$

$$\Rightarrow 8y^2 - 20y + 8 = 0$$

On solving, we get  $y = \frac{1}{2}$  or  $2$


$$\therefore y = \frac{\ell_1}{\ell_2} = \frac{1}{2} \text{ or } 2$$

274 (a)

Internal resistance,

$$r = R \left( \frac{l_1 - l_2}{l_2} \right) = 1 \left( \frac{540 - 500}{500} \right) = \frac{40}{500} = 0.08 \Omega$$

275 (b)

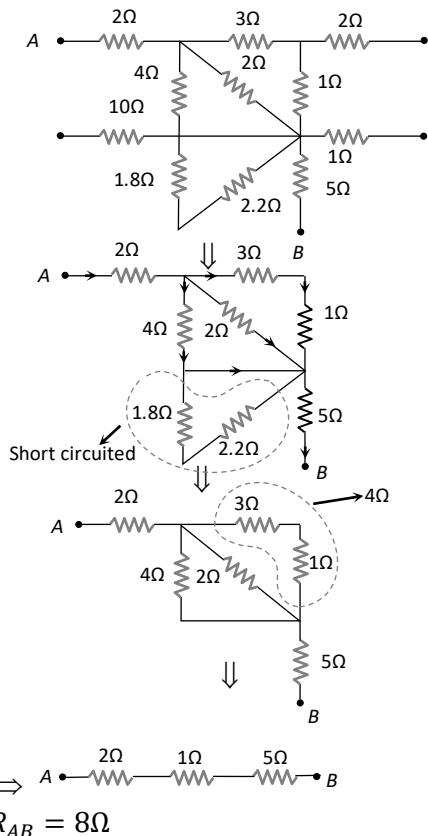

276 (c)

$$P \times t = ms \Delta t$$

$$\Rightarrow 2.1 \times 10^3 \times t$$

$$= 1.5 \times 4200 \times [(100 + 273) - (20 + 273)]$$

$$\Rightarrow = \frac{1.5 \times 4200 \times 80}{2.1 \times 10^3} = 240s$$

277 (a)

In potentiometer experiment in which we find internal resistance of a cell, let  $E$  be the emf of the cell and  $V$  the terminal potential difference, then

$$\frac{E}{V} = \frac{l_1}{l_2}$$

Where  $l_1$  and  $l_2$  are lengths of potentiometer wire with and without short circuited through a resistance.

Since,

$$\frac{E}{V} = \frac{R + r}{R} \quad [\because E = I(R + r) \text{ and } V = IR]$$

$$\therefore \frac{R + r}{R} = \frac{l_1}{l_2}$$

$$\text{or } 1 + \frac{r}{R} = \frac{110}{100} \text{ or } \frac{r}{R} = \frac{10}{100}$$

$$\text{or } r = \frac{1}{10} \times 10 = 1\Omega$$

279 (a)

Resistivity of a material is its intrinsic property and is constant at particular temperature.

Resistivity does not depend upon shape

280 (b)

Here internal resistance is given by the slope of graph

$$i. e. \frac{x}{y}. \text{ But conductance} = \frac{1}{\text{Resistance}} = \frac{y}{x}$$


281 (c)

No change in neutral temperature but temperature of inversion is

$$t_i = 2t_n - t_c \Rightarrow t_i = 2 \times 270 - 40 = 500^\circ\text{C}$$

282 (b)
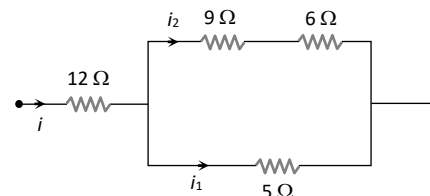
$$\frac{i_1}{i_2} = \frac{15}{5} = \frac{3}{1} \dots (i)$$



$$\text{Also } \frac{H}{t} = i^2 R \Rightarrow 45 = (i_1)^2 \times 5$$

$$\Rightarrow i_1 = 3 \text{ A and from equation (i) } i_2 = 1 \text{ A}$$

$$\text{So } i = i_1 + i_2 = 4 \text{ A}$$

Hence power developed in  $12 \Omega$  resistance

$$P = i^2 R = (4)^2 \times 12 = 192W$$


283 (c)

$$K = \frac{I}{\tan \theta} = \frac{2/\sqrt{3}}{\tan 60^\circ} = \frac{2}{3} \text{ A}$$

284 (d)

$$i = \frac{2E}{R + R_1 + R_2}$$
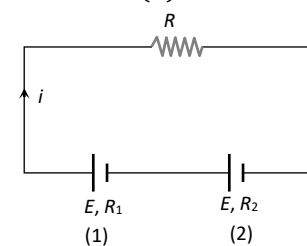
$$\text{From cell (2) } E = V + iR_2 = 0 + iR_2$$



$$\Rightarrow E = \frac{2E}{R + R_1 + R_2} \times R_2 \Rightarrow R = R_2 - R_1$$

285 (a)

Temperature coefficient of a semiconductor is negative

286 (d)

$$E = i_1(R_1 + r) = i_2(R_2 + r)$$

$$\text{On solving, } r = \frac{i_2 R_2 - i_1 R_1}{(i_1 - i_2)}$$

288 (c)

The circuit consists of three resistances ( $2R$ ,  $2R$  and  $R$ ) connected in parallel

289 (c)

Here resistances  $4 \Omega$ ,  $6\Omega$ ,  $12\Omega$  and  $24 \Omega$  are in

parallel. Their effective resistances,  $R_p$  will be

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{6} + \frac{1}{12} + \frac{1}{24}$$

$$= \frac{6 + 4 + 2 + 1}{24} = \frac{13}{24} \text{ or } R_p = \frac{24}{13}$$

Total resistance between A and B


$$= 3 + \frac{24}{13} + 5 = \frac{128}{13} = 9.85 \Omega$$

290 (d)

The current density of electrons in a metallic conductor =  $10^{22} \text{ cm}^{-3} = 10^{28} \text{ m}^{-3}$

291 (c)

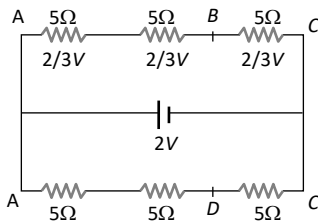The given circuit can be redrawn as follows



For identical resistance, potential difference distributes equally among all. Hence potential difference across each resistance is  $\frac{2}{3}V$ , and potential difference between A and B is  $\frac{4}{3}V$

292 (b)


Here, potential gradient,  $K = 10V\text{m}^{-1}$ ;

Potential difference across length  $l = Kl$

$$= 10 \times 0.5 = 5V$$

293 (d)

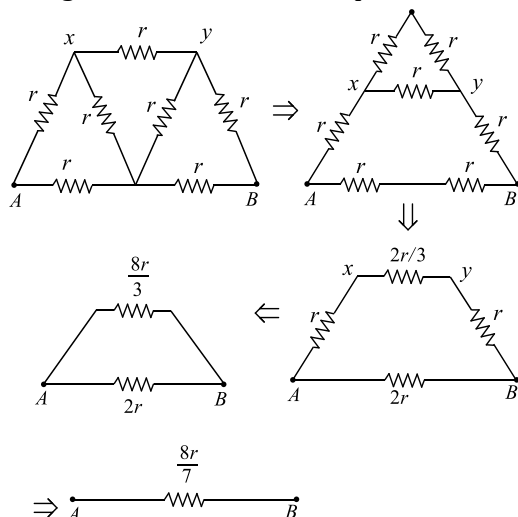The given circuit can be simplified as follows



294 (d)

$$R_{\text{total}} = 2 + \frac{6 \times 1.5}{6 + 1.5} = 3.2k\Omega$$

$$(a) I = \frac{24V}{3.2k\Omega} = 7.5\text{mA} = I_{R_1}$$

$$I_{R_2} = \left( \frac{R_L}{R_L + R_2} \right) I$$

$$I = \frac{1.5}{7.5} \times 7.5 = 1.5\text{mA}$$

$$I_{R_L} = 6\text{mA}$$

$$(b) V_{R_L} = (I_{R_L})(R_L) = 9V$$

$$(c) \frac{P_{R_1}}{P_{R_2}} = \frac{(I_{R_1}^2)R_1}{(I_{R_2}^2)R_2} = \frac{(7.5)^2(2)}{(1.5)^2(6)} = \frac{25}{3}$$

(d) When  $R_1$  and  $R_2$  are interchanged, then

$$\frac{R_2 R_L}{R_2 + R_L} = \frac{2 \times 1.5}{3.5} = \frac{6}{7}k\Omega$$

Now potential difference across  $R_L$  will be

$$V_L = 24 \left[ \frac{\frac{6}{7}}{6 + \frac{6}{7}} \right] 3V$$

Earlier it was 9V

Since,  $P = \frac{V^2}{R}$  or  $P \propto V^2$

In new situation potential difference has been decreased three times. Therefore, power dissipated will decrease by a factor of 9.

295 (b)

Mass of copper deposited,

$m = \text{volume} \times \text{density}$

$= (\text{area} \times \text{thickness}) \times \text{density}$

$$= [2 \times (12 \times 3) \times 0.002] \times 8.9 \text{ g}$$

$$t = \frac{m}{zI} = \frac{[2(12 \times 3) \times 0.002 \times 8.91]}{33 \times 10^{-5} \times 5} = 776\text{s.}$$

296 (c)

Suppose  $n$  resistors are used for the required job.

Suppose equivalent resistance of the combination is  $R'$  and according to energy conservation it's

current rating is  $i'$

Energy consumed by the combination =  $n \times$

(Energy consumed by each resistance)

$$\Rightarrow i'^2 R' = n \times i^2 R \Rightarrow n = \left( \frac{i'}{i} \right)^2 \times \left( \frac{R'}{R} \right)$$

$$= \left( \frac{4}{1} \right)^2 \times \left( \frac{5}{10} \right) = 8$$

297 (b)

$$i = \frac{24-12}{3} = 4 \text{ A, Time of charging } t = \frac{360}{V.i}$$

$$\Rightarrow t = \frac{360}{12 \times 4} = 7.5 \text{ hours}$$


298 (c)

Let  $V$  be the potential at C

Using Kirchhoff's first law  $i_1 + i_2 = i_3$

$$\frac{10 - V}{4} + \frac{5 - V}{2} = \frac{V - 0}{2}$$

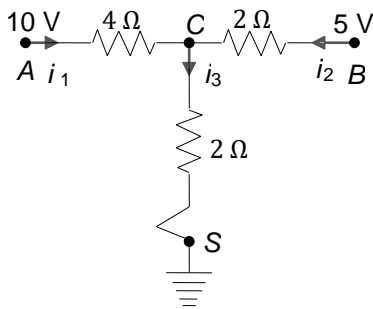On solving,  $V = 4$  Volt,  $i_3 = \frac{V}{2} = \frac{4}{2} = 2A$



299 (c)

$m = zlt$ ; so  $9 = z \times 10^5$  or  $z = 9/10^5 \text{ g } C^{-1}$   
 $m = zlt = (9 \times 10^5) \times 50 \times (20 \times 60) = 5.4 \text{ g.}$

300 (a)

Potential gradient =  $\frac{\text{Potential difference}}{\text{Length}}$

301 (d)

Charge supplied per minute =  $3.2 \times 60 = 192 \text{ C}$

Charge  $2e$  liberates one  $Cu^{+2}$  ion

$\therefore$  No of  $Cu^{+2}$  ion liberate by 192 C


$$= \frac{192}{2e} = \frac{192}{2 \times 1.6 \times 10^{-19}} = 6 \times 10^{20}$$

302 (a)

$$R = \frac{\rho l}{A} = 50 \times 10^{-8} \times \frac{50 \times 10^{-2}}{(50 \times 10^{-2})^2} = 10^{-6} \Omega$$

303 (b)

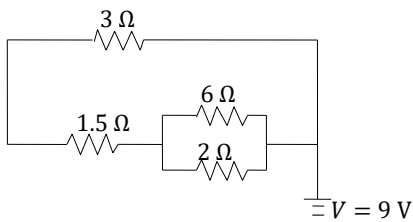The equivalent circuit of the given circuit is as shown



Resistances  $6\Omega$  and  $2\Omega$  are in parallel

$$\therefore R' = \frac{6 \times 2}{6 + 2} = \frac{3}{2} \Omega$$

Resistances  $\frac{3}{2}\Omega$  and  $1.5\Omega$  are in series

$$\therefore R'' = \frac{3}{2} + 1.5 = 3\Omega$$

Resistances  $3\Omega$  and  $3\Omega$  are in parallel


$$\therefore R = \frac{3 \times 3}{3 + 3} = \frac{3}{2}$$

The current,  $I = \frac{V}{R}$

$$= \frac{9}{3/2} = 6A$$

304 (d)

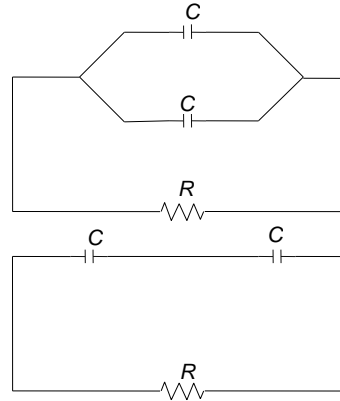If  $C_e$  be the effective capacitance, then



$$V_C = \frac{1}{2} V_0$$

$$\frac{q}{C_e} = \frac{q_0}{2C_e}$$

$$\Rightarrow q_0 \left(1 - e^{-\frac{t}{RC_e}}\right) = \frac{q_0}{2}$$

$$\Rightarrow t = RC_e \ln 2$$

For parallel grouping

$$C_e = \frac{2C}{2}$$

$$\therefore t_2 = 2RC \ln 2$$

For series grouping

$$C_e = \frac{C}{2}$$

$$t_1 = \frac{RC}{2} \ln 2$$

$$\frac{t_2}{t_1} = \frac{1}{4} t_2 = 2.5s$$

305 (b)

Resistance of combination  $R_e = 4R$

$$\frac{\Delta R_e}{R_e} = \frac{\Delta R}{R}$$

$$= \frac{5 \times 100}{100} = 5\%$$

306 (c)


Since  $H \propto i^2$ , so on doubling the current, the heat produced and hence the rise in temperature becomes four times

307 (b)

The given circuit can be redrawn as

$$\frac{i_1}{i_2} = \frac{9}{18} = \frac{1}{2}$$

and  $i = i_1 + i_2$

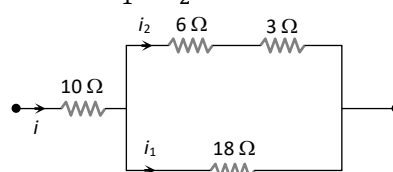

$$\Rightarrow \frac{i}{i_1} = 1 + \frac{i_2}{i_1} = 1 + 2 = 3$$



$$\text{From } P = i^2 R \Rightarrow \frac{P_{10\Omega}}{P_{18\Omega}} = \left(\frac{i}{i_1}\right)^2 \times \frac{10}{18} \Rightarrow P_{10\Omega} = 10W$$

308 (b)

$$t_n = \frac{\alpha}{\beta} = \left(\frac{500}{5}\right) = 100^\circ\text{C}$$

$$\text{Also } t_n = \frac{t_i + t_c}{2} \Rightarrow 100 = \frac{t_i + 0}{2} \Rightarrow t_i = 200^\circ\text{C}$$

309 (a)

According to Seebeck effect

310 (a)

$$R = \rho \frac{l}{A} \text{ and mass } m = \text{volume } (V) \times$$

$$\text{density}(d) = (A l)d$$

Since wires have same material so  $\rho$  and  $d$  is same for both

$$\text{Also they have same mass } \Rightarrow Al = \text{constant} \Rightarrow l \propto \frac{1}{A}$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{l_1}{l_2} \times \frac{A_2}{A_1} = \left(\frac{A_2}{A_1}\right)^2 = \left(\frac{r_2}{r_1}\right)^4$$

$$\Rightarrow \frac{34}{R_2} = \left(\frac{r}{2r}\right)^4 \Rightarrow R_2 = 544 \Omega$$

311 (a)

$$\text{Resistance of a bulb} = \frac{(\text{Rated voltage})^2}{\text{Rated power}}$$

$$\text{For a given voltage, } R \propto \frac{1}{P}$$

$$\therefore R_{40} > R_{60} > R_{100}$$

$$\text{Rate of heat produced, } H = I^2 R$$


When the bulbs are connected in series, the current flowing through each bulb is same

$$\therefore H \propto R. \text{ As } R_{40} > R_{60} > R_{100}$$

$$\therefore H_{40} > H_{60} > H_{100} \Rightarrow B_1 > B_2 > B_3$$

312 (c)
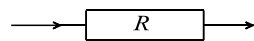
$$\text{Resistance of the slab} = \rho \frac{l}{A} \text{ where}$$



The potential across  $R$  is  $I \times R = V$

The length of the slab is doubled. Therefore the resistance is  $2R$ . Assuming that the same current is passed, the potential across the new resistance is  $l \times 2R = 2V$

313 (a)

The emf of the circuit is

$$E = E_1 + E_2 \\ = 4V + 2V = 6V$$

In the given circuit,  $3\Omega$  and  $6\Omega$  are connected in parallel, hence equivalent resistance is

$$\frac{1}{R'} = \frac{1}{3} + \frac{1}{6} = \frac{3}{6} = \frac{1}{2}$$

$$\Rightarrow R' = 2\Omega$$

Total resistance of circuit is

$$R = 1\Omega + 1\Omega + 2\Omega = 6\Omega$$

From Ohm's law  $V = iR$

$$\Rightarrow i = \frac{V}{R} = \frac{6}{6} = 1A$$

The  $3\Omega$  and  $6\Omega$  resistors are in parallel, hence

$$i_1 R_1 = i_2 R_2 = V$$

$$\therefore i_1 \times 3 = i_2 \times 6$$

$$\Rightarrow i_1 = 2i_2 \text{ and } i_1 + i_2 = 1$$

$$2i_2 + i_2 = 1$$


$$3i_2 = 1 \Rightarrow i_2 = \frac{1}{3}A$$

314 (a)

Kirchhoff's first law is based on the law of conservation of charge

315 (c)

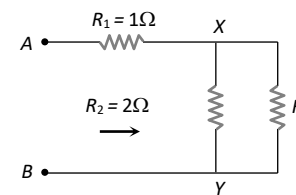Let the resultant resistance be  $R$ . If we add one more branch, then the resultant resistance would be the same because this is an infinite sequence



$$\therefore \frac{RR_2}{R + R_2} + R_1 = R \Rightarrow 2R + R + 2 = R^2 + 2R$$

$$\Rightarrow R^2 - R - 2 = 0 \Rightarrow R = -1 \text{ or } R = 2\text{ohm}$$

$$R = 2 + 2 + \frac{2 \times R}{2 + R} \Rightarrow 2R + R^2 = 8 + 4R + 2R$$

$$\Rightarrow R^2 - 4R - 8 = 0 \Rightarrow R = \frac{4 \pm \sqrt{16 + 32}}{2}$$

$$= 2 \pm 2\sqrt{3}$$

$R$  cannot be negative, hence  $R = 2 + 2\sqrt{3} = 5.46\Omega$

316 (a)

Here, all resistance are in parallel.

$$\therefore \Delta H = \frac{V^2}{R} t$$

$$\therefore \Delta H \propto \frac{1}{R}$$

Hence, (a) is correct.

318 (b)

Current,  $i = \frac{E}{R+r}$  when  $R$  decreases to 0,  $i = \frac{E}{r}$ .

Similarly, potential difference  $V = iR$  when  $R$  decreases to 0,

$$V = 0.$$

319 (b)

Kirchhoff's second law is based on the law of conservation of energy

320 (b)

Thermo-electric power  $P = \frac{dE}{d\theta}$ ; at  $t_n$ ,  $E \rightarrow$

maximum

So  $P \rightarrow$  zero

321 (a)

Heat produced  $H = \frac{V^2 t}{4.2R} = H \propto \frac{1}{R}$  Hence  $\frac{H_1}{H_2} = \frac{R_2}{R_1}$

322 (c)

$$\frac{H}{t} = P = \frac{V^2}{R} \Rightarrow P \propto \frac{1}{R} \text{ also } R \propto \frac{1}{A} \propto \frac{l^2 \rho}{A \cdot l \rho}$$

$$\Rightarrow R \propto \frac{l^2}{m} \Rightarrow R \propto l^2 \text{ [for same mass]}$$

$$\text{So } \frac{P_A}{P_B} = \frac{l_B^2}{l_A^2} = \frac{4}{1} \Rightarrow P_A = 20W$$

323 (d)

$$m_{Ag} = m_{Cu} \times E_{Ag}/E_{Cu} \\ = 2 \times 108 / (63.6/2) = 6.8 \text{ mg.}$$

324 (a)

$$\text{At neutral temperature, } \frac{dE}{dT} = 0$$

325 (a)

$$V_A - V_B = \text{emf of the cell} = 2V \\ \therefore U = \frac{1}{2} CV^2 = \frac{1}{2} \times 2 \times 10^{-6} \times (2)^2 = 4 \times 10^{-6} \text{ J}$$

326 (a)

The temperature of the wire increases to such a value at which, the heat produced per second equals heat lost per second due to radiation *ie*,  $I^2 \left( \frac{\rho l}{\pi r^2} \right) = H \times 2\pi r l$ , where *H* is heat lost per second per unit area due to radiation.

$$\text{Hence, } I^2 \propto r^3$$

$$\text{So } \frac{l_1^2}{l_2^2} = \frac{r_1^3}{r_2^3} \text{ or } r_2 = r_1 (I_2/I_1)^{2/3} \\ = 1 \times (3.0/1.5)^{2/3} = 4^{1/3} \text{ mm.}$$


327 (d)

$$\text{Charge} = \text{Current} \times \text{Time} = 5 \times 60 = 300 \text{ C}$$

328 (d)

$$\text{Resistance, } R = \frac{V}{i} = \cot 40^\circ$$

329 (a)

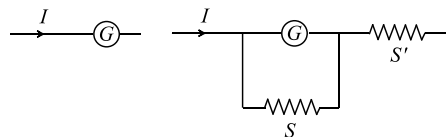

$$G = \left( \frac{GS}{G+S} \right) + S''$$

$$G - \frac{GS}{G+S} = S'' \therefore S'' = \frac{G^2}{G+S}$$

330 (c)

$$E - V = ir \text{ or } r = (E - V)/i$$

$$\text{and } V = iR = 4.5 \times 10 = 45V$$

$$\therefore r = \frac{(50 - 45)}{4.5} = \frac{5}{4.5}$$

$$= 1.10 \Omega$$

331 (a)

$\frac{R_1}{R_2} = \frac{P_2}{P_1} = \frac{100}{40} = \frac{5}{2}$ . Resistance of 40 W bulb is  $\frac{5}{2}$  times than 100 W. In series,  $P = i^2 R$  and in parallel,  $P = \frac{V^2}{R}$ . So 40 W in series and 100 W in parallel will glow brighter

332 (a)

A particular temperature, the resistance of a superconductor is zero

$$\Rightarrow G = \frac{1}{R} = \frac{1}{0} = \infty$$

333 (b)

$$\text{In series, } i_1 = \frac{2E}{2+2r}$$

$$\text{In parallel, } i_2 = \frac{E}{2+r} = \frac{2E}{4+r}$$

$$\text{Since } i_1 = i_2 \Rightarrow \frac{2E}{4+r} = \frac{2E}{2+2r} \Rightarrow r = 2\Omega$$

334 (b)

The amount of decomposition (*ie*, mass of the substance liberated during electrolysis) is proportional to ECE of the substance.

335 (a)


$$\text{In series, } i = \frac{3 \times 2}{3r+2} \dots \text{(i)}$$

$$\text{In parallel, } i = \frac{2}{r/3+2} = \frac{2 \times 3}{r+2 \times 3} \dots \text{(ii)}$$

$$\text{From Eqs. (i) and (ii), } 3r + 2 = r + 6 \text{ or } r = 2\Omega$$

$$\text{From eqs. (i), } i = \frac{3 \times 2}{3 \times 2 + 2} = 0.75A$$

336 (c)

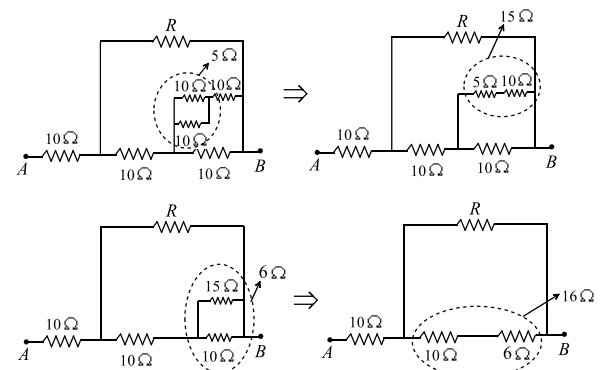

$$\therefore \frac{R \times 16}{R+16} + 10 = 18, \text{ on solving we get, } R = 16\Omega$$

337 (a)

When wire is stretched to doubled its length, its resistance becomes four times

338 (d)

$$\text{Current in wire } i = Anev_d$$

$$\text{Here, } i = 1A, n = 8 \times 10^{28} \text{ electron/m}^{-3}$$

$$A = 5 \times 10^{-7} \text{ m}^2$$

$$\therefore 1 = 8 \times 10^{28} \times 1.6 \times 10^{-19} \times 5 \times 10^{-7} \times v_d$$

$$\text{or } v_d = \frac{1}{8 \times 10^{28} \times 1.6 \times 10^{-19} \times 5 \times 10^{-7}}$$

Now,

$$t = \frac{1}{v_d} = 8 \times 10^{28} \times 1.6 \times 10^{-19} \times 5 \times 10^{-7}$$

$$= 64 \times 10^2 = 6.4 \times 10^3 \text{ s}$$

339 (c)

Voltmeter is an instrument which measure the potential difference between two points. A high resistance is connected in series with coil of the galvanometer to convert it into voltmeter. This resistance is either  $2000\Omega$  or more than that.

Resistance connected in series is given by

$$R = \frac{V}{I_g} - G \quad \dots (i)$$

Eq. (i) is the value of the resistance required to convert the galvanometer to voltmeter of range 0 to  $V$ .

From the relation

$$R = \frac{V}{I_g} - G$$

$$R = \frac{nV}{\left(\frac{V}{G}\right)} - G$$

$$\text{or } R = nG - G = G(n - 1)$$

$$\text{Hence, } R = (n - 1) G$$

340 (c)

We will require a voltmeter, an ammeter, a test resistor and a variable battery to verify Ohm's law.

Voltmeter which is made by connecting a high resistance with a galvanometer is connected in parallel with the test resistor.

Further, an ammeter which is formed by connecting a low resistance in parallel with galvanometer is required to measure the current through test resistor.

The correct option is (c).

341 (d)

A galvanometer can be converted into an ammeter by using a low resistance wire in parallel with the galvanometer. The range of ammeter can be increased but cannot be decreased. The reason is that a series resistor cannot change the current that will produce full deflection.

A shunt connected in parallel is given by

$$S = \frac{I_g G}{I - I_g}$$

If  $I < I_g$ , then the value of  $S$  is negative. Hence, a galvanometer cannot be converted into an ammeter of range  $I < I_g$ .

342 (c)

When current is passed through a junction of two different metals, the heat is either evolved or absorbed at the junction. This effect is known as Peltier effect.


343 (b)

$P_1 = P_2 = 60 \text{ W}$ ; when bulbs are connected in series then total power

$$P_s = \frac{P_1 P_2}{P_1 + P_2} = \frac{60 \times 60}{60 + 60} = 30 \text{ W}$$

344 (a)

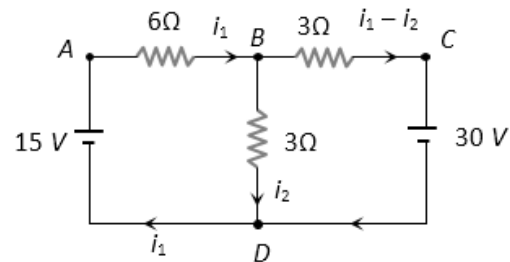The current in the circuit are assumed as shown in the fig.



Applying KVL along the loop  $ABDA$ , we get

$$-6i_1 - 3i_2 + 15 = 0 \text{ or } 2i_1 + i_2 = 5 \quad \dots (i)$$

Applying KVL along the loop  $BCDB$ , we get

$$-3(i_1 - i_2) - 30 + 3i_2 = 0 \text{ or } -i_1 + 2i_2 = 10$$

....(ii)

Solving equation (i) and (ii) for  $i_2$ , we get  $i_2 = 5 \text{ A}$

345 (a)

$E = at + bt^2$ . At temperature of inversion  $E$  is minimum

$$i.e., E = 0$$

$$\therefore at_i + bt_i^2 = 0, i.e., t_1 = -\frac{a}{b}$$

346 (c)

$R \propto \frac{1}{\tau}$ ; where  $\tau$  = Relaxation time

When lamp is switched on, temperature of filament increases, hence  $\tau$  decreases so  $R$  increases

347 (a)

Slope of the  $V - i$  curve at any point equals to resistance at that point. From the curve slope for  $T_1 > \text{slope for } T_2 \Rightarrow R_{T_1} > R_{T_2}$ . Also at higher temperature resistance will be higher so  $T_1 > T_2$

348 (b)

$$dQ = Idt \Rightarrow Q = \int_{t=2}^{t=3} Idt = \left[ 2 \int_2^3 t dt + 3 \int_2^3 t^2 dt \right]$$

$$= [t^2]_2^3 + [t^3]_2^3 = (9 - 4) + (27 - 8) = 5 + 19$$

$$= 24C$$

349 (d)

$$i = \frac{R}{r + R}$$

$$P = i^2 R$$

$$\Rightarrow P = \frac{E^2 R}{(r + R)^2}$$

Power is maximum when  $r=R$

$$\therefore P_{\max} = \frac{E^2}{4R}$$

$$\text{or } P_{\max} = \frac{E^2}{4r}$$

350 (c)

When a resistance of  $100\Omega$  is connected in series current,

$$i = \frac{V}{100 + R} \dots\dots\dots (i)$$

When a resistance of  $1000\Omega$  is connected in series, the its range double

$$\text{Current, } i = \frac{2V}{1100 + R} \dots\dots(ii)$$

From Eqs. (i) and (ii)

$$\frac{V}{100 + R} = \frac{2V}{100 + R}$$

$$R = 900\Omega$$

351 (d)

The rate at which heat is developed

$$H = \frac{V^2}{R} = \frac{(110)^2}{10} = 1210 \text{ W}$$

352 (b)

Shunt of an ammeter,

$$S = \frac{I_g \times G}{I - I_g}$$

$$= \frac{5 \times G}{100 - 5} = \frac{G}{19}$$

353 (b)

$$A = \pi r^2 = \rho l / R \text{ or } r = (\rho l / \pi R)^{1/2}$$

$$r = \left( \frac{1.7 \times 10^{-8} \times 0.5}{3.14 \times 2} \right)^{1/2} = 0.367 \text{ mm}$$

354 (c)

If a charged particle of charge  $q$  revolves in a circular orbit of radius  $r$  with frequency  $\nu$ , then the orbital current is given by

$$I = q\nu$$

$$\text{or } I = q \frac{\omega}{2\pi} \left( \because 2\pi\nu \Rightarrow \nu = \frac{\omega}{2\pi} \right)$$

$$I = \frac{e\nu}{2\pi r} \quad (\because \nu = r\omega)$$

355 (d)

For maximum power  $r = R$

356 (a)


Initially : Resistance of given cable

$$R = \rho \frac{l}{\pi \times (9 \times 10^{-3})^2} \dots(i)$$

Finally : Resistance of each insulated copper wire is

$$R' = \rho \frac{l}{\pi \times (3 \times 10^{-3})^2}. \text{ Hence equivalent resistance of}$$
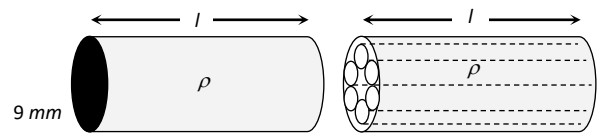
$$\text{cable } R_{eq} = \frac{R'}{6} = \frac{1}{6} \times \left( \rho \frac{l}{\pi \times (3 \times 10^{-3})^2} \right) \dots(ii)$$



on solving equation (i) and (ii), we get  $R_{eq} = 7.5 \Omega$

357 (b)

From the Ohm's law

$$I = \frac{2E}{2r + R}$$

In parallel combination of two cells, the current through the external resistance  $r$  will be


$$I' = \frac{E}{\frac{r}{2} + R} = \frac{2E}{r + 2R}$$

$$\text{If } I = I' \text{ then } 2r + R = r + 2R$$

$$\Rightarrow r = R = 3\Omega$$

358 (a)

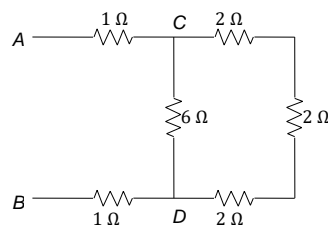Equivalent circuit of the given circuit is



Between points  $C$  and  $D$  resistors  $2\Omega$ ,  $2\Omega$  and  $2\Omega$  are in series, therefore, their equivalent resistance,

$$R' = 2 + 2 + 2 = 6\Omega$$

Resistors  $R'$  and  $6\Omega$  are in parallel, therefore their equivalent resistance is given by

$$\frac{1}{R''} = \frac{1}{6} + \frac{1}{6}$$

$$R'' = 3\Omega$$

Now between points  $A$  and  $B$   $1\Omega$ ,  $3\Omega$  and  $1\Omega$  are in series.

Therefore, resultant resistance is

$$R = 1 + 3 + 1 = 5\Omega$$

359 (b)

$$i = neAv_d \Rightarrow \frac{(v_d)_e}{(v_d)_h} = \frac{i_e}{i_h} \times \frac{n_h}{n_e} = \frac{7}{4} \times \frac{5}{7} = \frac{5}{4}$$

360 (c)

Electroplating only provides a thin deposition of a metal on the surface which in no way can give hardness to the metal

361 (b)

362 (c)

When there is no deflection, then this temperature is called inversion temperature. It is given by the relation

$$\theta_n = \frac{\theta_i + \theta_c}{2}$$

Where  $\theta_c$  is temperature of cold junction =  $20^\circ\text{C}$  and neutral temperature  $\theta_n = 270^\circ\text{C}$   
 $\therefore \theta_i = 2\theta_n - \theta_c = 540 - 20 = 520^\circ\text{C}$

363 (b)

$$\frac{E_1}{E_2} = \frac{l_1}{l_2} \Rightarrow \frac{1.08}{E_2} = \frac{400}{440}$$

$$\Rightarrow E_2 = \frac{440 \times 1.08}{400} = 1.188\text{V.}$$

364 (a)

The relative position of metals in the electro chemical series determines the emf between the two metals placed in an electrolyte.

365 (d)

$$E = \frac{e}{(R + R_h + r)L} \times l$$

$$= \frac{2}{(10 + 40 + 0)} \times \frac{10}{1} \times 0.4$$

$$= 0.16\text{V}$$

366 (b)

$$I = 4 - 0.08t \text{ A}$$

$$\text{Or } \frac{dq}{dt} = 4 - 0.08t \text{ A}$$

$$\text{or } q = \int_0^{50} (4 - 0.08t) dt \text{ C}$$

$$\text{or } Ne = \left[ 4t - \frac{0.08t^2}{2} \right]_0^{50} = 100 \text{ C}$$

Where  $N$  is number of electrons.

370 (c)

Given circuit can be redrawn as follows

$$\text{or } N = \frac{100}{e} = \frac{100}{1.6 \times 10^{-19}}$$

$$= 6.25 \times 10^{20}$$

367 (c)

$$i = \frac{E}{R + r} = \frac{2}{3.9 + 0.1} = 0.5;$$

$$V = E - ir = 2 - 0.5 \times 0.1 = 1.95\text{V}$$

368 (d)


For greater sensitivity of meter bridge the resistance ( $R$ ) taken in the resistance box should be such that the null point is nearly in the middle of the wire. In this position all resistance  $P$ ,  $Q$ ,  $R$  and  $S$  become nearly equal. The emf of cell depends upon the size and area of electrodes.

369 (c)

$$v_d = \frac{I}{nAl} = \frac{1}{nAe} \times \frac{V}{R}$$

$$= \frac{1}{nAe} \times \frac{V}{(\rho l/A)} = \frac{V}{ne\rho l}$$

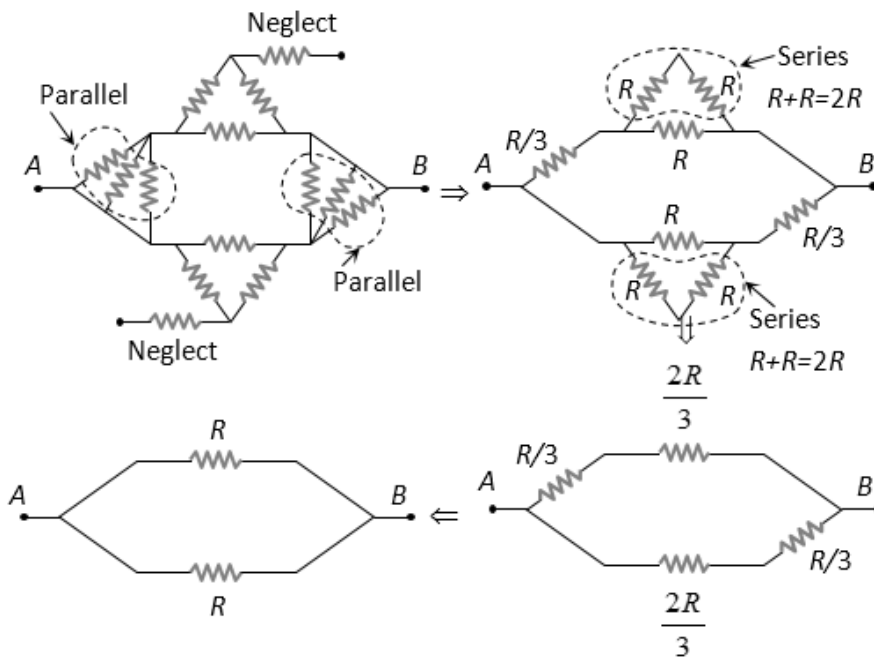As  $v_d$  is independent of area of cross-section hence drift velocity will not change, when diameter is doubled



$$\Rightarrow R_{eq} = \frac{R}{2}$$

371 (c)

By Wheatstone bridge,  $\frac{R}{80} = \frac{AC}{BC} = \frac{20}{80} \Rightarrow R = 20 \Omega$

372 (a)

$$P = \frac{V^2}{R} \Rightarrow P \propto \frac{1}{R} \text{ and } R \propto l$$

$$\therefore P \propto \frac{1}{l} \Rightarrow \frac{P_1}{P_2} = \frac{l_2}{l_1} = \frac{2}{1}$$

373 (a)

It is found that temperature of inversion ( $T_i$ ) is as much above the neutral temperature ( $T_n$ ) as neutral temperature is above the temperature of the cold junction ( $T$ ), i.e.,


$$T_i - T_n = T_n - T \text{ or } T_i = 2T_n - T$$

But, here the cold junction is kept at  $0^\circ\text{C}$ , hence  $T = 0$ .

$$\text{Thus, } T_i = 2T_n \text{ or } T_n = \frac{T_i}{2}$$

374 (b)

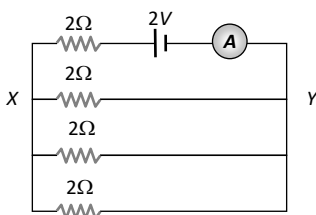Resistance across  $XY = \frac{2}{3} \Omega$



Total resistance

$$= 2 + \frac{2}{3} = \frac{8}{3} \Omega$$

Current through ammeter

$$= \frac{2}{8/3} = \frac{6}{8} = \frac{3}{4} \text{ A}$$

375 (c)

$$R = \frac{12 \times 4}{12 + 4} + 2 = 5 \Omega$$

$$I = \frac{E}{R + r} = \frac{12}{6} = 2 \text{ A}$$

$$I_1 + I_2 = 2 \text{ A}$$

$$I \propto \frac{1}{R}$$

$$\therefore I_1 = 0.5 \text{ A}, I_2 = 1.5 \text{ A}$$

377 (a)

Let the temperature of molten metal is  $t^\circ\text{C}$

The thermo-emf  $e = 10 \times 10^{-6} t \text{ volt}$

$$\text{Current in the circuit } \frac{e}{R + R_G} = \frac{10^{-5} t}{8 + 1.6} = \frac{10^{-5} t}{9.6} \text{ amp}$$

$$\text{But } i = \frac{V}{R_G} = \frac{8 \times 10^{-3}}{8}$$

$$\therefore \frac{10^{-5} t}{9.6} = \frac{8 \times 10^{-3}}{8} \text{ or } t = \frac{9.6 \times 10^{-3}}{10^{-5}} = 960^\circ\text{C}$$

378 (a)

$$P = \frac{V^2}{R}$$

$$\therefore R_{\text{hot}} = \frac{V^2}{P}$$

$$= \frac{200 \times 200}{1000} = 400 \Omega$$

$$R_{\text{cold}} = \frac{400}{10} = 40 \Omega$$

379 (b)

Given,  $E = 2.2 \text{ V}$ ,  $R = 5 \Omega$

$V = 1.8 \text{ V}$ ,  $r = ?$

Now current in the circuit

$$i = \frac{E}{R+r}$$

$$\text{or } \frac{V}{R} = \frac{E}{R+r}$$

$$\frac{1.8}{5} = \frac{2.2}{5+r}$$

$$\text{or } r = \frac{10}{9} \Omega$$

380 (a)

$E_1 E_2 = l_1 / l_2$ . As,  $E_1 / E_2$ , therefore  $l_1 > l_2$ .

Therefore the null point for the cell of emf  $E_2$  must be at shorter length than that of cell  $E_1$ . Thus null point on potentiometer wire should shift towards left of  $C$ .

381 (a)

Current given by cell

$$I = \frac{E}{R+r}$$

Power delivered in first case

$$P_1 = I^2 R_1 = \left( \frac{E}{R_1+r} \right)^2 R_1$$

Power delivered in second case

$$P_2 = I^2 R_2 = \left( \frac{E}{R_2+r} \right)^2 R_2$$

Power delivered is same in the both the cases.

$$\left( \frac{E}{R_1+r} \right)^2 R_1 = \left( \frac{E}{R_2+r} \right)^2 R_2$$

$$\frac{R_1}{(R_1+r)^2} = \frac{R_2}{(R_2+r)^2}$$

$$R_1(R_2^2 + r^2 + 2R_2r) = R_2(R_1^2 + r^2 + 2R_1r)$$

$$R_1R_2^2 + R_1r^2 + 2R_1R_2r = R_2R_1^2 + R_2r^2 + 2R_1R_2r$$


$$R_1R_2^2 - R_2R_1^2 = R_2r^2 - R_1r^2$$

$$R_1R_2(R_2 - R_1) = r^2(R_2 - R_1)$$

$$r = \sqrt{R_1R_2}$$

382 (b)

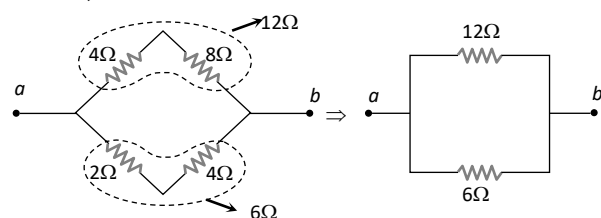Given circuit is a balanced Wheatstone bridge circuit, hence it can be redrawn as follows



$$R_{AB} = \frac{12 \times 6}{12 + 6} = 4 \Omega$$

383 (b)

In general, ammeter always reads less than the actual value because of its resistance

384 (a)

In the circuit shown total external resistance  $R =$

$2 \Omega$  + parallel combination of two  $4 \Omega$  resistors + parallel combination of three  $15 \Omega$  resistors

$$= 2 + \frac{4}{2} + \frac{15}{3} = 2 + 2 + 5 = 9 \Omega$$

As  $E = 10V$  and  $i = 1A$ , hence internal resistance  $r$  of the cell should have a value given by

$$E = i(R+r) \text{ or } r = \frac{E}{i} - R = \frac{10}{1} - 9 = 1 \Omega$$


If  $4 \Omega$  resistors are replaced by  $2 \Omega$  resistors, then as before

$$R' = 2 + \frac{2}{2} + \frac{15}{3} = 2 + 1 + 5 = 8 \Omega$$

$$\therefore \text{New circuit current } i' = \frac{E}{R'+r} = \frac{10}{8+1} = 1.11A$$

385 (c)

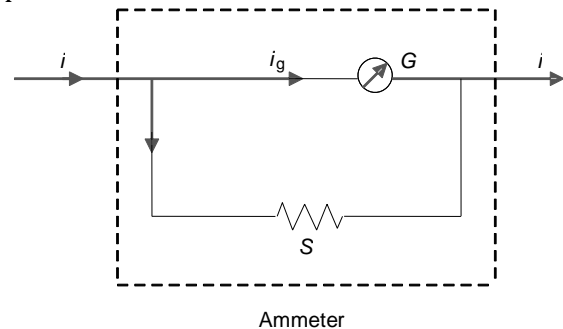Let  $G$  be resistance of galvanometer and  $i_g$  the current which on passing through the galvanometer produces full scale deflection. If  $i$  is the maximum current, and since,  $G$  and  $S$  are in parallel.



$$i_g \times G = (i - i_g) \times S$$

$$\Rightarrow \frac{i_g}{i} = \frac{S}{S+G}$$

Given,  $G=36 \Omega$ ,  $S=4 \Omega$

$$\therefore \frac{i_g}{i} = \frac{4}{36+4} = \frac{4}{40}$$

$$\Rightarrow i_g = \frac{i}{10}$$

$$\therefore 100 \times \frac{i_g}{i} = \frac{1}{10} \times 100$$

$$\Rightarrow \frac{i_e}{i} \% = 10\%$$

386 (d)

$$R = 91 \times 10^2 \approx 9.1k \Omega$$

387 (c)

$$r = \frac{(l_1 - l_2)}{l_2} \times R' = \left( \frac{60 - 50}{50} \right) \times 6 = 1.2 \Omega$$

388 (c)

$$R = \frac{\rho(L)}{A} = \frac{\rho L}{tL} = \frac{\rho}{t}$$

ie,  $R$  is independent of  $L$ .

Hence the correct option is (c).

389 (c)

$$q = \frac{m}{z} = \frac{1}{(1/96500,00)} = 96500,000 \text{ C}$$

$$V = \frac{H}{q} = \frac{34 \times 10^5 \times 4.2}{96500,000} = 1.48 = 1.5V.$$

390 (a)


The reciprocal of resistance is called conductance

391 (d)

In case of stretching of wire  $R \propto l^2$

$\Rightarrow$  If length becomes 3 times so Resistance becomes 9 times i.e.  $R' = 9 \times 20 = 180\Omega$

392 (b)

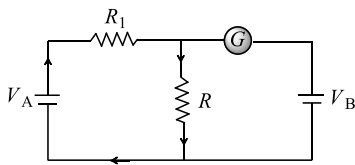

Since deflection in galvanometer is zero so current will flow as shown in the above diagram

$$\text{Current } I = \frac{V_A}{R_1 + R} = \frac{12}{500 + 100} = \frac{12}{600}$$

So  $V_B = IR$

$$= \frac{12}{600} \times 100 = 2V$$

393 (c)

In series combination of cells current,  $i = \frac{nE}{nr + R}$

In parallel combination of cell,  $i' = \frac{E}{(r/n) + R}$

$$\text{If } i = i' \text{ then } \frac{nE}{nr + R} = \frac{E}{(r/n) + R} = \frac{nE}{r + nR}$$

It will be so if  $r = R$

394 (b)

$$\begin{aligned} \text{Resistance of } 40 \text{ W bulb} &= \frac{240 \times 240}{40} \\ &= 1440 \Omega \end{aligned}$$

$$\text{It's safe current} = \frac{240}{1440} = 0.167 \text{ A}$$

$$\begin{aligned} \text{Resistance of } 60 \text{ W bulb} &= \frac{240 \times 240}{60} \\ &= 960 \Omega \end{aligned}$$

$$\text{It's safe current} = \frac{240}{960} = 0.25 \text{ A}$$

When connected in series to 420 V supply, then the current

$$\begin{aligned} I &= \frac{420}{1440 + 960} = \frac{420}{2400} \\ &= 0.175 \text{ A} \end{aligned}$$

Thus, current is greater for 40 W bulb, so it will fuse.

395 (d)

The sensitivity of the thermocouple will be

$$= 500 \mu V / ^\circ C - (-72 \mu V / ^\circ C) = 572 \mu V / ^\circ C$$

Therefore for a  $100^\circ C$  temperature difference, the thermo e.m.f. will be

$$\begin{aligned} E &= 572 \times 10^{-6} \times 100 (\text{volt}) = 57.2 \times 10^{-3} \\ &= 57.2 \text{ mV} \end{aligned}$$

396 (d)

The resistance of an ideal voltmeter is considered as infinite

397 (b)

For power to be maximum

External resistance = Equivalent internal resistance of the circuit

398 (a)

$$v_d = \frac{eE}{m} \tau = \frac{e}{m} \tau \left( \frac{V}{l} \right) \text{ or } v_d \propto V$$

Therefore, drift velocity is doubled


399 (c)

The specific resistance ( $\rho$ ) is the characteristic of the material of conductor. Its value depends only on the material of conductor and its temperature. Its value does not depend on the length and area of cross-section of the conductor.

400 (c)

$R_1$  and  $R_2$  are in series
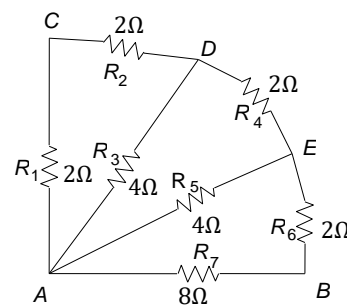
$$\therefore R_{12} = R_1 + R_2 = 4\Omega$$



$R_{12}$  and  $R_3$  are in parallel

$$\begin{aligned} R_{123} &= \frac{R_3 \times R_{12}}{R_3 + R_{12}} \\ &= \frac{4 \times 4}{4 + 4} \\ &= 2\Omega \end{aligned}$$

$R_{123}$  and  $R_4$  are in series

$$\begin{aligned} \therefore R_{1234} &= R_{123} + R_4 \\ &= 2\Omega + 2\Omega \\ &= 4\Omega \end{aligned}$$

$R_{1234}$  and  $R_5$  are in parallel

$$\therefore R_{12345} = 2\Omega$$

$R_{12345}$  and  $R_6$  are in series

$$2\Omega + 2\Omega = 4\Omega$$



$$= R_{123456}$$

Now,  $R_{123456}$  and  $R_7$  are in parallel

$$\begin{aligned} \therefore R_{\text{comb}} &= \frac{4 \times 8}{4 + 8} \\ &= \frac{32}{12} = \frac{8}{3} \Omega \end{aligned}$$

401 (c)

$$R = \rho \frac{l}{A} \Rightarrow 7 = \frac{64 \times 10^{-6} \times 198}{\frac{22}{7} \times r^2} \Rightarrow r = 0.024 \text{ cm}$$

402 (a)

Drift velocity is defined as the average velocity with which free electrons get defined towards the positive end of the conductor under the influence of an external electric field.

Drift velocity is given by

$$v_d = \frac{eE\tau}{m}$$

$$\text{But } E = \frac{V}{l}$$

(if  $l$  is length of the conductor and  $V$  is constant potential difference applied across the ends of the conductor)

$$\therefore v_d = \frac{eV\tau}{ml} \Rightarrow v_d \propto V$$

So, when the potential difference is doubled the drift velocity will be doubled.

403 (c)

Net voltage =  $12 - 8 = 4 \text{ V}$

Net resistance =  $9 + 2 + 1 = 12 \Omega$

Current through the circuit

$$= \frac{4}{12} = \frac{1}{3} \text{ A}$$

Terminal voltage across  $E_2$  is


$$= E_2 - Ir_2 = 12 - \frac{1}{3} \times 2$$

$$= 12 - \frac{2}{3} = \frac{34}{3} = 11.34 \text{ V}$$

404 (d)


Initially current through the voltmeter  $i_1 =$

$$\frac{V}{(3+2)} = \frac{V}{5}$$

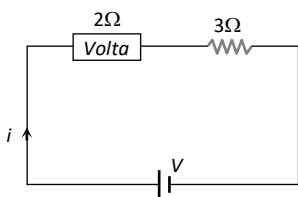

$$\text{Finally main current } i = \frac{V}{3+1} = \frac{V}{4}$$
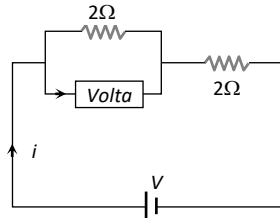
$$\text{Hence current through voltmeter } i_2 = \frac{V}{8}$$



$$\therefore \text{Rate of deposition } (R) = \frac{m}{t} = Zi \Rightarrow R \propto i$$

$$\therefore \% \text{ drop in rate} = \frac{R_2 - R_1}{R_1} \times 100 = \frac{i_2 - i_1}{i_1} \times 100$$

$$= \frac{\left(\frac{V}{8} - \frac{V}{5}\right)}{\frac{V}{5}} \times 100 = -37.5\%$$

405 (b)

$$Pt = mS\theta$$

$$P = \frac{1 \times 4200 \times 15}{60} \text{ W} = 1050 \text{ W}$$

406 (d)

Heating effect of current

407 (c)

$$R = \frac{230 \times 230}{100} = 529 \Omega$$

$$\therefore H = \frac{V^2}{R} \times t = \frac{115 \times 115}{529} \times 10 \times 60 = 15 \text{ kJ}$$

408 (b)

Potentiometer is based on null deflection

409 (c)

Due to the negligible temperature co-efficient of resistance of constantan wire, there is no change in its resistance value with change in temperature

410 (a)

Neutral temperature is defined as temperature of a hot junction of a thermocouple at which the electromotive force of the thermocouple attains its maximum value when cold junction is maintained at a constant temperature of  $0^\circ \text{C}$ . Hence, for a given thermocouple neutral temperature is a constant.

411 (a)

For one wire cable,

$$\text{Resistance, } R' = \rho l / \pi (9 \times 10^{-3})^2 = 5 \Omega$$

For other wire of cable,

$$\text{Resistance, } R' = \rho l / \pi (3 \times 10^{-3})^2$$

$$= 9^2 \times 5 / 3^2 = 45 \Omega$$

When six wires each of resistance  $R'$  are connected in parallel, their effective resistance

will be

$$R_p = \frac{R'}{6} = \frac{45}{6} = 7.5 \Omega$$

412 (a)

After short circuiting,  $R_2$  becomes meaningless

413 (c)

In series,

$$P_s = \frac{P_1 \times P_2}{P_1 + P_2} = 12 \text{ W}$$

In parallel,  $P_p = P_1 + P_2 = 50 \text{ W}$

$$\therefore P_1 P_2 = 12 \times 50 = 600$$

$$\begin{aligned} \text{Now, } (P_1 - P_2)^2 &= (P_1 + P_2)^2 - 4P_1 P_2 \\ &= (50)^2 - 4 \times 600 \\ &= 2500 - 2400 = 100 \end{aligned}$$

$$\therefore P_1 - P_2 = 10$$

Or  $P_1 = 30 \text{ W}, P_2 = 20 \text{ W}$

$$\therefore \frac{P_1}{P_2} = \frac{3}{2}$$

414 (c)

Lowest resistance will be in the case when all the resistors are connected in parallel

$$\frac{1}{R} = \frac{1}{0.1} + \frac{1}{0.1} \dots 10 \text{ times}$$

$$\frac{1}{R} = 10 + 10 \dots 10 \text{ times}$$

$$\frac{1}{R} = 100 \text{ i.e. } R = \frac{1}{100} \Omega$$

415 (d)

$$i = \frac{e}{t} = \frac{e}{2\pi r/v} = \frac{ev}{2\pi r}$$

Here,  $v = \frac{e^2}{h}$  and  $r = h^2/me^2$

$$\therefore i = \frac{e(e^2/h)}{2\pi(h^2/me^2)} = \frac{e^3 \times me^2}{2\pi h^3} = \frac{me^5}{2\pi h^3}$$

$$i = \frac{4\pi^2 me^5}{h^3}$$

416 (c)

For the same length and same material,

$$\frac{R_2}{R_1} = \frac{A_1}{A_2} = \frac{3}{1} \text{ or } R_2 = 3R_1$$

The resistance of thick wire,  $R_1 = 10 \Omega$

The resistance of thin wire

$$= 3R_1 = 3 \times 10 = 30 \Omega$$

Total resistance =  $10 + 30 = 40 \Omega$

417 (c)

Resistance of copper part of wire  $R_c = \frac{\rho_c L}{A_c} = \frac{\rho_c L}{\pi r^2}$

and

Resistance of nickel portion of wire  $R_n = \frac{\rho_n L}{A_n} = \frac{\rho_n L}{\pi(R^2 - r^2)}$

As these two resistances are in parallel, hence conductance

$$\begin{aligned} \text{of the nickelled wire } C &= \frac{1}{R} = \frac{1}{R_c} + \frac{1}{R_n} = \frac{\pi r^2}{\rho_c L} + \frac{\pi(R^2 - r^2)}{\rho_n L} \\ &= \frac{\pi}{L} \left[ \frac{r^2}{\rho_c} + \frac{R^2 - r^2}{\rho_n} \right] \end{aligned}$$


418 (a)

All the conductors have equal lengths. Area of cross-section of A is  $\{(\sqrt{3}a)^2 - (\sqrt{2}a)^2\} = a^2$

Similarly area of cross-section of B = Area of cross-section of C =  $a^2$

Hence according to formula  $R = \rho \frac{l}{A}$ ; resistances of all the conductors are equal i.e.  $R_A = R_B = R_C$

419 (c)

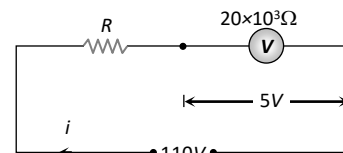


$$\text{Here } i = \frac{110}{20 \times 10^3 + R}$$

$$\begin{aligned} \therefore V = iR &\Rightarrow 5 = \left( \frac{110}{20 \times 10^3 + R} \right) \times 20 \times 10^3 \\ &\Rightarrow 10^5 + 5R = 22 \times 10^5 \Rightarrow R = 21 \times \frac{10^5}{5} \\ &= 420 \text{ K}\Omega \end{aligned}$$

420 (a)

Here,  $V_2 = V_3$

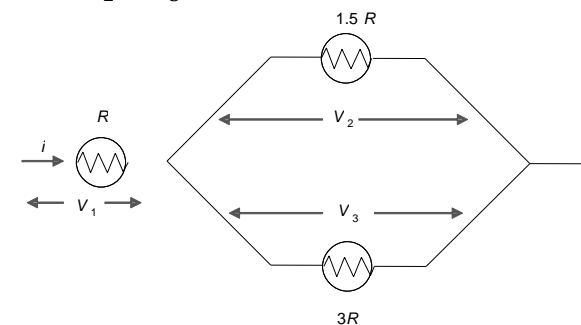

$$\text{i.e., } i_2 \times 1.5R = 3R \times i_3$$

$$\text{And } i_2 + i_3 = i$$

$$\Rightarrow i_2 = \frac{2i}{3} \text{ and } i_3 = \frac{i}{3}$$

Now,  $V_i = iR$

$$V_2 = \frac{2i}{3} \times 1.5R = iR$$

$$V_3 = \frac{i}{3} \times 3R = iR$$

ie,  $V_1 = V_2 = V_3$

421 (a)

Equivalent resistance  $R = 4 + \frac{3 \times 6}{3+6} = 6\Omega$  and main

$$\text{current } i = \frac{E}{R} = \frac{3}{6} = 0.5A$$

Now potential difference across the combination

$$\text{of } 3\Omega \text{ and } 6\Omega, V = 0.5 \times \left(\frac{3 \times 6}{3+6}\right) = 1\text{Volt}$$

The same potential difference also develops across  $3\Omega$  resistance

422 (c)

$$v_d = \frac{I}{nAe} = \frac{20}{10^{29} \times 10^{-6} \times 1.6 \times 10^{-19}} = 1.25 \times 10^{-3} \text{m/s}$$

423 (c)

In series combination, the net resistance

$$R_s = R + 2R = 3R$$

Heat produced in  $R_s$ ,

$$H_s = \frac{V^2}{R_s} = \frac{V^2}{3R} \quad \dots (i)$$

In parallel combination, the net resistance

$$R_p = \frac{R \times 2R}{R + 2R} = \frac{2R^2}{3R} = \frac{2}{3} R$$

Heat produced in  $R_p$ ,

$$H_p = \frac{V^2}{R_p} = \frac{V^2}{2R/3} = \frac{3V^2}{2R} \quad \dots (ii)$$

Dividing Eq. (i) by Eq. (ii), we obtain

$$\frac{H_s}{H_p} = \frac{V^2/3R}{3V^2/2R} = \frac{2}{9}$$

424 (d)

$$E = 2.2V, R = 4\Omega, V = 2V$$

$$r = \left(\frac{E}{V} - 1\right)R = \left(\frac{2.2}{2} - 1\right) \times 4 = 0.1 \times 4 = 0.4\Omega$$

425 (a)

Thermo electric power,  $S \propto \theta$

$$\therefore \frac{S_{100}}{S_{80}} = \frac{100}{80} \text{ or } S_{100} = S_{80} \times \frac{100}{80} = \frac{5}{4} S_{80}$$

Therefore % change in thermo electric power

$$= \left(\frac{S_{100} - S_{80}}{S_{80}}\right) \times 100$$

$$= \left(\frac{\frac{5}{4}S_{80} - S_{80}}{S_{80}}\right) \times 100$$

$$= 25\%$$

426 (c)

The bulbs are in series, hence they will have the same current through them

427 (c)

$$\text{By using } i = \frac{E}{R+r}$$

$$\Rightarrow 0.5 = \frac{E}{11+r} \Rightarrow E = 5.5 + 0.5r \quad \dots (i)$$

$$\text{and } 0.9 = \frac{E}{5+r} \Rightarrow E = 4.5 + 0.9r \quad \dots (ii)$$

On solving these equations, we have  $r = 2.5\Omega$

428 (d)

Terminal voltage of the battery after closing the circuit is

$$V = E - ir$$

$$= 10 - 0.5 \times 3$$

$$= 10 - 1.5 = 8.5V$$

429 (a)

$$\sigma_i = \frac{\theta}{i} = \frac{\theta}{iG} \cdot G = \sigma_v G \Rightarrow \frac{\sigma_i}{G} = \sigma_v$$

430 (b)

$$\text{Energy liberated} = \frac{V^2}{R} t$$

$$= \frac{(120)^2}{6} \times (10 \times 60) = 14.4 \times 10^5 \text{ J}$$

431 (c)

$$R = \rho \frac{l}{A}$$

432 (a)

As the current in heater filament increases, it gets more heated, hence its temperature increases and thereby its resistance increases. Due to which the current will decrease. Hence the variation of  $V$  and  $i$  for heater filament will as shown in Fig.(a)

433 (d)

$$\text{By using } H = \sigma Q \Delta \theta$$

$$\Rightarrow H = (10 \times 10^{-6}) \times 10 \times (60 - 50) = 10^{-3} \text{ J} = 1 \text{ mJ}$$

434 (b)

$$E_{\text{Ni-Cu}} = at + bt^2$$

$$= (16.3 \times 10^{-6})(100) + (-0.021 \times 10^{-6}) \times (100)^2$$

$$= 1.42 \times 10^{-3} \text{ V}$$

435 (d)

$$\text{From the relation, current } i = \frac{V}{r}$$

$$\text{or } 4 = \frac{2}{r}$$

or  $r = \frac{1}{2} \Omega$

436 (b)

For balanced Wheatstone bridge  $\frac{P}{Q} = \frac{R}{S}$

$$\Rightarrow \frac{12}{(1/2)} = \frac{x+6}{(1/2)} \Rightarrow x = 6\Omega$$

437 (c)

On doubling the length of wire its resistance is doubled and slope of  $V - I$  graph is doubled

438 (d)

Heat generated in both the cases will be same because the capacitor has the same energy initially

$$= \frac{1}{2} CV^2 = \frac{1}{2} \times 200 \times 10^{-6} \times (200)^2 = 4J$$

439 (a)

$E \propto l$  (balancing length)

440 (a)

The first two bands indicate the first two significant figures of the resistance in ohm. The third band indicates the decimal multiplier and the last band stands for the tolerance in percent about the indicated value

443 (d)

Effective resistance between the points A and B is

$$R = \frac{32}{12} = \frac{8}{3} \Omega$$

444 (b)

$$R_1 + R_2 = 9 \text{ and } \frac{R_1 R_2}{R_1 + R_2} = 2 \Rightarrow R_1 R_2 = 18$$

$$R_1 - R_2 = \sqrt{(R_1 + R_2)^2 - 4R_1 R_2} = \sqrt{81 - 72} = 3$$

$$R_1 = 6\Omega, R_2 = 3\Omega$$

445 (b)


$$\rho - \text{same}, l - \text{same}, A_2 = \frac{1}{4} A_1 \left[ \text{as } r_2 = \frac{r_1}{2} \right]$$

$$\text{By using } R = \rho \frac{l}{A} \Rightarrow \frac{R_1}{R_2} = \frac{A_2}{A_1} \Rightarrow \frac{R_1}{8} = \frac{1}{4} \Rightarrow R_1 = 2\Omega$$

$$\text{Hence, } R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{2 \times 8}{(2+8)} = \frac{8}{5} \Omega$$

446 (c)

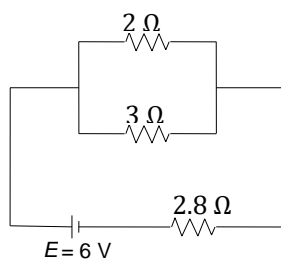
In the steady state, no current flows through the branch containing the capacitor. So, the equivalent circuit will be of the form as shown below:



The effective resistance of the circuit is

$$R = \frac{2 \times 3}{2 + 3} + 2.8 = 1.2 + 2.8 = 4\Omega$$

The current through the circuit is

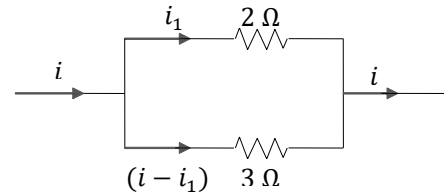

$$i = \frac{E}{R} = \frac{6}{4} = 1.5A$$

Let current  $i_1$  flows through  $2\Omega$  resistance.

$$\therefore 2 \times i_1 = (i - i_1) \times 3$$

$$\Rightarrow 2i_1 = (1.5 - i_1) \times 3$$

$$\Rightarrow 2i_1 = 4.5 - 3i_1$$

$$\Rightarrow 5i_1 = 4.5$$

$$\Rightarrow i_1 = 0.9A$$

447 (a)

The equivalent resistance between C and D is

$$\frac{1}{R'} = \frac{1}{6} + \frac{1}{6} + \frac{1}{3} = \frac{2}{3} \text{ or } R' = \frac{3}{2} = 1.5\Omega$$

Now the equivalent resistance between A and B as  $R' = 1.5\Omega$  and  $2.5\Omega$  are connected in series, so

$$R'' = 1.5 + 2.5 = 4\Omega$$

Now by ohm's law, potential difference between A and B is given by  $V_A - V_B = iR = 2 \times 4.0 = 8 \text{ volt}$


448 (d)

To find equivalent resistance across

BC, AB and AC is in series

$$R' = 6 + 6 = 12\Omega$$

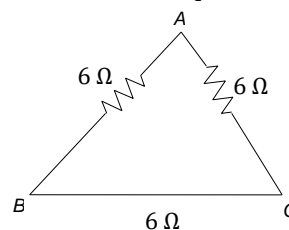$12\Omega$  and  $6\Omega$  is in parallel



Total resistance,

$$R = \frac{12 \times 6}{12 + 6}$$

$$R = \frac{72}{18} = 4\Omega$$

449 (d)

$$R_{200} = \frac{R_{800}}{1 + \alpha t}$$

$$R_{200} = \frac{R_{800}}{1 + 4 \times 10^{-4} \times 600} = \frac{R_{800}}{1.24}$$


$$\frac{V^2}{R_{800}} = P \quad \dots\dots(i)$$

$$\text{and } \frac{V^2}{R_{200}} = P' \quad \dots\dots(ii)$$

$$\therefore \frac{P'}{P} = \frac{R_{800}}{R_{200}} = \frac{R_{800}}{\left(\frac{R_{800}}{1.24}\right)}$$

$$P' = 1.24P = 1.24 \times 500 = 620 \text{ W}$$

450 (b)

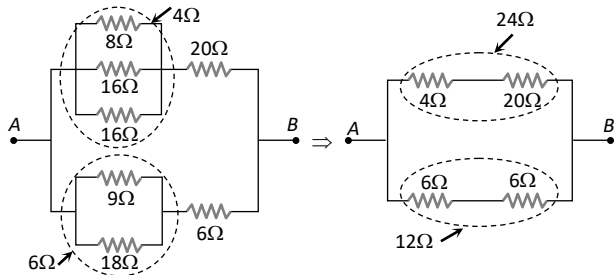

$$R_{AB} = \frac{24 \times 12}{(24 + 12)} = 8\Omega$$

451 (c)

Let resistors  $A, B$  and  $C$  have equal resistance  $R$ .

Let  $I$  be the total current then the current in resistor  $A$  is  $I$  and in resistor  $B$  and  $C$  are  $I/2$ .

So, heat produced in resistor  $A$  is

$$H_A = I^2 R \quad \dots (i)$$

and heat produced in resistor  $B$  is

$$H_B = \left(\frac{I}{2}\right)^2 R = \frac{I^2 R}{4} \quad \dots (ii)$$

and heat produced in resistor  $C$  is

$$H_C = \frac{I^2 R}{4} \quad \dots (iii)$$


Hence, it is clear that the heat produced will be maximum in  $A$ .

452 (c)

$$i = \frac{q}{t} = \frac{4}{2} = 2 \text{ ampere}$$

453 (d)

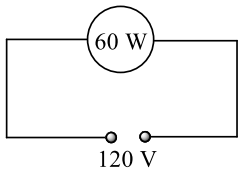
$$R_{60} = \frac{120 \times 120}{60} = 240\Omega$$



$$\text{Current} = \frac{120}{240+60} \text{ A} = \frac{120}{246} \text{ A}$$

Voltage across bulb
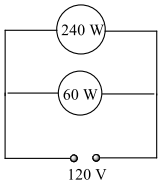
$$= \frac{120}{246} \times 240 \text{ volt} = 117.1 \text{ volt}$$



$$R_{240} = \frac{120 \times 120}{240} = 60\Omega$$

Resistance of parallel combination

$$= \frac{60 \times 240}{60 + 240} = 48\Omega.$$

Total resistance =  $(48 + 6)\Omega = 54\Omega$ .

$$\text{Current } I = \frac{120}{54} \text{ A}$$

Voltage across parallel combination

$$= \frac{120}{54} \times 48 \text{ volt} = 106.7 \text{ volt}$$

Change in voltage =  $(117.1 - 106.7) = 10.4 \text{ V}$ .

454 (c)

$$R = \frac{V^2}{P} \text{ or } R \propto V^2 \therefore \frac{R_1}{R_2} = \frac{(200)^2}{(300)^2} = \frac{4}{9}$$

When bulbs are connected in series, the current  $I$  is same through each. As  $P = I^2 R$  or  $P \propto R$  (as  $I$  is same in series),

$$\text{so } \frac{P_1}{P_2} = \frac{R_1}{R_2} = \frac{4}{9}$$

455 (c)

On stretching, volume ( $V$ ) remains constant. So

$$V = Al \text{ or } l = V/A.$$

$$\text{Now, } R = \frac{\rho l}{A} = \frac{\rho V}{A^2} = \frac{\rho V}{\pi^2 D^4 / 16} = \frac{16\rho V}{\pi^2 D^4}$$


Taking logarithm of both the side and differentiating it we get

$$\frac{\Delta R}{R} = -4 \frac{\Delta D}{D} \text{ or } \frac{\Delta R}{R} = -4 \times 0.25 = 1.0\%$$

456 (c)

Here,  $2\Omega, 3\Omega$  and  $6\Omega$  are in parallel. So potential drop across them will be the same. As heat

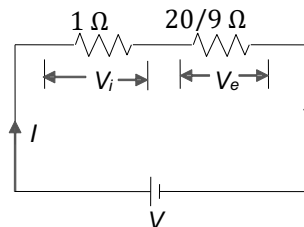produced,  $= \frac{V^2}{R} t$  i.e.,  $H \propto \frac{1}{R}$ , so maximum heat will be generated across  $2\Omega$  resistance. Similarly  $4\Omega$  and  $5\Omega$  are also in parallel, so more heat will be generated across  $4\Omega$ . Now the effective circuit will become



$$\text{Total resistance, } = 1 + \frac{20}{9} = \frac{29}{9} \Omega$$

$$\text{Current, } I = \frac{V}{29/9} = \frac{9V}{29} \text{ A}$$

$$V_1 = \frac{9V}{29} \times 1 = \frac{9}{29} V$$

$$\text{and } V_2 = \frac{9V}{29} \times \frac{20}{9} = \frac{20V}{29}$$

Power spent across  $2 \Omega$ ,

$$P_1 = \frac{V_1^2}{2} = \frac{\left(\frac{9V}{29}\right)^2}{2} = \frac{40.5V^2}{(29)^2}$$

Power spent across 4  $\Omega$ ,

$$P_2 = \frac{V_2^2}{4} = \frac{\left(\frac{20V}{29}\right)^2}{4} = \frac{50V^2}{(29)^2}$$

$\therefore P_2 > P_1$ . Hence maximum heat is produced in  $4\Omega$  resistance.

457 (a)

When ammeter is connected in parallel to the circuit, net resistance of the circuit decreases. Hence more current is drawn from the battery, which damages the ammeter

458 (a)

According to kirchhoff's voltage law only option (a) is correct

459 (c)

Total resistance of the circuit =  $\frac{80}{2} + 20 = 60 \Omega$


$$\Rightarrow \text{Main current } i = \frac{2}{60} = \frac{1}{30} A$$

Combination of voltmeter and  $80\Omega$  resistance is connected in series with  $20\Omega$ , so current through  $20\Omega$  and this combination will be same =  $\frac{1}{30} A$

Since the resistance of voltmeter is also  $80\Omega$ , so this current is equally distributed in  $80\Omega$  resistance and voltmeter [i. e.  $\frac{1}{60} A$  through each]

$$\text{P.D. across } 80\Omega \text{ resistance} = \frac{1}{60} \times 80 = 1.33V$$

460 (c)

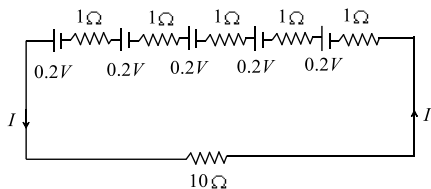

Here, emf of each cell,  $\varepsilon = 0.2V$

Internal resistance of each cell,  $r = 1\Omega$

External resistance,  $R = 10\Omega$

The total emf of 5 cells =  $5\varepsilon = 5(0.2)V = 1V$

Total internal resistance of 5 cells =  $5r =$

$$5(1)\Omega = 5\Omega$$

Total resistance of the circuit =  $R + 5r = 10 +$

$$5 = 15\Omega$$

The current in the external circuit,

$$I = \frac{5\varepsilon}{R + 5r} = \frac{1V}{15\Omega} = \frac{1}{15} A$$

461 (c)

Potential gradient

$$x = \frac{e}{(R + R_h + r)} \cdot \frac{R}{L}$$

$$\Rightarrow x = \frac{2}{(990 + 10)} \times \frac{10}{2}$$


$$= 0.01 \text{ Vm}^{-1}$$

462 (d)

$$\frac{i_g}{i} = \frac{S}{G + S} = \frac{4}{36 + 4} = \frac{4}{40} = \frac{1}{10}$$

463 (b)

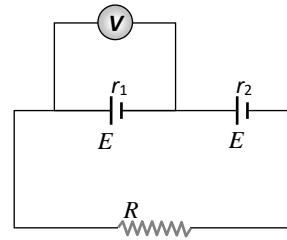Let the voltage across any one cell is  $V$ , then



$$V = E - ir = E - r_1 \left( \frac{2E}{r_1 + r_2 + R} \right)$$

But  $V = 0$


$$\Rightarrow E - \frac{2Er_1}{r_1 + r_2 + R} = 0$$

$$\Rightarrow r_1 + r_2 + R = 2r_1$$


$$\Rightarrow R = r_1 - r_2$$

464 (b)

The given circuit can be redrawn as

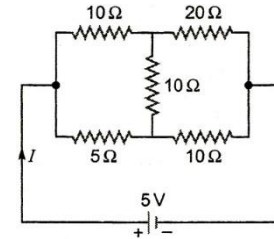

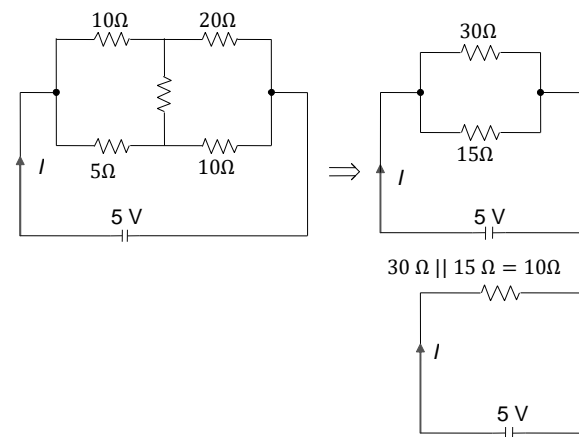Which is a balanced Wheatstone's bridge and hence, no current flows in the centre resistor, so equivalent circuit would be as shown below.



$$\text{So, } I = \frac{V}{R} = \frac{5}{10} = 0.5A$$

465 (b)

$$q = it = n \times 2e$$

$$n = \frac{it}{2e} = \frac{2 \times 32}{2 \times 1.6 \times 10^{-19}} = 2 \times 10^{20}$$

466 (a)

Rate of flow of electrons in a conductor is low but

number density of free electrons in a conductor is very high. The drifting of electrons over the entire length of the conductor contributes to the current throughout the conductor

467 (b)

$$m = Z i t \Rightarrow 20 \times 10^{-3} = \left( \frac{32}{96500} \right) \times 0.15 \times t$$

$$= 6.7 \text{ min} = 6 \text{ min. } 42 \text{ sec}$$

469 (a)

$$\frac{1}{R_1} = \frac{1}{10} + \frac{1}{2.5} = \frac{5}{10} = \frac{1}{2} \Rightarrow R_1 = 2\Omega$$

Now  $2\Omega$  and  $10\Omega$  are in series

$$R_2 = 10 + 2 = 12\Omega$$

$R_2$  and  $12\Omega$  are in parallel

$$\frac{1}{R_3} = \frac{1}{12} + \frac{1}{12} \Rightarrow R_3 = 6\Omega$$

Now  $R_3$  and  $6\Omega$  are in series

$$R_4 = 10 + 6 = 16\Omega$$

Now,  $R_4$  and  $16\Omega$  are in parallel

$$\therefore \frac{1}{R} = \frac{1}{16} + \frac{1}{16}$$

$$\Rightarrow R = 3\Omega$$

470 (d)

$$P_1 = \frac{(220)^2}{R_1} \text{ and } P_2 = \frac{(220 \times 0.8)^2}{R_2}$$

$$\frac{P_2}{P_1} = \frac{(220 \times 0.8)^2}{(220)^2} \times \frac{R_1}{R_2} \Rightarrow \frac{P_2}{P_1} = (0.8)^2 \times \frac{R_1}{R_2}$$

Here,  $R_2 < R_1$  (because voltage decreases from  $220V \rightarrow 220 \times 0.8V$ )

It means heat produced  $\rightarrow$  decreases)

$$\text{So } \frac{R_1}{R_2} > 1 \Rightarrow P_2 > (0.8)^2 P_1 \Rightarrow P_2 > (0.8)^2 \times$$

$$100 \text{ W}$$

$$\text{Also } \frac{P_2}{P_1} = \frac{(220 \times 0.8)^2 i_2}{220^2 i_1}, \text{ Since } i_2 < i_1 \text{ [we expect]}$$

$$\text{So } \frac{P_2}{P_1} < 0.8 \Rightarrow P_2 < (100 \times 0.8)$$

Hence the actual power would be between  $100 \times (0.8)^2 \text{ W}$  and

$$(100 \times 0.8) \text{ W}$$

471 (a)

$$v_d = i/n A e; \text{ where } n = N_p/M$$

$$= 6.023 \times 10^{26} \times 9 \times 10^3 / 63 = 0.860 \times 10^{29}$$

$$= 8.6 \times 10^{28}$$

$$\text{and } A = \pi D^2 / 4 = \frac{22}{7} \times (10^{-3})^2 / 4 \text{ m}^2;$$

$$= \frac{11}{14} \times 10^{-6} \text{ m}^2$$

$$v_d = \frac{1.1}{8.6 \times 10^{28} \times \frac{11}{14} \times 10^{-6} \times 1.6 \times 10^{-19}}$$

$$= \frac{1}{9.6 \times 10^{+3}} = \frac{100 \times 10^{-4}}{96} = 1.0 \times 10^{-4} \text{ m/s}$$

$$= 0.1 \text{ mms}^{-1}$$

472 (c)

Charge flowing in 30 min,

$q =$  area under graph

$$= \left[ \frac{0.1 \times 10}{2} + 0.1 \times 10 + \frac{0.1 \times 10}{2} \right] \times 60$$

$$= 120 \text{ C}$$

$$\therefore m = zq = \frac{M}{F} q = \frac{31.5}{96500} \times 120 = 0.039 \text{ g}$$

473 (b)

When wire is cut into two equal parts then power dissipated by each part is  $2P_1$

So their parallel combination will dissipate power

$$P_2 = 2P_1 + 2P_1 = 4P_1$$

Which gives  $\frac{P_2}{P_1} = 4$

474 (c)

$$i = \frac{dQ}{dt} \Rightarrow dQ = idt \Rightarrow Q$$


$$= \int_{t_1}^{t_2} idt = \int_0^5 (1.2t + 3) dt$$

$$= \left[ \frac{1.2t^2}{2} + 3t \right]_0^5 = 30 \text{ C}$$

475 (c)

When each bulb is glowing at full power,
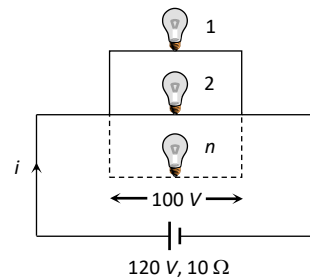
$$\text{Current from each bulb} = i' = \frac{50}{100} = \frac{1}{2} \text{ A}$$



$$\text{So main current } i = \frac{n}{2} \text{ A}$$

$$\text{Also } E = V + ir \Rightarrow 120 = 100 + \left( \frac{n}{2} \right) \times 10 \Rightarrow n =$$

$$4$$

476 (c)

$$R' = \frac{R}{n} = \frac{1}{10} = 0.1\Omega$$

477 (c)


$$\text{Shunt resistances } S = \frac{i_g G}{(i - i_g)} = \frac{10 \times 99}{(100 - 10)} = 11 \Omega$$

478 (a)

$$\text{Potential gradient } x = \frac{V}{L} = \frac{iR}{L} = \frac{i(\frac{\rho L}{A})}{L} = \frac{i\rho}{A}$$

479 (a)

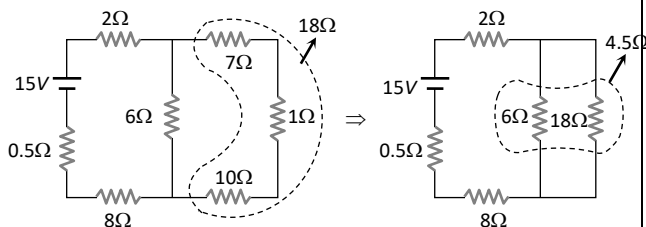The given circuit can be simplified as follows



On further solving equivalent resistance  $R = 15 \Omega$

$$\text{Hence current from the battery } i = \frac{15}{15} = 1 \text{ A}$$

480 (b)

Let  $R$  be the resistance of each bulb.

$$\text{We have } P = \frac{V^2}{R}$$

$$\text{or } R = \frac{V^2}{P} = \frac{V^2}{100}$$

When the bulbs are connected in series, the voltage across each of them is  $V/2$ . Hence, the total power consumed is

$$P' = \frac{\left(\frac{V}{2}\right)^2}{R} + \frac{\left(\frac{V}{2}\right)^2}{R} = \frac{V^2}{2R}$$

$$\therefore P' = \frac{P}{2} = \frac{100}{2} = 50 \text{ W}$$

481 (d)

$$R = \frac{\rho l}{A}$$

$$\text{or } R \propto l$$

$$\therefore \frac{R_1}{R_2} = \frac{l_1}{l_2} = \frac{L}{L/4} = 4$$

$$\text{Or } R_2 = \frac{R}{4} \quad (\because R_1 = R)$$

In parallel combination of such four resistances.

$$\frac{1}{R'} = \frac{1}{R/4} + \frac{1}{R/4} + \frac{1}{R/4} + \frac{1}{R/4}$$

$$\text{or } \frac{1}{R'} = \frac{1}{R/4} + \frac{1}{R/4} + \frac{1}{R/4} + \frac{1}{R/4}$$

$$\text{or } \frac{1}{R'} = \frac{4}{R} + \frac{4}{R} + \frac{4}{R} + \frac{4}{R}$$

$$\text{or } \frac{1}{R'} = \frac{16}{R}$$

$$\text{or } R' = \frac{R}{16}$$

482 (d)

$$\frac{i_g}{i} = \frac{S}{G + S} \Rightarrow \frac{5}{100} = \frac{S}{G + S} \Rightarrow S = \frac{G}{19}$$

483 (c)

$$\text{Total kWh consumed} = \frac{60 \times 8 \times 30}{1000} = 14.4$$

$$\text{Hence cost} = 14.4 \times 1.25 = 18 \text{ Rs}$$

484 (d)

$$R_1 = \rho \frac{l_1}{A_1} \text{ and } R_2 = \rho \frac{l_2}{A_2} \Rightarrow \frac{R_1}{R_2} = \frac{l_1}{l_2} \cdot \frac{A_2}{A_1} = \frac{l_1}{l_2} \left(\frac{r_2}{r_1}\right)^2$$

$$\text{Given } \frac{l_1}{l_2} = \frac{1}{2} \text{ and } \frac{r_1}{r_2} = \frac{2}{1} \text{ or } \frac{r_2}{r_1} = \frac{1}{2} \Rightarrow \frac{R_1}{R_2} = \frac{1}{8}$$

$$\therefore \text{Ratio of heats } \frac{H_1}{H_2} = \frac{V^2/R_1}{V^2/R_2} = \frac{R_2}{R_1} = \frac{8}{1}$$

485 (b)

$$W = qV \text{ also } P = i \times V = \frac{W}{t}$$

486 (c)

According to Faraday's first law of electrolysis is  $m = zIt$


where  $z$  is the electrochemical equivalent of the substance

As voltmeters are connected in series, same current will pass through them for same time

$$\therefore \frac{m_{Cu}}{m_{Cr}} = \frac{z_{Cu}}{z_{Cr}} \text{ or } \frac{z_{Cu}}{z_{Cr}} = \frac{m_{Cu}}{m_{Cr}} = \frac{0.475}{0.130} = 3.65$$

487 (a)

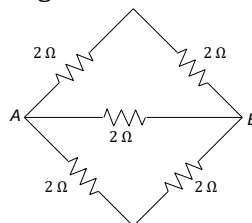Given circuit is a balanced Wheatstone bridge. So, diagonal resistance of  $2 \Omega$  will be ineffective.



Equivalent resistance of upper arms

$$= 2 + 2 = 4 \Omega$$

Equivalent resistance of lower arms

$$= 2 + 2 = 4 \Omega$$

$$R_{AB} = \frac{4 \times 4}{4 + 4} = 2 \Omega$$

488 (d)

In series, effective resistance,

$$R_{eff} = R_1 + R_2 + R_3 \Rightarrow \frac{1}{\sigma_{eff}} = \frac{1}{\sigma_1} + \frac{1}{\sigma_2} + \frac{1}{\sigma_3}$$

$$= \frac{\sigma_2 \sigma_3 + \sigma_1 \sigma_3 + \sigma_1 \sigma_2}{\sigma_1 \sigma_2 \sigma_3}$$

$$\therefore \sigma_{eff} = \frac{\sigma_1 \sigma_2 \sigma_3}{\sigma_2 \sigma_3 + \sigma_1 \sigma_3 + \sigma_1 \sigma_2}$$

489 (b)

The resistance of a metal increases with increasing temperature this is because, with increase in temperature the ions of the conductor vibrate with greater amplitude and the collision between ions and electrons becomes more frequent.

490 (a)

The power drawn by the bulb is



$$P = \frac{V^2}{R}$$

$$\Rightarrow R = \frac{V^2}{P}$$

$$\text{or } R \propto \frac{1}{P}$$

(as  $V$  is same in parallel)

It means that greater power will have less resistance and therefore, draws more current. Hence, current flowing in bulb  $B$  will be more.

491 (c)

Human body, though has a large resistance of the order, of  $k\Omega$  (say  $10k\Omega$ ), is very sensitive to minute currents even as low as a few  $mA$ . Electrons, excites and disorders the nervous system of the body and hence one fails to control the activity of the body

492 (c)


$$\text{Resistance of bulb } R = \frac{V^2}{P} = \frac{220 \times 220}{100} = 484\Omega$$

Power when the bulb of operated on a voltage

$$V' = 110V \text{ will be } P' = \frac{V'^2}{R} = \frac{110 \times 110}{484} = 25W$$

493 (c)

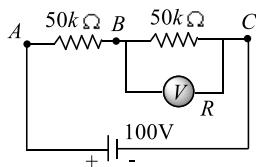Internal resistance of voltmeter is  $R$   
Therefore effective resistance across  $B$  and  $C$ ,



$R''$  is given by

$$\frac{1}{R''} = \frac{1}{R} + \frac{1}{50} = \frac{50 + R}{50R}$$

$$\Rightarrow R'' = \left( \frac{50R}{50 + R} \right)$$

According to ohm's law

$$V'' = IR''$$

$$\Rightarrow \frac{100}{3} = I \cdot \left( \frac{50R}{50 + R} \right)$$

$$\Rightarrow \frac{100}{3} \left( \frac{50+R}{50R} \right) = I \dots (ii)$$

Now, total resistance of circuit

$$R'''' = 50 + \frac{50R}{50 + R}$$

$$\Rightarrow R'' = \frac{(2500 + 100R)}{(50 + R)}$$

$$\text{Now, } V'' = IR''$$

$$\Rightarrow 100 = \frac{100}{3} \left( \frac{50 + R}{50R} \right) \frac{2500 + 100R}{(50 + R)}$$

$$\Rightarrow 150R = 2500 + 100R$$

$$\Rightarrow R = 50 k\Omega$$

494 (a)

Equivalent resistance in the second case =  $R_1 + R_2 = R$

Now, we know that  $P \propto \frac{1}{R}$

Since in the second case the resistance ( $R_1 + R_2$ ) is higher than that in the first case ( $R_1$ )

Therefore power dissipation in the second case will be decreased

495 (c)

$$\text{Heat } H = \frac{V^2 t}{R} \Rightarrow H \propto \frac{1}{R} \quad [\text{If } V, t \text{ constant}]$$

$$\Rightarrow \frac{H_S}{H_P} = \frac{R_P}{R_S} = \frac{\left( \frac{R \times 2R}{3R} \right)}{(R + 2R)} = \frac{2}{9}$$

496 (a)

$$P = \frac{W}{t} = Vi \Rightarrow V = \frac{W}{it} = \frac{1000}{2 \times 6 \times 60} = 1.38 V$$

497 (b)

$$\text{Heat produced by the heater } H = \frac{V^2}{R} \times t$$

For 220V heater heat produced

$$H_1 = \frac{(220)^2}{R} \times 5$$

For 110V heater heat produced

$$H_2 = \frac{(110)^2}{R} \times L$$

Now,

$$H_1 = H_2$$

$$\frac{110 \times 110}{R} t = \frac{220 \times 220 \times 5}{R}$$

$$t = 20 \text{ min}$$

498 (c)

Equivalent resistance of the circuit  $R_{eq} = 100\Omega$

Current through the circuit  $i = \frac{2.4}{100} A$

P.D. across combination of voltmeter and  $100\Omega$

$$\text{Resistance} = \frac{2.4}{100} \times 50 = 1.2V$$

Since the voltmeter and  $100 \Omega$  resistance are in parallel, so the voltmeter reads the same value *i.e.*  $1.2V$


499 (b)

$$i = \frac{12}{(1 + 1) + 0.4} = 5A$$

500 (b)

Here,  $I = I_1 + I_2 \dots (i)$
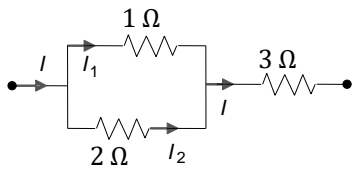
$$\text{and } \frac{I_1}{I_2} = \frac{1}{2} = 2$$



$$\therefore I = I_1 + I_2 = 2I_2 + I_2$$

$$\therefore I_2 = \frac{I}{3} \text{ and } I_1 = \frac{2I}{3}$$

$$\therefore P = I^2 \times 3 = 3I^2$$

$$P_1 = I_1^2 \times 1 = \left(\frac{2I}{3}\right)^2 \times 1 = \frac{4I^2}{9}$$



$$P_2 = I_2^2 \times 2 = \frac{I^2}{9} \times 2 = \frac{2}{9}I^2$$

$$P_3 = I^2 \times 3 = 3I^2$$

$$\therefore P_1 : P_2 : P_3 = \frac{4}{9} : \frac{2}{9} : 3 = 4 : 2 : 27$$

501 (b)

The figure can be drawn as follows

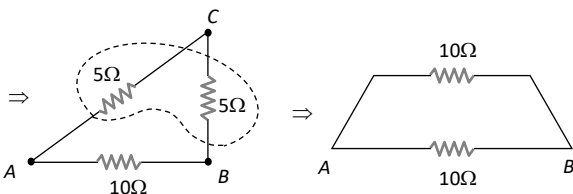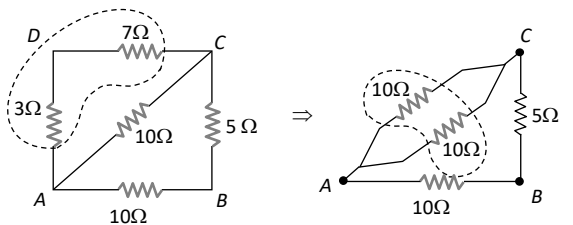

$$\Rightarrow R_{AB} = 5\Omega$$

502 (c)

The ratio of the weights deposited on cathodes will be in the ratio of their chemical equivalents. The chemical equivalent of copper = At. Wt/2 and that of silver = At. Wt/1.

503 (c)

A fully charged capacitor draws no current. Therefore, no current flows in arm  $GHF$ . So the  $R$  of arm  $HF$  is ineffective. The total resistance of the resistors in circuit

$$\text{is } R' = \frac{(R+R) \times R}{(R+R) \times R} + R$$

$$= \frac{(2+2) \times 2}{(2+2) + 2} + 2 = \frac{10}{3}\Omega$$

$$\text{Total current, } i = \frac{E}{R'} = \frac{10}{(10/3)} = 3A$$

In parallel circuit, the current divides in the inverse ratio of resistance, so current in arm

$ABGD = 1A$  and current in arm  $AD = 2A$

Potential difference between  $G$  and  $D$

$$= V_G - V_D = 1 \times 2 = 2V$$

Potential difference between  $D$  and  $F$

$$= V_D - V_F = 3 \times 2 = 6V$$

$$\therefore V_G - V_F = (V_G - V_D) + (V_D - V_F)$$

$$= 2 + 6 = 8V$$

Potential difference across capacitor =  $V_G - V_F = 8V$

504 (c)

Amount of metallic sodium appearing,

$$m = Zit = \left(\frac{A}{VF}\right)it$$

$$= \left(\frac{23}{1 \times 96500}\right) \times 16 \times 10 \times 60$$

$$= 2.3 \text{ gm}$$

505 (c)

$$V = E - IR = 15 - 10 \times 0.05 = 14.5V$$

506 (a)

Resistance of voltmeter should be high

507 (b)

By balanced Wheatstone bridge condition  $\frac{16}{X} = \frac{4}{0.5}$

$$\Rightarrow X = \frac{8}{4} = 2\Omega$$

509 (b)

From the given circuit

$$V_A - (6 \times 2) - 12 - (9 \times 2) + 4 - (5 \times 2) = V_B$$

$$\text{Or } V_A - 12 - 12 - 18 + 4 - 10 = V_B$$

$$\text{Or } V_A - V_B = 48 \text{ volt}$$

510 (d)

Let  $R_0$  be the initial resistance of both conductors.

$\therefore$  At temperature  $\theta$  their resistances will be,

$$R_1 = R_0(1 + \alpha_1\theta)$$

$$\text{and } R_2 = R_0(1 + \alpha_2\theta)$$

For series combination,  $R_s = R_1 + R_2$

$$R_s(1 + \alpha_s\theta) = R_0(1 + \alpha_1\theta) + R_0(1 + \alpha_2\theta)$$

Where,  $R_{s0} = R_0 + R_0 = 2R_0$

$$\therefore 2R_0(1 + \alpha_s\theta) = 2R_0 + R_0\theta(\alpha_1 + \alpha_2)$$

$$\text{or } \alpha_s = \frac{\alpha_1 + \alpha_2}{2}$$

For parallel combination,

$$R_p = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{p0}(1 + \alpha_p\theta) = \frac{R_0(1 + \alpha_1\theta)R_0(1 + \alpha_2\theta)}{R_0(1 + \alpha_1\theta) + R_0(1 + \alpha_2\theta)}$$

Where,  $R_{p0} = \frac{R_0 R_0}{R_0 + R_0} = \frac{R_0}{2}$

$$\therefore \frac{R_0}{2} (1 + \alpha_p \theta) = \frac{R_0^2 (1 + \alpha_1 \theta + \alpha_2 \theta + \alpha_1 \alpha_2 \theta^2)}{R_0 (2 + \alpha_1 \theta + \alpha_2 \theta)}$$

as  $\alpha_1$  and  $\alpha_2$  are small quantities.

$\therefore \alpha_1 \alpha_2$  is negligible.

$$\text{or } \alpha_p = \frac{\alpha_1 + \alpha_2}{2 + (\alpha_1 + \alpha_2)\theta} = \frac{\alpha_1 + \alpha_2}{2} \left[ 1 - \left( \frac{\alpha_1 + \alpha_2}{2} \right) \theta \right]$$

as  $(\alpha_1 + \alpha_2)^2$  is negligible

$$\therefore \alpha_p = \frac{\alpha_1 + \alpha_2}{2}$$

511 (c)

Current through resistance  $R$  will be zero if

$$\frac{E}{R_2} = \frac{E_1}{R_1 + R_2} \text{ or } E_1 = \frac{E(R_1 + R_2)}{R_2}$$

512 (a)

$$m = Zit \Rightarrow \frac{m}{Zit} = 1 [\text{constant}]$$

513 (d)

Drift velocity = mobility  $\times$  intensity of electric field

$$\text{or } v_d = \mu E \text{ or } \mu = \frac{v_d}{E}$$

$$\text{or } \mu = \frac{v_d}{V/l} \quad \left( \because E = \frac{V}{l} \right)$$

$$\therefore \mu = \frac{0.5 \times 2}{220} = 4.5 \times 10^{-3}$$

$$\approx 5 \times 10^{-3} \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$$

515 (a)

Heat produced by heater is given by

$$H = Pt$$

$$\text{Given, } P = 100 \text{ W, } t = 2 \text{ min} = 2 \times 60 \text{ s} = 120 \text{ s}$$

$$\therefore H = 100 \times 120 = 12 \times 10^3 \text{ J}$$

516 (c)

$$v_d = \frac{i}{nAe} = \frac{1.344}{10^{-2} \times 1.6 \times 10^{-19} \times 8.4 \times 10^{22}}$$

$$= \frac{1.344}{10 \times 1.6 \times 8.4} = 0.01 \text{ cm/s} = 0.1 \text{ mm/s}$$

517 (d)

$$t_i = 2t_n - t_c \Rightarrow t_i = 2 \times 350 - 30 = 670^\circ \text{C}$$

518 (a)

Because with rise in temperature resistance of conductor increases, so graph between  $V$  and  $i$  becomes non linear

519 (b)

In VI graph, we will not get a straight line in case of liquids

520 (c)

$$\text{Here, } V = 10 \text{ V, } G = 500 \Omega$$

$$i_g = \frac{V}{G} = \frac{10}{500} = 2 \times 10^{-2} \text{ A}$$

Now,

$$S = \frac{i_g G}{i - i_g} = \frac{2 \times 10^{-2} \times 500}{10 - 2 \times 10^{-2}} \approx 1 \Omega \text{ in parallel.}$$

521 (a)

$$\frac{R_1}{R_2} = \left( \frac{r_2}{r_1} \right)^4 \Rightarrow \frac{R}{R_2} = \left( \frac{nr}{r} \right)^4 \Rightarrow R_2 = \frac{R}{n^4}$$

522 (c)

Slope is zero at neutral temperature

523 (d)

$$l = \frac{R\pi r^2}{\rho} = \frac{4.2 \times 3.14 \times (0.2 \times 10^{-3})^2}{48 \times 10^{-8}} = 1.1 \text{ m}$$

524 (c)

According to Kirchoff's first rule

$$I + 4 + 2 - 3 - 5 = 0$$

$$I + 6 - 8 = 0$$

$$\Rightarrow I = 2 \text{ A}$$

525 (d)

Wire  $AB$  is uniform so current through wire  $AB$  at every across section will be same. Hence current density,  $J (= i/A)$  at every point of the wire will be same

526 (d)

After connecting a resistance  $R$  in parallel with voltmeter its effective resistance decreases. Hence less voltage appears across it *i.e.*  $V$  will decrease. Since overall resistance decreases so more current will flow *i.e.*  $A$  will increase

527 (c)

$$v_d = \frac{J}{ne} \Rightarrow v_d \propto J \text{ [current density]}$$

$$J_1 = \frac{i}{A} \text{ and } J_2 = \frac{2i}{2A} = \frac{i}{A} = J_1; \therefore (v_d)_1 = (v_d)_2 = v$$

528 (a)

For a balance Wheatstone bridge

$$\frac{A}{B} = \frac{D}{C} \Rightarrow \frac{10}{5} \neq \frac{4}{4} \text{ [Unbalanced]}$$

$$\frac{A'}{B} = \frac{D}{C} \Rightarrow \frac{A'}{5} = \frac{4}{4} \Rightarrow A' = 5 \Omega$$

$A'(5\Omega)$  is obtained by connecting a  $10 \Omega$  resistance in parallel with  $A$

529 (b)

Let the e.m.f. of cell be  $E$  and internal resistance be  $r$

$$\text{Then } 0.5 = \frac{E}{(r+2)} \text{ and } 0.25 = \frac{E}{(r+5)}$$

$$\text{On dividing, } 2 = \frac{5+r}{2+r} \Rightarrow r = 1 \Omega$$

530 (b)

Mass of water = volume  $\times$  density

$$= 1000 \times 1 = 1000 \text{ g.}$$

Heat taken by water =  $mc \Delta\theta$

$$= 1000 \times 1(37 - 22) \text{ cal}$$

$$= 1000 \times 15 \times 4.2 \text{ J}$$

$$\text{Power of geyser} = \frac{\text{energy spent}}{\text{time}}$$

$$= \frac{1000 \times 15 \times 4.2}{60} = 1050 \text{ W.}$$

531 (b)

E.m.f. is the value of voltage, when no current is drawn from the circuit so  $E = 2V$ .

$$\text{Also } r = \text{slope} = \frac{2}{5} = 0.4\Omega$$

532 (c)

They are the resistors made up of semiconductors whose resistance decreases with the increase in temperature. This implies that they have negative and high temperature coefficient of resistivity. They are usually made of metal oxides with high temperature coefficient of resistivity.

533 (c)

$$\text{Strength} = 5 \times 18 = 90AH$$

534 (c)

$$V = E - ir = 12 - 60 \times 5 \times 10^{-2} = 9V$$

535 (b)

$$\text{Effective emf of circuit} = 10 - 3 = 7V$$

$$\text{Total resistance of circuit} = 2 + 5 + 3 + 4 = 14\Omega$$

$$\text{Current, } i = 7/14 = 0.5 \text{ A}$$

$$\text{Potential difference between } A \text{ and } D = 0.5 \times 10 = 5V$$

$$\text{Potential at } D = 10 - 5 = 5V$$

Hence,  $E$  cannot be at zero potential, as there is potential drop at  $E$

536 (a)

When a constant current is passed through a wire of uniform cross-section, the potential difference across any portion of the wire is directly proportional to the length of that portion.

$$\text{Potential gradient} = 0.2 \text{ mVcm}^{-1}$$

$$\therefore \text{Potential difference across potentiometer wire} = 0.02 \times 1 = 0.02V$$

$$\text{Total resistance} = r + R = 490 + R$$

$$\therefore \frac{V_1}{V_2} = \frac{R_1}{R_2}$$

$$\Rightarrow \frac{0.02}{2} = \frac{R}{490 + R}$$

$$\Rightarrow R = 4.9\Omega$$

537 (c)

Given  $V_1 = 50 \text{ volt}$ ,  $i_1 = 11A$ ;  $V_2 = 60 \text{ volt}$ ,  $i_2 = 1A$

If  $e.m.f.$  and internal resistance of battery are  $E$  and  $r$  respectively then  $P.D.$  across terminals of

battery,

$$V = E - ir$$

$$\text{We have } 50 = E - 11r \dots(i)$$

$$\text{And } 60 = E - 1r \dots(ii)$$

From (i) and (ii),

$$E = 61V \text{ and } r = 1\Omega$$

538 (d)

$$R_1 + R_2 = R_1(1 + \alpha t) + R_2(1 - \beta t)$$

$$\Rightarrow R_1 + R_2 = R_1 + R_2 + R_1\alpha t - R_2\beta t \Rightarrow \frac{R_1}{R_2} = \frac{\beta}{\alpha}$$

539 (d)

$$V_2 = \frac{22.4 \times 1}{1} = 22.4 \text{ litre at NTP}$$

$$\therefore 11.2 \text{ litre of } H_2 \text{ is liberated by } 96,500 \text{ C}$$


$$\therefore 22.4 \text{ litre of } H_2 \text{ is liberated by } 96500 \times 2 = 1,93,000 \text{ C}$$

540 (b)

The moving coil galvanometer have their coil wound on a metallic (copper or aluminium) frame, so as to make the motion dead beat due to the production of eddy currents. In the ballistic galvanometer, on the other hand, the damping is to be reduced to the minimum and hence the frame is of a non-conducting material *eg*, paper or bamboo.


541 (b)

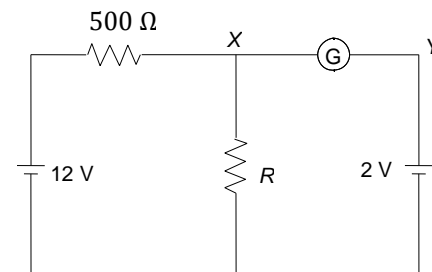The galvanometer shows zero deflection *ie*, current through  $XY$  is zero.



As a result potential drop across  $R$  is  $2V$ , circuit can be redrawn as

$$I = \frac{12}{500 + R}$$

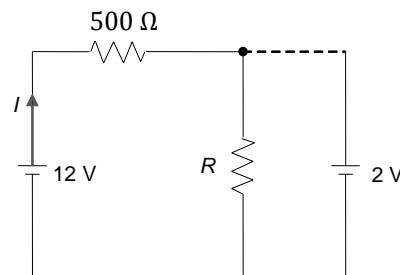

Voltage across  $R$ ,  $V = IR$

$$\Rightarrow 2 = \frac{12}{500 + R} \times R$$

$$\Rightarrow 1000 + 2R = 12R$$

$$\Rightarrow R = 100\Omega$$

543 (b)

Production of e.m.f. by temperature difference is known as Seebeck effect

545 (c)

From Joule's law,

$$H = \frac{V^2 t}{RJ} \text{ cal}$$

Where  $V$  is potential difference,  $t$  the time and  $R$  the resistance.

$$R = R_1 + R_2$$

$$\text{Let } \frac{t}{R} = \frac{HJ}{V^2} = \text{constant} = k$$

$$\Rightarrow R_1 = kt_1 \text{ and } R_2 = kt_2$$

$$\therefore kt = kt_1 + kt_2$$

$$\text{Or } t = 15 + 20$$

$$t = 35 \text{ min}$$

546 (d)

In a conductor, the electron number density  $ie$ , number of electrons per unit volume of a conductor is very large ( $\approx 10^{28} \text{ m}^{-3}$ ), so large current in a conductor is obtained irrespective of their small drift speed.

547 (c)

As resistances are in parallel

$$\frac{1}{R_{eq}} = \frac{1}{220} + \frac{1}{220} + \dots \text{ 5000 times}$$


$$\frac{1}{R_{eq}} = \frac{5000}{220}$$

$$R_{eq} = \frac{220}{5000}$$

$$I = \frac{220}{5000}$$

$$I = 5000 \text{ A}$$

548 (b)

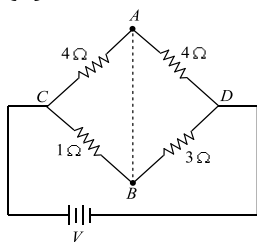

Current through arm  $CAD$ ,  $I = \frac{V}{8} \text{ amp}$

Potential difference between  $C$  and  $A = V_C - V_A$

$$= \frac{V}{8} \times 4 = \frac{V}{2} \text{ volt}$$

Current through  $CBD$ ,  $I'' = \frac{V}{4} \text{ amp}$

Potential difference between  $C$  and  $B = V_C - V_B$

$$= \frac{V}{4} \times 1 = \frac{V}{4} \text{ volt}$$

Potential between  $A$  and  $B = V_A - V_B$

$$\therefore V_A - V_B = V_C - V_B - (V_C - V_A) = \frac{V}{4} - \frac{V}{2} = -\frac{V}{4}$$

$$\Rightarrow V_A - V_B < 0 \text{ or, } V_A < V_B$$


as  $V_A < V_B$ , so direction of current will be  $B$  to  $A$

549 (c)

Here points  $B$  and  $D$  are common. So  $2R$  in arm  $DC$  and  $2R$  in arm  $CB$  are in parallel between  $C$  and  $B$ . Their effective resistances

$$= \frac{2R \times 2R}{2R + 2R} = R$$

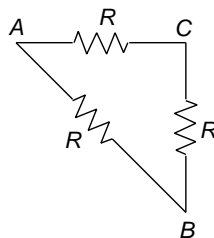The modified and simpler circuit will be shown in figure. The effective resistance between  $A$  and  $B$  is




$$R_{\text{eff}} = \frac{R \times (R + R)}{R + (R + R)} = \frac{2}{3} R$$

550 (d)

Full scale deflection current
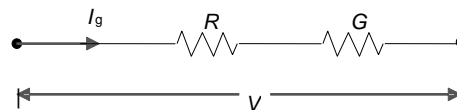
$$= \frac{150}{10} \text{ mA} = 15 \text{ mA}$$



Full scale deflection voltage

$$= \frac{150}{2} \text{ mV} = 75 \text{ mV}$$

Galvanometer resistance

$$G = \frac{75 \text{ mV}}{15 \text{ mA}} = 5 \Omega$$

Required full scale deflection voltage.

$$V = 1 \times 150 = 150 \text{ volt}$$

Let resistance to be connected in series is  $R$ .

$$\Rightarrow V = I_g(R + G)$$

$$\therefore 150 = 15 \times 10^{-3}(R + 5)$$

$$\Rightarrow 10^4 = R + 5$$

$$\Rightarrow R = 10000 - 5 = 9995$$

551 (c)


Total energy stored in capacitor,  $E_{\text{total}} = \frac{1}{2} CV^2$   
 $= \frac{1}{2} \times 3 \times 10^{-6} \times 10^2 = 1.5 \times 10^{-4} \text{ J}$

Energy dissipated in  $2\Omega = \frac{2}{(2+4)} \times E_{\text{total}}$   
 $= \frac{2}{6} \times 1.5 \times 10^{-4} = 0.5 \times 10^{-4} \text{ J} = 0.05 \text{ mJ}$

552 (d)

The equivalent circuit of these network is as shown in figure, which is a balanced Wheatstone bridge. Therefore no current will flow in the resistance of arm  $PQ$ . When cell is connected to points  $A$  and  $B$

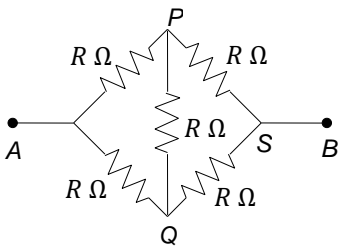Therefore effective resistance of arm  $APS = (R + R = 2R)$  will be in parallel to the total resistance of arm  $AQS (= R + R = 2R)$



$\therefore$  Equivalent resistance  $= \frac{2R \times 2R}{2R + 2R} = R\Omega$

553 (a)

The tolerance level of resistance is mostly 1%, 2%, 5% and 10%. In old days 20% was also common, but these are now rare. Now a days 5% tolerance in trends.

554 (c)

Resistance of wire given by

$$R = \rho \frac{l}{A}$$

Also, volume (V) = Length (l)  $\times$  Area (A)

Where,  $A = \pi r^2$  (r is radius)

When the wire is stretched its volume (V) remains constant.

Hence,

$$R = \frac{\rho V}{\pi^2 r^4} \dots (i)$$

When radius is halved

$$R' = \frac{\rho V}{\pi r^2 \left(\frac{r}{2}\right)^4} \dots (ii)$$

$$\therefore \frac{R'}{R} = \frac{16\rho V}{\pi^2 r^4} \times \frac{\pi^2 r^4}{\rho V} = 16$$

$$\Rightarrow R' = 16R$$

Hence, new resistance increases to sixteen times its original value.

555 (d)

Comparing the given equation with standard equation

$$E = \alpha t + \frac{1}{2} \beta t^2$$

$$\alpha = 40 \text{ and } \frac{1}{2} \beta = -\frac{1}{20} \Rightarrow \beta = -\frac{1}{10}$$

$$\text{Hence neutral temperature } t_n = -\frac{\alpha}{\beta} = \frac{-40}{-1/10}$$

$$\Rightarrow t_n = 400^\circ\text{C}$$

**Alternate solution :** We know at neutral temperature

$$\frac{dE}{d\theta} = 0$$

$$E = 40\theta - \frac{\theta^2}{20} \Rightarrow 40 - \frac{2\theta}{20} = 0 \Rightarrow \theta = 400^\circ\text{C}$$

556 (d)

Only current through the conductor of non-uniform area of cross-section is constant. Drift velocity or drift speed vary inversely with the area of cross-section of the conductor

557 (d)

Equivalent resistance between  $P$  and  $Q$

$$\frac{1}{R_{PQ}} = \frac{1}{(6+2)} + \frac{1}{3} + \frac{1}{(4+12)} \Rightarrow R_{PQ} = \frac{48}{25} \Omega$$


Current between  $P$  and  $Q$ ;  $i = 1.5 \text{ A}$

So, potential difference between  $P$  and  $Q$

$$V_{PQ} = 1.5 \times \frac{48}{25} = 2.88 \text{ V}$$

559 (c)

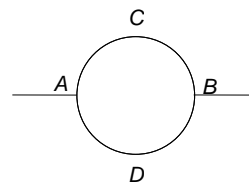Given that the resistance of the total wire is  $4\Omega$ .



Here,  $ACB(2\Omega)$  and  $ADB(2\Omega)$  are in parallel.

So, the resistance across any diameter is

$$\Rightarrow \frac{1}{R} = \frac{1}{2} + \frac{1}{2} = \frac{2}{2} = 1$$

$$\Rightarrow R = 1\Omega$$

560 (c)

$$\text{Resistance, } R = \frac{\rho l}{A}$$

$$\text{For wire P, } 20 = \frac{\rho l}{\pi r^2} \dots (i)$$

Similarly for wire Q,

$$8 = \frac{\rho(2l)}{\pi(r')^2} \dots (ii)$$

Dividing Eq.(i) by Eq. (ii), we have

$$\frac{20}{8} = \frac{\rho l}{\pi r^2} \times \frac{\pi(r')^2}{\rho(2l)}$$

$$\Rightarrow 5 = \left(\frac{r'}{r}\right)^2$$

$$\Rightarrow r' = \sqrt{5}r$$

561 (d)

Voltage across  $B_3$  is greatest hence  $B_3$  will show maximum brightness. In series combination of bulbs, the bulb of lesser wattage will glow more bright. Hence  $W_2 > W_1$ .

So,  $W_1 < W_2 < W_3$ .

562 (b)

Specific resistance  $k = \frac{E}{j}$

563 (d)

Kirchhoff's 1st law or KCL states that the algebraic sum of current meeting at any junction is equal to zero. In other words we can say that "the sum of all the currents directed towards a junction in a circuit is equal to the sum of all the currents directed away from that junction." Thus, no charge has been accumulated at any junction *i.e.*, charge is conserved, and hence, we can say that KCL ( $\sum i = 0$ ) is based on conservation of charge. Kirchhoff's 2nd law or KVL states that algebraic sum of changes in potential around any closed resistor loop must be zero. In other words "around any closed loop, voltage drops are equal to voltage rises". No energy is gained or lost in circulating a charge around a loop, thus, we can say that KVL is based on conservation of energy.

564 (a)

The circuit diagram may be redrawn as shown here.

$$\text{Obviously, } I_{CAD} = I_{CBD} = \frac{2}{12} \text{ A}$$

$$\therefore V_C - V_A = \frac{2}{15} \text{ A} \times 5\Omega = \frac{2}{3} \text{ V}$$

$$\text{and } V_C - V_B = \frac{2}{15} \text{ A} \times 10\Omega = \frac{4}{3} \text{ V}$$

$$\therefore V_A - V_B = (V_C - V_B) - (V_C - V_A) = \frac{4}{3} \text{ V} - \frac{2}{3} \text{ V}$$

$$= \frac{2}{3} \text{ V}$$

566 (a)

$$R = \frac{V}{i_g} - G = \frac{10}{10 \times 10^{-3}} - 1 = 999\Omega$$

567 (c)

$$R_{t_1} = R_1(1 + \alpha_1 t) \text{ and } R_{t_2} = R_2(1 + \alpha_2 t)$$

$$\text{Also } R_{eq} = R_{t_1} + R_{t_2} \Rightarrow R_{eq} = R_1 + R_2 + (R_1\alpha_1 + R_2\alpha_2)t$$

$$\Rightarrow R_{eq} = (R_1 + R_2) \left[ 1 + \left( \frac{R_1\alpha_1 + R_2\alpha_2}{R_1 + R_2} \right) \cdot t \right]$$

$$\text{So } \alpha_{eff} = \frac{R_1\alpha_1 + R_2\alpha_2}{R_1 + R_2}$$

569 (b)

$$m = \rho V$$

$$\text{If } V \text{ is the volume, then } V = \frac{m}{\rho} = \frac{zit}{\rho}$$

$$\text{Thickness} = \frac{zit}{A\rho} = \frac{3.3 \times 10^{-7} \times 1.5 \times 20 \times 60}{50 \times 10^{-4} \times 9000}$$

$$\text{Thickness} = 1.3 \times 10^{-5} \text{ m}$$

570 (c)

If resistance does not vary with temperature  $P$  consumed

$$= \left(\frac{V_A}{V_R}\right)^2 \times P_R = \left(\frac{110}{220}\right)^2 \times 100 = 25 \text{ W. But in}$$

second case resistance decreases so consumed power will be more than 25 W

571 (c)

$$V_p - V_q = \left(\frac{6}{3} + \frac{12 \times 6}{12 + 6}\right)(0.5) = (2 + 4)(0.5) = 3 \text{ V}$$

572 (b)

$$\frac{m_{H_2}}{M_{Cu}} = \frac{W_{H_2}}{W_{Cu}} = \frac{1}{\left(\frac{63.5}{2}\right)}$$

$$\Rightarrow m_{H_2} = \frac{2}{63.5} \times 0.3175 = 0.01 \text{ g}$$

2g of  $H_2$  occupies volume at NTP = 22.4 L

$\Rightarrow$  0.01 g of  $H_2$  occupies volume at NTP given by:

$$V = \frac{22.4}{2} \times 0.01 \text{ L}$$

$$\Rightarrow V = 11.2 \times 0.01 \times 1000 \text{ cc} = 112 \text{ cc}$$


573 (c)

$$H = \frac{V^2 t}{4.2 R} \text{ or } \frac{H}{t} = \frac{V^2}{4.2 R}$$

$$\Rightarrow 800 = \frac{20 \times 20}{4.2 \times R} \Rightarrow R = \frac{5}{42} = 0.119 \approx 0.12\Omega$$

574 (b)

The circuit will be as shown

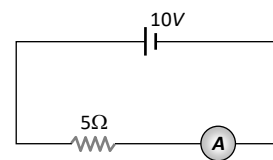


$$i = \frac{10}{5} = 2 \text{ A}$$

575 (b)

$R = \frac{\rho l}{a}$  for first wire and  $R' = \frac{\rho l}{4a} = \frac{R}{4}$  for second wire

576 (c)

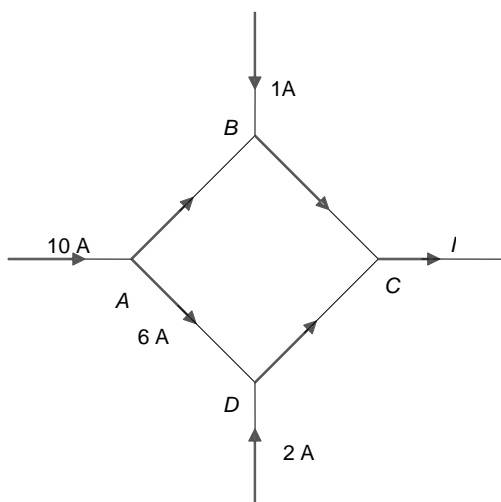Regarding Kirchhoff's junction rule, the circuit can be redrawn as



Current in arm,  $AB = 10 - 6 = 4A$

Current in arm,  $DC = 6 + 2 = 8A$

Current in arm,  $BC = 4 + 1 = 5A$

Hence,  $I = 5 + 8 = 13A$

577 (d)

By using  $R = \frac{V}{i_g} - G \Rightarrow R = \frac{100}{5 \times 10^{-3}} - 5 = 19,995\Omega$

578 (a)

Thermo-emf of thermocouple  $= 25 \frac{\mu V}{^\circ C}$ .

Let  $\theta$  be the smallest temperature difference.

Therefore, after connecting the thermocouple with the galvanometer, thermo-emf

$$E = \left(25 \frac{\mu V}{^\circ C}\right) \times \theta(^\circ C)$$

$$= 250 \times 10^{-6} V$$

Potential drop developed across the galvanometer

$$= iR = 10^{-5} \times 40 = 4 \times 10^{-4} V$$

$$\therefore 4 \times 10^{-4} = 250 \times 10^{-6}$$

$$\therefore \theta = \frac{4}{25} \times 10^2 = 16^\circ C$$

579 (d)

Current density of drinking electrons  $j = nev$

$$n = 5 \times 10^7 \text{ cm}^{-3} = 5 \times 10^7 \times 10^6 \text{ m}^{-3}$$

$$v = 0.4 \text{ ms}^{-1}, e = 1.6 \times 10^{-19} \text{ C} \Rightarrow j$$

$$= 3.2 \times 10^{-6} \text{ Am}^{-2}$$

Current density of ions  $= (4 - 3.2) \times 10^{-6} =$

$$0.8 \times 10^{-6} \frac{A}{m^2}$$

This gives  $v$  for ions  $= 0.1 \text{ ms}^{-1}$

580 (a)

$$V_A + V_B + V_C \propto 740$$

$$V_A + V_B \propto 440$$

$$V_B + V_C \propto 540$$

Hence  $V_A : V_B : V_C = 1 : 1.2 : 3.5$

581 (c)

The number density ( $n$ ) of conduction electrons in the copper is a characteristic of the copper and

is about  $10^{29}$  at room temperature for both the copper rod  $X$  and the thin copper wire  $Y$ .

Both  $X$  and  $Y$  carry the same current  $I$  since they are joined in series

From  $I = nAvq$

Where  $q$  is the electron charge of  $1.6 \times 10^{-19} \text{ C}$ ,  $v$  is the drift velocity in the conductor and  $A$  is the cross-sectional area of the conductor.

We may conclude that rod  $X$  has a lower drift velocity of electrons compared to wire  $Y$  since rod  $X$  has a larger cross-sectional area. This is so because the electrons in  $X$  collide more often with one another and with the copper ions when drifting towards the positive end. Thus, the mean time between collisions of the electrons is more in  $X$  than  $Y$ .


582 (a)

As steady current is flowing through the conductor, hence the number of electrons entering from one end and outgoing from the other end of any segment is equal. Hence charge will be zero

583 (d)

The given circuit can be simplified as shown below in circuit  $R_2, R_5$  and  $R_3, R_4$  are in series and then their resultant is connected parallel.

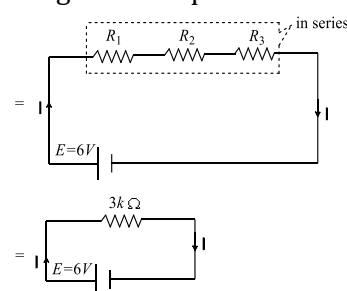Similarly  $R_7, R_8$  and  $R_6, R_9$  are in series and their resultant is connected parallel on simplifying this we get their equivalent circuit



Now current in circuit

$$I = \frac{V}{R} = \frac{6}{3 \times 10^3 \Omega} \times 10^3 = 2 \text{ mA}$$

584 (c)

For a galvanometer

$$NIAB = C\theta$$

$$\Rightarrow \frac{\theta}{I} = \frac{NAB}{C}$$

Here,  $\frac{\theta}{I}$  is called the sensitivity of galvanometer so to increase the sensitivity of galvanometer,  $C$  should be decreased and  $N, A$  and  $B$  should be increased

586 (c)

$$E = 2.2 \text{ volt}, V = 1.8 \text{ volt}, R = 5R$$



$$r = \left(\frac{E}{V} - 1\right)R = \left(\frac{2.2}{1.8} - 1\right) \times 5 = 1.1\Omega$$

587 (b)

$z = m/It$ . From graph,  $It = \text{Area } OABC$

$$= \frac{1}{2}(10 + 30) \times \frac{100}{1000} = 2$$


$$\therefore z = m/2 = -0.5 \text{ m}$$

588 (c)

$$I = \frac{2E}{R + r_1 + r_2}$$

Potential difference across first cell

$$V = E - Ir_1 = 0$$

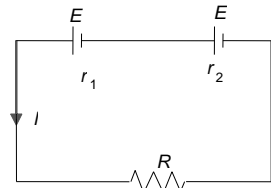

$$E - \frac{2Er_1}{R + r_1 + r_2} = 0$$

$$\left[\frac{R + r_1 + r_2 - 2r_1}{R + r_1 + r_2}\right] = 0$$


$$\Rightarrow R + r_2 - r_1 = 0$$

$$\Rightarrow R = r_1 - r_2$$

589 (d)

Resistivity depends only on the material of the conductor

590 (d)

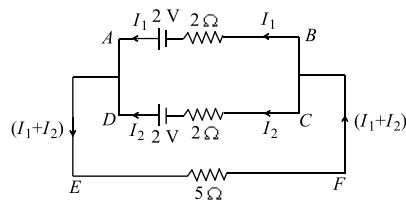

Applying Kirchhoff's second law for closed loop AEFBA,

We get

$$-(I_1 + I_2) \times 5 - I_1 \times 2 + 2 = 0 \text{ or } 7I_1 + 5I_2 = 2$$

...(i)

Again, applying Kirchhoff's second law for a closed loop DEFCD, we get

$$-(I_1 + I_2) \times 5 - I_2 \times 2 + 2 = 0$$

$$\text{or } 5I_1 + 7I_2 = 2 \quad \dots(\text{ii})$$

Multiplying (i) by 5 and (ii) by 7, we get

$$35I_1 + 25I_2 = 10 \quad \dots(\text{iii})$$

$$35I_1 + 49I_2 = 14 \quad \dots(\text{iv})$$

Subtracting (iv) from (iii) we get,

$$-24I_2 = -4 \Rightarrow I_2 = \frac{1}{6}A$$

Substituting the value of  $I_2$  in equation (i), we get

$$7I_1 = 2 - 5 \times \frac{1}{6} \Rightarrow 7I_1 = \frac{7}{6} \Rightarrow I_1 = \frac{1}{6}A$$

The current through the  $5\Omega$  is

$$= I_1 + I_2 = \frac{1}{6}A + \frac{1}{6}A = \frac{1}{3}A$$

591 (a)

Chemical energy reduced

$$= VIt$$

$$= 6 \times 5 \times 6 \times 60 = 10800$$

$$= 1.08 \times 10^4 \text{ J}$$

592 (a)

$$H_1 = \frac{V^2}{R} t$$

$$H_2 = \frac{V^2}{R/2} t$$

$$\therefore \frac{H_2}{H_1} = 2$$

$$\Rightarrow H_2 = 2H_1$$

593 (b)

$$\therefore i_g = 10\% \text{ of } i = \frac{i}{10} \Rightarrow S = \frac{G}{(n-1)} = \frac{90}{(10-1)} = 10\Omega$$

594 (b)

$$E = K(T - T_r)T_0 + \frac{1}{2}K(T^2 - T_r^2)$$

$$\frac{dE}{dT} = KT_0 + \frac{1}{2}K \times 2T = KT_0 + KT$$

At temperature  $T = T_0/2$ ,

$$\text{Thermo-electric power is } \frac{dE}{dT} = KT_0 + K \frac{T_0}{2} =$$

$$\frac{3}{2}KT_0.$$


595 (c)

$$\text{Cost} = \left(\frac{60 \times 8 \times 30}{1000}\right) \times 1.25 = \text{Rs } 18.$$

596 (c)

Let potential of  $P_1$  is 0 V and potential of  $P_2$  is  $V_0$ .

Now apply KCL at  $P_2$ .

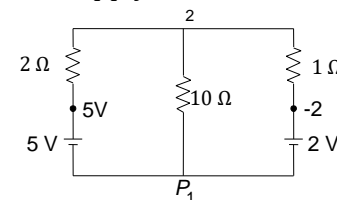

$$\frac{V_0 - 5}{2} + \frac{V_0 - 0}{10} + \frac{V_0 - (-2)}{1} = 0$$


$$\Rightarrow V_0 = \frac{5}{16}$$

So, current through  $10\Omega$  resistor is

$$\frac{V_0}{10} \text{ from } P_2 \text{ to } P_1.$$

597 (a)

Given current  $I = 2A$

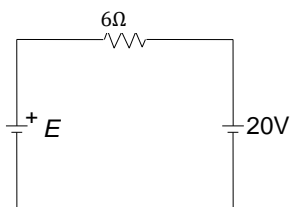

(i) If current is in clockwise direction then from Kirchhoff's second law

$$6 \times 2 + 20 - E = 0$$

$$\Rightarrow E = 32V$$

(ii) If the current is in anticlockwise direction, then

$$6 \times 2 + E - 20 = 0$$

$$\Rightarrow E - 8 = 0$$

$$E = 8$$

598 (b)

According to Kirchhoff's law  $i_{CD} = i_2 + i_3$

599 (d)

Short circuited current  $i = \frac{nE}{nr} = \frac{E}{r}$  i.e.  $i$  doesn't depend upon  $n$

600 (c)

When  $A$  is area of cross-section of wire, and  $n$  be number of free electrons per unit volume, then relation between electric current ( $i$ ) and drift velocity ( $v_d$ ) is

$$i = neAv_d$$

Number of atoms in 63 g of copper is equal to Avogadro's number i.e.  $6 \times 10^{23}$

Volume of 63 g copper

$$= \frac{63}{\text{density}} = \frac{63}{9} = 7 \text{ cm}^3$$

$$n = \frac{6.02 \times 10^{23}}{7} \text{ per cm}^3$$

$$= \left( \frac{6.02 \times 10^{29}}{7} \right) \text{ per m}^3$$

$$\text{Area } A = \pi r^2$$

$$= \pi(0.5 \times 10^{-3})^2 \text{ m}^2$$

Hence, drift velocity

$$v_d$$

$$= \frac{1.1}{\left( \frac{6.02 \times 10^{29}}{7} \right) \times 1.6 \times 10^{-19} \times \pi \times (0.5 \times 10^{-3})^2}$$

$$v_d = 0.1 \times 10^{-3} \text{ ms}^{-1}$$

$$v_d = 0.1 \text{ mms}^{-1}$$

601 (b)

$$R = \frac{\rho l}{A} = \frac{\rho l}{V/l} = \frac{\rho l^2}{V}$$

$$\text{or } l = \left( \frac{RV}{\rho} \right)^{1/2} = \left( \frac{3 \times 3}{\rho} \right)^{1/2} = \frac{3}{\sqrt{\rho}}$$

602 (a)

An emf of the order of a few microvolt is generated which is proportional to  $(t_2 - t_1)$ .

603 (a)

If  $m$  = Number of rows

And  $n$  = Number of cells in a row

$$\text{Then } m \times n = 100 \quad \dots(i)$$

Also condition of maximum current is  $R = \frac{nr}{m}$

$$\Rightarrow 25 = \frac{1 \times n}{m} \Rightarrow n = 25m \quad \dots(ii)$$

On solving (i) and (ii),  $m = 2$

604 (d)

According to Faraday's law of electrolysis

$$m = zit$$

Here,  $i = 1.5 \text{ A}$ ,  $t = 10 \text{ min} = 10 \times 60 \text{ s}$

$$z = 30 \times 10^{-5} \text{ gC}^{-1}$$

Hence, mass of copper deposited on the electrode

$$m = 30 \times 10^{-5} \times 1.5 \times 10 \times 60 = 27 \times 10^{-2} = 0.27 \text{ g}$$

605 (d)

Let  $d$  be the density of the material of copper wire. Let  $l_1, l_2$  be the lengths of copper wires of diameter 1 mm and 2 mm respectively. As

$$\text{Mass} = \text{volume} \times \text{density} = (\pi D^2/4)l \cdot d$$

$$\text{So, } 1 = \frac{\pi(10^{-3})^2}{4} l_1 \times d = \pi \times \frac{(2 \times 10^{-3})^2}{4} l_2 \times d$$

$$\text{or } l_1 = 4l_2$$

$$\text{Now, } R = \frac{\rho l}{\pi D^2/4} \text{ i.e., } R \propto \frac{l}{D^2}$$

$$\therefore \frac{R_1}{R_2} = \frac{l_1}{l_2} \times \frac{D_2^2}{D_1^2} = 4 \times 2^2 = 16$$

606 (a)

$$\text{Potential gradient} = \frac{e}{(R+R_h+r)} \cdot \frac{R}{L}$$

$$= \frac{2}{(15+5+0)} \times \frac{5}{1} = 0.5 \frac{V}{m} = 0.005 \frac{V}{cm}$$

608 (d)

$$E = \frac{e}{(R+R_h+r)} \cdot \frac{R}{L} \times l \Rightarrow 0.4$$

$$= \frac{5}{(5+45+0)} \times \frac{5}{10} \times l$$

$$\Rightarrow l = 8 \text{ m}$$

609 (b)

$$\text{Charge} \rightarrow q = \frac{m}{z}$$

Where,  $z$  = electro chemical equivalent

$$\therefore z = \frac{m}{It} = \frac{0.067}{1 \times 60} = 0.001117$$

$$q = \frac{108}{0.001117} = 9.67 \times 10^4 \text{ C/g}_{\text{eq}}$$

610 (a)

Work done in delivering  $q$  coulomb of charge from clouds to ground.

$$W = Vq$$

$$= 4 \times 10^6 \times 4 = 16 \times 10^6 \text{ J}$$

The power of lighting strike is

$$P = \frac{W}{t} = \frac{16 \times 10^6}{0.1} = 160 \times 10^6 \text{ W}$$

$$= 160 \text{ MW}$$

611 (c)

In closed loop  $ABGFEHA$

$$10 - i_2 \times 1 + i_1 \times 0.5 - 6 = 0$$

$$0.5i_1 - i_2 = -4$$

In closed loop  $BCDEB$

$$(i_1 + i_2) \times 12 + i_2 \times 1 - 10 = 0$$

$$12i_1 + 13i_2 = 10$$

From Eqs. (i) and (ii)

$$i_2 = 2.87 \text{ A}$$

612 (c)

Applying  $P = \frac{V^2}{R}$

$$R_1 = 1 \Omega, R_2 = 0.5 \Omega \text{ and } R_3 = 2 \Omega, V_1 = V_2 = V_3$$

$$= 3 \text{ volt}$$

$$\therefore P_1 = \frac{(3)^2}{1} = 9 \text{ W}$$


$$P_2 = \frac{(3)^2}{0.5} = 18 \text{ W and}$$

$$P_3 = \frac{(3)^2}{2} = 4.5 \text{ W}$$

$$\therefore P_2 > P_1 > P_3$$

613 (d)

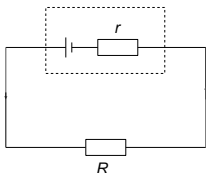Assuming current  $I$  flows through the circuit



$$\text{Energy dissipated in load} = I^2 R$$

$$\text{Energy dissipated in the complete circuit} = I^2 (r + R)$$

$$\therefore \text{The efficiency} = \frac{I^2 R}{I^2 (R+r)} = \frac{R}{R+r}$$

Relation between resistance, mass and cross-sectional area

$$R = \rho \frac{l \times \alpha}{\alpha \times \alpha} \text{ or } R = \rho \frac{V}{\alpha^2}$$

$$R = \rho \frac{m}{d \alpha^2} = \left[ \frac{\rho}{d} \right] \frac{m}{\alpha^2}$$

$$I \propto \frac{m}{\alpha^2}$$

614 (c)

From

$$R_t = R_0(1 + \alpha t)$$

$$5 = R_0(1 + 50\alpha) \dots (i)$$

$$\text{and } 6 = R_0(1 + 100\alpha) \dots (ii)$$

$$\therefore \frac{5}{6} = \frac{1 + 50\alpha}{1 + 100\alpha}$$

$$\Rightarrow \alpha = \frac{1}{200}$$


Putting value of  $\alpha$  in Eq. (i), we get

$$5 = R_0 \left( 1 + 50 \times \frac{1}{200} \right)$$

$$\therefore R_0 = 4 \Omega$$

615 (d)

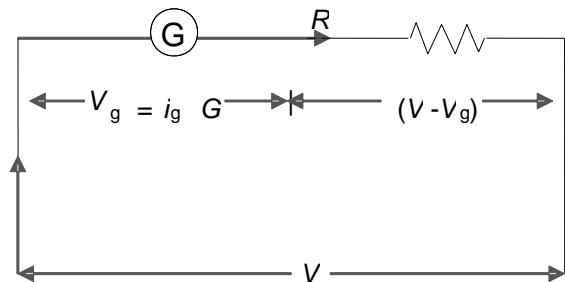To convert a moving coil galvanometer (MCG) into a voltmeter a high resistance  $R$  is connected in series with (MCG) as shown below.



616 (a)

(i) Rate of chemical energy consumption

$$= 1.5 \times 2 = 3 \text{ W}$$

(ii) Rate of energy dissipation inside the cell

$$= 2 \times 2 \times 0.1 = 0.4 \text{ W}$$

(iii) Rate of energy dissipation inside the resistor

$$= (3 - 0.4) \text{ W} = 2.6 \text{ W}$$

(iv) Power output of source =  $(3 - 0.4) \text{ W} = 2.6 \text{ W}$

\*  $EI$  represents rate of chemical energy consumption of the cell.

\*  $I^2 r$  represents the rate of energy dissipation inside the cell.


\*  $(EI - I^2 r)$  represents the power output of the source of emf.

617 (d)

As resistance  $\propto$  Length


$$\therefore \text{Resistance of each arm} = \frac{12}{3} = 4 \Omega$$
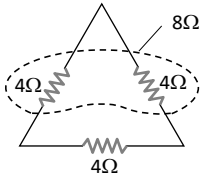
$$\therefore R_{\text{effective}} = \frac{4 \times 8}{4 + 8} = \frac{8}{3} \Omega$$



618 (a)

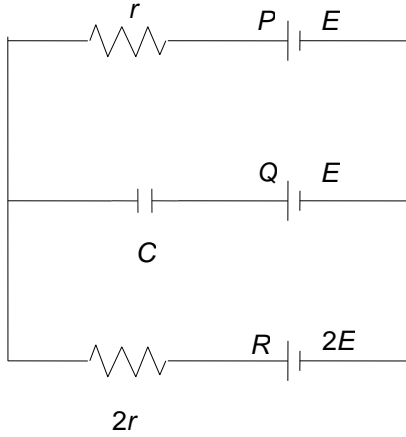In the steady state, no current flows through capacitor branch.



Current in the circuit


$$i = \frac{\text{net emf}}{\text{net resistance}} = \frac{2E - E}{r + 2r} = \frac{E}{3r}$$

So, potential drop across capacitor

$$V = ir = \frac{E}{3r} \times r = \frac{E}{3}$$

619 (a)

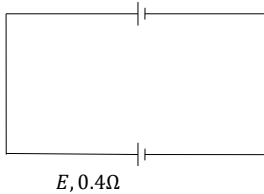Given that, the resultant voltage across the battery is  $1.5V$



Let  $I$  be the current in the circuit then total resistance  $= 0.6\Omega$

Hence,  $V = IR$

$$\Rightarrow 1.5 = I \times 0.6$$

$$\Rightarrow I = \frac{1.5}{0.6} \Rightarrow I = \frac{5}{2} A$$

Now, applying Kirchoff's second law in the circuit

$$0.4I + 0.2I + 1.2 - E = 0$$

$$0.6 \times \frac{5}{2} + 1.2 = E$$

$$\Rightarrow E = 2.7V$$

620 (a)


Effective resistance of  $n$  resistance each of the

resistance  $r$  in series  $R_s = r \times n = R$  (as per question); so  $r = R/n$ . When these resistances are connected in parallel, the effective resistance

$$R_p = r/n = \frac{R/n}{n} = R/n^2$$

621 (c)

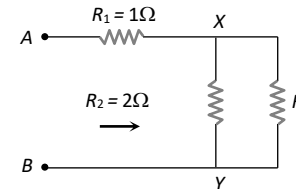Let the resultant resistance be  $R$ . If we add one more branch, then the resultant resistance would be the same because this is an infinite sequence



$$\therefore \frac{RR_2}{R + R_2} + R_1 = R \Rightarrow 2R + R + 2 = R^2 + 2R$$

$$\Rightarrow R^2 - R - 2 = 0 \Rightarrow R = -1 \text{ or } R = 2\text{ohm}$$

622 (b)

When two similar bulbs of different powers are connected in series, then

$$\frac{1}{P} = \frac{1}{P_1} + \frac{1}{P_2}$$

Given,  $P_1 = 200 \text{ W}, P_2 = 100 \text{ W}$

$$\Rightarrow \frac{1}{P} = \frac{1}{200} + \frac{1}{100}$$

$$\Rightarrow P = \frac{200}{3} = 66.7 \text{ W}$$

623 (b)


This is a balanced Wheatstone bridge circuit. So potential at  $B$  and  $D$  will be same and no current flows through  $4R$  resistance

624 (a)

Equivalent resistance of the circuit  $R = \frac{3}{2}\Omega$

$\therefore$  Current through the circuit  $i = \frac{V}{R} = \frac{3}{3/2} = 2A$


625 (d)

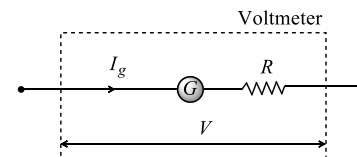

Here,  $V = 10 \text{ V}, R = 10k\Omega, G = 100 \Omega = 0.1 k\Omega$

$$V = I_g(G + R)$$
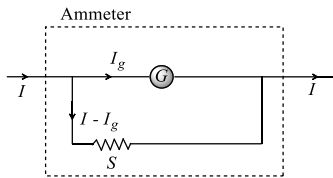
$$I_g = \frac{V}{G + R} = \frac{10V}{(10 + 0.1)k\Omega} = \frac{10V}{10.1k\Omega} = 0.99mA \approx 1 \text{ mA}$$



Here,  $I = 1A, (I - I_g)S = I_g G$

$$S = \frac{I_g G}{I - I_g} = \frac{1 \times 10^{-3} \times 100}{1 - 1 \times 10^{-3}}$$

$$\approx \frac{100 \times 10^{-3}}{1} = \frac{100}{1000} \Omega = \frac{1}{10} \Omega = 0.1 \Omega$$

626 (c)

Resistance,  $R = \frac{\rho \lambda}{A}$

For given problem,

$$R \propto \lambda^2$$

$$\therefore \frac{R_1}{R_2} = \frac{\lambda_1^2}{\lambda_2^2}$$

$$R_2 = \left(\frac{\lambda_2}{\lambda_1}\right)^2 \times R_1 = 15.6 \Omega$$


627 (b)

$$E = \frac{e}{(R + R_h + r)} \cdot \frac{R}{L} \times l$$

$$\Rightarrow 10 \times 10^{-3} = \frac{2}{(10 + R + 0)} \times \frac{10}{1} \times 0.4 \Rightarrow R = 790 \Omega$$

628 (a)

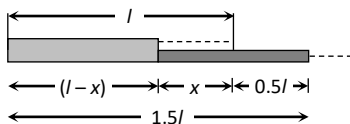Let  $l$  be the original length of wire and  $x$  be its length stretched uniformly such that final length is  $1.5l$




Then  $4R = \rho \frac{(l-x)}{A} + \rho \frac{(0.5l+x)}{A'}$  where  $A' = \frac{x}{(0.5l+x)} A$

$$\therefore 4\rho \frac{l}{A} = \rho \frac{l-x}{A} + \rho \frac{(0.5l+x)^2}{xA}$$

$$\text{or } 4l = l - x + \frac{1l^2}{4x} + \frac{x^2}{x} + \frac{lx}{x} \text{ or } \frac{x}{l} = \frac{1}{8}$$

629 (b)

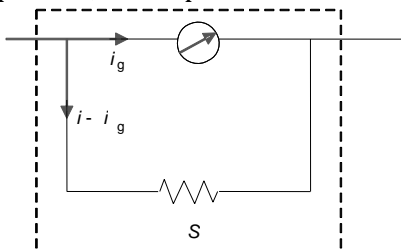The galvanometer  $G$  and shunt  $S$  is connected in parallel, hence potential difference is the same.



$$\therefore i_g \times G = (i - i_g) \times S$$

$$\Rightarrow \frac{i_g}{i - i_g} = \frac{S}{G} = \frac{5}{50} = \frac{1}{10}$$

$$\Rightarrow 10i_g = i - i_g$$

$$\Rightarrow 11i_g = i$$

$$\Rightarrow \frac{i_g}{i} = \frac{1}{11}$$

630 (d)


If  $T$  is the smallest temperature difference that can be detected, then

$$40 \times 10^{-6} T = 100 \times 10^{-6}$$

$$\Rightarrow T = 2.5^\circ \text{C}$$

631 (a)

The circuit diagram is follows:

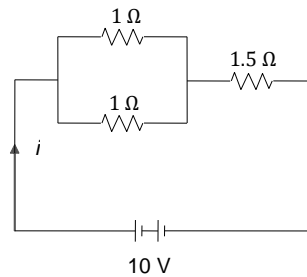

For  $1\Omega$  resistors in parallel, the resultant resistance is

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

Where,  $R_1 = R_2 = 1\Omega$

$$\therefore \frac{1}{R} = \frac{1}{1} + \frac{1}{1} = \frac{2}{1}$$

$$\Rightarrow R = 0.5\Omega$$

This  $0.5\Omega$  resistor is connected in series with  $1.5\Omega$  resistor.

Hence, equivalent resistance is

$$R' = 0.5 + 1.5 = 2\Omega$$


From Ohm's law, current flowing in the circuit is given by

$$V = iR$$

$$\Rightarrow i = \frac{V}{R} = \frac{10}{2} = 5A$$

632 (b)

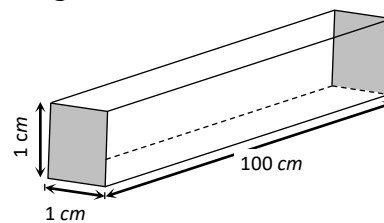
Length  $l = 1 \text{ cm} = 10^{-2} \text{ m}$



Area of cross-section  $A = 1 \text{ cm} \times 100 \text{ cm}$   
 $= 100 \text{ cm}^2 = 10^{-2} \text{ m}^2$

$$\text{Resistance } R = 3 \times 10^{-7} \times \frac{10^{-2}}{10^{-2}} = 3 \times 10^{-7} \Omega$$

633 (a)

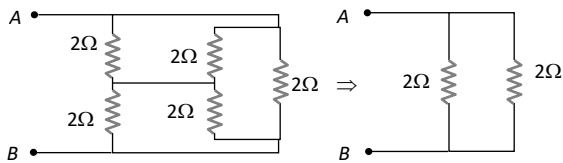

$$R_{AB} = \frac{2 \times 2}{2 + 2} = 1\Omega$$

634 (c)

$R_2, R_3$  and  $R_4$  are in parallel order, so their equivalent resistance

$$\begin{aligned} \frac{1}{R'} &= \frac{1}{R^2} + \frac{1}{R^3} + \frac{1}{R^4} \\ &= \frac{1}{50} + \frac{1}{50} + \frac{1}{75} \\ &= \frac{30 + 30 + 20}{1500} \\ &= \frac{80}{1500} = \frac{4}{75} \end{aligned}$$

$$\therefore R' = \frac{75}{4}\Omega$$

$$\begin{aligned} R &= R_1 + R' = 100 + \frac{75}{4} \\ &= \frac{475}{4}\Omega = 118.75\Omega \end{aligned}$$

635 (d)

Two resistances in series are connected in parallel with the third. Hence  $\frac{1}{R_p} = \frac{1}{4} + \frac{1}{8} = \frac{3}{8} \Rightarrow R_p = \frac{8}{3}\Omega$

636 (c)

Manganin or constantan are used for making the potentiometer wire

637 (c)

$$\frac{J_1}{J_2} = \frac{I/\pi r_1^2}{I/\pi r_2^2} = \left(\frac{r_2}{r_1}\right)^2 = \left(\frac{3}{1}\right)^2 = \frac{9}{1}$$

638 (b)

When temperature of the hot junction of a thermocouple rises, the thermo-emf increases and becomes maximum at a particular temperature. This temperature is called neutral temperature.

$$\text{Given, } e = at + \frac{1}{2}bt^2$$

Differentiating with respect to  $t$ , we get

$$\frac{de}{dt} = a + bt$$

For maximum value of  $e$ ,

$$\frac{de}{dt} = 0$$

$$\therefore a + bt = 0$$

$$\Rightarrow t = -\frac{a}{b}$$

639 (a)

$$R = 32 \times 10^4 \pm 5\%$$

640 (d)

$$H = i^2 RT = i^2 \left(\frac{\rho l}{A}\right) t = \frac{i^2 \rho V t}{A^2} \quad [V = \text{volume} = Al]$$

$$\Rightarrow H \propto \frac{1}{r^4} \Rightarrow \frac{H_1}{H_2} = \left(\frac{r_2}{r_1}\right)^4 = \left(\frac{2}{1}\right)^4 = \frac{16}{1}$$

642 (c)

When key  $K$  is opened, bulb  $B_2$  will not draw any current from the source, so that terminal voltage of source increases. Hence, power consumed by bulb increases, so light of the bulb becomes more. The brightness of bulb  $B_1$  decreases.

643 (b)

Let the internal resistance of cell be  $r$ , then

$$i = \frac{E}{R + r} \Rightarrow 15 = \frac{1.5}{0.04 + r} \Rightarrow r = 0.06\Omega$$

644 (d)

Given circuit is a balanced Wheatstone bridge circuit. So there will be no change in equivalent resistance. Hence no further current will be drawn

645 (d)

Current through arm  $ABC$ ,

$$= 4/(40 + 60) = 0.04 \text{ A}$$

Potential difference across  $A$  and  $B$ ,

$$V_A - V_B = 0.04 \times 40 = 1.6\text{V}$$

Current through arm  $ADC$ ,

$$= 4/(90 + 110) = 4/200\text{A}$$

Potential difference between  $A$  and  $D$ ,

$$V_A - V_D = \frac{4}{200} \times 90 = 1.8\text{V}$$

$$\therefore V_B - V_D = (V_A - V_D) - (V_A - V_B)$$

$$1.8 - 1.6 = 0.2 \text{ V}$$

646 (b)

Given that,

$$\frac{l_1}{l_2} = \frac{4}{3} \text{ and } \frac{r_1}{r_2} = \frac{2}{3}$$

Here,  $l_1$  and  $l_2$  are the length of the wires while  $r_1$  and  $r_2$  are the radii of the wires.

Now, we know that

$$V = IR \Rightarrow IR = \text{constant}$$

$$\Rightarrow I_1 R_1 = I_2 R_2$$

$$\text{or } \frac{I_1}{I_2} = \frac{R_2}{R_1} \dots (i)$$

But we know that the resistance of the wire is

$$R = \frac{\rho l}{A}$$

Hence, from Eq (i)

$$\frac{I_1}{I_2} = \frac{\rho l_2 / A_2}{\rho l_1 / A_1}$$

Here,

$$R_1 = \frac{\rho l_1}{A_1}, R_2 = \frac{\rho l_2}{A_2} \text{ and } \rho_1 = \rho_2 = \rho$$

Because both wires are of same material.

$$\therefore \frac{I_1}{I_2} = \frac{l_2 A_1}{l_1 A_2}$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{l_2 \pi r_1^2}{l_1 \pi r_2^2}$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{l_2 r_1^2}{l_1 r_2^2}$$

$$\text{Here, } \frac{l_2}{l_1} = \frac{3}{4} \text{ and } \frac{r_1}{r_2} = \frac{2}{3}$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{3}{4} \times \left(\frac{2}{3}\right)^2$$

$$\text{Or } \frac{I_1}{I_2} = \frac{1}{3}$$

647 (a)

When temperature is raised, the ions/atoms of the conductor start vibrating with increased amplitude of vibration and greater frequency. Due to which the electrons moving towards the positive end of conductor will suffer more rapid collisions and hence time of relaxation ( $\tau$ ) decreases. As  $v_d \propto \tau$ , thus drift velocity decrease. Therefore  $v_d \propto 1/T$

648 (d)

$$R_{AB} = \frac{R}{3} + R = \frac{2}{3} + 2 = \frac{8}{3} = 2\frac{2}{3} \Omega$$

649 (b)

$$i = \frac{dQ}{dt} = 10 + 4t \text{ or } dQ = (10 + 4t)dt$$

$$\text{Integrating it, we get } Q = 10t + \frac{4t^2}{2} = 10t + 2t^2$$

$$\text{When } t = 10\text{s}, Q = 10 \times 10 + 2 \times 10^2 = 300 \text{ C}$$

650 (b)

Let  $q$  be the charge flowing through copper voltmeter.

The charge flowing through silver voltmeter =  $(2000 - q)$

$$\text{Now, } m = z_{\text{Cu}} q = z_{\text{Ag}} \times (2000 - q);$$

$$\therefore q = \frac{Z_{\text{Ag}}}{Z_{\text{Cu}}} \times (2000 - q)$$


$$= \frac{1.008 \times 10^{-6}}{3.36 \times 10^{-7}} \times (2000 - q)$$

$$q = 1500 \text{ C}$$

651 (c)

Bulbs  $A$  and  $B$  are in parallel.

There, effective power is

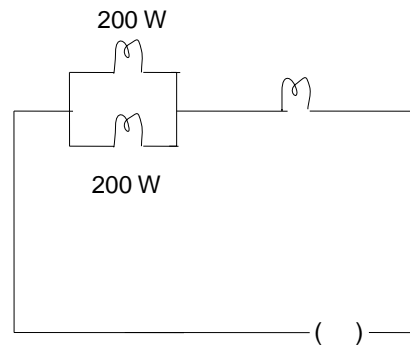

$$P' = P_A + P_B = 200 + 200 = 400 \text{ W}$$

Now  $P'$  and bulb  $C$  are in series. So, the resultant power of the combination is

$$P'' = \frac{400 \times 400}{400 + 400} = 200 \text{ W}$$

652 (c)

Resistances at  $C$  and  $B$  are not in the circuit. Use laws of resistances in series and parallel excluding the two resistance

653 (b)

Potential gradient along wire

$$= \frac{\text{potential difference along wire}}{\text{length of wire}}$$

$$\therefore 0.1 \times 10^{-3} = \frac{I \times 40}{1000} \text{ Vcm}^{-1}$$

Current in wire.

$$I = \frac{1}{400} A \text{ or } I = \frac{E}{R + R'}$$

$$\therefore \frac{1}{40 + R} = \frac{I}{400}$$

$$\text{Or } R = 800 - 40 = 760 \Omega$$

654 (b)

Just for your knowledge remember, voltaic cell uses dil.  $H_2SO_4$ ; Dry cell uses  $NH_4Cl + ZnCl_2$  paste; Daniel cell uses dil.  $H_2SO_4$ ; Lead Accumulator uses dil.  $H_2SO_4$  and  $Ni-Fe$  cell or Alkaline Accumulator uses  $KOH$  solution

655 (d)

Temperature of cold junction  $T_c$ , temperature of inversion  $T_i$  and neutral temperature  $T_n$  are related as follows

$$T_n = \frac{T_i + T_c}{2} \Rightarrow T_i = 2T_n - T_c$$

As  $T_n$  is constant for a given thermocouple  $T_i$  decreases with increase in  $T_c$

656 (b)

$$P = i^2 R \Rightarrow \frac{\Delta P}{P} = \frac{2\Delta i}{i} \quad [R \rightarrow \text{Constant}]$$

$$\Rightarrow \% \text{ change in power} = 2 \times \% \text{ change in current}$$


$$= 2 \times 1 = 2\%$$

658 (c)

$$\text{Power loss in transmission } P_L = \frac{P^2 R}{V^2} \Rightarrow P_L \propto \frac{1}{V^2}$$

659 (a)

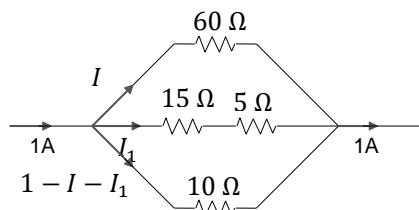All the resistances are in parallel order, so voltage across them will be equal.



$$\therefore 60I = (15 + 5)I_1$$

$$\Rightarrow 60I = 20I_1$$

$$\Rightarrow I_1 = 3I$$

$$\text{Again } (15 + 5)I_1 = 10(1 - I - I_1)$$

$$\Rightarrow 2I_1 = 1 - I - I_1$$

$$\Rightarrow 2(3I) = 1 - I - 3I$$

$$\Rightarrow 6I + 4I = 1$$


$$\Rightarrow 10I = 1$$

$$\therefore I = \frac{1}{10} = 0.1 \text{ A}$$

660 (b)

Equivalent circuit of this combination of resistances is as shown in figure. The effective resistance of arm
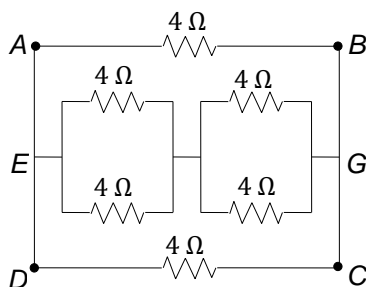
$$EG = \frac{4 \times 4}{4 + 4} = 2\Omega$$




Total resistances between A and B will be

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{4} + \frac{1}{4} = \frac{3}{4} \text{ or } R = \frac{4}{3}\Omega$$

661 (c)

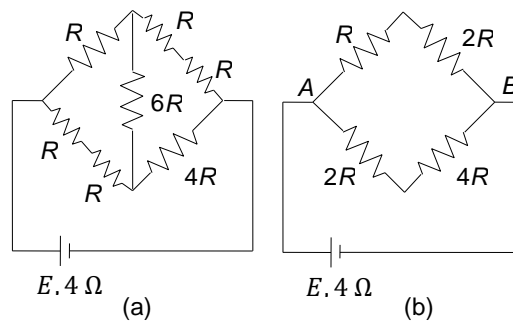The equivalent circuit is as shown in figure (a) and (b)



Since, the network of resistances is a balanced Wheat stone bridge, so resistance between points A and B of network figure (b) is given by

$$\frac{1}{R'} = \frac{1}{3R} + \frac{1}{6R} = \frac{2 + 1}{6R} = \frac{1}{2R} \text{ or } R' = 2R$$

For maximum power to the network,  $R'$  should be equal to internal resistance of the battery. So

$$R' = 2R = 4 \text{ or } R = 4/2 = 2\Omega$$

662 (d)

Let  $x$  watt be the power loss in transmission line in the form of heat

$$\therefore x = \left(\frac{P}{V}\right)^2 R = \left(\frac{10 \times 1000}{200}\right)^2 \times 0.2$$

$$= 500 \text{ W} = 0.5 \text{ kW}$$

Efficiency of transmission

$$= \frac{\text{power delivered by line}}{\text{power supplied to line}} = \frac{10 \text{ kW}}{10 \text{ kW} + x \text{ kW}}$$

$$= \frac{10}{10 + 0.5} = \frac{10}{10.5} = 0.95 = 95\%$$

663 (a)

$$H_1 = H_2 \Rightarrow \frac{v^2}{R} t_1 = \frac{v^2}{2R} t_2 \Rightarrow t_2 = 2t_1 \Rightarrow t_1 = 30 \text{ min}$$

$$\therefore t_2 = 60 \text{ min}$$

664 (a)

Significant figures		Multiplier
Brown	Black	Brown
1	0	$10^1$

$$\therefore R = 10 \times 10^1 = 100 \Omega$$

665 (a)

$$i = \frac{V}{R} \Rightarrow 2 = \frac{6}{\frac{6 \times 3}{6+3} + R} = \frac{6}{2 + R} \Rightarrow R = 1 \Omega$$

666 (c)

$$m = zq, z = \text{atomic mass / valence}$$

667 (b)

Resistance of series combination of  $3 \Omega$  and  $1 \Omega$  is  $R_1 = 3 + 1 = 4\Omega, R_2 = 8\Omega$

Let  $i$  be the total current in the circuit



Current through  $R_1$  is  $i_1 = \frac{i \times R_2}{R_1 + R_2} = \frac{i \times 8}{12} = \frac{2i}{3}$

Current through  $R_2$  is  $i_2 = \frac{i \times R_1}{R_1 + R_2} = \frac{i \times 4}{12} = \frac{i}{3}$

Power dissipated in  $3\Omega$  resistor is  $P_1 = i_1^2 \times 3$  ... (i)

Power dissipated in  $8\Omega$  resistor is  $P_2 = i_2^2 \times 8$  ... (ii)

$$\therefore \frac{P_1}{P_2} = \frac{i_1^2 \times 3}{i_2^2 \times 8} \text{ or } \frac{P_1}{P_2} = \frac{(2i/3)^2 \times 3}{(i/3)^2 \times 8} = \frac{12}{8} = \frac{3}{2}$$

$$P_1 = \frac{3}{2} \times P_2 = \frac{3}{2} \times 2 = 3 \text{ watt}$$

$\therefore$  Power dissipated across  $3\Omega$  resistor is 3 watt

668 (b)

The filament of the heater reaches its steady resistance when the heater reaches its steady temperature, which is much higher than the room temperature. The resistance at room temperature is thus much lower than the resistance at its steady state. When the heater is switched on, it draws a larger current than its steady state current. As the filament heats up, its resistance increases and current falls to steady state value

669 (d)

When cells are in series, emf of the combination of cells increases

670 (b)

Give that,

$$\frac{l_1}{l_2} = \frac{d_1}{d_2} = \frac{\rho_1}{\rho_2} = \frac{1}{2}$$

and  $R_1 = 10\Omega$

We know that, the resistance of the wire

$$R = \frac{\rho l}{A} = \frac{\rho l}{\pi \left(\frac{d}{2}\right)^2} = \frac{4\rho l}{\pi d^2} \left[ \because A = \pi \left(\frac{d}{2}\right)^2 \right]$$

So, the resistance of first wire is

$$R_1 = \frac{4\rho_1 l_1}{\pi d_1^2} \dots (i)$$

and the resistance of the second wire is

$$R_2 = \frac{4\rho_2 l_2}{\pi d_2^2} \dots (ii)$$

On dividing Eq. (ii) by Eq (i)

$$\begin{aligned} \frac{R_2}{R_1} &= \frac{\rho_2}{\rho_1} \times \frac{l_2}{l_1} \times \frac{d_1^2}{d_2^2} \\ \Rightarrow \frac{R_2}{10} &= \frac{2}{1} \times \frac{2}{1} \times \left(\frac{1}{2}\right)^2 \\ \Rightarrow \frac{R_2}{10} &= 1 \Rightarrow R_2 = 10\Omega \end{aligned}$$

671 (d)

Net resistance of  $3\Omega$  and  $7\Omega$  resistors (in series)  
 $R' = 3 + 7 = 10\Omega$

$R'$  and  $10\Omega$  are in parallel, so

$$R' = \frac{10 \times 10}{10 + 10} = 5\Omega$$

$R'$  and  $5\Omega$  are in series, so

$$R' = 5 + 5 = 10\Omega$$


Now,  $R'$  and  $10\Omega$  are in parallel, so

$$R = \frac{10 \times 10}{10 + 10} = 5\Omega$$

672 (c)

In mixed grouping the current in the external circuit will be maximum when the internal resistance of the battery is equal to the external resistance,

$$R = \frac{mr}{n}$$

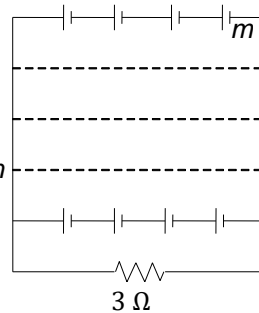

Given,  $R = 3\Omega, r = 0.5\Omega$

$$\therefore 3 = \frac{m}{n} \times 0.5$$

$$\Rightarrow \frac{m}{n} = 6$$

$$\Rightarrow m = 6n$$

Total number of cells =  $m \times n = 24$  ... (i)

From Eqs. (i) and (ii), we get ... (ii)

$$6n \times n = 24$$

$$\Rightarrow 6n^2 = 24$$

$$\Rightarrow n^2 = 4$$


$$\Rightarrow n = 2, m = 12$$

673 (c)

$$R_A = \frac{\rho l}{l \times t} = \frac{\rho}{t} \text{ and } R_B = \frac{\rho \times 2l}{2l \times t} = \frac{\rho}{t} \text{ i.e. } \frac{R_A}{R_B} = 1 : 1$$

674 (d)

The network can be redrawn as follows

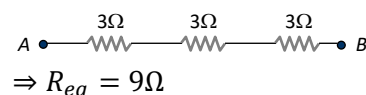

$$\Rightarrow R_{eq} = 9\Omega$$

675 (a)

Current flowing through both the bars is equal. Now, the heat produced is given by

$$H = I^2 R t$$

$$\text{or } H \propto R \text{ or } \frac{H_{AB}}{H_{BC}} = \frac{R_{AB}}{R_{BC}}$$

$$= \frac{(1/2r)^2}{(1/r)^2} \left( \because R \propto \frac{1}{A} \propto \frac{1}{r^2} \right)$$

$$= \frac{1}{4}$$

$$\text{or } H_{BC} = 4H_{AB}$$

677 (a)

Applying Kirchoff's law

$$(2 + 2) = (0.1 + 0.3 + 0.2)i \Rightarrow i = \frac{20}{3} A$$

Hence potential difference across A

$$= 2 - 0.1 \times \frac{20}{3} = \frac{4}{3} V \text{ [less than } 2V]$$

$$\text{Potential difference across } B = 2 - 0.3 \times \frac{20}{3} = 0$$

678 (b)


Here S consist of  $S_1$  and  $S_2$  arranged in parallel, hence

$$S = \frac{S_1 S_2}{S_1 + S_2}$$

$$\text{So, the balance condition will be } \frac{P}{Q} = \frac{R}{S} = \frac{R(S_1 + S_2)}{S_1 S_2}$$

679 (b)
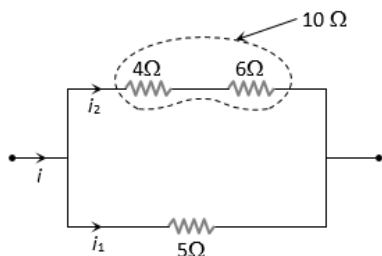
$$\frac{i_1}{i_2} = \frac{R_2}{R_1} = \frac{10}{5} = \frac{2}{1}$$



Also heat produced per sec i.e.  $\frac{H}{t} = P = i^2 R$

$$\Rightarrow \frac{P_5}{P_4} = \left( \frac{i_1}{i_2} \right)^2 \times \frac{5}{4} = \left( \frac{2}{1} \right)^2 \times \frac{5}{4} = \frac{5}{1} \Rightarrow P_4 = \frac{10}{5} = 2 \text{ cal/s}$$

680 (b)

$$\text{Here, } r = \frac{l_1 - l_2}{l_2} \times 2\Omega$$

Where  $l_1 = 240 \text{ cm}$ ,  $l_2 = 120 \text{ cm}$

$$\begin{aligned} \therefore r &= \frac{240 - 120}{120} \times 2 \\ &= \frac{120}{120} \times 2 \times 2\Omega \end{aligned}$$

681 (c)

Drift velocity  $v_d = \frac{i}{neA} \Rightarrow v_d \propto \frac{1}{A}$  or  $v_d \propto \frac{1}{d^2}$

$$\Rightarrow \frac{v_P}{v_Q} = \left( \frac{d_Q}{d_P} \right)^2 = \left( \frac{d/2}{d} \right)^2 = \frac{1}{4} \Rightarrow v_P = \frac{1}{4} v_Q$$

682 (b)

Because as temperature increases, the resistivity

increases and hence the relaxation time decreases for conductors ( $\tau \propto \frac{1}{\rho}$ )

683 (b)

Given, that, the two resistances  $R$  and  $2R$  are connected in parallel so the potential drop is equal for both.

The thermal energy developed in a circuit is

$$\begin{aligned} H &= \frac{V^2 t}{R} \Rightarrow H \propto \frac{1}{R} \\ \Rightarrow \frac{H_1}{H_2} &= \frac{R_2}{R_1} \Rightarrow \frac{H_1}{H_2} = \frac{2R}{R} \end{aligned}$$

[Here,  $R_1 = R$ ,  $R_2 = 2R$ ]

$$\text{Or } H_1 : H_2 = 2 : 1$$

684 (b)

When switch S is pressed, the resistance of circuit decreases. Hence, the current in bulb A will increase but the current in bulb B will decrease. Hence, the brightness of bulb A will increase and that of bulb B will decrease.

685 (b)

The equivalent resistance between two corners of equilateral triangle having resistance  $R$  in each arm =  $\frac{2R}{3} = 2 \times \frac{4}{3} = \frac{8}{3}\Omega$


686 (c)

$$\text{Thermal power in } A = P_A = \left( \frac{2i}{3} \right)^2 3R = \frac{4}{3} i^2 R$$

$$\text{Thermal power in } B = P_B = \left( \frac{i}{3} \right)^2 6R = \frac{2}{3} i^2 R$$

Thermal power in

$$C = P_C = i^2 R$$

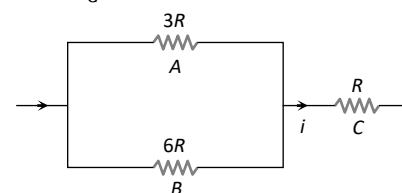

$$\Rightarrow P_A : P_B : P_C$$

$$= \frac{4}{3} : \frac{2}{3} : 1 = 4 : 2 : 3$$

687 (b)

Let  $n$  be the number of wrongly connected cells  
Number of cells helping one another =  $(12 - n)$

Total e.m.f. of such cells =  $(12 - n)E$

Total e.m.f. of cells opposing =  $nE$

Resultant e.m.f. of battery =  $(12 - n)E - nE = (12 - 2n)E$

Total resistance of cells =  $12r$

( $\because$  resistance remains same irrespective of connections of cells)

With additional cells

(a) Total e.m.f. of cells when additional cells help

$$\text{battery} = (12 - 2n)E + 2E$$

$$\text{Total resistance} = 12r + 2r = 14r$$

$$\therefore \frac{(12-2n)E+2E}{14r} = 3 \quad \dots(i)$$

(b) Similarly when additional cells oppose the battery

$$\frac{(12-2n)E-2E}{14r} = 2 \quad \dots(ii)$$

Solving (i) and (ii),  $n = 1$

688 (b)

$$\text{By using } \frac{P}{Q} = \frac{R}{S} \Rightarrow \frac{2}{2} = \frac{2}{\frac{6S}{(6+S)}} \Rightarrow S = 3\Omega$$

689 (c)

$$R = \frac{V}{i_g} - G = \frac{6}{6 \times 10^{-3}} - 25 = 975\Omega \text{ [In series]}$$

690 (c)

$$\therefore [\epsilon_0] = [M^{-1}L^{-3}T^4A^2] \text{ and } [E] = [MLT^{-3}A^{-1}]$$

$$\therefore \left[ \frac{1}{2} \epsilon_0 E^2 \right] = [M^{-1}L^{-3}T^4A^2] \times [MLT^{-3}A^{-1}]^2$$

$$= [ML^{-1}T^{-2}]$$

691 (c)

For figure (i)  $i_1 = 7A$

For figure (ii)  $i_2 = 4 + 3 = 7A$

For figure (iii)  $i_3 = 5 + 2 = 7A$

For figure (iv)  $i_4 = 6 - 1 = 5A$

692 (c)

Length of the wire is

$$l = \frac{RA}{\rho}$$

$$\therefore l = \frac{4 \times \pi \times (0.7 \times 10^{-3})^2}{2.2 \times 10^{-8}} = 280m$$

693 (a)

$$\text{Resistance of } V_1 = 80 \times 200 = 16000\Omega$$

$$\text{Resistance of } V_2 = 32000\Omega$$

The current flowing in the circuit is given by

$$i = \frac{80}{16000} = \frac{1}{200}A$$

Total resistance of the circuit

$$= 16000 + 32000 = 48000\Omega$$

Line voltage =  $iR$

$$= \frac{48000}{200} = 240V$$

694 (a)

According to ohm's law  $V = iR$

$$\Rightarrow \log_e V = \log_e i$$

$$+ \log_e R$$

$$\Rightarrow \log_e i = \log_e V - \log_e R$$

The graph between  $\log_e i$  and  $\log_e V$  will be a straight line which cuts  $\log_e V$  axis and its gradient will be positive

695 (d)

Current for 50 divisions,

$$I_g = \frac{1 \times 50}{10} = 2mA$$

$$\therefore \frac{I_g}{I} = \frac{S}{S+G}$$

$$\Rightarrow I = \left( \frac{S+G}{S} \right) I_g$$

Or

$$I = \left( \frac{4+20}{4} \right) 5mA = 30mA$$


696 (c)

As voltage across the resistors  $R_2$  and  $R_3$  is same and they show same dissipation of energy, so using the relation for energy,  $H =$

$\frac{V^2}{R}t$ , we have  $R_2 = R_3$ . Thus, the current in each

resistor  $R_2$  and  $R_3$  will be  $I/2$

ie,  $I_1 = I/2$  and  $I_2 = I/2$

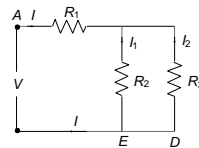

Since the energy dissipation is same in all the three resistors, so

$$I^2 R_1 t = I_1^2 R_2 t$$

$$\text{or } I^2 R_1 t = (I/2)^2 R_2 t$$

$$\text{or } R_1 = R_2/4$$

697 (c)

According to Faraday's first law of electrolysis, mass deposited

$$m = ZIt$$

Where  $Z$  = electrochemical equivalent of substance

$$\therefore \frac{m_1}{m_2} = \frac{I_1}{I_2} \times \frac{t_1}{t_2}$$

$$\text{Or } \frac{xg}{m_2} = \frac{4A}{6A} \times \frac{60 \text{ min}}{40 \text{ min}} \text{ or } m^2 = xg$$

698 (d)

$$S = \left( \frac{100-l}{l} \right) \cdot R$$


$$\text{Initially, } 30 = \left( \frac{100-l}{l} \right) \times 10 \Rightarrow l = 25cm$$

$$\text{Finally, } 10 = \left( \frac{100-l}{l} \right) \times 30 \Rightarrow l = 75cm$$

So, shift = 50cm

699 (b)

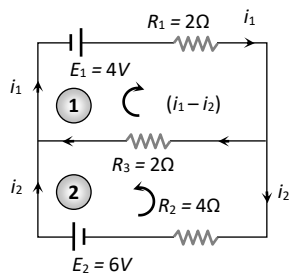Applying Kirchoff's law for the loops (1) and (2) as shown in figure



For loop (1)

$$-2i_1 - 2(i_1 - i_2) + 4 = 0$$

$$\Rightarrow 2i_1 - i_2 = 2 \quad \dots(i)$$

For loop (2)

$$-2(i_1 - i_2) + 4i_2 - 6 = 0$$

$$\Rightarrow -i_1 + 3i_2 = 3 \quad \dots(ii)$$

On solving equation (i) and (ii),  $i_1 = 1.8A$

700 (c)

$$\text{Current, } i = \frac{dQ}{dt} = \frac{d}{dt}(5t^2 + 3t + 1) = 10t + 3$$

When  $t=5s$

$$i = 10 \times 5 + 3 = 53A$$

701 (a)

Because  $H_2O$  is used as electrolyte

702 (c)

In a potentiometer there is no current drawn from the cell whose emf is to be measured whereas a voltmeter always draws some current from the cell. Hence, the emf of a cell can be measured accurately using a potentiometer.

703 (d)

For balanced Wheatstone bridge

$$\frac{P}{R} = \frac{S}{Q}$$

704 (c)

Resistance of the wire is given by

$$R = \rho \frac{l}{A} = \rho \frac{l^2}{Al} = \frac{\rho l^2}{V} \quad (\because Al = V)$$

So,

$$R \propto l^2 \quad (\text{if density remains same})$$

$$\text{or } \frac{R'}{R} = \frac{(2l)^2}{(l)^2} = 4$$

$$R' = 4R$$

Hence, change in resistance

$$= 4R - R = 3R$$

$$\text{Therefore, } \frac{\text{change in resistance}}{\text{original resistance}} = \frac{3R}{1R} = 3:1$$

705 (c)

$$\text{Resistance of a bulb} = \frac{(\text{Rated voltage})^2}{(\text{Rated power})}$$

$$R_{B_1} = \frac{(220)^2}{40} \Omega \text{ and } R_{B_2} = \frac{(220)^2}{60} \Omega$$

When the bulbs are connected in series,

$$R_S = R_{B_1} + R_{B_2}$$

$$= \frac{(220)^2}{40} + \frac{(220)^2}{60} = (220)^2 \left[ \frac{1}{40} + \frac{1}{60} \right]$$

$$= (220)^2 \left[ \frac{60 + 40}{60 \times 40} \right] = (220)^2 \left( \frac{100}{2400} \right) = \frac{(220)^2}{24}$$

$$\therefore P_1 = \frac{V_S^2}{R_S} = (220)^2 \times \frac{24}{(220)^2} = 24W$$

When the bulbs are connected in parallel

$$\frac{1}{R_p} = \frac{1}{R_{B_1}} + \frac{1}{R_{B_2}} \Rightarrow \frac{1}{R_p} = \frac{40}{(220)^2} + \frac{60}{(220)^2}$$

$$\frac{1}{R_p} = \frac{100}{(220)^2} \text{ or } R_p = \frac{(220)^2}{100}$$

$$\therefore P_2 = \frac{V_S^2}{R_p} = (220)^2 \times \frac{100}{(220)^2} = 100W$$

$$\therefore \frac{P_1}{P_2} = \frac{24W}{100W} = 0.24$$

706 (d)

The resistance  $AB$ ,  $BC$  and  $CD$  in series. The total resistance is

$$R_1 = 2 + 2 + 2 = 6\Omega$$

The resistance  $AE$ ,  $EF$  and  $FD$  in series. The total resistance is

$$R_2 = 2 + 2 + 2 = 6\Omega$$

The resistance  $BE$  and  $CF$  are in effective

$\therefore R_1$  and  $R_2$  are in parallel

$\therefore$  The total resistance

$$R = \frac{6 \times 6}{6 + 6} = 3\Omega$$

The current in the circuit

$$I = \frac{V}{R} = \frac{3}{3} = 1.0A$$

707 (b)

$$P \propto \frac{1}{R} \text{ and } R \propto l \Rightarrow P \propto \frac{1}{l}$$

$$\Rightarrow \frac{P_1}{P_2} = \frac{l_2}{l_1} \Rightarrow \frac{P_1}{P_2} = \frac{(100 - 10)}{100} = \frac{90}{100} \Rightarrow P_2$$

$$= 1.11P_1$$

$$\% \text{ change in power} = \frac{P_2 - P_1}{P_1} \times 100 = 11\%$$

708 (d)

Potential difference across  $PQ$  i.e. p.d. across the resistance of  $20\Omega$  is  $V = i \times 20$

$$\text{and } i = \frac{48}{(100+100+80+20)} = 0.16A$$

$$\therefore V = 0.16 \times 20 = 3.2V$$

709 (b)


$$\text{Drift velocity, } v_d = \frac{I}{neA}$$

$$\Rightarrow v_d = \frac{5}{(5 \times 10^{26}) \times (1.6 \times 10^{-19}) \times (4 \times 10^{-6})}$$

$$= \frac{1}{64} = 1.56 \times 10^{-2} \text{ms}^{-1}$$

710 (c)

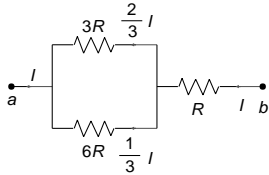Let current flow from  $b$  to  $a$  as shown



Ratio of thermal power is  $\left(\frac{2}{3}I\right)^2 3R : \left(\frac{1}{3}I\right)^2 6R : I^2 R$   
 or  $\frac{4}{3} : \frac{2}{3} : 1$  or  $4 : 2 : 3$ .

711 (c)

Both plates have same thickness,

$$R_R = \frac{\rho l}{ld} \text{ and } R_S = \frac{\rho 2l}{2ld}$$

$$\therefore \frac{R_1}{R_2} = 1$$

712 (c)

$$R = 56 \times 10 \pm 10\% = 560 + 10\%$$


713 (b)

$$R \propto \frac{l}{r^2} \Rightarrow \frac{R_2}{R_1} = \frac{l_2}{l_1} \times \frac{r_1^2}{r_2^2} = \left(\frac{2}{1}\right) \times \left(\frac{1}{2}\right)^2 = \frac{1}{2}$$

$\Rightarrow R_2 = \frac{R_1}{2}$ , specific resistance doesn't depend upon length, and radius

714 (d)

The circuit reduces to

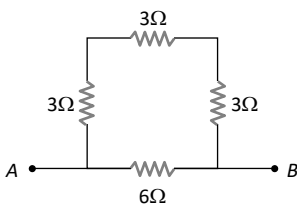

$$R_{AB} = \frac{9 \times 6}{9 + 6} = \frac{9 \times 6}{15} = \frac{18}{5} = 3.6\Omega$$

715 (c)

For semiconductor the temperature coefficient of resistance ( $\alpha$ ) is negative. Hence, resistivity will decrease with the temperature rise.

716 (b)


$$\frac{R_1}{R_2} = \frac{m_1}{a_1^2} \times \frac{a_2^2}{m_2}$$

$$= \left(\frac{m_1}{m_2}\right) \left(\frac{a_2}{a_1}\right)^2 = \left(\frac{1}{2}\right) (1)^2 = \frac{1}{2}$$

$$\frac{Q_1}{Q_2} = \frac{I^2 R_1 t}{I^2 R_2 t} = \frac{1}{2}$$

717 (a)

$$R_{AB} = \frac{R/2}{2} = \frac{R}{4}$$

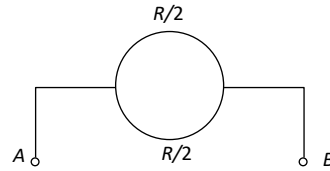


718 (a)

$$\frac{R_1}{R_2} = \left(\frac{l_1}{l_2}\right)^2 \Rightarrow \frac{10}{R_2} = \left(\frac{5}{20}\right)^2 = \frac{1}{16} = R_2 = 160\Omega$$

719 (a)

In closed loop  $EFGDE$

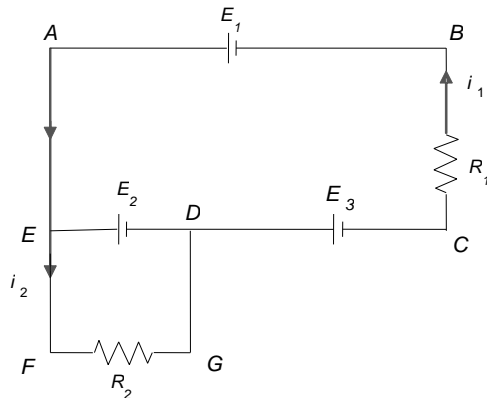

$$i_2 R_2 = E_2$$

$$i_2 \times 30 = 3$$

$$i_2 = 0.1A$$

In closed loop  $ABCEA$

$$-i_1 R_1 - E_1 + E_2 + E_3 = 0$$

$$-i_1 \times 10 - 3 + 3 + 2 = 0$$

$$i_1 = 0.2A$$

720 (a)

If  $E$  is the emf of the battery,  $r$  the internal resistance,  $i$  the current drawn and  $V$  the PD across the plates of battery, then

$$V = E - ir$$

**Case I** When the direction of current in the battery

is from -ve to +ve or outside +ve to -ve, then

$$i = +ve \quad (\text{during discharging})$$

$$V < E$$

**Case II** When the direction of current in the

battery is from +ve to -ve or outside -ve to +ve, then

$$i = -ve \quad (\text{during discharging})$$

$$V = E + ir$$

$$\Rightarrow V > E$$

**Case III** When zero current, then

$$i = 0$$

$$V = E$$

721 (b)

If  $B_2$  or  $B_3$  is disconnected, resistance is increased.

Due to which current in the circuit is decreased.

Therefore bulb  $B$ , will become dimmer.

722 (d)

Specific resistance doesn't depend upon length and area

723 (a)

$$m = Zit \Rightarrow Z = \frac{m}{it} = \frac{4.572}{5 \times 45 \times 60} = 3.387 \times 10^{-4} \text{ gm/C}$$


724 (a)

Red, brown, orange, silver red and brown represents the first two significant figures

Significant figures		Multiplier	Tolerance
Red	Brown	Orange	Silver
2	1	$10^3$	$\pm 10\%$

$$\therefore R = 21 \times 10^3 \pm 10\%$$

725 (a)

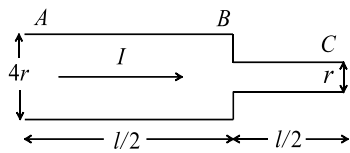

$$V_{AB} = I \cdot R_{AB} = \frac{I \cdot \rho \cdot L_{AB}}{A_1} = \frac{I \cdot \rho \cdot \left(\frac{L}{2}\right)}{\pi(2r)^2} = \frac{I \rho \cdot \left(\frac{L}{2}\right)}{\pi 4r^2}$$

$$V_{AB} = \frac{I \rho \cdot L}{8\pi r^2}$$

$$V_{BC} = I \cdot R_{BC} = \frac{I \cdot \rho \cdot L}{A_2}$$

$$= \frac{I \cdot \rho \cdot \frac{L}{2}}{\pi(r^2)} = \frac{I \cdot \rho \cdot L}{2\pi r^2} \Rightarrow \frac{V_{AB}}{V_{BC}} = \frac{\frac{I \rho L}{8\pi r^2}}{\frac{I \rho L}{2\pi r^2}} = \frac{2}{8} = \frac{1}{4}$$

$$V_{AB} = \frac{V_{BC}}{4}$$

Now for power loss


$$P_{AB} = V_{AB} \cdot I$$

$$P_{BC} = V_{BC} \cdot I$$

$$\frac{P_{AB}}{P_{BC}} = \frac{V_{AB}}{V_{BC}} = \frac{1}{4} \Rightarrow V_{AB} = \frac{P_{BC}}{4}$$

726 (c)
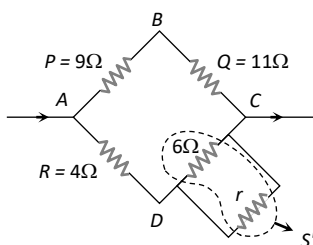
$$\frac{P}{Q} = \frac{R}{S'} \text{ [For balancing bridge]}$$



$$\Rightarrow S' = \frac{4 \times 11}{9} = \frac{44}{9}$$

$$\Rightarrow \frac{1}{S'} = \frac{1}{r} + \frac{1}{6}$$

$$\Rightarrow \frac{9}{44} - \frac{1}{6} = \frac{1}{r}$$

$$\Rightarrow r = \frac{132}{5} = 26.4 \Omega$$

727 (c)

Resistance of galvanometer

$$G = 50 \Omega$$

Full scale current  $i_g = 0.05$

$$A = 2.97 \times 10^{-2} \text{ cm}^2 = 2.97 \times 10^{-2} \times 10^{-4} \text{ m}^2 = 2.97 \times 10^{-6} \text{ m}^2$$

$$i = 5A$$

$$\rho = 5 \times 10^{-7} \Omega \text{m}$$


Required resistance to convert the galvanometer into ammeter.

$$R = \frac{i_g G}{i - i_g} = \frac{0.05 \times 50}{5 - 0.05} = \frac{2.5}{4.95}$$

$$\rho \frac{l}{A} = \frac{50}{99}$$

$$l = \frac{50}{99} \times \frac{A}{\rho} = \frac{50}{99} \times \frac{2.97 \times 10^{-6}}{5 \times 10^{-7}} = \frac{50}{99} \times \frac{29.7}{5} = 10 \times 0.3 = 3 \text{ m}$$

728 (c)

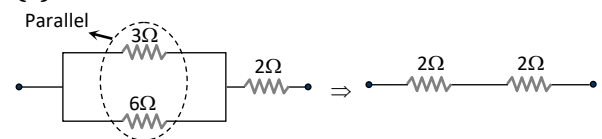


$$R_{eq} = 4 \Omega$$

729 (a)

Given, resistance of uniform wire = 24Ω.

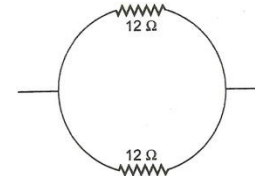When the wire is bent in the form of a circle, then resistance will divide the wire in two equal at opposite point in parallel



The effective resistance between the two end points on any diameter of the circle.


$$R = \frac{12 \times 12}{12 + 12}$$

$$\text{or } R = \frac{144}{24}$$

$$\text{or } R = 6 \Omega$$

731 (a)

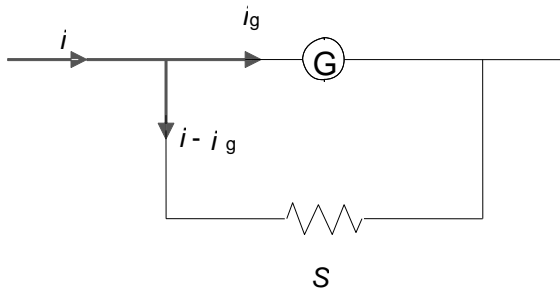To convert a galvanometer into an ammeter, a shunt resistance in parallel is connected to galvanometer.



Since, galvanometer  $G$  and shunt  $S$  are in parallel, hence

$$i_g G = (i - i_g) S$$

$$\Rightarrow S = \frac{i_g G}{i - i_g} = \frac{4 \times 10^{-3} \times 15}{6 - 4 \times 10^{-3}}$$

$$= \frac{60 \times 10^{-3}}{5.996} = 10 \times 10^{-3} \Omega = 10 \text{ m}\Omega$$

732 (b)

Here,  $m = 1 \text{ g} = 10^{-3} \text{ kg}$ ;  
 $z = 1.044 \times 10^{-8} \text{ kg C}^{-1}$   
 $H = 34 \text{ k cal.} = 34 \times 1000 \times 4.2 \text{ J}$   
 $q = \frac{m}{z} = \frac{10^{-3}}{1.044 \times 10^{-8}} = \frac{10^5}{1.044} \text{ C}$   
and  $V = \frac{H}{q} = \frac{34 \times 1000 \times 4.2}{(10^5/1.044)} = 1.5 \text{ V.}$

733 (c)

$$2 = \frac{\epsilon}{2 + r}$$

$$0.5 = \frac{\epsilon}{9 + r} \text{ or } \frac{2}{0.5} = \frac{9 + r}{2 + r} \therefore r = \frac{1}{3} \Omega$$

734 (c)

$$L \propto l$$

$$\frac{L_1}{L_2} = \frac{l_1}{l_2}$$

$$\frac{10}{11} = \frac{2.5}{l_2}$$

$$10l_2 = 2.5 \times 11$$

$$l_2 = \frac{2.5 \times 11}{10} = 2.75 \text{ m}$$

735 (d)

$$R = \rho l / A = 10$$

Now length  $l_1 = l + l/10 = 11l/10$

$$\therefore \text{New area } A_1 = Al/l_1$$


$$\therefore \text{New resistance,}$$

$$R_1 = \rho l_1 / A_1 = \rho(11l/10) / (10/11)A$$

$$= \frac{121 \rho l}{100 A} = \frac{121}{100} \times 10 = 12.1 \Omega$$

736 (a)

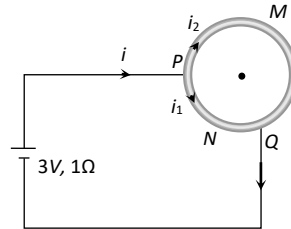In the following figure  
Resistance of part  $PNQ$ ;



$$R_1 = \frac{10}{4} = 2.5 \Omega \text{ and}$$

Resistance of part  $PMQ$ ;

$$R_2 = \frac{3}{4} \times 10 = 7.5 \Omega$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{2.5 \times 7.5}{(2.5 + 7.5)} = \frac{15}{8} \Omega$$

Main Current  $i = \frac{3}{\frac{15}{8} + 1} = \frac{24}{23} \text{ A}$

So,  $i_1 = i \times \left( \frac{R_2}{R_1 + R_2} \right) = \frac{24}{23} \times \left( \frac{7.5}{2.5 + 7.5} \right) = \frac{18}{23} \text{ A}$

and  $i_2 = i - i_1 = \frac{24}{23} - \frac{18}{23} = \frac{6}{23} \text{ A}$

737 (a)

Wheatstone bridge is balanced, therefore  
 $\frac{P}{Q} = \frac{R}{S}$  or  $1 = \frac{10}{S} \Rightarrow S = 10 \text{ ohm}$

738 (c)

$$v_d = \frac{I}{nAe} = \frac{20}{10^{29} \times 10^{-6} \times 1.6 \times 10^{-19}}$$

$$= 1.25 \times 10^{-3} \text{ m/s}$$

739 (d)


The resistance are connected in parallel hence, voltage will remain constant

$$E = \frac{V^2 t}{R}$$

$$\Rightarrow E \propto \frac{1}{R}$$

$$\frac{E_1}{E_2} = \frac{R_2}{R_1} = \frac{2R}{R} = \frac{2}{1}$$

740 (c)

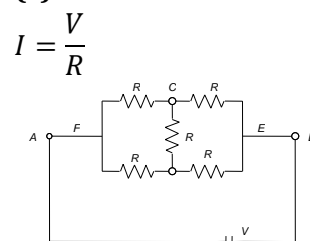

$$\therefore \text{Current in FC} = \frac{1}{2} = \frac{V}{2R}$$

741 (a)

Current sensitivity of a galvanometer is defined as the deflection produced in the galvanometer when a unit current flows through it.

If  $\theta$  is the deflection in the galvanometer when current  $I$  is passed through it, then

$$\text{Current Sensitivity } I_s = \frac{\theta}{I} = \frac{nBA}{k}$$

where  $k$  be restoring torque per unit twist,  $n$  be number of turns in the coil,  $B$  is strength of magnetic field in which coil is suspended,  $A$  be area of coil.

Since, restoring per unit twist (torsional constant) is minimum for galvanometer  $A$ , hence more sensitive.

742 (b)

Let the resistance of voltmeter is  $G\Omega$ .

$\therefore$  Total resistance of the circuit

$$R = \left( \frac{G \times 100}{G + 100} + 50 \right) \Omega$$

Total current

$$i = \frac{V}{G} = \frac{10}{\left( \frac{G \times 100}{G + 100} + 50 \right)}$$

Voltage across  $100\Omega$  resistance

$$= i \left( \frac{G \times 100}{G + 100} \right) = \frac{10}{\left( \frac{G \times 100}{G + 100} + 50 \right)} \times \left( \frac{G \times 100}{G + 100} \right)$$

Reading of voltmeter =  $5V$

$\therefore$  Voltage across  $100\Omega = 5V$


$$\therefore 5 = \frac{10}{\left( \frac{G \times 100}{G + 100} + 50 \right)} \times \left( \frac{G \times 100}{G + 100} \right)$$

On solving  $G = 100\Omega$

743 (b)

The distribution of current is as shown in figure.

As per question,

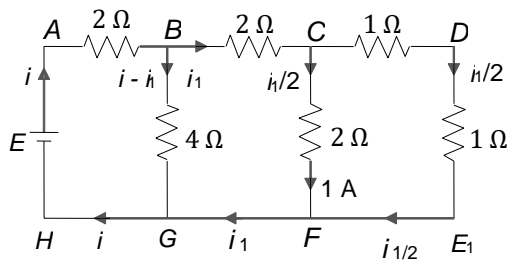

$$\frac{i_1}{2} = 1 \text{ or } i_1 = 2A$$

In a closed circuit  $ACFG$

$$2i + 2 \times \frac{i_1}{2} - 4(i - i_1) = 0$$

$$7i_1 = 4i$$

$$\text{or } i = \frac{7}{4}i_1 = \frac{7}{4} \times 2 = \frac{7}{2}A$$

Total resistance of the circuit between  $A$  and  $H$  is

$$= 2 + \frac{4 \times 3}{4 + 3} = \frac{26}{7}$$

$$\text{EMF of cell is } E = \frac{7}{2} \times \frac{26}{7} = 13V$$

744 (c)

$$i = q/T = qv$$

$$= 2 \times 10^{-2} \times 30 = 0.6 A$$

745 (a)

$$\text{Current } i = \frac{q}{t} = \frac{CV}{t} = \frac{(10 \times 10^{-6}) \times 40}{0.2}$$

$$= 2 \times 10^{-3} A = 2 \text{ mA}$$

746 (c)

Resistance of electric bulb  $R = \frac{V^2}{P}$  where subscripts denote for rated parameters.

$$R = \frac{(220)^2}{100}$$

Power consumed at  $110V$ ,  $P_{\text{consumed}} = \frac{V^2}{R}$

$$\therefore P_{\text{consumed}} = \frac{(110)^2}{(220)^2/100} = 25 \text{ W}$$


747 (c)

$$i = \frac{2 + 2}{1 + 1.9 + 0.9} = \frac{4}{3.8} A$$

$$\text{For cell } A \quad E = V + ir \Rightarrow V = 2 - \frac{4}{3.8} \times 1.9 = 0$$

748 (b)

The given circuit is

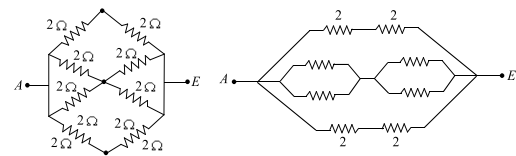

$$\frac{1}{\text{Req.}} = \frac{1}{4} + \frac{1}{2} + \frac{1}{4} \Rightarrow \frac{1}{\text{Req.}} = \frac{4}{4} \Rightarrow \text{Req.} = 1\Omega$$

749 (c)

$$R_1 \propto \frac{l}{A} \Rightarrow R_2 \propto \frac{2l}{2A} \text{ i.e. } R_2 \propto \frac{l}{A}$$

$$\therefore R_1 = R_2$$

751 (d)

$$R \propto l$$

Hence every new piece will have a resistance  $\frac{R}{10}$ . If

two pieces are connected in series, then their

$$\text{resistance} = \frac{2R}{10} = \frac{R}{5}$$

If 5 such combinations are joined in parallel, then

$$\text{net resistance} = \frac{R}{5 \times 5} = \frac{R}{25}$$

752 (b)


The current in a conductor depends on the drift velocity of electrons

753 (b)

The circuit arrangement shown in figure (b) is the



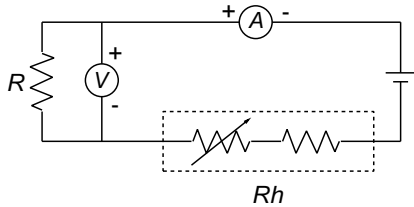correct arrangement for verification of Ohm's law. For convenience the same figure has been redrawn here. In the figure,  $R$  is the resistance, for which Ohm's law is to be verified. Voltmeter  $V$  is connected to its parallel and ammeter, cell and rheostat arrangement in the series.




754 (b)

$$\text{Resistivity, } \rho = \frac{m_e}{ne^2\tau}$$

$$\text{Conductivity, } \sigma = \frac{1}{\rho} = \frac{ne^2\tau}{m_e}$$

755 (a)

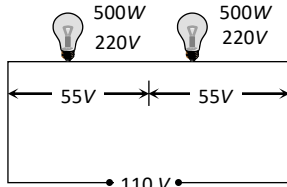Voltage across each bulb  $V' = \frac{110}{2} = 55V$  so, power consumed by each bulb will be




$$P' = \left(\frac{55}{220}\right)^2 \times 500$$

$$= \frac{125}{4} W$$

756 (b)

$$Q = at - bt^2$$
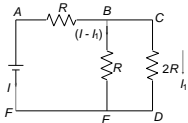
$$I = \frac{dQ}{dt} = a - 2bt \quad \dots (i)$$



Where,  $t = t_0, I = 0$

In loop BCDEB  $I_1(2R) - (I - I_1)R = 0$

or  $3I_1 = I$

$$\therefore I_1 = \frac{I}{3} = \frac{a - 2bt}{3}$$

$$\therefore H = \int_0^{t_0} I_1^2(2R) dt$$

$$= \frac{2R}{9} \int_0^{t_0} (a - 2bt)^2 dt$$

$$= \frac{2R}{9} \left[ \int_0^{t_0} (a^2 - 4b^2t^2 - 4at) dt \right]$$

$$= \frac{2R}{9} \left[ \left\{ a^2t + \frac{4b^2t^2}{3} - \frac{4bat}{2} \right\}_0^{t_0} \right]$$

$$= \frac{2R}{9} \left[ a^2t_0 + \frac{4b^2t_0^3}{3} - 2bat_0^2 \right]$$

but  $t_0 = \frac{a}{2b}$  [from Eqn.(i)]

$$H = \frac{2R}{9} \left[ a^2 \times \frac{a}{2b} + \frac{4b^2}{3} \frac{a^3}{8b^3} - 2ab \frac{a^2}{4b^2} \right]$$

$$= \frac{2R}{9} \left[ \frac{a^3}{2b} + \frac{a^3}{6b} - \frac{a^3}{2b} \right] = \frac{a^3R}{27b}$$

757 (d)

The energy stored in the capacitor  $= \frac{1}{2} CV^2$ ;

This energy will be converted into heat in the resistor.


$$H = \frac{1}{2} \times 4 \times 10^{-6} \times 400 \times 400$$

$$= 32 \times 10^{-2}$$

$$= 0.32 \text{ J}$$

758 (c)

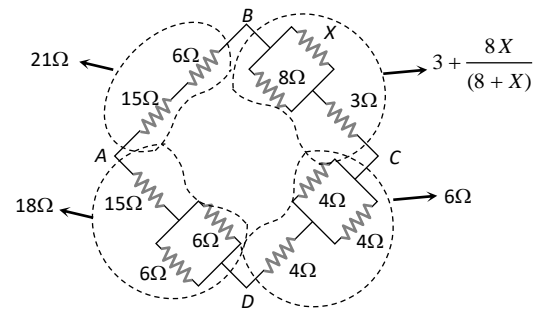Potential difference between  $B$  and  $D$  is zero, it means Wheatstone bridge is in balanced condition



$$\text{So } \frac{P}{Q} = \frac{R}{S} \Rightarrow \frac{21}{3 + \frac{8X}{8+X}} = \frac{18}{6} \Rightarrow X = 8\Omega$$

759 (d)

Resistance of heater

$$R_H = \frac{V^2}{P} = \frac{(100)^2}{1000} = 10 \Omega$$

Total resistance of circuit

$$R' = 10 + \frac{10 \times R}{10 + R} = \frac{100 + 20R}{10 + R}$$

Current in heater

$$I_H = I \cdot \frac{R}{10 + R} = \frac{100}{10 + 20R} \times \frac{R}{(10 + R)} = \frac{5 \times R}{5 + R}$$

$$\therefore \text{Power } P = I_H^2 R_H \Rightarrow \frac{25R}{(5 + R)^2} \times 10 = 62.5$$

$$\therefore R = 5\Omega$$

760 (d)

Let  $m_1 = m$ , then  $m_2 = 3m$  and  $m_3 = 5m$ . Again let  $L_3 = l$ , then  $L_2 = 3l$  and  $L_1 = 5l$ . If  $\sigma$  be the density of copper, then

$$A_1 = \frac{m_1}{L_1\sigma} = \frac{m}{5l\sigma}, A_2 = \frac{3m}{3l\sigma} \text{ and } A_3 = \frac{5m}{l\sigma}$$

Hence  $A_2 = \frac{5A_1}{3}$  and  $A_3 = 25A_1$


$$\therefore R_1 = \frac{\rho L_1}{A_1} = \frac{\rho \cdot 5l}{A_1}, R_2 = \frac{\rho L_2}{A_2} = \frac{\rho \cdot 3l}{5A_1} = \frac{3}{25}R_1,$$

$$\text{and } R_3 = \frac{\rho L_3}{A_3} = \frac{\rho l}{25A_1} = \frac{R_1}{125}$$

$$\therefore R_1 : R_2 : R_3 = R_1 : \frac{3}{25}R_1 : \frac{R_1}{125} = 125 : 15 : 1$$

761 (b)

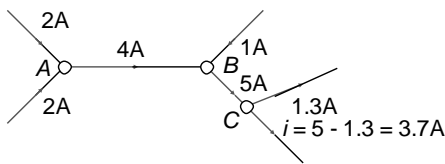Using Kirchhoffs first law we can find current distribution in the given part of electric circuit as shown in the adjoining figure. From figure  $i = 1.7A$



762 (b)

$$R = \frac{\rho L}{A}; R_1 = \frac{\rho 2L}{A} = 2R$$


$$m = A L d; m_1 = A 2 L d = 2m$$

$$\text{Now, } \frac{(3V)^2 t}{R} = mc\Delta T \quad \dots(i)$$

$$\text{and } \frac{(NV)^2 t}{2R} = 2mc\Delta T \quad \dots(ii)$$

Solving (i) and (ii), we get  $N = 6$ .

763 (a)

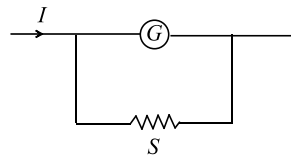

$$\frac{GS}{G+S} = \frac{V_G}{I} = \frac{25 \times 10^{-3}}{25}$$

$$\frac{GS}{G+S} = 0.001\Omega$$

Here  $S \ll G$  So

$$S = 0.001\Omega$$

764 (a)

$$P_{Rated} = \frac{V_{Rated}^2}{R} \Rightarrow R \propto \frac{1}{P_{Rated}} \quad [V - \text{constant}]$$

So bulb of high power will have less resistance

765 (a)

$$m = Zi t \Rightarrow i = \frac{m}{Zt} = \frac{0.99}{0.00033 \times 1200} = 2.5A$$

Hence heat generated in the coil is

$$H = i^2 R t = (2.5)^2 \times 0.1 \times 1200 = 750 J$$

766 (d)

The three resistances between A and B are parallel,

$$\frac{1}{R_{comb}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{9} + \frac{1}{9} + \frac{1}{9}$$

$$\frac{1}{R_{comb}} = \frac{3}{9}$$

$$\Rightarrow R_{comb} = 3\Omega$$

768 (d)

The temperature difference is  $20^\circ C = 20 K$ . So that thermo emf developed  $E = \alpha\theta = 40 \frac{\mu V}{K} \times 20K = 800 \mu V$

$$\text{Hence total emf} = 150 \times 800 = 12 \times 10^4 \mu V = 120 mV$$

769 (c)

Given, Thomson's coefficient,  $\sigma = 3\mu V/^\circ C$

$$\sigma = \frac{dV}{dT}$$

$$\text{or } dV = \sigma dT$$

$$\text{so } V = \sigma(T_2 - T_1)$$

$$\text{or } 3 \times 10^{-4} = 3 \times 10^{-6}(T_2 - 20)$$

$$\text{or } 100 + 20 = T_2$$

$$\text{or } T_2 = 120^\circ C$$

770 (d)

Terminal voltage  $V = E - Ir$ . Hence the graph between  $V$  and  $i$  will be a straight line having negative slope and positive intercept.


Thermal power generated in the external circuit  $P = EI - I^2 r$ . Hence graph between  $P$  and  $I$  will be a parabola passing through origin.

Also at an instant, thermal power generated in the cell  $= i^2 r$  and total electrical power generated in the cell  $= Ei$ . Hence the fraction  $\eta = \frac{i^2 r}{EI} = \left(\frac{r}{E}\right) I$ ;

so  $\eta \propto I$ . It means graph between  $\eta$  and  $I$  will be a straight line passing through origin

771 (d)

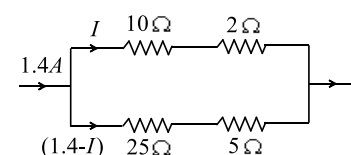Since it's a balanced Wheatstone bridge, the circuit can be redrawn as



$$12I = 30(1.4 I)$$

$$12I = 42 - 30I$$

$$\therefore I = 1 A$$

772 (c)

We know that when current flow is same then resistors are connected in series, hence resultant resistance is

$$R' = R_1 + R_2 = 10\Omega + 20\Omega = 30\Omega$$

Also since, cell are connected in opposite

directions, the resultant emf is

$$E = E_1 - E_2 = 5V - 2V = 3V$$

From Ohm's law  $E = iR$

$$\therefore i = \frac{E}{R} = \frac{3}{30} = 0.1A$$

773 (b)

In parallel,

$$\begin{aligned} R_p &= \frac{R_1 R_2}{R_1 + R_2} \\ &= \frac{5.0 \times 10.0}{5.0 + 10.0} \\ &= \frac{50}{15} = 3.3\Omega \end{aligned}$$


Also,

$$\begin{aligned} \frac{\Delta R_p}{R_p} \times 100 &= \frac{\Delta R_1}{R_1} \times 100 + \frac{\Delta R_2}{R_2} \times 100 \\ &\quad + \frac{\Delta(R_1 + R_2)}{R_1 + R_2} \times 100 \\ &= \frac{0.2}{5.0} \times 100 + \frac{0.1}{10.0} \times 100 + \frac{0.3}{15} \times 100 \\ &= 7\% \end{aligned}$$

$$R_p = 3.3\Omega \pm 7\%$$

774 (b)

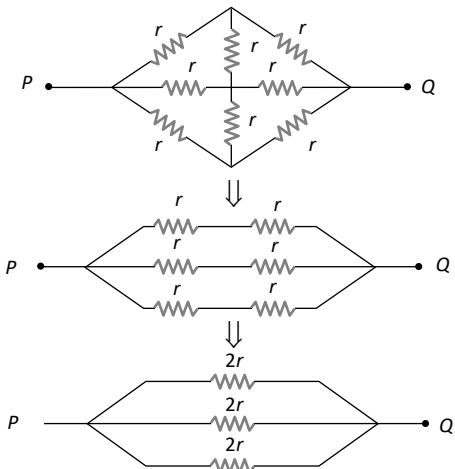The given circuit can be simplified as follows



$$R' = \frac{2r}{3} = \frac{2}{3} \times \frac{3}{2} = 1\Omega$$

775 (c)

Given,  $R_{300} = 0.3\Omega$ ,  $R_t = 0.6\Omega$

$$T = 300K = 27^\circ C$$

Temperature coefficient of resistance,

$$\alpha = 1.5 \times 10^{-3} K^{-1}$$

$$\therefore R_{300} = R_0(1 + \alpha \times 27)$$

$$0.3 = R_0(1 + 1.5 \times 10^{-3} \times 27) \dots (i)$$

$$\text{Again, } R_t = R_0(1 + \alpha t)$$

$$0.6 = R_0(1 + 1.5 \times 10^{-3} \times 27) \dots (ii)$$

Dividing Eq. (ii) by Eq. (i), we get

$$\frac{0.6}{0.3} = \frac{1 + 1.5 \times 10^{-3} t}{1 + 1.5 \times 10^{-3} \times 27}$$

$$\Rightarrow 2(1 + 1.5 \times 10^{-3} \times 27) = 1 + 1.5 \times 10^{-3} t$$

$$\Rightarrow 2 + 81 \times 10^{-3} = 1 + 1.5 \times 10^{-3} t$$

$$\Rightarrow 2 + 0.081 = 1 + 1.5 \times 10^{-3} t$$

$$\Rightarrow t = \frac{1.081}{1.5 \times 10^{-3}} = 720^\circ C = 993K$$

776 (c)

Temperature coefficient of resistance =  $\frac{1}{R_t} \frac{dR}{dt}$

$$= \frac{1}{R_0(1 + \alpha t + \beta t^2)} \frac{d}{dt} R_0(1 + \alpha t + \beta t^2)$$

$$= \frac{\alpha + 2\beta t}{1 + \alpha t + \beta t^2}$$

778 (a)

$$r = \left( \frac{l_1 - l_2}{l_2} \right) \times R' \Rightarrow r = \left( \frac{55 - 50}{50} \right) \times 10 = 1\Omega$$

779 (a)


$$\begin{aligned} R_1 &= \frac{\rho_1 l_1}{A} \text{ and } R_2 = \frac{\rho_2 l_2}{A}. \text{ In series } R_{eq} = R_1 + R_2 \\ \frac{\rho_{eq}(l_1 + l_2)}{A} &= \frac{\rho_1 l_1}{A} + \frac{\rho_2 l_2}{A} \Rightarrow \rho_{eq} = \frac{\rho_1 l_1 + \rho_2 l_2}{l_1 + l_2} \end{aligned}$$

780 (d)

In parallel combination  $E_{eq} = E = 6V$

781 (b)

From the figure

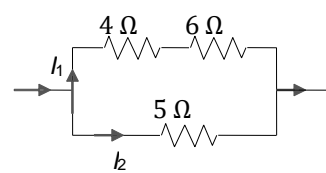

$$10I_1 = 5I_2 \quad I_2 = 2I_1 \dots (i)$$

Heat produced in resistance

$$I_2^2 R = I_2^2 \times 5$$

$$\therefore \times 5 = 10 \text{ cal s}^{-1} \dots (ii)$$

From Eqs. (i) and (ii), we have

$$I_1 = \frac{I_2}{2} = \frac{\sqrt{2}}{2} = \frac{1}{\sqrt{2}} A$$

Hence, heat produced in resistance of  $4\Omega$

$$I_2^2 \times 4 = \frac{1}{2} \times 4 = 2 \text{ cal s}^{-1}$$

782 (b)

No current flows through the capacitor branch in steady state. Total current supplied by the battery

$$i = \frac{6}{2.8 + 1.2} = \frac{3}{2}$$

$$\text{Current through } 2\Omega \text{ resistor} = \frac{3}{2} \times \frac{3}{5} = 0.9A$$

783 (d)

96500 coulombs of charge is needed to deposit one gram equivalent of an element at an electrode

784 (d)

Pressing the key does not disturb current in all resistances as the bridge is balanced. Therefore,

deflection in the galvanometer in whatever direction it was, will stay

785 (c)

Same mass, same material *i. e.* volume is same or  $Al = \text{constant}$

$$\text{Also, } R = \rho \frac{l}{A} \Rightarrow \frac{R_1}{R_2} = \frac{l_1}{l_2} \times \frac{A_2}{A_1} = \left(\frac{A_2}{A_1}\right)^2 = \left(\frac{d_2}{d_1}\right)^4$$

$$\Rightarrow \frac{24}{R_2} = \left(\frac{d}{d/2}\right)^4 = 16 \Rightarrow R_2 = 1.5\Omega$$

786 (b)

$$\pi = T dE/dT.$$

787 (d)

Resistance of the lamp

$$R_0 = \frac{V^2}{P} = \frac{(30)^2}{90} = 10 \Omega$$

Current in the lamp

$$i = \frac{30}{10} = 3 \Omega$$

When lamp is operated on a 120 V, then resistance

$$R' = \frac{V'}{i} = \frac{120}{30} = 40 \Omega$$

Thus, for proper glow, the resistance required to be put in series will be

$$R = R' - R_0 = 40 - 10 = 30 \Omega$$

789 (a)

When  $r$  is internal resistance of the battery and  $i$  the charging current, then

$$V = E + ir$$

$$V = 2 + 5 \times 0.1 = 2.5V$$

791 (b)

$$\text{Current flowing in the circuit } i = \frac{E}{R} = \frac{10-4}{20+10} = \frac{1}{5} A$$

$$\text{P.D. across } AC = \frac{1}{5} \times 20 = 4V$$

$$\text{P.D. across } AN = 4 + 4 = 8V$$

792 (d)

$$\rho = R \frac{A}{l} = \frac{V}{i} \times \frac{A}{l} = \frac{2}{4} \times \frac{10^{-6}}{0.5} = 10^{-6} \Omega m$$

793 (d)

Given,  $V = 1V$

$$I_g = 1mA$$

$$I_g = 1 \times 10^{-3} A$$

Resistance of galvanometer

$$R_g = 50\Omega$$

$$R_g = \frac{V}{I_g} - R_g$$

$$\text{or } R_s = \frac{1}{10^{-3}} - 50$$

$$\text{or } R_1 = 950\Omega$$

$$R'_2 = \frac{10}{10^{-3}} - 50 = 9950\Omega$$

$$\text{or } R_2 = R'_2 - R_1 = 9950 - 950$$

$$\text{or } R_2 = 9000\Omega$$


794 (a)

$$\text{Neutral temperature, } T_n = \frac{T_i + T_c}{2}$$

$$\text{or } T_i = 2T_n - T_c = 540^\circ C.$$

795 (c)

The simplified circuit is shown below

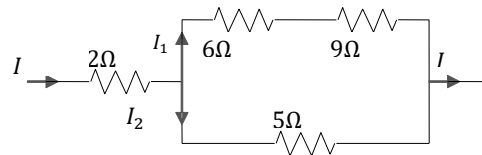

From figure,

$$15 I_1 = 5 I_2 \text{ or } I_2 = \frac{15 I_1}{5} = 3 I_1$$

$$\therefore I = I_1 + I_2 = \frac{I_2}{3} + I_2 = \frac{4 I_2}{3} \quad \dots (i)$$

$$\text{But } I_2^2 \times 5 = 42$$

$$\text{Or } I_2^2 = \frac{42}{5} = 8.4$$

Putting value of  $I_2$  in Eq. (i), we get

$$I = \frac{4}{3} \times \sqrt{8.4}$$

Therefore, heat dissipated across 2  $\Omega$

$$= I^2 \times 2 = \frac{16}{9} \times 8.4 \times 2$$

$$\approx 30 \text{ Js}^{-1}$$

796 (a)

The resistance of a conductor

$$\therefore R = \rho \frac{1}{\pi r^2}$$

$$\Rightarrow R \propto \frac{1}{r^2}$$

$$(a) R_1 = \frac{50}{(0.25 \times 10^{-1})^2} = 800 \times 10^2 \Omega$$

$$(b) R_2 = \frac{100}{(0.5 \times 10^{-1})^2} = 400 \times 10^2 \Omega$$

$$(c) R_3 = \frac{200}{(1 \times 10^{-1})^2} = 200 \times 10^2 \Omega$$

$$(d) R_4 = \frac{300}{(1.5 \times 10^{-1})^2} = 133.3 \times 10^2 \Omega$$

Hence, electrical resistance of first wire is maximum.

797 (b)

Using the concept of balanced wheat stone bridge, we have

$$\frac{P}{Q} = \frac{R}{S}$$


$$\frac{x}{52 + 1} = \frac{10}{48 + 2}$$

$$x = \frac{10 \times 53}{50}$$

$$= 10.6\Omega$$

798 (c)

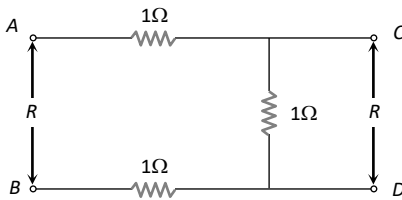Let equivalent resistance between  $A$  and  $B$  be  $R$ , then equivalent resistance between  $C$  and  $D$  will also be  $R$



$$R' = \frac{R}{R+1} + 2 = R$$

$$\Rightarrow R^2 - 2R - 2 = 0$$

$$\therefore R = \frac{2 \pm \sqrt{4+8}}{2} = \sqrt{3} + 1$$

799 (d)

Change  $q = it = 0.5 \text{ A} \times 3600 \text{ sec} = 1800 \text{ coulomb}$

800 (d)

$$\text{Power } P = \frac{V^2}{R} \Rightarrow 300 = \frac{220 \times 220}{R}$$

$$R = \frac{22 \times 22}{3}$$

$$\text{Again } P = \frac{110 \times 110 \times 3}{22 \times 22}$$

$$P = 75$$

$$P\% = \frac{75 \times 100}{300} = 25\%$$

The percentage reduction in power

$$P = 100 - 25 = 75\%$$

801 (d)

Neutral temperature is independent of temperature of cold junction.

802 (d)

Let the resistance of the lamp filament be  $R$ . Then  $100 = (220)^2/R$ . When the voltage drops, expected power is

$$P = (220 \times 0.3)^2/R'$$

Here,  $R'$  will be less than  $R$ , because now the rise in temperature will be less. Therefore,  $P$  is more than  $(220 \times 0.9)^2 R = 81 \text{ W}$ . But it will not be 90% of earlier value, because fall in temperature is small. Hence, option (d) is correct.

803 (a)

Electric fuse is a type of over current protection device. They are engineered to contribute a negligible amount of extra resistance to the circuits they protect. This is largely accomplished by making the fuse wire as short as possible. Fuses are primarily rated as current amperes. A fuse wire of certain material and gauge will blow at a certain current no matter how long it is.

Since, length is not a factor in current rating the shorter it can be made the less resistance it will have end to end.

804 (b)

Given,  $I = 1 \text{ A}$ ,  $t = 10 \text{ s}$ ,  $q = It$ ,  $q = 10 \text{ C}$

Charge of  $\text{Cu}^{2+} = 2e = 2 \times 1.6 \times 10^{-19} \text{ C}$

The number of copper atoms deposited at the cathode

$$= \frac{10}{2 \times 1.6 \times 10^{-19}} = 3.1 \times 10^{19}$$

805 (c)

Ohm's Law is not obeyed by semiconductors

806 (c)

$$\frac{i}{i_g} = 1 + \frac{G}{S} \Rightarrow \frac{1}{10^{-3}} = 1 + \frac{20}{S} \Rightarrow S = \frac{20}{900} \approx 0.02\Omega$$

807 (d)

The resistance of voltmeter is too high, so that it draws negligible current from the circuit, hence potential drop in the external circuit is also negligible

808 (d)

Full deflection current  $i_g = 25 \times 4 \times 10^{-4} = 100 \times 10^{-4} \text{ A}$


Using  $R = \frac{V}{I_g} - G = \frac{25}{100 \times 10^{-4}} - 50 = 2450\Omega$  in

series

809 (a)

The resistance of 25 W bulb is greater than 100 W bulb. So for the same current, heat produced will be more in 25 W bulb. So it will glow more brightly

810 (d)

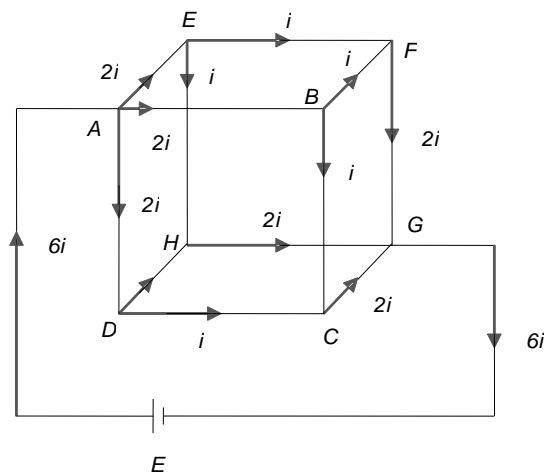

Let  $ABCDEFGH$  be the skeleton cube formed by joining twelve equal wires each of resistance  $r$ . Let the current enters the cube at corner  $A$  and after

passing through all twelve wires, let the current leaves at  $G$ , a corner diagonally opposite to corner  $A$ .

For the sake of convenience, let us suppose that the total current is  $6i$ . At  $A$ , this current is divided into three equal parts each ( $2i$ ) along  $AE$ ,  $AB$  and  $AD$  as the resistance along these paths are equal and their end points are equidistant from exit point  $G$ . At the points  $E$ ,  $B$  and  $D$ , each part is further divided into two equal parts each part equal to  $i$ . The distribution of current in the various arms of skeleton cube is shown according to Kirchhoff's first law. The current leaving the cube at  $G$  is again  $6i$ .

Applying Kirchhoff's second law to the closed circuit  $ADCGA$ , we get

$$2ir + ir + 2ir = E$$

$$\text{Or } 5ir = E \quad \dots(i)$$

Where  $E$  is the emf of the cell of negligible internal resistance. If  $R$  is the resistance of the cube between the diagonally opposite corners  $A$  and  $G$ , then according to Ohm's law, we have

$$6i \times R = E \quad \dots(ii)$$

From Eqs. (i) and (ii), we have

$$6iR = 5ir$$

$$\text{Or } R = \frac{5}{6}r$$

$$\text{Hence, } r = 6\Omega$$

$$\therefore R = \frac{5}{6} \times 6 \quad \text{or } R = 5\Omega$$

811 (c)

$$P = \frac{V^2}{R} = \frac{(18)^2}{6} = 54W$$

812 (d)

$$R_{\text{series}} = R_1 + R_2 + R_3 + \dots$$

813 (c)

Since current  $i$  is independent of the value of  $R_6$ , it is clear that the circuit is of a balanced Wheatstone bridge. As per condition of balance, we have

$$\frac{R_1}{R_3} = \frac{R_2}{R_4} \Rightarrow R_1 R_4 = R_2 R_3$$

814 (b)

If we take  $R_1 = 4\Omega$ ,  $R_2 = 12\Omega$ , then in series resistance

$$R = R_1 + R_2 = 4 + 12 = 16\Omega$$

In parallel, resistance

$$R = \frac{4 \times 12}{4 + 12} = 3\Omega$$

So,  $R_1 = 4\Omega$  and  $R_2 = 12\Omega$

815 (d)

$$\begin{aligned} \text{Watt hour efficiency} &= \frac{\text{Discharging energy}}{\text{Charging energy}} \\ &= \frac{14 \times 5 \times 15}{15 \times 8 \times 10} = 0.875 = 87.5\% \end{aligned}$$

816 (a)

$$\text{Effective emf in circuit} = 100 - 12 = 88V$$

Current in circuit

$$i = \frac{\text{effective emf}}{\text{resistance}} = \frac{88}{R}$$

$$\text{Or } R = \frac{88}{i} = \frac{88}{1} = 88\Omega$$

817 (c)

These questions are done by hit and trial method only. You check all the options one by one till you get the final desired result

819 (a)

Total external resistance

$$R' = R/3$$

For maximum heat generation

$$R_{\text{ext}} = r_{\text{int}}$$

$$\frac{R}{3} = 0.1$$

$$R = 0.3 \Omega$$

820 (a)

Neutral temperature remains same.

$$\text{Inversion temperature, } T_i = 2T_n - T_c$$

$$= 2 \times 285 - 10 = 560^\circ\text{C}$$

821 (c)

$$\frac{V^2}{R} + \frac{V^5}{5} = 4 \times \left( \frac{V^2}{R+5} \right) \quad \text{or } \frac{R+5}{5R} = \frac{4}{R+5}$$

On solving, we get  $R = 5\Omega$ .

822 (a)

It is called safe current and is proportional to  $r^{3/2}$

823 (c)

$$\text{By using } R_t = R_0(1 + \alpha t)$$

$$3 \times R_0 = R_0(1 + 4 \times 10^{-3}t) \Rightarrow t = 500^\circ\text{C}$$

825 (b)

$$\text{Thickness } d = \frac{V}{A} = \frac{m}{\rho A} = \frac{zIt}{\rho A}$$

$$= \frac{(3.3 \times 10^7) \times (1.5) \times (20 \times 60)}{9000 \times (50 \times 10 \times 2) \times 10^{-4}} = 6.6 \times 10^{-6} \text{ m.}$$

826 (b)

Total resistance between points  $P$  and  $Q$ ,

If  $m$  gram of the ice mean  $m$  given time  $t$ , then As per question,

$$(10)^2 \times \frac{20}{3} (10 \times 60) = m \times 80 \times 4.2$$

$$\text{or } m = \frac{100 \times 20 \times 10 \times 60}{3 \times 80 \times 4.2} = 1.19 \times 10^3 \text{ g}$$

$$= 1.19 \text{ kg.}$$

827 (c)

For a two cell battery

$$I = \frac{2E}{2r} = \frac{E}{r}$$

Similarly, for a  $n$  cell battery

$$I = \frac{nE}{nr} = \frac{E}{r}$$

So, current in the circuit does not depend on number of cells in the battery.

Hence, the correct graph will be (c).

828 (b)

$m = Zi t$  and  $i t = \text{Area of given curve}$

= Area of triangle + Area of rectangle

$$\Rightarrow i t = \frac{1}{2} \times (2 \times 60) \times 1 + (6 - 2) \times 60 \times 1$$

$$= 300$$

$$\therefore Z = \frac{m}{i t} = \frac{m}{300}$$


829 (d)

As circuit is open, therefore no current flows through circuit.

Hence, potential difference across  $X$  and  $Y$  = emf of battery = 120V.

830 (b)

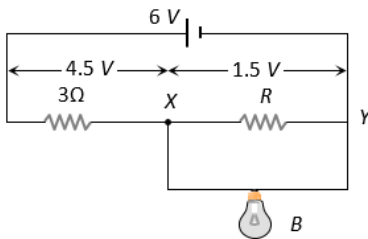When bulb glows with full intensity, then voltage across it will be 1.5 V and voltage across 3  $\Omega$  resistance will be 4.5 V



Current through 3  $\Omega$  resistance  $i = \frac{4.5}{3} = 1.5A$

Same current will flow between  $X$  and  $Y$

So  $V_{XY} = iR_{XY} \Rightarrow 1.5 = 1.5R_{XY} \Rightarrow R_{XY} = 1\Omega$

831 (c)

$$R = R_1 + R_2 = \frac{\rho_1 l}{A} + \frac{\rho_2 l}{A} = (\rho_1 + \rho_2) \frac{l}{A} \dots(i)$$

$$R = \frac{\rho(2l)}{A} \dots(ii)$$

From Eqs.(i) and (ii),  $2\rho = \rho_1 + \rho_2$  or  $\rho = \frac{\rho_1 + \rho_2}{2}$

833 (b)

Because  $H$  has positive charge

834 (a)

$$\text{Resistance of 25 W bulb} = \frac{220 \times 220}{25} = 1936 \Omega$$

$$\text{It's safe current} = \frac{220}{1936} = 0.11 A$$

$$\text{Resistance of 100 W bulb} = \frac{220 \times 220}{100} = 484 \Omega$$

$$\text{It's safe current} = \frac{220}{484} = 0.48 A$$

when connected in series to 440 V supply, then the current

$$i = \frac{440}{(1936 + 484)}$$

$$= 0.18 A$$

Thus, current is greater for 25 W bulb, so it will fuse.

835 (b)

$$\text{Potential gradient} = \frac{e.R}{(R+r).L} = \frac{10 \times 3}{(3+3) \times 5}$$

$$= 1V/m = 10 mV/cm$$


836 (a)

$$\text{Power dissipated } P = \frac{V^2}{R_{\text{eff}}};$$


$R_{\text{eff}}$  is least in case of figure (a). Hence power dissipated in circuit (a) is maximum

838 (b)

Required arrangement is shown in figure.

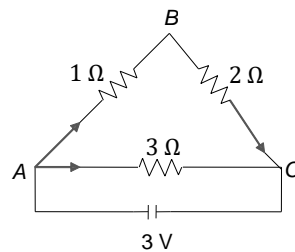


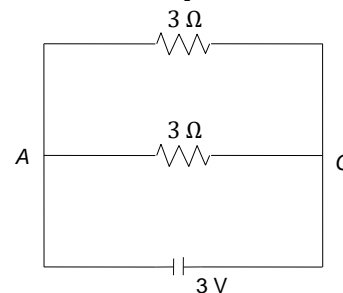The equivalent circuit will look like (since the two resistances of 1  $\Omega$  and 2  $\Omega$  are in series, which from 3  $\Omega$  which is in parallel with 3  $\Omega$  resistance).



Therefore, the effective resistance is
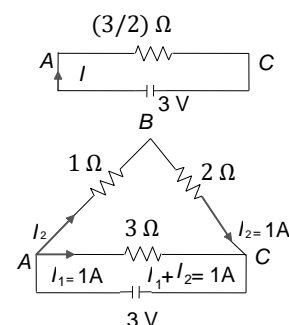
$$\frac{(1 + 2) \times 3}{(1 + 2) + 3} = \frac{3}{2} \Omega$$



$\therefore$  Current in the circuit,

$$I = \frac{3}{\left(\frac{3}{2}\right)} = 2A$$

$$\therefore \text{Current in } 3\Omega \text{ resistor} = \frac{l}{2} = 1A$$

839 (c)

$$m_{Ag}/m_{Zn} = E_{Ag}/E_{Zn} = 108/31$$

$$\text{or } m_{Ag} = m_{Zn} \times 108/31 = w \times 108/31$$

$$3.48w = 3.5w$$

840 (a)

Meter bridge is an arrangement which works on Wheatstone's principle, so the balancing condition is

$$\frac{R}{S} = \frac{l_1}{l_2}$$

$$\text{Where } l_2 = 100 - l_1$$

$$\text{Ist case } R = X, S = Y, l_1 = 20 \text{ cm}, l_2 = 100 - 20 = 80 \text{ cm}$$

$$\therefore \frac{X}{Y} = \frac{20}{80} \quad \dots (i)$$

**IInd Case** Let the position null point is obtained at a distance  $l$  from same end.

$$\therefore R = 4X, S = Y, l_1 = l, l_2 = 100 - l$$

So, from Eq. (i)

$$\frac{4X}{Y} = \frac{l}{100 - l}$$

$$\Rightarrow \frac{X}{Y} = \frac{l}{4(100 - l)} \quad \dots (ii)$$

Therefore, form Eqs. (i) and (ii)

$$\frac{l}{4(100 - l)} = \frac{20}{80}$$

$$\Rightarrow \frac{l}{4(100 - l)} = \frac{1}{4}$$


$$\Rightarrow l = 100 - l$$

$$\Rightarrow 2l = 100$$

$$\text{Hence, } l = 50 \text{ cm}$$

841 (a)

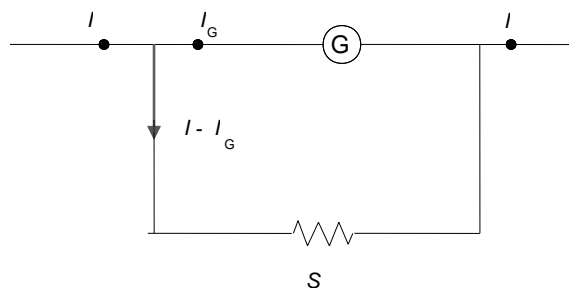Given, galvanometer resistance  $G = 240\Omega$



Shunt resistance  $S = ?$

$$I_G = \frac{4}{100} I$$

From figure voltage through the circuit.

$$(I - I_G)S = I_G G$$

$$\text{or } \left(I - \frac{4I}{100}\right)S = \frac{4I}{100} \times 240$$

$$\text{or } S = \frac{4 \times 240}{96} = 10\Omega$$

842 (b)

In series, the current  $I$ , is same in two bulbs.

$$\text{Resistance } R = \frac{V^2}{P}$$

And potential drop  $(V) = IR$

$\therefore$  Potential difference across 60 W bulb is greater than the potential difference across 200 W bulb.

844 (a)

$$E = xl = i\rho l \Rightarrow i = \frac{E}{\rho l} = \frac{2.4 \times 10^{-3}}{1.2 \times 5} = 4 \times 10^{-4} A$$

845 (c)

Since the unit of electrical energy is kilowatt hour (kWh),

So total number of units consumed is

$$N = (0.1 \times 8 + 0.3 \times 4) \times 30$$

(Because June has 30 days)

$$\therefore N = 60 \text{ units}$$

$$\text{Total cost} = 60 \times 0.5 = 30 \text{ Rs.}$$

846 (b)

To shift the balance point on higher length, the potential gradient of the wire is to be decreased.

The same can be obtained by decreasing the current of the main circuit, which is possible by increasing the resistance in series of potentiometer wire.

847 (b)

$$\frac{7}{12} = \frac{1}{4} + \frac{1}{R} \Rightarrow R = 3\Omega$$

848 (d)

$$\text{Current in the bulb} = \frac{P}{V} = \frac{4.5}{1.5} = 3A$$

$$\text{Current in } 1\Omega \text{ resistance} = \frac{1.5}{1} = 1.5A$$

$$\text{Hence total current from the cell } i = 3 + 1.5 = 4.5A$$

$$\text{By using } E = V + ir \Rightarrow E = 1.5 + 4.5 \times (2.67) = 13.5V$$

849 (d)

Colliding electrons lose their kinetic energy as heat

850 (a)

$$\text{Thermo electric power } E = k \left( TT_0 - T_0 T_r - \frac{1}{2} T_0^2 + \frac{1}{2} T_r^2 \right)$$

$$S = \frac{dE}{dT} = k \left[ T - 0 - \frac{1}{2} \times 2T + 0 \right]$$

$$= k[T_0 - T]$$

$$\text{At } T = T_0/2$$



$$S = \frac{1}{2}kT_0$$

851 (c)

Power of the combination  $P_s = \frac{P}{n} = \frac{1000}{2} = 500W$

852 (b)

For no current through galvanometer, we have

$$\left(\frac{E_1}{500 + X}\right)X = E \Rightarrow \left(\frac{12}{500 + X}\right)X = 2 \Rightarrow X = 100\Omega$$

853 (c)

$E_1 = ?$ ,  $l_1 = 60cm$ ;  $E_2 = 3V$ ,  $l_2 = 45cm$

In balance condition

$$\frac{E_1}{E_2} = \frac{l_1}{l_2} \Rightarrow \frac{E_1}{3} = \frac{60}{45} \Rightarrow E_1 = 4 \text{ volt}$$

854 (d)

$$\frac{E_1}{E_2} = \frac{l_1 + l_2}{l_1 - l_2} = \frac{(6 + 2)}{(6 - 2)} = \frac{2}{1}$$

855 (a)

According to Seebeck effect

856 (a)

From Kirchhoff's first law at junction P,

$$I_1 + I_2 = 6 \dots (i)$$

From Kirchhoff's second law to the closed circuit PQRP,

$$-2I_1 - 2I_1 + 2I_2 = 0$$

$$\Rightarrow -4I_1 + 2I_2 = 0$$

$$\Rightarrow 2I_1 - I_2 = 0 \dots \dots (ii)$$

Adding Eqs. (i) and (ii), we get


$$3I_1 = 6 \Rightarrow I_1 = 2A$$

From Eq. (i),

$$I_2 = 6 - 2 = 4A$$

857 (b)

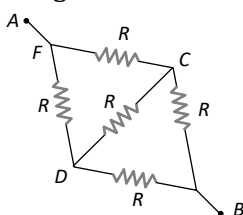The given circuit can be redrawn as follows



Equivalent resistance between A and B is  $R$  and current  $i = \frac{V}{R}$

858 (d)

Resistance of a conductor

$$R = \frac{\rho l}{A} \dots \dots \dots (i)$$

As  $\rho$  depends on the material, so  $R$  depends on the material.

According to the given formula in Eq.(i), it depends on length. Moreover resistance  $\propto$  temperature.

If  $R_0$  = resistance of conductor at  $0^\circ C$ ,


$R_t$  = resistance of conductor at  $t^\circ C$ , and  $\alpha, \beta$  = temperature coefficient of resistance, then

$$R_t = R_0(1 + \alpha t + \beta t^2)$$

The resistance of a straight conductor does not depend on shape of cross-section.

859 (d)

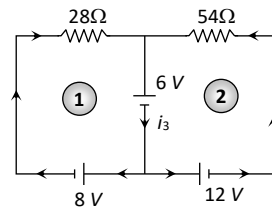Suppose current through different paths of the circuit is as follows :



After applying KVL for loop (1) and loop (2)

$$\text{We get } 28i_1 = -6 - 8 \Rightarrow i_1 = -\frac{1}{2}A$$

$$\text{and } 54i_2 = -6 - 12 \Rightarrow i_2 = -\frac{1}{3}A$$

$$\text{hence } i_3 = i_1 + i_2 = -\frac{5}{6}A$$

860 (d)

$$i^2 R t = m s \Delta t$$

$$\Rightarrow (4)^2 \times 7 \times 3 \times 60$$

$$= 0.1 \times 4.2 \times 10^3 \times [T - (20 + 273)]$$

$$\therefore T = 341 \text{ K} = 68^\circ C$$

861 (a)

Current through R is maximum when total internal resistance of the circuit is equal to external resistance

862 (c)

A voltmeter is a high resistance device and is always connected in parallel with the circuit. While an ammeter is a low resistance device and is always connected in series with the circuit. So, to use voltmeter in place of ammeter a high resistance must be connected in series with the circuit.

863 (a)

$$R = \frac{V}{i} = \rho \frac{l}{A} \Rightarrow \frac{2}{4} = \rho \frac{50 \times 10^{-2}}{(1 \times 10^{-3})^2} \Rightarrow \rho = 1 \times 10^{-6} \Omega m$$

864 (a)

$$P = \frac{V^2}{R}$$

$$\therefore R_{\text{hot}} = \frac{V^2}{R} = \frac{200 \times 200}{100} = 400\Omega$$

$$R_{\text{cold}} = \frac{400}{100} = 40\Omega$$

865 (b)

Current,  $i = (2.9 \times 10^{18} + 1.2 \times 10^{18}) \times 1.6 \times 10^{-19}$

$= 0.66 \text{ A towards right}$

866 (b)

$3 = 1.5(1 + r) \Rightarrow r = 1\Omega$

867 (d)

When a single heater (resistance  $R_1 = R$ ) is connected to 220 V, then it will consume a power  $P_1 = 1000 \text{ W}$ . If two such identical heaters are connected in parallel (total resistance  $R_2 = R_1/2 = R/2$ ) to some source, then it will consume power  $P_2$ .


$\frac{P_2}{P_1} = \frac{R_1}{R_2}$

$\Rightarrow P_2 = 2P_1$

$P_2 = 2000 \text{ W}$


868 (a)

A voltmeter is an instrument used to measure the potential difference between two points in an electrical circuit directly in volts. Voltmeter is essentially a galvanometer which is connected in parallel across two points in the circuit between which the potential difference is to be measured. The potential difference read by the voltmeter is slightly less than the actual value to be measured. Hence, the resistance of the voltmeter should be as high as possible so, that on connecting it in a circuit across two points the potential difference may not fall appreciably.

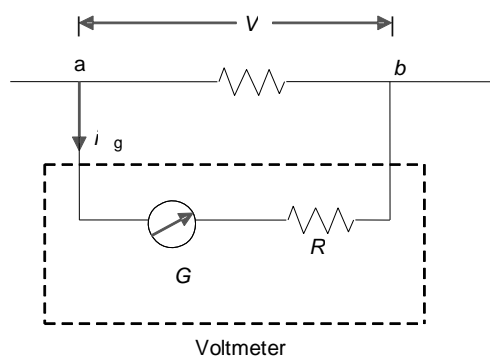


Hence, a voltmeter is made by connecting a high resistance in series with a pivoted type moving coil galvanometer  $G$ . The value of  $R$  depends upon the range of the required voltmeter.

869 (b)

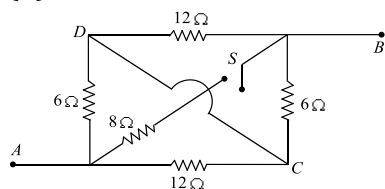

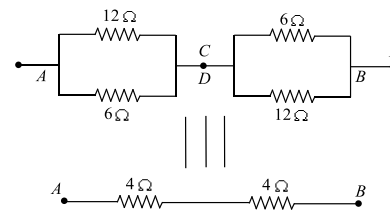
When switch S is open, the corresponding equivalent circuit diagram is as shown in the figure



The equivalent resistance between A and B is

$R_{eq} = \frac{12 \times 6}{12 + 6} + \frac{6 \times 12}{6 + 12} = 4 + 4 = 8\Omega$

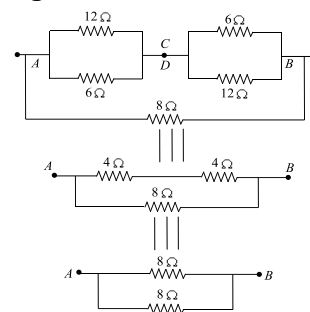When switch S is closed, the corresponding equivalent circuit diagram is as shown in the figure below



The equivalent resistance A and B is

$R'_{eq} = \frac{8 \times 8}{8 + 8} = 4\Omega$

870 (d)

The bridge ABCD is balanced if

$\frac{10}{R_1} = \frac{30}{9} \Rightarrow R_1 = 3\Omega$

When the bridge is balanced, no current flows in the arm BD. Therefore,  $R_2$  can have any finite value

871 (d)

Resistance of each part will be  $\frac{R}{n}$ ; such  $n$  parts are joined in parallel so  $R_{eq} = \frac{R}{n^2}$

872 (a)

The rate of dissipation of electric energy is called electric power

$W = Vit$

The electric power dissipated will be is given by

$P = \frac{W}{t} = \frac{Vit}{t} = Vi$   
 $= \frac{V^2}{R} \dots(i)$

When resistance is doubled, then let electric power is  $P'$ .

$\therefore P' = \frac{V^2}{2R} \dots(ii)$

From Eqs, (i) and (ii), we get

$P' = \frac{1}{2} P$

So, power becomes  $\frac{1}{2}$  of initial value.

873 (d)


Bulb (I): Rated current  $I_1 = \frac{P}{V} = \frac{40}{220} = \frac{2}{11} \text{ amp}$

Resistance  $R_1 = \frac{V^2}{P} = \frac{(220)^2}{40} = 1210 \Omega$

Bulb (II): Rated current  $I_2 = \frac{100}{220} = \frac{5}{11} \text{ amp}$

Resistance  $R_2 = \frac{(220)^2}{100} = 484 \Omega$

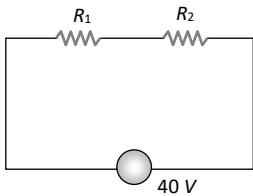When both are connected in series across 40 V supply



Total current through supply

$$I = \frac{40}{P_1 + P_2} = \frac{40}{1210 + 484} = \frac{40}{1254} = 0.03A$$

This current is less than the rated current of each bulb. So neither bulb will fuse

**Short Trick :** Since  $V_{Applied} < V_{Rated}$ , neither bulb will fuse

874 (c)

$m = zit$

$$9 = z \times 10^5 \Rightarrow z = \frac{9}{10^5} \text{ g C}^{-1}$$

$$\therefore m = zit = 9 \times 10^{-5} \times 50 \times (20 \times 60) = 5.4 \text{ g.}$$

875 (a)

For maximum energy, we have

External resistance of the circuit

= Equivalent internal resistance of the circuit

$$i.e. R = \frac{r}{2}$$

876 (a)

Given problem is the case of mixed grouping of cells

So total current produced  $i = \frac{nE}{R + \frac{nr}{m}}$

Here  $m = 100, n = 5000, R = 500 \Omega$

$E = 0.15 \text{ V}$  and  $r = 0.25 \Omega$

$$\Rightarrow i = \frac{5000 \times 0.15}{500 + \frac{5000 \times 0.25}{100}} = \frac{750}{512.5} \approx 1.5 \text{ A}$$

877 (c)

Let time taken in boiling the water by the heater is  $t$  s. Then

$$Q = ms\Delta T \Rightarrow \frac{Pt}{J} = ms\Delta T$$

$$\therefore \frac{836}{4.2} t = 1 \times 1000(40 - 10)$$

$$\frac{836}{4.2} t = 1000 \times 30$$

$$t = \frac{1000 \times 30 \times 4.2}{836} = 150s$$

878 (a)

Effective resistance of three resistances between C and

$$D = \frac{R \times 2R}{R + 2R} = \frac{2}{3}R$$

Total resistance between A and B

$$= R + \frac{2}{3}R + R = \frac{8}{3}R = \frac{8}{3} \times 3 = 8 \Omega$$

879 (a)

Heat produced  $H = Vit = Pt$

Where,  $P = Vi$  watt

$$\therefore H = 500 \times 15 \times 60 = 45 \times 10^4 \text{ J}$$

Heat absorbed by water = mass  $\times$  specific heat capacity

$\times$  rise in temperature

$$= 1 \times 4200 \times (100 - 15)$$

$$= 4.2 \times 85 \times 10^{-3}$$

$$\text{Efficiency} = \frac{\text{heat absorbed}}{\text{heat produced}} \times 100$$

$$= \frac{85 \times 4.2 \times 10^3}{45 \times 10^4} \times 100 = 79\%$$

880 (b)

If number of collisions of the free electrons with the lattice is decreased, the time of relaxation of electrons will increase. Due to which drift velocity of electrons will increase and hence current will increase

881 (a)

Power is the amount of work done or energy ( $Q$ ) transferred per unit of time ( $t$ ).

$$\therefore P = \frac{H}{t}$$

$$H = mc \Delta \theta$$

Where  $m$  is mass,  $c$  the specific heat and  $\Delta \theta$  the temperature difference.

$$\therefore P = \frac{mc \Delta \theta}{t}$$

$$\Delta \theta = (35 - 20)^\circ \text{C} = 15^\circ \text{C}$$

$$C = 1000, 4.2 \text{ J} = 1 \text{ cal}$$

$$t = 1 \text{ min} = 60s$$

$$\therefore P = \frac{1 \times 1000 \times 15 \times 4.2}{60} \text{ Js}^{-1} = 1050 \text{ W}$$

882 (b)

Drift velocity,

$$v_d = \frac{i}{neA}$$

Where  $i$  is current,  $n$  the number of electrons,  $e$  the electron charge and  $A$  the area of cross-section of wire.

Number of electrons per unit volume

$$n = \frac{2 \times 10^{21}}{A \times 100}$$

So, current in the wire

$$i = neAv_d$$

$$i = \frac{2 \times 10^{21}}{A \times 100} \times 1.6 \times 10^{-19} \times A \times 0.25 = 0.8A$$

883 (d)

Resistance of a conductor,  $R = \frac{m \cdot l}{ne^2 \tau A}$

Where the symbols have their usual meaning

As the temperature increases, the relaxation time  $\tau$  decreases

884 (c)

$$\text{In India, power, } P_1 = \frac{V^2}{R} = \frac{220^2}{R}$$


$$\text{In USA, power, } P_2 = \frac{V'^2}{R'} = \frac{(110)^2}{R'}$$

$$\text{As } P_1 = P_2, \text{ so } \frac{220^2}{R} = \frac{(110)^2}{R'}$$

$$\text{or } R' = \frac{(110)^2}{(220)^2} R = \frac{R}{4}$$

885 (c)

Moving anticlockwise from  $A$

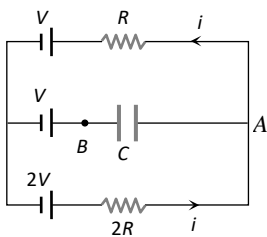

$$-iR - V + 2V - 2iR = 0$$

$$\text{or } 3iR = V \text{ or } i = \frac{V}{3R}$$

$$V_A - V_B = iR + V - V = iR$$

$$\Rightarrow \text{Potential drop across } C = \frac{V}{3}$$

886 (c)

If  $l$  is the balancing length for  $R_1$ , and  $l'$  for  $R_2$ ,

$$\frac{V_0}{L_0} \cdot l = \frac{ER_1}{(r+R_1+R_2)} \Rightarrow \frac{V_0}{L_0} \cdot l = \frac{ER_1}{(r_1+9R_1)} \text{ as } R_2 = 8R_1$$

$$\frac{V_0}{L_0} l' = \frac{E \cdot R_2}{(r_1 + 9R_1)} = \frac{E \cdot 8R_1}{(r_1 + 9R_1)}$$

$$\therefore \frac{l'}{l} = \frac{R_2}{R_1} = \frac{8R_1}{R_1} \Rightarrow l' = 8l$$

887 (c)

Production of heat at junctions due to current is known as Peltier effect

889 (c)

If volume and density remains same, then resistance of wire

$$R \propto l^2$$

Where  $l$  is the length of the wire

$$\therefore R' = \left(1 + \frac{10}{100}l\right)^2 = \left(\frac{11}{10}\right)^2 R$$

Hence,

$$\frac{R' - R}{R} = \frac{21}{100} = 21\%$$

Therefore, change in resistance of wire = 21%

890 (c)


$$\text{In series } i = \frac{nE}{nr+R} \Rightarrow 0.6 = \frac{n \times 1.5}{n \times 0.5 \times 20} \Rightarrow n = 10$$

891 (d)

The temperature coefficient of resistivity for thermister is negative. Therefore by increase in temperature the resistivity of the thermister decreases.

892 (d)

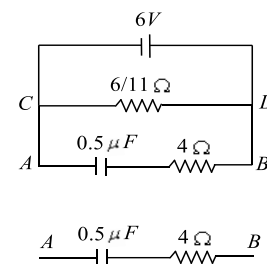In steady state capacitor is fully charged and no current flows through it



$\therefore$  No current passes through  $4\Omega$

$$\frac{1}{R_{eff}} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3}$$

$$= \frac{6 + 3 + 2}{6} = \frac{11}{6}$$

$$\Rightarrow R_{eff} = \frac{6}{11} \Omega$$

$$\text{Current} = \frac{6 \times 11}{6} = 11A$$

$$Q = CV = 0.5 \times 10^{-6} \times 6 = 3.0 \times 10^{-6} C = 3\mu C$$

893 (b)

Let  $R = 100\Omega$

$$\therefore R' = 100 + 100 \times \frac{10}{100}$$

$$= 110\Omega$$

$$\therefore \Delta R = R' - R$$

$$= 110 - 99 = 11\Omega$$

894 (b)

$$R \propto \frac{l}{A} \propto \frac{l}{d^2} \Rightarrow \frac{R_1}{R_2} = \frac{l_1}{l_2} \times \left(\frac{d_2}{d_1}\right)^2 = \frac{L}{4L} \left(\frac{2d}{d}\right)^2 = 1$$

$$\Rightarrow R_2 = R_1 = R$$

895 (d)

Effective value of resistance of parallel


combination of  $20\Omega$ ,  $30\Omega$ ,  $60\Omega$  is  $R_1$ , where

$$\frac{1}{R_1} = \frac{1}{20} + \frac{1}{30} + \frac{1}{60} = \frac{3+2+1}{60} = \frac{6}{60} = \frac{1}{10}$$

$$R_1 = 10\Omega$$

Similarly effective value of parallel combination of  $24\Omega$  and  $8\Omega$  resistance is given by
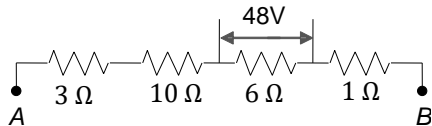
$$R_2 = \frac{24 \times 8}{24 + 8} = 6\Omega$$



Hence, the circuit may be redrawn as shown in the adjacent figure, where total resistance across  $A$  and  $B$ ,  $R = 3 + 10 + 6 + 1 = 20\Omega$ . As potential across  $R_2 (= 6\Omega)$  is  $48\text{ V}$ , hence

$$V_{AB} = 48 \times \frac{R}{R_2} = \frac{48 \times 20}{6} = 160\text{ V}$$

896 (b)

$$\begin{aligned} m &= z I t = z \left( \frac{P}{V} \right) t \\ &= 0.367 \times 10^{-6} \left( \frac{100 \times 1000}{125} \right) \times 60 \text{ kg} \\ &= 0.017616 \text{ kg} = 17.616 \text{ g} \end{aligned}$$

897 (d)

$$\frac{X}{1} = \frac{20}{80} \Rightarrow X = \frac{1}{4} \Omega = 0.25\Omega$$

898 (a)

As we know that,

$$\begin{aligned} P &= \frac{V^2}{R} \\ \Rightarrow R &= \frac{V^2}{P} \\ \Rightarrow R &\propto \frac{1}{P} \end{aligned}$$

Hence, the resistance of  $25\text{ W}$  bulb is greater than the resistance of  $100\text{ W}$  bulb.

Now, both the bulbs are joined in series so the current will be same.

So, heat produced by the bulbs

$$H = i^2 R t \Rightarrow H \propto R$$

So, the heat produced by the  $25\text{ W}$  bulb is greater than the bulb of  $100\text{ W}$ , because its resistance is more than that of  $100\text{ W}$  bulb. Hence,  $25\text{ W}$  bulb will glow brighter.

899 (b)

Temperature of inversion is

$$T_i = 2T_n - T_0$$

$$\therefore T_i = 2 \times 270 - 10 = 530^\circ\text{C}$$

900 (d)

$$\frac{i}{ig} = 1 + \frac{G}{S} \Rightarrow \frac{5}{1} = 1 + \frac{60}{S} \Rightarrow S = 15\Omega$$

901 (a)

$$R = G(n - 1) = 50 \times 10^3 (3 - 1) = 10^5 \Omega$$

902 (c)

$$R_{\text{bulb}} = \frac{220^2}{100} = 484\Omega;$$

$$R_{\text{geyser}} = \frac{220^2}{1000} = 48.4\Omega$$

When only bulb is on,

$$V_{\text{bulb}} = \frac{220 \times 484}{484 + 6} = 217.4 \text{ volt}$$

When geyser is also switched on, effective resistance of bulb and geyser

$$= \frac{484 \times 48.4}{484 + 48.4} = 44 \Omega$$


$$V_{\text{bulb}} = \frac{220 \times 44}{(44 + 6)} = 193.6 \text{ V}$$

Hence, the potential drop =  $217.4 \times 193.6 = 23.8 \text{ V} \approx 24 \text{ V}$ .

903 (d)

$$\text{Resistance between } A \text{ and } B = \frac{1000 \times 500}{(1500)} = \frac{1000}{3}$$

So, equivalent resistance of the circuit

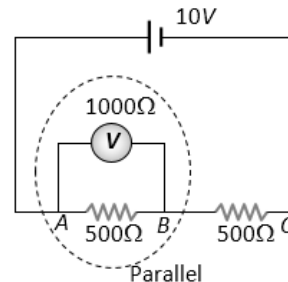

$$R_{eq} = 500 + \frac{1000}{3} = \frac{2500}{3}$$

$\therefore$  Current drawn from the cell

$$i = \frac{10}{(2500/3)} = \frac{3}{250} \text{ A}$$

Reading of voltmeter *i.e.*

$$\text{Potential difference across } AB = \frac{3}{250} \times \frac{1000}{3} = 4 \text{ V}$$

904 (a)

In figure (b) current through  $R_2 = i - \frac{i}{10} = \frac{9i}{10}$

Potential difference across  $R_2 =$  Potential difference across

$$R \Rightarrow R_2 \times \frac{9}{10} i = R \times \frac{i}{10} \text{ i.e. } R_2 = \frac{R}{9} = \frac{11}{9} \Omega$$

$$R_{eq} = \frac{R_2 \times R}{(R_2 + R)} = \frac{\frac{11}{9} \times \frac{11}{1}}{\frac{11}{9} + \frac{11}{1}} = \frac{11}{10} \Omega$$

$$\text{Total circuit resistance} = \frac{11}{10} + R_1 = R = 11 \Rightarrow$$

$$R_1 = 9.9\Omega$$


905 (c)

Number attached for brown, black, green and silver are 0, 5,  $\pm 10\%$  Therefore the resistance of given resistor

$$= 10 \times 10^5 \Omega \pm 10\% = 1.0 \times 10^6 \Omega \pm 10\%$$

906 (d)

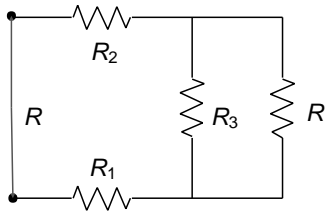Let  $R$  be the equivalent resistance. Then addition/subtraction of one more set of resistors  $R_1, R_2$  and  $R_3$  will not affect the total resistance. Thus,



$$R = R_1 + (\text{parallel combination of } R \text{ and } R_2) + R_3$$

$$R = R_1 + \left( \frac{RR_2}{R + R_2} \right) + R_3$$

$$\Rightarrow R^2 + RR_3 = RR_1 + R_1R_3 + RR_2 + R_2R_3$$

$$\Rightarrow R^2 - R(R_1 + R_2) = (R_2 + R_1)R_3 = 0$$

$$\Rightarrow R = \frac{(R_1 + R_2) \pm \sqrt{(R_1 + R_2)^2 + 4(R_1 + R_2)R_3}}{2}$$

As  $R$  cannot be negative, hence

$$R = \frac{1}{2} \left[ (R_1 + R_2) + \sqrt{(R_1 + R_2)^2 + 4(R_1 + R_2)R_3} \right]$$

$$= \frac{1}{2} \left[ (R_1 + R_2) + \sqrt{(R_1 + R_2)(R_1 + R_2 + 4R_3)} \right]$$

907 (b)

$$P \propto \frac{1}{R} \Rightarrow \frac{P_1}{P_2} = \frac{R_2}{R_1} \Rightarrow \frac{200}{100} = \frac{R_2}{R_1} \Rightarrow R_2 = 2R_1$$

908 (d)

$$\text{Equivalent weight of copper} = \frac{64}{2} = 32$$

Equivalent weight of Cu

Equivalent weight of Ag

$$= \frac{\text{Weight of Cu deposited}}{\text{Weight of Ag deposited}}$$

$$\text{Weight of copper deposited} = \frac{10.8 \times 32}{108} = 3.2 \text{ gm}$$

909 (a)

The balance condition of a meter bridge experiment

$$\frac{R}{S} = \frac{l_1}{(100 - l_1)}$$

Here,  $R = R_1, S = R_2$

$$\therefore \frac{R_1}{R_2} = \frac{l_1}{(100 - l_1)}$$

Ist case

$$\frac{R_1 + 10}{R_2} = \frac{50}{50} \dots \dots (i)$$

$$\Rightarrow R_1 + 10 = R_2$$

IInd case

$$\frac{R_1}{R_2} = \frac{40}{60}$$

$$\Rightarrow R_2 = \frac{60}{40} R_1 \dots \dots (ii)$$

So, Eqs. (i) and (ii) give

$$R_1 + 10 = \frac{60}{40} R_1$$

$$\Rightarrow \frac{60}{40} R_1 - R_1 = 10$$

$$\Rightarrow \frac{20}{40} R_1 = 10$$

$$\Rightarrow R_1 = \frac{10 \times 40}{20}$$

$$\therefore R_1 = 20\Omega$$

910 (d)

Resistance of original wire is

$$R = \rho \frac{l}{A}$$

$\rho$ , being the specific resistance of wire. When the wire is cut in two equal halves then resistance becomes

$$R' = \frac{\rho l/2}{A} = \frac{R}{2}$$

Thus, the net resistance of parallel combination of two halves is given by

$$R_{\text{net}} = \frac{R' \times R'}{R' + R'} = \frac{R'}{2} = \frac{R}{2 \times 2} = \frac{6}{4} = 1.5\Omega$$

911 (c)

Charge ( $q$ ) is given by

$$q = \int I dt$$

Given,  $I = 1.2t + 3$

Integrating the expression using

$$\int x^n dx = \frac{x^{n+1}}{n+1}$$

We have

$$q = \int I dt = 1.2 \int t dt + 3 \int dt$$

$$q = 1.2 \left[ \frac{t^2}{2} \right]_0^5 + 3[t]_0^5$$

$$q = \frac{1.2}{2} \times 25 + 3 \times 5$$

$$q = 15 + 15 = 30C$$

912 (d)

Equivalent resistance of parallel resistors is always less than any of the member of the resistance system

913 (b)

Supercurrent always flows on the surface of the superconductor.

914 (a)

$$0.9(2 + r) = 0.3(7 + r) \Rightarrow 6 + 3r = 7 + r \Rightarrow r = 0.5 \Omega$$

915 (c)

$$i = \frac{m}{Zt} = \frac{0.972}{0.00018 \times 3 \times 3600} = 0.5 A$$

916 (a)

$$T_n = \frac{T_i + T_c}{2} \Rightarrow T_i = 2T_n - T_c$$

917 (b)

$$E = 16T - 0.04T^2$$

At temperature of inversion,  $E = 0$

$$\therefore 16T_i - 0.04T_i^2 = 0$$

$$\Rightarrow T = \frac{16}{0.04} = 400^\circ C$$

918 (c)

For portion  $CD$  slope of the curve is negative *i. e.* resistance is negative

919 (d)


In the normal condition current flows from  $X$  to  $Y$  through cold junction. After increasing the temperature of hot junction beyond temperature of inversion the current is reversed *i. e.*  $X$  to  $Y$  through hot junction or  $Y$  to  $X$  through cold junction

920 (c)

$$R = kl_1 \text{ and } R + X = kl_2$$

921 (c)

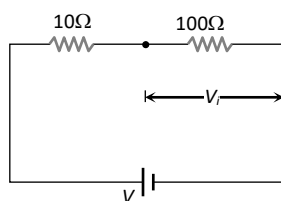Before connecting the voltmeter, potential difference across  $100\Omega$  resistance




$$V_1 = \frac{100}{(100 + 10)} \times V = \frac{10}{11} V$$

Finally after connecting voltmeter across  $100\Omega$  equivalent resistance

$$\frac{100 \times 900}{(100 + 900)} = 90\Omega$$

Final potential difference

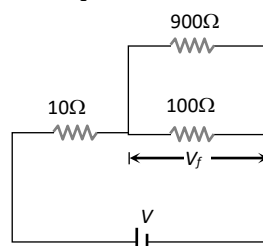

$$V_f = \frac{90}{(90 + 10)} \times V = \frac{9}{10} V$$

$$\% \text{ error} = \frac{V_i - V_f}{V_i} \times 100$$

$$= \frac{\frac{10}{11} V - \frac{9}{10} V}{\frac{10}{11} V} \times 100 = 1.0$$

923 (a)

From Joule's law, the heat produced is given by

$$P = \frac{V^2}{R}$$

Where  $V$  is potential and  $R$  the resistance.


When one bulb is fused, the total resistance of the circuit decreases. Hence, ( $P$ ) illumination increases.

924 (b)

$$S = \frac{i_g \times G}{i - i_g} = \frac{10 \times 10^{-3} \times 50}{1 - 10^{-3} \times 10} = \frac{50}{99} \Omega \text{ in parallel}$$


925 (d)

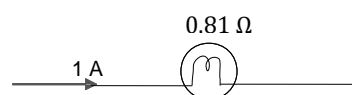To increase the range of ammeter we have to connect a small resistance in parallel



(shunt), let its value be  $R$ .

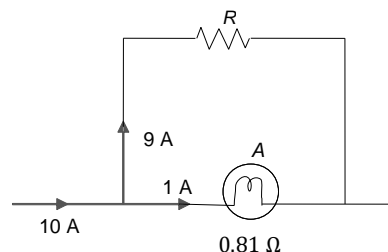Apply KCL at junction to divide the current.



Voltage across  $R$  = Voltage across ammeter

$$\Rightarrow 9R = 0.81 \times 1$$


$$\Rightarrow R = \frac{0.81}{9} = 0.09\Omega$$

926 (d)

Consider a concentric spherical shell of radius  $x$

and thickness  $dx$  as showing in figure. Its resistance,  $dR$  is

$$dR = \frac{\rho dx}{4\pi x^2}$$

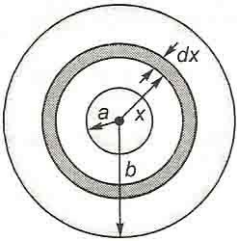

$$\therefore \text{Total resistance, } R = \frac{\rho}{4\pi} \int_a^b \frac{dx}{x^2} = \frac{\rho}{4\pi} \left[ \frac{1}{a} - \frac{1}{b} \right]$$

927 (a)

Cu voltameter with soluble electrodes obeys ohm's law. In water voltameter, in the beginning when  $V$  is small ( $< 1.7 \text{ volt}$ ), very little current flows, the voltameter does not obey ohm's law. As soon as  $V$  exceeds  $1.7 \text{ volt}$  (back e.m.f.) the current increases steadily according to ohm's law

928 (d)

The resistance  $R$  of a particular conductor is related to the resistivity  $\rho$  of its material by

$$R = \frac{\rho l}{A}$$

Or

$$\rho = \text{resistivity} = \frac{RA}{l}$$

Given,  $R=0.072\Omega$

$$A = 2\text{mm} \times 2\text{mm} = 4 \times 10^{-6}\text{m}^2, l=12$$

$$\therefore \rho = \frac{0.072 \times 4 \times 10^{-6}}{12}$$

$$= 2.4 \times 10^{-8}\Omega\text{m}$$

929 (b)

Shunt

$$S = \frac{I_g G}{I - I_g}$$

$$\text{Here, } \frac{I_g}{I} = \frac{1}{34}$$

$$\therefore \frac{1}{34} = \frac{S}{S + G}$$

$$\therefore S = \frac{G}{33} = \frac{3663}{33} = 111\Omega$$

930 (b)

$$R_{AB} = R_1 + \frac{R_2 R_3}{R_2 + R_3} + R_4 = 2 + \frac{4 \times 4}{4 + 4} + 2 = 6\Omega$$

931 (a)

Effective resistance  $R_p$  of  $4\Omega$ ,  $6\Omega$  and  $12\Omega$  in parallel will be

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{6} + \frac{1}{12} = \frac{6}{12} = \frac{1}{2} \text{ or } R_p = 2\Omega$$

$$\text{Total resistance of circuit} = 2 + 2 = 4\Omega$$


$$\text{The battery current, } i = 4/4 = 1\text{A}$$

932 (d)

The  $x$  be the total resistance of infinite network of resistance connected to points  $A$  and  $B$ . Therefore the addition of one step of resistances in the infinite network of resistances will not change the total resistance  $x$  of the network. Therefore equivalent circuit will be as shown in figure. Then total resistances between  $A'$  and  $B'$  is  $x$  given by

$$x = 1 + \frac{1 + x}{1 + x} = \frac{1 + 2x}{1 + x}$$

$$\text{or } x + x^2 = 1 + 2x$$

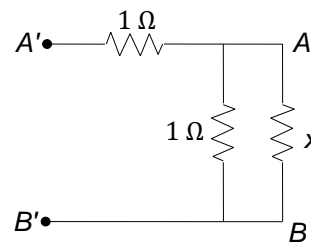


$$\text{or } x^2 - x - 1 = 0 \text{ or } x = \frac{1 \pm \sqrt{5}}{2} = \frac{1 + \sqrt{5}}{2}$$

Since negative value of  $R$  is not possible

933 (c)

Current capacity of a fuse wire should be slightly greater than the total rated load current

934 (a)

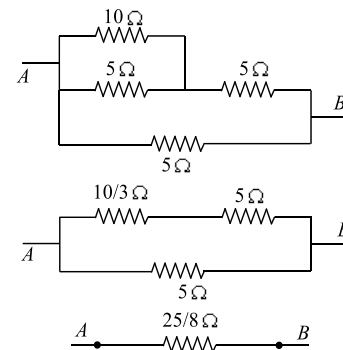

$$R_{AB} = 3.12\Omega$$

935 (b)


$i^2 R t = C \theta = 3C$ ;  $C$  = Thermal capacity

when  $i_1 = 2i \Rightarrow C \theta_1 = 4i^2 R t = 4 \times 3C \Rightarrow \theta_1 = 12^\circ\text{C}$

936 (a)



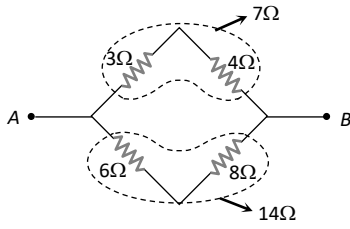The given circuit is a balanced Wheatstone bridge, hence it can be redrawn as follows



$$\Rightarrow R_{eq} = \frac{7 \times 14}{(7 + 14)} = \frac{14}{3} \Omega$$

938 (d)


Battery is short circuited so potential difference is zero

939 (c)

When we measure the emf of a cell by the potentiometer then no current flows in the circuit in zero-deflection condition *ie*, cell is in open circuit. Thus, in this condition the actual value of a cell is found. In this way, potentiometer is equivalent to an ideal voltmeter of infinite resistance.

940 (a)

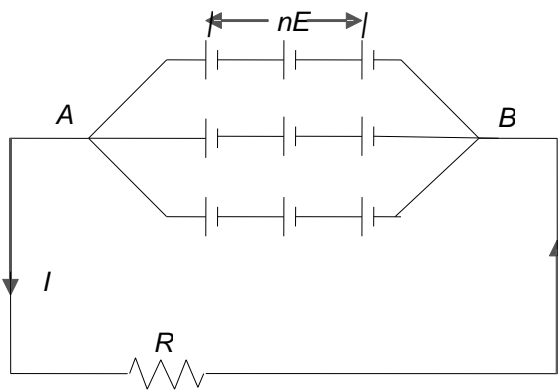If the cells are connected as shown in figure, they are said to be connected in mixed grouping. Let there be  $n$  cells in series in one row and  $m$  rows of cells in parallel. Suppose all the cells are identical. Let each cell be of emf  $E$  and internal resistance  $r$ .



In each row, there are  $n$  cells in series, therefore their total internal resistance =  $nr$ .

Their total emf =  $nE$ .

Since, there are  $m$  rows of cells in parallel therefore, total internal resistance ( $r_p$ ) of all the cells is given by

$$\frac{1}{r_p} = \frac{1}{nr} + \frac{1}{nr} + \dots \text{ upto } m \text{ terms}$$

$$= \frac{m}{nr}$$

$$\text{or } r_p = \frac{nr}{m}$$

Total resistance in their circuit =  $R + nr/m$

Effective emf of all the cells =  $nE$

The current in the external resistance is given by

$$I = \frac{nE}{R + nr/m} = \frac{mnE}{mR + nr}$$

The current  $I$  will be maximum, if  $mR + nr$  is minimum.

Mathematically, it can be shown that  $mR + nr$  is minimum, if

$$mR = nr$$

$$\text{or } R = \frac{nr}{m}$$

Here,  $mn = 45$  (given)....(i)

and  $m \times 2.5 = n \times 0.5$

Or  $n = 5m$  .....(ii)

From Eqs. (i) and (ii), we have

$$5m^2 = 45$$

$$\text{or } m^2 = 9$$

$$\text{or } m = 3$$

$$\therefore n = 15$$

941 (d)

The thermo-couple works in a closed circuit. Since the two pipes are isolated, only  $b$  and  $a$  are closed-circuits.

In circuit  $b$ , the two constantan wires to the cold copper

pipe produce 2 opposing currents.

In circuit  $a$ , the copper-constantan junction is maintained across the cold pipe. A steady current can flow.

942 (c)

$$E = 40t + \frac{1}{10}t^2 \text{ at}$$

Inversion,  $E$  will be minimum

$$\frac{dE}{dt} = 0$$

$$\frac{d}{dt} \left( 40t + \frac{1}{10}t^2 \right) = 0$$

$$40 + \frac{1}{5}t = 0$$

$$t = -40 \times 5$$

$$t = -200^\circ\text{C}$$

943 (b)

Hydrogen liberated per sec =  $\frac{0.224}{100} \text{ L s}^{-1}$ .

In order to liberate 11.2 L of hydrogen per sec

charge passed =  $96500 \text{ C s}^{-1}$

To liberate =  $\frac{0.224}{100} \text{ L s}^{-1}$  of hydrogen

$$= \frac{96500}{11.2} \times \frac{0.224}{100}$$


$$= 19.30 \text{ Cs}^{-1} = 19.3A$$

944 (d)

The speed at which current travels through the conductors means the speed of electric effect travelling through conductor which is at a speed of light

945 (a)

The circuit can be drawn as follows

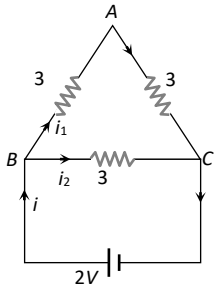

$$\text{Equivalent resistance } R = \frac{3 \times (3+3)}{3+(3+3)} = 2\Omega$$

$$\text{Current } i = \frac{2}{2} = 1A. \text{ So, } i_1 = 1 \times \left(\frac{3}{3+6}\right) = \frac{1}{3}A$$

$$\text{Potential difference between A and B} = \frac{1}{3} \times 3 = 1\text{volt}$$

946 (a)

$$P = \frac{V^2}{R} \Rightarrow 100 = \frac{(200)^2}{R} \Rightarrow R = \frac{4 \times 10^4}{10^2} = 400 \Omega$$

$$\text{Now, } i = \frac{V}{R} = \frac{100}{400} = \frac{1}{4} \text{ amp}$$

947 (a)

The potential difference across  $300 \Omega = 60 - 30 = 30V$  Therefore the effective resistance of voltmeter resistance  $R$  and  $400 \Omega$  in parallel will be equal to  $300 \Omega$ , as  $60 V$  is equally divided between two parts. So  $300 = \frac{R \times 400}{R + 400}$

$$\text{or } 300R + 120000 = 400R \text{ or } R = 1200 \Omega$$

948 (b)

When 1 bulb fuses, the total resistance of the circuit decreases hence the current increases. Since  $P = i^2 R$ , therefore illumination increases

949 (a)

$$\text{Here } R_{XWY} = \frac{R}{2\pi r} \times (r\alpha) = \frac{R\alpha}{2\pi} \left[ \because \alpha = \frac{l}{r} \right]$$

$$\text{and } R_{XZY} = \frac{R}{2\pi r} \times r(2\pi - \alpha) = \frac{R}{2\pi} (2\pi - \alpha)$$

$$R_{eq} = \frac{R_{XWY} R_{XZY}}{R_{XWY} + R_{XZY}} = \frac{\frac{R\alpha}{2\pi} \times \frac{R}{2\pi} (2\pi - \alpha)}{\frac{R\alpha}{2\pi} + \frac{R(2\pi - \alpha)}{2\pi}}$$

$$= \frac{R\alpha}{4\pi^2} (2\pi - \alpha)$$

950 (a)

$$q = it = \text{current} \times \text{time}$$

951 (a)

As galvanometer deflection remains unaffected with switch  $S$  open or closed, hence the bridge circuit is balanced. Hence,  $I_p = I_Q$  and  $I_R = I_G$

However, as  $P \neq R$ , hence  $I_P \neq I_R$

952 (d)

Resistance of bulb,

$$R = \frac{V^2}{P} = \frac{220 \times 220}{300} = \frac{484}{3} \Omega$$

$$\text{New power, } P' = \frac{(110)^2}{R} = \frac{110 \times 110}{484/3} = 75 \text{ watt}$$

reduction

$$\text{Of power} = \frac{300-75}{300} \times 100 = 75\%$$

953 (a)

Peltier coefficient is directly proportional to absolute temperature  $T$ .

954 (a)

Resistance of a wire  $R = \frac{\rho L}{A} = \frac{4\rho L}{\pi D^2}$  where  $D$  is diameter of wire

As  $R \propto L$  and  $R \propto \frac{1}{D^2}$ , hence it is clear that resistance will be maximum if  $\frac{L}{D^2}$  is maximum. On calculation we find

$$\frac{L}{D^2} \text{ maximum when, } L = 50 \text{ cm and } D = 0.5 \text{ mm}$$

955 (b)

$$i \propto \frac{1}{R}$$

956 (d)

$$V = xl \Rightarrow iR = xl$$

$$\Rightarrow i \times 10 = \left(\frac{2 \times 10^{-3}}{10^{-2}}\right) \times 50 \times 10^{-2} = 0.1$$

$$\Rightarrow i = 10 \times 10^{-3} A = 10 \text{ mA}$$

957 (b)

The power of 1<sup>st</sup> bulb

$$P_1 = \frac{V^2}{R_1} = \frac{(220)^2}{R_1}$$

$$100 = \frac{(220)^2}{R_1}$$

$$\text{or } R_1 = \frac{200 \times 200}{100} = 400 \Omega$$

The power of 2<sup>nd</sup> bulb

$$P_2 = \frac{(200)^2}{R_2}$$

$$\text{or } 200 = \frac{(200)^2}{R_2}$$

$$\text{or } R_2 = \frac{200 \times 200}{200} = 200 \Omega$$

The bulbs are joined in series.

So,  $R = R_1 + R_2$   
 $= 400 + 200 = 600 \Omega$


The total power

$$P = \frac{V^2}{R} = \frac{(200)^2}{600}$$

$$P = 66.7 \text{ W}$$

958 (a)

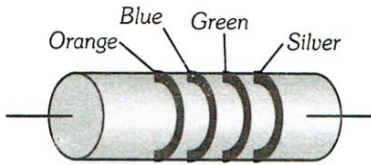First colour gives first digit, second colour gives second digit and third colour gives the multiplier and fourth colour gives the tolerance



$$= 36 \times 10^5 \Omega \pm 10\%$$

959 (c)


According to loop rule,

$$2.5 - 0.5I - 2I = 0$$

$$\Rightarrow I = 1 \text{ A}$$

$$V_A - V_B = \frac{q_o}{C} = 2I = 2 \text{ V}$$
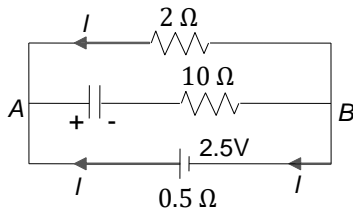
$$q_o = C \times 2 = 2 \times 10^{-6} \times 2 = 4 \mu\text{C}$$



960 (d)

In Stretching of wire  $R \propto l^2 \Rightarrow \frac{R_1}{R_2} = \left(\frac{l_1}{l_2}\right)^2$

If  $l_1 = 100$ , then  $l_2 = 110 \Rightarrow \frac{R_1}{R_2} = \left(\frac{100}{110}\right)^2$


$$\Rightarrow R_2 = 1.21 R_1$$

Resistivity doesn't change with stretching

961 (c)

For conductor A,  $R_A = \frac{\rho l}{\pi r_1^2}$ ,

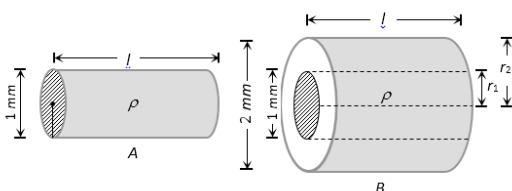For conductor B,  $R_B = \frac{\rho l}{\pi(r_2^2 - r_1^2)}$



$$\Rightarrow \frac{R_A}{R_B} = \frac{r_2^2 - r_1^2}{r_1^2} = \left(\frac{r_2}{r_1}\right)^2 - 1 = \left(\frac{d_2}{d_1}\right)^2 - 1$$

$$= \left(\frac{2}{1}\right)^2 - 1 = 3$$

962 (b)

Shunt is connected to the galvanometer

$$i_g = \frac{iS}{S + G}$$

$$1 = \frac{100 \times 1}{(1 + G)}$$

$$\Rightarrow G = 99 \Omega$$

964 (b)

$$\text{Energy} = P \times t = 2 \times 1 \times 30 = 60 \text{ kWh} = 60 \text{ unit}$$

965 (c)

BC, CD and BA are known resistance.

The unknown resistance is connected between A and D.

Hence, the correct option is (c).

966 (a)

$$R_{PQ} = \frac{5}{11}r, R_{QR} = \frac{4}{11}r \text{ and } R_{PR} = \frac{3}{11}r$$

$\therefore R_{PQ}$  is maximum.

967 (a)

For ohmic resistance  $V \propto i \Rightarrow V = Ri$  (here R is constant)

968 (b)

During charging of lead-acid accumulator, the specific gravity of  $\text{H}_2\text{SO}_4$  increases.

969 (a)

$$m = Zit$$

$$\frac{200}{100} = \frac{108}{96500} \times I \times 60 \times 60$$

$$I = 50 \text{ mA}$$

970 (b)

Let the length of various edges in increase order be  $l, x, 2l$  respectively

$$R_{\max} = \frac{\rho 2l}{xl} = \frac{2\rho}{x}; R_{\min} = \frac{\rho l}{2lx} = \frac{\rho}{2x}$$

$$\therefore \frac{R_{\max}}{R_{\min}} = 4$$

971 (b)

$$i = \frac{E}{R + r} \Rightarrow 1 = \frac{4}{2 + r} = r = 2 \Omega$$

Short circuit, is when terminals of battery are connected directly, then current which flows is

$$i_{\text{SC}} = \frac{E}{r} = \frac{4}{2} = 2 \text{ A}$$

972 (b)

$$i = \frac{E}{r} = \frac{6}{0.5} = 12 \text{ amp}$$

973 (a)

Internal resistance  $\propto \frac{1}{\text{Temperature}}$

974 (c)

Resistance are in parallel

$$\therefore R_{eq} = \frac{R}{3}$$

975 (d)

$E = \frac{V}{l}$ ;  $E$  is constant (volt. gradient)

$$\Rightarrow \frac{V_1}{l_1} = \frac{V_2}{l_2} \Rightarrow \frac{1.1}{140} = \frac{V}{180} \Rightarrow V = \frac{180 \times 1.1}{140} = 1.41 \text{ V}$$

976 (c)

The current in the circuit  $= \frac{8}{5+1} = \frac{4}{3}$

Now  $V_C - V_E = \frac{4}{3} \times 1 \Rightarrow V_E = -\frac{4}{3} \text{ V}$

977 (b)

Here, the resistance of  $400 \Omega$  and  $10000 \Omega$  are in parallel, their effective resistance  $R_p$  will be

$$R_p = \frac{400 \times 10,000}{400 + 10,000} = \frac{5000}{13} \Omega$$

Total resistance of circuit

$$= \frac{5000}{13} + 800 = \frac{15400}{13} \Omega$$

Current in the circuit,  $i = \frac{6}{15400/13} = \frac{39}{7700} \text{ A}$


Potential difference across voltmeter  $= iR_p =$

$$\frac{39}{7700} \times \frac{5000}{13}$$

$$= 1.95 \text{ A}$$

978 (b)

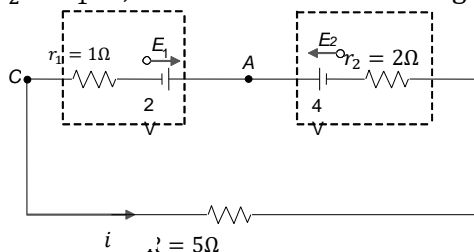Emf's  $E_1$  and  $E_2$  are opposing each other. Since  $E_2 > E_1$  so, current will move from right to left.



Current in circuit

$$i = \frac{E_2 - E_1}{R + r_1 + r_2} = \frac{4 - 2}{5 + 1 + 2} = \frac{2}{8} = 0.25 \text{ A}$$

The potential drop between points  $A$  and  $C$  is

$$V_A - V_C = E_1 + ir_1 = 2 + (0.25 \times 1)$$

$$= 2.25 \text{ V}$$

979 (a)


Magnetic field due to a long straight wire of radius  $a$  carrying current  $I$  at a point distant  $r$  from the centre of the wire is given as follows

$$B = \frac{\mu_0 I r}{2\pi a^2} \text{ for } r < a$$

$$B = \frac{\mu_0 I}{2\pi r} \text{ for } r = a$$

$$B = \frac{\mu_0 I}{2\pi r} \text{ for } r > a$$

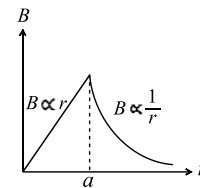The variation of magnetic field  $B$  with distance  $r$  from the centre of wire is shown in the figure



980 (b)

Let resistivity at a distance ' $x$ ' from left end be  $\rho = (\rho_0 + ax)$ . Then electric field intensity at a distance ' $x$ ' from left and will be equal to  $E = \frac{i\rho}{A} = \frac{i(\rho_0 + ax)}{A}$

Where  $i$  is the current flowing through the conductor. It means  $E \propto \rho$  or  $E$  varies linearly with distance ' $x$ '. But at  $x = 0$ ,  $E$  has non-zero value. Hence (b) is correct

981 (c)

$$P_{\max} = \frac{E^2}{4r} = \frac{(2)^2}{4 \times 0.5} = 2 \text{ W}$$

982 (a)

$$\frac{V^2}{R} = P \Rightarrow R = \frac{V^2}{P} = \frac{220 \times 220}{100} = 484 \Omega$$

984 (b)

Let  $i$  be the current through arm  $ADC$ . Then current through arm  $ABC = (2.1 - i)$ . As there is no deflection in the galvanometer, hence

$$(20 + 5)i = (8 + 2)(2.1 - i)$$

$$\text{or } 25i = 21 - 10i \text{ or } 35i = 21$$

$$\text{or } i = 21/35 = 3/5 = 0.6 \text{ A}$$


985 (c)

Resistance of bulb is constant

$$P = \frac{v^2}{R} \Rightarrow \frac{\Delta P}{P} = \frac{2\Delta V}{V} + \frac{\Delta R}{R}$$

$$\frac{\Delta P}{P} = 2 \times 2.5 + 0 = 5\%$$

986 (c)

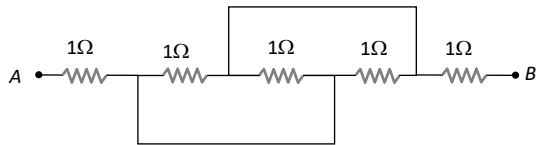

$$R_{AB} = 2 + \frac{1}{3} = 2\frac{1}{3} \Omega$$

987 (b)

The temperature of the wire increase to such a value at which the heat produced per second equals heat lost per second due to radiation.

$$i^2 \left( \frac{\rho l}{\pi r^2} \right) = H \times 2\pi r l$$

Where  $H$  is heat lost per second per unit area due to radiation.

Hence,  $i^2 \propto r^3$

$$\text{So, } \frac{i_1^2}{i_2^2} = \frac{r_1^3}{r_2^3}$$

$$\text{Or } r_2 = r_1 \left( \frac{i_2}{i_1} \right)^{\frac{2}{3}}$$


[Here :  $r_1 = 1 \text{ mm}$ ,  $i_1 = 1.5 \text{ A}$ ,  $i_2 = 3 \text{ A}$ ]

$$r_2 = 1 \times \left( \frac{3}{1.5} \right)^{2/3} = 4^{1/3} \text{ mm}$$

988 (b)

Here,  $I_g = 1 \text{ A}$

$I = 10 \text{ A}$

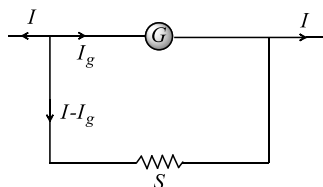

From figure

$$I_g G = (I - I_g) S$$

$$\frac{G}{S} = \frac{I - I_g}{I_g}$$

Substituting the given values, we get

$$\frac{G}{S} = \frac{10 \text{ A} - 1 \text{ A}}{1 \text{ A}} = \frac{9}{1}$$

989 (b)

$$i = \frac{V}{R} = \frac{Q}{t} \Rightarrow Q = \frac{Vt}{R} = \frac{20 \times 2 \times 60}{10} = 240 \text{ C}$$

991 (a)

$$v_d = \frac{e}{m} \times \frac{V}{l} \tau \text{ or } v_d = \frac{e}{m} \cdot \frac{El}{l} \tau [\because V = El]$$

$$\therefore v_d \propto E$$


992 (c)

$$418t = 1 \times 4180 \times 20 \text{ or } t = 200 \text{ s}$$

Note that in this case,  $C = 418 \text{ J/kg}^{-1} [\text{C}^{-1}]$

$$J = 4.18 \text{ J cal}^{-1}$$

993 (c)

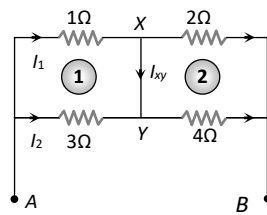

$$-i_1 + 0 \times i_{xy} + 3i_2 = 0 \text{ i.e. } i_1 = 3i_2 \quad \dots(i)$$

$$\text{Also } -2(i_1 - i_{xy}) + 4(i_2 + i_{xy}) = 0$$

$$\text{i.e. } 2i_1 - 4i_2 = 6i_{xy} \quad \dots(ii)$$

$$\text{Also } V_{AB} - 1 \times i_1 - 2(i_1 - i_{xy}) = 0 \Rightarrow 50 = i_1 + 2(i_1 - i_{xy})$$

$$= 3i_1 - 2i_{xy} \quad \dots(iii)$$


Solving (i), (ii) and (iii),  $i_{xy} = 2 \text{ A}$

994 (c)

By Kirchoff's current law

995 (b)

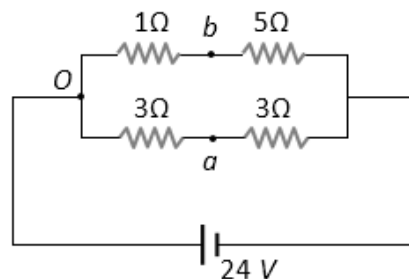Switch  $S_2$  is open so capacitor is not in circuit



$$\text{Current through } 3\Omega \text{ resistor} = \frac{24}{3+3} = 4 \text{ A}$$

Let potential of point 'O' shown in fig. is  $V_0$

Then using ohm's law

$$V_0 - V_a = 3 \times 4 = 12 \text{ V} \quad \dots(i)$$

$$\text{Now current through } 5\Omega \text{ resistor} = \frac{24}{5+1} = 4 \text{ A}$$

$$\text{So } V_0 - V_b = 4 \times 1 = 4 \text{ V} \quad \dots(ii)$$

$$\text{From equation (i) and (ii) } V_b - V_a = 12 - 4 = 8 \text{ V}$$

996 (c)


$$i = \frac{ne}{t} = \frac{62.5 \times 10^{18} \times 1.6 \times 10^{-19}}{1} = 10 \text{ ampere}$$

997 (a)

In parallel  $P_{Consumed} \propto P_{Rated}$

998 (c)

The figure can be drawn as follows

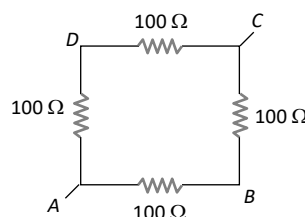

$$R_{AC} = \frac{200 \times 200}{200 + 200} = 100 \Omega$$

999 (a)

Heat gained by water = Heat supplied by container heat lost

$$\Rightarrow mS\Delta\theta = 1000t - 160t$$

$$\Rightarrow t = \frac{2 \times 4.2 \times 1000 \times 50}{840} = 8 \text{ min } 20 \text{ sec}$$

100 (d)

0 As batteries wear out, temperature of filament of flash light attains lesser value, therefore intensity of radiation reduces. Also dominating wavelength ( $\lambda_m$ ) in spectrum, which is the red colour, increases

100 (c)

1 Potential gradient ( $x$ ) =  $\frac{i\rho}{A} = \frac{0.1 \times 10^{-7}}{10^{-6}} = 10^{-2} \text{ V/m}$

100 (c)

2 Energy =  $\frac{V^2}{R} t = \frac{200 \times 200 \times 2}{80} = 1000 \text{ Wh}$

100 (d)

4 If the voltmeter is ideal then given circuit is an open circuit, so reading of voltmeter is equal to the e.m.f. of cell i. e., 6V

100 (a)

7 Resistance of each bulb  $R = V^2/P$ .  
When connected in series total resistance of bulbs =  $2R$

Current in each bulb,  $I = V'/2R$ ;

Power generated by each bulb =  $I^2 R$

$$= \left(\frac{V'}{2R}\right)^2 \times R = \frac{V'^2}{4R} = \frac{V'^2}{(V^2/P)}$$

$$= \frac{(110)^2 \times 500}{4 \times (220)^2} = 31.25 \text{ W}$$

100 (a)

8  $P = Vi = 250 \times 2 = 500 \text{ W}$

100 (a)

9  $i_g = i \frac{S}{G+S} \Rightarrow 10 \times 10^{-3}$

$$= \frac{S}{100+S} \times 100 \times 10^{-3}$$

$$90 S = 1000 \Rightarrow S = \frac{1000}{90} = 11.11 \Omega$$

101 (c)

0 In balance condition, no current will flow through the branch containing S

101 (d)

1 At time  $t = 0$  i. e. when capacitor is charging, current


$$i = \frac{2}{1000} = 2 \text{ mA}$$

When capacitor is full charged, no current will pass through it, hence current through the circuit

$$i = \frac{2}{2000} = 1 \text{ mA}$$

101 (c)

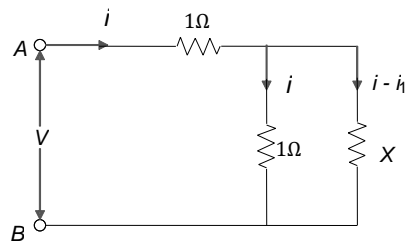2 Let  $x$  be the equivalent resistance of entire network between A and B. Hence, we have



$R_{AB} = 1 +$  resistance of parallel combination of  $1\Omega$  and  $x\Omega$

$$\therefore R_{AB} = 1 + \frac{x}{1+x}$$

$$\therefore x = 1 + \frac{x}{1+x}$$

$$\Rightarrow x + x^2 = 1 + x + x$$

$$\Rightarrow x^2 - x - 1 = 0$$

$$\Rightarrow x = \frac{1 + \sqrt{1+4}}{2}$$

$$= \frac{1 + \sqrt{5}}{2} \Omega$$

101 (b)

3 Energy,  $E = 1 \text{ kWh} = 3.6 \times 10^6 \text{ J} = QV$   
or  $Q = E/V$

$$m = zQ = z \frac{E}{V}$$

$$= \frac{(0.33 \times 10^{-6})(3.6 \times 10^6)}{66} = 1.8 \text{ kg.}$$

101 (b)

4 Current from D to C = 1A

$$\therefore V_D - V_C = 2 \times 1 = 2V$$

$$V_A = 0 \therefore V_C = 1V, \therefore V_D - V_C = 2$$

$$\Rightarrow V_D - 1 = 2 \therefore V_D = 3V$$

$$\therefore V_D - V_B = 2 \therefore 3 - V_B = 2 \therefore V_B = 1V$$

101 (b)

7 Here,  $E_1 = 0.9V, \theta - \theta_0 = 75E; E_2 = ?$  when  $\theta'_0 = \theta_0 + 15$

$$\therefore \text{temperature difference } \theta - \theta'_0 = \theta - (\theta_0 + 15) = (\theta - \theta_0) - 15 = 75 - 15 = 60 \text{ K}$$

$$\text{As } \frac{E_2}{E_1} = \frac{\theta - \theta'_0}{\theta - \theta_0} = \frac{60}{75} = \frac{4}{5}$$

or % decrease in thermo emf

$$= \frac{E_1 - E_2}{E_1} \times 100 = \left(1 - \frac{E_2}{E_1}\right) \times 100$$

$$= \left(1 - \frac{4}{5}\right) \times 100 = 20\%$$

101 (d)

8 When one cell is wrongly connected in series, the emf of cells decrease by  $2E$ , but internal

resistance of cells remains the same for all the cells.

$$\text{Current in the circuit is } i = \frac{(n-2)E}{nr} \times r$$

Potential difference across each cell is

$$V = E - Ir = E - \frac{(n-2)E}{nr} \times r = \frac{2E}{n}$$

101 (c)

$$9 \quad 2R > 20 \Rightarrow R > 10\Omega$$

102 (d)

0 After some time, thermal equilibrium will reach

102 (b)

1 For maximum power  $R_{\text{ext}} = R_{\text{int}}$

When batteries are connected in parallel.

$$R_{\text{int}} = \frac{1}{2} = 0.5\Omega$$

$$\text{Current } I = \frac{E}{R_{\text{ext}} + R_{\text{int}}} = \frac{2}{0.5 + 0.5} = 2\Omega$$

Maximum power is given by

$$P_{\text{max}} = i^2 R_{\text{ext}}$$

$$\Rightarrow P_{\text{max}} = (2)^2 \times 0.5 = 2 \text{ W}$$

If we assume batteries to be connected in series, then

$$R_{\text{int}} = 1 + 1 = 2\Omega$$

$$\text{Current } I = \frac{2E}{R_{\text{ext}} + R_{\text{int}}} = \frac{2 \times 2}{2 + 2} = 1 \text{ A}$$

So, maximum power is now given by

$$P_{\text{max}} = i^2 R_{\text{ext}} = 1 \times 2 = 2 \text{ W}$$

In either case  $P_{\text{max}} = 2 \text{ W}$

102 (a)

2 For  $E$  to be maximum

$$\frac{dE}{dT} = 20 \times 10^{-6} - 0.02 \times 10^{-6} \times 2T = 0$$

$$\Rightarrow T_n = 500^\circ\text{C}$$

$$\therefore E_{\text{max}} = 20 \times 10^{-6}(500) - 0.02 \times$$

$$10^{-6}(500)^2 = 5 \text{ mV}$$


102 (b)

3 In parallel  $\frac{1}{t_p} = \frac{1}{t_1} + \frac{1}{t_2}$

$$t_p = \frac{t_1 t_2}{t_1 + t_2}$$

102 (b)

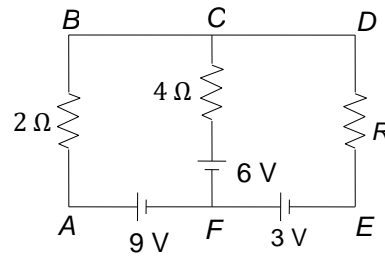4 Since no current is to flow in the  $4\Omega$  resistance, hence resistance  $4\Omega$  becomes ineffective in current.



Current through resistances  $2\Omega$  is


$$i = \frac{9 - 6}{2} = \frac{3}{2} \text{ A}$$

In circuit  $ABCDEF A$ ,  $9 - 3 = (2 + R) \times \frac{3}{2}$

$$\text{or } 12 = 6 + 3R \text{ or } R = 2\Omega$$

102 (a)

5

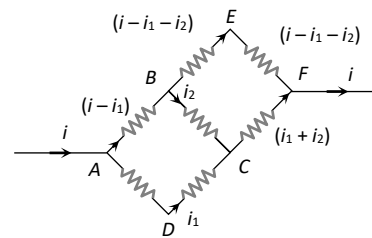

Applying Kirchhoff's law in mesh  $ABCD A$

$$-10(i - i_1) - 10i_2 + 20i_1 = 0 \Rightarrow 3i_1 - i_2 = i$$

...(i)

And in mesh  $BEFCB$

$$-20(i - i_1 - i_2) + 10(i_1 + i_2) + 10i_2 = 0$$

$$\Rightarrow 3i_1 + 4i_2 = 2i \quad \dots(\text{ii})$$

From equation (i) and (ii)

$$i_1 = \frac{2i}{5}, i_2 = \frac{i}{5} \Rightarrow i_{AD} = \frac{2i}{5}$$

102 (c)

6

For constant voltage, we know that  $P \propto \frac{1}{R}$

So higher the power, lower will be the resistance

102 (c)

7

Current through  $6\Omega$  resistance in parallel with  $3\Omega$  resistance =  $0.4 \text{ A}$

So total current =  $0.8 + 0.4 = 1.2 \text{ A}$

Potential drop across  $4\Omega = 1.2 \times 4 = 4.8 \text{ V}$

102 (c)

8

$$\frac{E_1}{E_2} = \frac{l_1 + l_2}{l_1 - l_2} = \frac{58 + 29}{58 - 29} = \frac{3}{1}$$

102 (c)

9

$$I = \frac{E}{R + r}$$

$$I = \frac{E}{R} = \text{constant}$$

where,  $R$  = external resistance

$r$  = internal resistance = 0


103 (a)

$$P_{Rated} \propto \frac{1}{R} \text{ and } R \propto \frac{1}{[\text{Thickness of filament}]^2}$$

$$\text{So } P_{Rated} \propto (\text{Thickness of filament})^2$$

103 (a)

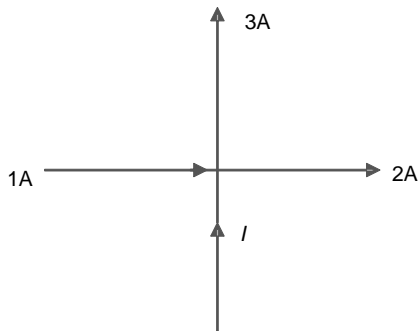1 From Kirchhoff's first law, in an electric circuit the algebraic sum of the currents meeting at any junction is zero,



$$\text{i.e., } \sum i = 0$$

$\therefore$  Taking inward direction of current as positive and outward as negative, we have

$$1A - 3A - 2A + I = 0$$

$$\Rightarrow I = 4A$$

103 (d)

2 Thermal energy is resistor is  $U = i^2 R t$

$$R = R_0(1 + \alpha\theta) \Rightarrow U = i^2 R_0(1 + \alpha\theta)t \text{ [where } \theta = \text{temp]}$$

$$\text{So } \frac{dU}{dt} = i^2 R_0(1 + \alpha\theta)$$

With time temperature increases, hence  $dU/dt$  increases. This is best shown by curve (d)

103 (b)

3 Here two cells are in series

$$\text{Therefore total emf} = 2E$$

$$\text{Total resistance} = R + 2r$$

$$\therefore i = \frac{2E}{R + 2r} = \frac{2 \times 1.45}{1.5 + 2 \times 0.15} = \frac{2.9}{1.8} = \frac{29}{18} = 1.611 \text{ amp}$$

103 (b)

$$4 \quad E = \alpha T + \frac{1}{2} \beta T^2$$

For inversion temperature

$$E = 0, \quad T = \frac{-2\alpha}{\beta}$$

Thermo electric power

$$P = \frac{dE}{dT} = \alpha + \frac{1}{2} \beta \cdot (2T) \Rightarrow \alpha + \beta \cdot T$$

$$\alpha + \beta \left( \frac{-2\alpha}{\beta} \right) = \alpha - 2\alpha = -\alpha$$

103 (c)

5 Resistance of shunted ammeter =  $\frac{GS}{G+S}$

$$\text{Also } \frac{i}{i_g} = 1 + \frac{G}{S} \Rightarrow \frac{GS}{G+S} = \frac{i_g G}{i}$$

$$\Rightarrow \frac{GS}{G+S} = \frac{0.05 \times 120}{10} = 0.6 \Omega$$

103 (a)

$$6 \quad i = 6 \times 10^{15} \times 1.6 \times 10^{-19} = 0.96 \text{ mA}$$

103 (d)

8 To convert galvanometer into voltmeter, the necessary value of resistance to be connected in series with the galvanometer is

$$R = \frac{V}{I_g} - G$$

$$= \frac{50}{10 \times 10^{-3}} - 40$$

$$= 5000 - 40 = 4960 \Omega$$

103 (b)

9 To obtain minimum resistance, all resistors must be connected in parallel.

Hence equivalent resistance of combination of combination =  $\frac{r}{10}$

104 (a)

0 Total e.m.f. =  $nE$ , Total resistance  $R + nr \Rightarrow i = \frac{nE}{R+nr}$

104 (c)

$$2 \quad \text{Potential gradient } x = \frac{e}{(R+R_h+r)} \cdot \frac{R}{L}$$

$$\Rightarrow \frac{10^{-3}}{10^{-2}} = \frac{2}{(3 + R_h + 0)} \times \frac{3}{1} \Rightarrow R_h = 57 \Omega$$

104 (c)

$$3 \quad R = \frac{V^2}{P} = \frac{(220)^2}{60} = 807 \Omega$$

104 (a)

$$4 \quad I = \frac{m}{Zt} = \frac{2.68}{\frac{108}{96500} \times 10 \times 60} = \frac{2.68}{108} \times \frac{965}{6} \approx 4 \text{ A}$$

$$\text{Energy} = I^2 R t = 4^2 \times 20 \times 600 = 192 \text{ kJ}$$

104 (c)

5 From Joule's law, for a current carrying conductor at a definite temperature the rate of production of heat is given by

$$H = Vit$$

Where  $i$  is current,  $V$  the potential difference and  $t$  the time.

$$\text{Given, } V = 1.5 \text{ volt, } i = 2.1 \text{ A, } t = 1 \text{ s}$$

$$\therefore H = 15 \times 2.1 \times 1 = 31.5 \text{ J}$$

$$\text{Also, } 1 \text{ cal} = 4.2 \text{ J}$$

$$\therefore H = \frac{31.5}{4.2} = 7.5 \text{ cal}$$

104 (c)



6 Power of bulb,  $P = \frac{V^2}{R}$

$$\therefore \frac{P_2}{P_1} = \frac{R_1}{R_2}$$

$$\text{Or } \frac{R_1}{R_2} = \frac{100}{200} = 0.5$$

104 (c)

7  $m = zq$

$$\Rightarrow q = \frac{m}{z} = \frac{5 \times 10^{-3}}{3.387 \times 10^{-7}}$$

$$q = 1.476 \times 10^4 \text{ C}$$

Since a current of 1 A for 1 h gives a charge of 3600 C,

$$\therefore 1 \text{ A h} = 3600 \text{ C}$$

$$\Rightarrow q = \frac{1.476 \times 10^4}{3600} \text{ Ah} = 4.1 \text{ Ah}$$

104 (c)

8 Resistance of each bulb =  $\frac{(220)^2}{60}$

If the number of bulbs is  $n$  then effective resistance

$$= \frac{(220)^2}{60n}$$

$$\therefore i = 9 = \frac{V}{R_{\text{eff}}} = \frac{220 \times 60n}{220 \times 220} \Rightarrow n = 33$$

104 (b)

9  $R_2 = R_0(1 + \alpha t_2)$  and  $R_{t_1} = R_0(1 + \alpha t_1)$

$$\therefore \frac{R_{t_2}}{R_{t_1}} = \frac{1 + \alpha t_2}{1 + \alpha t_1}$$

$$\text{or } \frac{1.5}{1} = \frac{1 + 0.00125 \times t_2}{1 + 0.00125 \times 27}$$

On solving we get;  $t_2 = 454^\circ\text{C} = 454 + 273 = 727\text{K}$

105 (d)

0 Heat produced = energy stored in capacitor  
 $= \frac{1}{2} CV^2 = \frac{1}{2} \times (10 \times 10^{-6}) \times (500)^2 = 1.25 \text{ J}$

105 (b)

1 Let  $I$  be the total current passing through balanced wheat stone bridge. Current through arms of resistances  $P$  and

$Q$  in series is

$$I_1 = \frac{I \times 300}{330 + 110} = \frac{3}{4} I \text{ and current through arms of}$$

$$\text{Resistances } R \text{ and } S \text{ in series is } I_2 = \frac{I \times 110}{330 + 110} = \frac{1}{4} I$$

$\therefore$  Ratio of heat developed per sec

$$H_P : H_Q : H_R : H_S$$

$$= \left(\frac{3}{4}I\right)^2 \times 100 : \left(\frac{3}{4}I\right)^2 \times 10 : \left(\frac{1}{4}I\right)^2 \times 300$$

$$: \left(\frac{1}{4}I\right)^2 \times 30$$

$$= 30 : 3 : 10 : 1.$$

105 (a)

2 The resistivity of metal increases when it is converted into an alloy

$$\rho' > \rho$$

105 (c)

4 Charge delivered to cathode per second

$$= \frac{0.002 \times 10^{25} \times 2 \times 1.6 \times 10^{-19}}{100 \times 60}$$

$$= 1.06 \text{ C}$$

105 (d)

5 Here,  $R_{20} = 20, R_{500} = 60\Omega, R_t = 25\Omega,$

$$\therefore R_t = R_0(1 + \alpha t)$$

Where  $\alpha$  is the temperature coefficient of resistance.

$$\therefore R_{20} = R_0(1 + \alpha \times 20)$$

$$\text{or } 20 = R_0(1 + \alpha \times 20) \quad \dots (i)$$

$$R_{500} = R_0(1 + \alpha \times 500)$$

$$\text{or } 60 = R_0(1 + \alpha \times 500) \quad \dots (ii)$$

Dividing Eq. (ii) by Eq. (i), we get

$$\frac{60}{20} = \frac{1 + \alpha \times 500}{1 + \alpha \times 20}$$

$$\text{or } 3 + 60\alpha = 1 + 500\alpha$$

$$\text{or } \alpha = \frac{2}{440} = \frac{1}{220} \text{ } ^\circ\text{C}^{-1}$$

$$\text{Again, } R_{20} = R_0(1 + \alpha \times 20)$$

$$\text{or } 20 = R_0 \left(1 + \frac{1}{220} \times 20\right) \dots (iii)$$

$$R_t = R_0(1 + \alpha t)$$

$$25 = R_0 \left(1 + \frac{1}{220} \times t\right) \dots (iv)$$

Dividing Eq. (iv) by Eq. (iii), we get


$$\frac{25}{20} = \frac{\left(1 + \frac{1}{220} \times t\right)}{\left(1 + \frac{1}{220} \times 20\right)} \Rightarrow 4 + \frac{4t}{220} = 5 + \frac{100}{220}$$

$$\text{or } t = 80^\circ\text{C}$$

105 (b)

6  $R_N = R + R/3$

$$= 4R/3$$

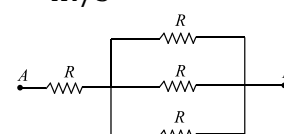

105 (c)

7 The total emf =  $E + E = 2E$

Total resistance =  $R + r_1 + r_2$

$\therefore$  Current flowing through the circuit

$$i = \frac{2E}{R + r_1 + r_2}$$

According to question  $E = ir_1$

$$\Rightarrow i = \frac{E}{r_1}$$

$$\therefore \frac{E}{r_1} = \frac{2E}{R + r_1 + r_2}$$

$$R = r_1 - r_2$$

105 (a)

8 Power  $P = VI = 250 \times 4 = 1000W = 1kW$

Energy  $= P \times t = 1 kW \times 60 sec = 60 kJ$

105 (c)

9 For the given meter bridge

$$\frac{P}{Q} = \frac{l_1}{100 - l_1}$$

$$l_1 = 55cm \Rightarrow 100 - l_1 = 45cm$$

$$\therefore P = 3Q$$

$$\Rightarrow Q = 3 \times \frac{45}{55} = 3 \times \frac{9}{11} = \frac{27}{11} \Omega$$

When  $x$  is connected in series with  $P$ ,  $l_1 = 75cm$

$$\Rightarrow \frac{P+x}{Q} = \frac{75cm}{25cm} \Rightarrow 3+x = 3 \times \frac{27}{11}$$

$$\Rightarrow x = \frac{81}{11} - 3 \Rightarrow x = \frac{48}{11} \Omega$$

106 (a)

0 The capacitance ( $C$ ) of a capacitor is defined as the ratio of the charge ( $q$ ) given to the rise in the potential ( $V$ ) of the conductor. When the plates are moved apart, the charge remains constant, hence

$$q = CV = \text{constant} \dots \dots \dots (i)$$

Capacitance ( $C$ ) of a parallel plate capacitor is given by

$$C = \frac{\epsilon_0 A}{d} \dots \dots \dots (ii)$$

Where  $A$  is area of plates and  $d$  the separation between them.

From Eqs. (i) and (ii), we have

$$q = \frac{\epsilon_0 A}{d} \cdot V = \text{constant}$$

When plates are moved apart,  $d$  increases, hence value of  $C$  decreases and in order that charge ( $q$ ) remains constant  $V$  increases.

106 (c)

1 Resistance of the combination

$$R' = \frac{10 \times 10}{10 + 10} + 10 = 15 \Omega$$

$$\therefore P = I^2 R \Rightarrow I \propto R$$

$$\therefore \frac{P}{P'} = \frac{R}{R'} \Rightarrow P' = \frac{15}{10} \times 20 = 30 \Omega$$

106 (d)


2 Suppose resistance of wires are  $R_1$  and  $R_2$  then

$$\frac{6}{5} = \frac{R_1 R_2}{R_1 + R_2}. \text{ If } R_2 \text{ breaks then } R_1 = 2 \Omega$$

$$\text{Hence, } \frac{6}{5} = \frac{2 \times R_2}{2 + R_2} \Rightarrow R_2 = 3 \Omega$$

106 (d)

3 The equivalent circuit is given by

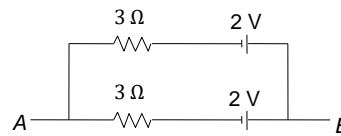

Since,  $V_A = V_B$

Potential difference is zero.

106 (b)

4 From balanced Wheatstone bridge concept,

$$\frac{550 \Omega}{R} = \frac{20}{80}$$

$$\Rightarrow R = 220 \Omega$$

106 (a)

5 Voltage across parallel combination is same. The equivalent resistance of upper branch

$$R = 4 + 6 = 10 \Omega$$

$$\text{So, } I_1 \times 10 = I_2 \times 10$$

$$\text{Or } I_1 = I_2 = I \quad (\text{say})$$

ie, Same current is flowing through both branches.

Now, it is given that

$$H_{4\Omega} = 10 \text{ cal}$$

$$\text{Or } I^2 t \times 4 = 10$$

$$\text{Or } I^2 t = \frac{10}{4}$$

Therefore, heat produced in  $10 \Omega$  resistance is

$$H_{10\Omega} = 10 \times I^2 t = \frac{10 \times 10}{4} = 25 \text{ cal}$$

106 (d)

$$6 \quad V_2 = \frac{P_1 V_1}{P_2} = \frac{22.4 \times 2}{1} = 44.8 \text{ L}$$

11.2 L of  $H_2$  is liberated by charge = 96500 C

44.8 L of  $H_2$  is liberated by charge

$$= \frac{96500}{11.2} \times 44.8 = 386000 \text{ C}$$

106 (b)


7 When switch  $S$  is open total current through ammeter

$$i = \frac{20}{(3+2)} = 4A$$

$$\text{When switch is closed } i = \frac{20}{3+(2||2)} = 5A$$

106 (b)

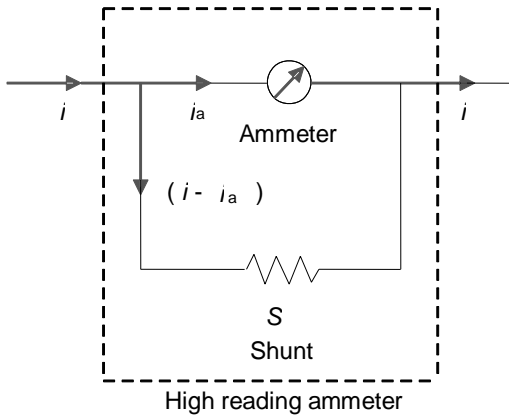9 Let  $i_a$  be the current flowing through ammeter and  $i$  the total current. So, a current  $i - i_a$  will flow through shunt resistance.



Potential difference across ammeter and shunt resistance is same,

$$\text{i.e., } i_a \times R = (i - i_a) \times S$$

$$\text{or } S = \frac{i_a R}{i - i_a} \dots \dots \dots (i)$$

Given,  $i_a = 100A, i = 750A, R = 13\Omega$

$$\text{Hence, } S = \frac{100 \times 13}{750 - 100} = 2\Omega$$

107 (b)

0 Faraday constant = 1 mole electron charge =  $Ne$   
 $= 6.02 \times 10^{23} \times 1.6 \times 10^{-19} = 96500$

107 (a)

1 Since  $R \propto l^2 \Rightarrow$  If length is increased by 10%, resistance increases by almost 20%  
 Hence new resistance  $R' = 10 + 20\%$  of 10  
 $= 10 + \frac{20}{100} \times 10 = 12\Omega$

107 (d)

2 Given  $l' = l + 100\%$  of  $l = 2l$   
 Initial volume = final volume  
 i.e.,  $\pi r^2 l = \pi r'^2 l'$   
 $\Rightarrow r'^2 = \frac{r^2 l}{l'} = r^2 \times \frac{l}{2l}$   
 $\Rightarrow r'^2 = \frac{r^2}{2}$   
 $\therefore R' = \rho \frac{l'}{A'} = \rho \frac{2l}{\pi r'^2} \quad (\because R = \frac{\rho l}{A})$   
 $= \frac{\rho 4l}{\pi r^2}$   
 Thus,  $\Delta R = R' - R = 4R - R = 3R$   
 $\therefore \% \Delta R = \frac{3R}{R} \times 100\%$   
 $= 300\%$

107 (b)

3  $R_{1000} = V^2/750$  and  $R_{200} = V^2/P$ ;  
 Now,  $R_{1000} = R_{200}(1 + \alpha \times 800)$   
 So,  $\frac{V^2}{750} = \frac{V^2}{P}(1 + 4 \times 10^{-4} \times 800)$   
 or  $P = 750(1 + 0.32) = 990 \text{ W}$

107 (d)

4 Mass,  $M = \text{volume} \times \text{density} = Al \times d$

$$\text{or } A = M/ld$$

$$\text{Resistance } R = \rho l/A = \rho l/(M/ld)$$

$$= \frac{\rho l^2 d}{M}$$

$$\text{So } R \propto l^2/M$$

$$\text{Thus, } R_1 : R_2 : R_3 = \frac{l_1^2}{M_1} : \frac{l_2^2}{M_2} : \frac{l_3^2}{M_3}$$

$$= \frac{3^2}{1} : \frac{2^2}{2} : \frac{1^2}{3} = 27 : 6 : 1$$

107 (c)

$$5 \text{ By using } v_d = \frac{i}{neA} = \frac{100}{10^{28} \times 1.6 \times 10^{-19} \times \frac{\pi}{4} \times (0.02)^2}$$

$$= 2 \times 10^{-4} \text{ m/sec}$$

107 (a)

$$6 \frac{R_A}{R_B} = \left(\frac{r_B}{r_A}\right)^4 \Rightarrow \frac{R_A}{R_B} = \left(\frac{1}{2}\right)^4 = \frac{1}{16} \Rightarrow R_B = 16R_A$$

When  $R_A$  and  $R_B$  are connected in parallel then equivalent resistance

$$R_{eq} = \frac{R_A R_B}{(R_A + R_B)} = \frac{16}{17} R_A$$

If  $R_A = 4.25\Omega$  then  $R_{eq} = 4\Omega$  i.e. option (a) is correct

107 (d)

$$7 P = i^2 R \Rightarrow 22.5 = (15)^2 \times R \Rightarrow R = 0.10 \Omega$$

107 (d)

$$8 V = E - ir = 1.5 - 2 \times 0.15 = 1.20 \text{ Volt}$$

107 (d)

9 To draw maximum current from a combination of cells, external resistance  $R = \frac{nr}{m}$ . Therefore, grouping of cells depends upon the relative values of internal and external resistance.

108 (a)

0 Watt-hour meter measures electric energy

108 (a)

1 If a motor of 12 HP works for 10 days at the rate of 8 h/day then

$$\text{Energy consumption} = \text{Power} \times \text{time}$$

$$= 12 \times 746 \frac{J}{s} \times (80 \times 60 \times 60)s$$

$$= 12 \times 746 \times 80 \times 60 \times 60 J = 2.5 \times 10^9 J$$

$$\text{Rate of energy} = 50 \frac{\text{paise}}{\text{kWh}}$$


$$\therefore 3.6 \times 10^6 J \text{ energy cost} = \text{Rs } 0.5$$

$$\therefore 2.5 \times 10^9 J \text{ energy cost} = \frac{2.5 \times 10^9}{2 \times 3.6 \times 10^6} = \text{Rs } 347$$

108 (b)

$$2 \text{ Resistance of } CD \text{ arm} = 2r \cos 72^\circ = 0.62r$$

Resistance of CBFC branch

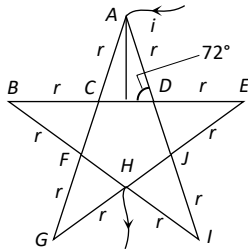

$$\frac{1}{R} = \frac{1}{2r} + \frac{1}{0.62r} = \frac{1}{r} \left( \frac{2.62}{2 \times 0.62} \right)$$

$$\frac{1}{R} = \frac{2.62}{1.24r} \quad \therefore R = \frac{1.24r}{2.62}$$

$$\text{Equivalent } R' = 2R + r = 2 \times \frac{1.24r}{2.62} + r$$

$$= r \left( \frac{2.48}{2.62} + 1 \right) = 1.946r$$

Because the star circuit is symmetrical about the line AH

$\therefore$  Equivalent resistance between A and H

$$\frac{1}{R_{eq}} = \frac{1}{R'} + \frac{1}{R'}$$

$$\Rightarrow R_{eq} = \frac{R'}{2} = \frac{1.946}{2} r = 0.973r$$

108 (d)

3 Here  $n = \frac{10}{2} = 5$

$$\therefore R = (n - 1)G = (5 - 1)2000 = 8000 \Omega$$


108 (c)

4 Seebeck arranged the metals in a certain sequence are called the thermoelectric series. The direction of current at the hot junction is from metal occurring earlier in series to one occurring later in series. Some of the substances in series are Bi, Ni, Co, Pd, Pt, Cu, Mn, Hg, Pb, Sn, Au, Ag, Zn, Cd, Fe, Sb, Te.

The more separated the metals are in the series, the greater is the value of thermo-emf generated. Thus, emf developed in Sb-Bi thermocouple is higher than other thermocouples.

108 (c)

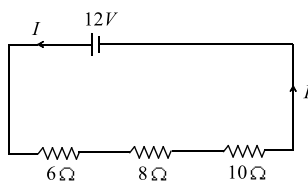5 Before connecting E, the circuit diagram is as shown in the figure



The equivalent resistance of the given circuit is  $R_{eq} = 6 \Omega + 8 \Omega + 10 \Omega = 24 \Omega$

$$\text{Current in the circuit, } I = \frac{12V}{24\Omega} = \frac{1}{2} A$$

Before connecting E, the current through 8 Ω is

$$I = \frac{1}{2} A$$

After connecting E, the current through 8 Ω is also

$$I = \frac{1}{2} A$$

$$\therefore E = \frac{1}{2} A \times 8\Omega = 4V$$

108 (b)

6 At constant p.d., heat produced =  $\frac{V^2}{R} i.e. H \propto \frac{1}{R}$

108 (b)


7 Given current through 4Ω resistance

Is 1A, so P.D. across upper Branch

i.e. P.D. between P and M is 4V

Hence P.D. between M & N is

$$\frac{1}{1 + 0.25} \times 4 = 3.2V$$

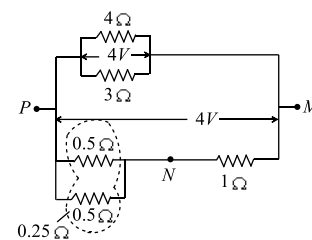

108 (d)

8  $\frac{dE}{dT} = 4 - \frac{2T}{200} 4 - \frac{T}{100}$ ;

At neutral point,  $T = T_n$ .

$$\frac{dT}{dT} = 0 = 4 - T_n/100$$

$$\text{or } T_n = 400^\circ C, T_i = 2T_n - T_0$$

$$= 2 \times 400 - 0 = 800^\circ C$$

108 (d)

9 In the above question for calculating equivalent

resistance between two opposite square faces

$l = 100 \text{ cm} = 1m, A = 1 \text{ cm}^2 = 10^{-4} m^2$ , so

resistance

$$R = 3 \times 10^{-7} \times \frac{1}{10^{-4}} = 3 \times 10^{-3} \Omega$$

109 (a)

0 The balanced condition for Wheatstone bridge is

$$\frac{P}{Q} = \frac{R}{S}$$

as is obvious from the given values.

No, current flows through galvanometer is zero.

Now, P and R are in series, so

$$\text{Resistance } R_1 = P + R = 10 + 15 = 25\Omega$$

Similarly, Q and S are in series, so

$$\text{Resistance } R_2 = R + S = 20 + 30 = 50\Omega$$

Net resistance of the network as  $R_1$  and  $R_2$  are in parallel.

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\therefore R = \frac{25 \times 50}{25 + 50} = \frac{50}{3} \Omega$$

Hence,

$$I = \frac{V}{R} = \frac{6}{\frac{50}{3}} = 0.36A$$

109 (b)

1  $H = I^2 R t = mc\Delta\theta$

$$\therefore \Delta\theta \propto I^2$$

$$\text{Hence } \frac{\Delta\theta^2}{\Delta\theta_2} = \left(\frac{I_2}{I_1}\right)^2 \text{ or } \frac{\Delta\theta^2}{3} = \left(\frac{2I+I}{I}\right)^2$$

$$\text{or } \Delta\theta_2 = 9 \times 3 = 27^\circ\text{C.}$$

109 (a)

2  $m n = 20 \dots(i)$

$$\text{For maximum current } R = n r / m$$

$$\text{or } 2.5 = n \times 0.5 / m \text{ or } n = 5m$$

$$\text{From Eq.(i), } m \times 5m = 20 \text{ or } m^2 = 4$$

$$\text{or } m = 2. \text{ Therefore, } n = 5 \times 2 = 10$$

109 (b)

3 The resistance of ammeter is very low, so when it is used in parallel through a circuit then excess current will flow through it thus, damaging it.

109 (d)

4 Zero (No potential difference across voltmeter)

109 (a)

5 When two batteries are in series to the external resistance

$$R, \text{ total resistance of the circuit}$$

$$= R + 2r = R + 2 \times 1 = R + 2\Omega$$

$$\text{Total emf of batteries} = 2+2 = 4 \text{ V}$$

$$\therefore \text{Joule power across } R$$

$$= \left(\frac{4}{R+2}\right)^2 \times R = \frac{4^2 R}{(R-2)^2 + 8R}$$

$$\text{Joule power will be maximum if } R - 2 = 0$$

$$\text{or } R = 2\Omega$$

$$\therefore \text{Maximum joulean power} = \frac{4^2 \times 2}{(2-2)^2 + 8 \times 2} = 2 \text{ watt}$$

109 (a)

6 Assume thermo emf  $E$  is directly proportional to temperature difference  $T$ .

$$\text{ie, } E = aT$$

$$a = \frac{1}{100} = 10^{-2} \text{VK}^{-1}$$

When cold junction is heated by 20 K, the temperature

difference  $T$  between junction becomes 80K, then thermo

emf

$$E = aT = 10^{-2} \times 80 = 0.8 \text{ V}$$

Percentage change of emf

$$= \frac{E - E'}{E} \times 100$$

$$= \frac{1 - 0.8}{1} \times 100 = 20\%$$


109 (b)

7 In parallel,  $x = \frac{R}{n} \quad R = nx$

In series,  $R + R + R \dots n \text{ times} = nR = n(nx) = n^2x$

109 (c)

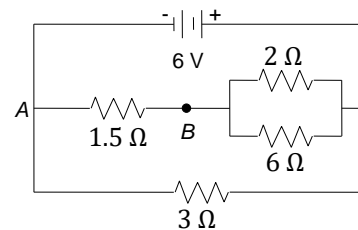8 The given circuit may be redrawn as shown in adjacent figure. Resistance of parallel combination of  $2\Omega$  and  $6\Omega$ ,



$$R_1 = \frac{2 \times 6}{2 + 6} = 1.5\Omega$$

Now resistance of  $ABC$  arm =  $1.5 + 1.5 = 3\Omega$

and total network resistance  $R = \frac{3 \times 3}{3+3} = 1.5\Omega$

$$\therefore \text{Total current supplied by the battery } i = \frac{6V}{1.5\Omega} =$$

$$4A$$

109 (d)

$$9 \quad i_g = i \frac{S}{G+S} \Rightarrow 0.01 = 10 \frac{S}{25+S}$$

$$\Rightarrow 1000S = 25 + S \Rightarrow S = \frac{25}{999} \Omega$$

110 (a)

0 Surface area of earth,  $A = 4\pi r^2$

Charge entering the earth per sec per unit area

$$J = 0.15 \times 1.6 \times 10^{-19} \text{Cm}^{-2}\text{s}^{-1}$$

$$= 0.15 \times 1.6 \times 10^{-19} \times 10^4 \text{Cm}^{-2}\text{s}^{-1}$$

$$\therefore \text{Current, } i = JA = J4\pi r^2$$

$$= 0.15 \times 1.6 \times 10^{-19} \times 10^4 \times 4 \times 3.14 \times (6.4 \times 10^6)^2 \text{ on solving}$$

$$i = 0.12 \text{ A}$$

110 (a)

1 Slope of the graph will give us reciprocal of resistance. Here resistance at temperature  $T_1$  is

greater than that at  $T_2$ . Since resistance of metallic wire is more at higher temperature than at lower temperature, hence  $T_1 > T_2$

110 (c)

2 An  $\alpha$  -particle has a charge equal to 2 protons. Motion of  $\alpha$  particle to the left, motion of proton towards left and motion of electrons towards right, all will produce conventional current towards left. The total current will be


$$i = 10^{19} \times (2 \times 1.6 \times 10^{-19}) \\ + 10^{19} \times (1.6 \times 10^{-19}) + 10^{19} \times (1.6 \times 10^{-19}) \\ = 6.4 \text{ A}$$

110 (b)

3  $I = \frac{P}{V} = \frac{550}{220} = 2.5 \text{ A}$

110 (a)

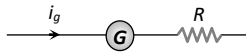
4  $(R + G)i_g = V \Rightarrow (R + G) = \frac{V}{i_g}$



$\therefore$  Value of  $R$  is nearly equal to  $6k\Omega$   
This is connected in series in a voltmeter

110 (a)

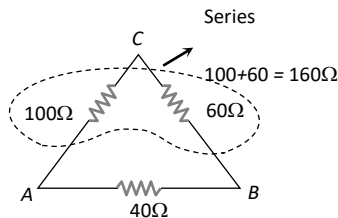5  $R = \frac{160 \times 40}{160 + 40} = 32\Omega$



110 (b)

6  $V = i \cdot R = \frac{e}{(R + R_h + r)} \cdot R \Rightarrow 10^{-3} \\ = \frac{2}{(10 + R + r)} \times 10 \\ \Rightarrow R = 19,989\Omega$

110 (a)

7 For maximum joule heat produced in resistor external resistance = Internal resistance

110 (a)

8 In parallel,  $\frac{H_1}{H_2} = \frac{P_1 t}{P_2 t} = \frac{P_1}{P_2} = \frac{500}{200} = \frac{5}{2}$

In series,  $\frac{H_1}{H_2} = \frac{I^2 R_1 t}{I^2 R_2 t} = \frac{R_1}{R_2} = \frac{V^2/P_1}{V^2/P_2} \\ = \frac{P_2}{P_1} = \frac{200}{500} = \frac{2}{5}$

110 (b)

9 Let the original resistance is  $R \Omega$ .

$$\therefore V = IR$$

$$V = 5 \times R = 5R \quad \dots(i)$$

When  $2 \Omega$  resistance is inserted, then total resistance

$$= (R+2) \Omega$$

$$\therefore V = I' (R + 2) = 4(R + 2) \quad \dots(ii)$$

From Eqs. (i) and (ii), we get

$$5R = 4(R + 2)$$

$$\therefore R = 8 \Omega$$

111 (b)


0 Emf  $E = 5V$ , Internal resistance  $r = \frac{5}{10} = 0.5\Omega$   
Current through the resistance  $i = \frac{5}{(2+0.5)} = 2A$

111 (c)

1 At null point, no current flows through galvanometer. Therefore, the resistance connected in series with galvanometer, at null point position will be in effective. Thus, null point is obtained on potentiometer wire at the original position after the removal wire at the original position after the removal of series resistance from galvanometer

111 (b)

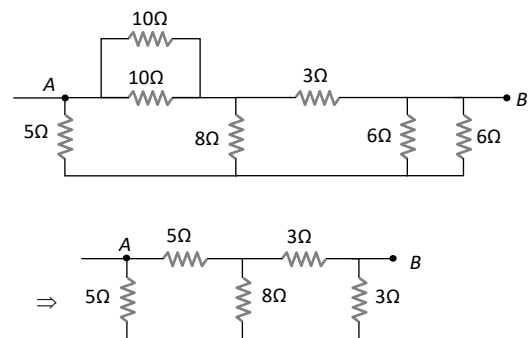3 The given circuit can be simplified as follows



Now it is a balanced Wheatstone bridge

So,

$$\Rightarrow R_{AB} = \frac{8 \times 8}{8 + 8} = \frac{64}{16} = 4\Omega$$

111 (a)

4 Current,  $I = \frac{q}{t} = \frac{3000C}{10 \times 60s} = 5A$

111 (b)

5 Resistance of parallel group =  $\frac{R}{2}$

$$\therefore \text{Total equivalent resistance} = 4 \times \frac{R}{2} = 2R$$

111 (d)

6 If resistance of each bulb be  $R$ , then bias voltage  $V$

is same in both cases, hence  $P = \frac{v^2}{R_{\text{total}}}$

In the case  $R_{\text{total}} = 50R$  and in second case  $49R$

$$\therefore \frac{P_1}{P_2} = \left(\frac{49}{50}\right)^2 \Rightarrow P_2 = \left(\frac{50}{49}\right)^2 \cdot P_1$$

or  $P_2 > P_1$

111 (d)

$$7 \quad V_{AB} = 4 = \frac{5X + 2 \times 10}{X + 10} \Rightarrow X = 20\Omega, \left[ v = \frac{E_2 r_1 + E_1 r_2}{r_1 + r_2} \right]$$

111 (a)

$$8 \quad H = i^2 R t \Rightarrow \frac{H}{t} = i^2 R = \frac{i^2 \rho l}{\pi r^2}$$

111 (c)

$$9 \quad \text{Resistance} = \rho \frac{l}{A}$$

$$\therefore \frac{R_1}{R_2} = \frac{\rho_1}{\rho_2} \times \frac{l_1}{l_2} \times \frac{A_2}{A_1} = \frac{2}{3} \times \frac{3}{4} \times \frac{5}{4} = \frac{5}{8}$$

112 (c)

0 Because in series current is same

112 (a)

1 The effective resistance between two diagonally opposite ends =  $5R/6$

112 (c)

$$2 \quad \frac{m_1}{m_2} = \frac{Z_1}{Z_2} \Rightarrow m_2 = \frac{m_1 Z_2}{Z_1} = \frac{14 \times 1.2 \times 10^{-6}}{7 \times 10^{-6}} = 2.4g$$

112 (c)

3 Current through each arm

PRQ and PSQ = 1A

$$V_p - V_R = 3v$$

$$V_p - V_s = 7V$$

From Eqs. (i) and (ii), we get

$$V_R - V_s = +4V$$

112 (a)

4 The effective resistance of combined wire

$$\rho \left( \frac{l+l}{A} \right) = \frac{\rho_1 l}{A} + \frac{\rho_2 l}{A}$$

( $\therefore$  total length  $L = l + l$ )


Or

$$\rho = \frac{\rho_1 + \rho_2}{2}$$

112 (a)

5 The circuit diagram with current variation can be drawn as

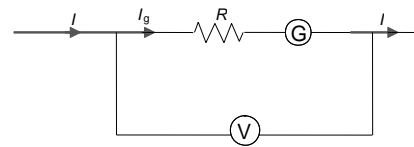Let current  $I_g$  flows through R and G.



For a voltmeter with full scale reading, we have

$$V = I_g (G + R)$$

$$\text{or } R = \frac{V}{I_g} - G$$

Given,  $G = 2\Omega$ ,  $V = 12\text{volt}$ ,  $I_g = 0.1A$

$$\therefore R = \frac{12}{0.1} - 2 = 120 - 2 = 118\Omega$$

112 (c)

6 Because given voltage is very high

112 (c)

7 When cells are connected in series: emf increase but current capacity remains unchanged. The emf of 6 cells in series =  $6 \times 1.5 = 9V$  and current capacity = 5A h

112 (c)

$$8 \quad H = \frac{V^2}{R} \times t = \frac{(210)^2}{20} \times 1 = mL$$

$$\therefore \frac{(210)^2}{20} = m \times 80 \times 4.2 \Rightarrow m = 6.56 \text{ g/s}$$

112 (d)

$$9 \quad \text{By using } \frac{i}{i_g} = 1 + \frac{G}{S}$$

$$\Rightarrow \frac{i}{100 \times 10^{-3}} = 1 + \frac{1000}{S} \Rightarrow S = \frac{1000}{9} = 111\Omega$$

113 (b)


$$0 \quad R \propto \frac{1}{A} \Rightarrow R \propto \frac{1}{r^2} \propto \frac{1}{d^2} \quad [d = \text{diameter of wire}]$$

113 (c)

1 The graph between thermo emf and temperature of hot junction is parabolic in shape

113 (d)

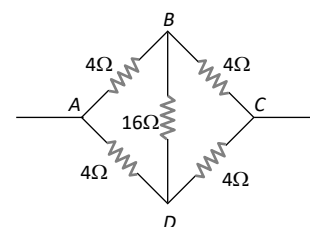2 According to the principle of Wheatstone's bridge, the effective resistance between the given points is  $4\Omega$



113 (d)

$$3 \quad P = \frac{V^2}{R} \text{ so } R = \frac{V^2}{P} \Rightarrow R_1 = \frac{V^2}{100} \text{ and } R_2 = R_3 = \frac{V^2}{60}$$

$$\text{Now } W_1 = \frac{(250)^2}{(R_1 + R_2)^2} \cdot R_1, W_2 = \frac{(250)^2}{(R_1 + R_2)^2} \cdot R_2$$

$$\text{and } W_3 = \frac{(250)^2}{R_3}$$

$$W_1 : W_2 : W_3 = 15 : 25 : 64 \text{ or } W_1 < W_2 < W_3$$

113 (c)

4 The voltmeter is assumed to have infinite resistance. Hence  $(1 + 2 + 1) + 4 = 8\Omega$

113 (b)

5  $W = JH \Rightarrow P \times t = J \times ms \Delta\theta$

$$\Rightarrow t = \frac{J \times m \times s \Delta\theta}{P} \quad [\text{For water 1 litre} = 1 \text{ kg}]$$

$$\Rightarrow t = \frac{4.2 \times 1 \times 1000 \times (40 - 10)}{836} = 150 \text{ sec}$$



Short Trick : use formula  $t = \frac{4200 \times m \times \Delta\theta}{P}$

113 (a)

6  $R > 2\Omega$

$$\therefore 100 - x > x$$
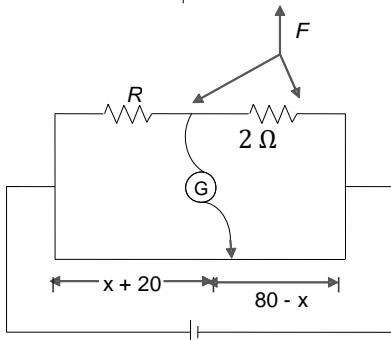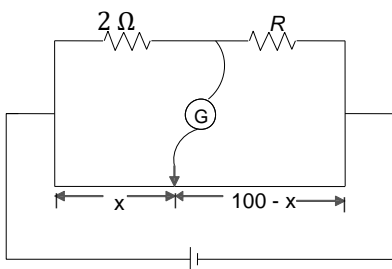
$$\text{Applying, } \frac{P}{Q} = \frac{R}{S}$$



We have

$$\frac{2}{R} = \frac{x}{100 - x} \quad \dots (i)$$

$$\frac{R}{2} = \frac{x + 20}{80 - x} \quad \dots (ii)$$

Solving Eqs. (i) and (ii), we get

$$R = 3\Omega$$

113 (a)

7 Length of wire =  $2\pi r = 2\pi(0.1) = 0.2\pi m$

Resistance of complete wire =  $12 \times 0.2\pi = 2.4\pi\Omega$

$\therefore$  Resistance of each semicircle =  $1.2\pi\Omega$

Hence equivalent resistance  $R_{AB} = \frac{1.2\pi}{2} = 0.6\pi\Omega$

113 (c)

8 Resistivity  $\rho = \frac{RA}{l}$

$$\Rightarrow \rho \propto R$$

$\therefore$  Metals have low resistance, therefore they have low resistivity.

113 (c)

9 Voltmeter has high resistance and is always

connected in parallel with the circuit. So, to convert a galvanometer into voltmeter, a high resistance must be connected in series with it so that it draws negligible current from the circuit.

114 (a)

$$0 \quad E = V + ir$$

After short-circuiting,  $V = 0 \Rightarrow r = \frac{E}{i} = \frac{2}{4} = 0.5\Omega$


114 (d)

1 Applying Kirchoff's law at point D, we get

$$I_1 = I_2 + I_3$$

$$\frac{V_A - V_D}{10} = \frac{V_D - 0}{20} + \frac{V_D - V_C}{30}$$
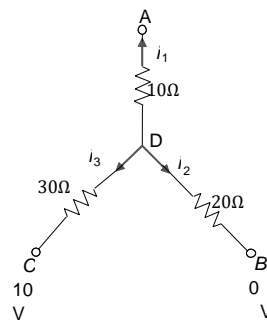
$$\text{or } 70 - V_D = \frac{V_D}{2} + \frac{V_D - 10}{3}$$



$$\Rightarrow V_D = 40V$$

$$\Rightarrow i_1 = \frac{70 - 40}{10} = 3A$$

$$i_2 = \frac{40 - 0}{20} = 2A$$

$$\text{and } i_3 = \frac{40 - 10}{30} = 1A$$

114 (c)

$$2 \quad P_{consumed} = \left(\frac{V_A}{V_R}\right)^2 \times P_R = \left(\frac{110}{115}\right)^2 \times 500$$

$$= 457.46 W$$

So, percentage drop in power output

$$= \frac{(500 - 457.46)}{500} \times 100 = 8.6\%$$

114 (b)

$$3 \quad \frac{P}{Q} = \frac{1/3}{1 - 1/3} = \frac{1/3}{2/3}$$

$$\Rightarrow P:Q = 1:2$$

$$P = k, \quad Q = 2k$$

$$\frac{P + 6}{Q} = \frac{\frac{2}{3}}{1 - \frac{2}{3}}$$

$$\Rightarrow \frac{P + 6}{Q} = \frac{2}{1}$$

$$\frac{k + 6}{2k} = \frac{2}{1}$$

$$\Rightarrow k + 6 = 4k$$

$$\Rightarrow k = 2$$

$$\therefore P = 2\Omega, Q = 4\Omega$$



114 (d)

$$I = \frac{E}{R + r/4} = \frac{2}{2 + 1/4} = \frac{2}{2.25} = 0.888A$$

114 (b)

5 Resistors are connected in series. So current through each resistor will be same

$$\Rightarrow i = \frac{12 - 8}{R_3} = \frac{8 - 4}{R_2} = \frac{4 - 0}{R_1} \Rightarrow \frac{4}{R_3} = \frac{4}{R_2} = \frac{4}{R_1}$$

So,  $R_1 : R_2 : R_3 :: 1 : 1 : 1$

114 (b)

6 Let the resistance of the two heaters be denoted by  $R_1$  and  $R_2$ .

$$\text{Then, } R_1 = \frac{V^2}{P_1}$$

$$R_2 = \frac{V^2}{P_2}$$

In parallel combination of resistances,

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{P_p}{V^2} = \frac{P_1}{V^2} + \frac{P_2}{V^2}$$

$$P_p = P_1 + P_2$$

Given,  $P_1 = 1000 \text{ W}$

$$P_2 = 1000 \text{ W}$$

$$\therefore P_p = 1000 + 1000$$


Hence,  $P_p = 2000 \text{ W}$

114 (a)

7 By using  $R = \rho \cdot \frac{l}{A}$ ; here  $A = \pi(r_2^2 - r_1^2)$

Outer radius  $r_2 = 5 \text{ cm}$

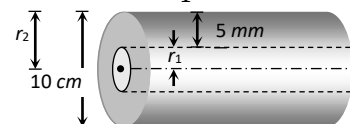Inner radius  $r_1 = 5 - 0.5 = 4.5 \text{ cm}$



$$\text{So } R = 1.7 \times 10^{-8} \times \frac{5}{\pi\{(5 \times 10^{-2})^2 - (4.5 \times 10^{-2})^2\}}$$

$$= 5.6 \times 10^{-5} \Omega$$

114 (a)

8  $m \propto q \Rightarrow m \propto it$

114 (d)

9 Potential gradient is given by

$$k = \frac{V}{l} = \frac{IR}{l} \quad (\because V = IR)$$

$$= \frac{I \times \rho l / A}{l} \quad (\because R = \frac{\rho l}{A})$$

$$= \frac{I\rho}{A}$$

$$\therefore k = \frac{0.01 \times 10^{-3} \times 10^9 \times 10^{-2}}{10^{-2} \times 10^{-4}} = 10^8 \text{Vm}^{-1}$$

115 (d)

$$R = \frac{V}{i_g} - G = \frac{100}{10 \times 10^{-3}} - 25 = 9975 \Omega$$

115 (a)

1 Resistivity of combination

$$= (1 + 2 + 3 + \dots + n)$$

$$= \frac{n(n+1)}{2}$$

115 (b)

2 Here  $P_1 = i^2 \times \frac{r}{3}, P_2 = i^2 \times 3r,$

$$P_3 = i^2 \left( \frac{r}{2} + r \right) = \frac{3}{2} i^2 r$$

$$\text{and } P_4 = i^2 \left[ \frac{2r \times 2r}{2r + 2r} \right] = i^2 r$$


So it is obvious that  $P_2 > P_3 > P_4 > P_1$

115 (c)

3 In series  $P' = \frac{P}{n} = \frac{60}{3} = 20 \text{ watts}$

115 (b)

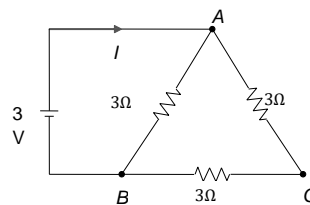4 Resistance in the arms  $AC$  and  $BC$  are in series,



$$\therefore R' = 3 + 3 = 6 \Omega$$

Now,  $R'$  and  $3 \Omega$  are in parallel,

$$\therefore R_{\text{eq}} = \frac{6 \times 3}{6 + 3} = 2 \Omega$$

Now,  $V = IR$

$$\Rightarrow I = \frac{3}{2} = 1.5A$$

115 (d)

5 The residence of conductor

$$R = \frac{\rho l}{A} = \frac{1}{\pi r^2}$$

$$\text{or } R \propto \frac{l}{r^2}$$

$$\therefore \frac{R_1}{R_2} = \frac{l_1}{l_2} \times \frac{r_2^2}{r_1^2} = \frac{2}{1} \times \left( \frac{2}{1} \right)^2 = \frac{8}{1}$$

Thermal potential between the ends of the roads are same. So, heat conducted per second

$$H = \frac{Q}{t} \propto \frac{1}{R}$$

$$\therefore \frac{H_1}{H_2} = \frac{R_2}{R_1} = \frac{1}{8} = 1:8$$

115 (b)

6 We know,  $\frac{V^2 t}{4.2 R} = Q = ms d\theta$

Let,  $N$  = initial number of turns

$R$  = resistance of the coil

$$\Rightarrow R = \rho \frac{L}{A} = \frac{\rho \times N \times 2\pi r}{A}$$

$$\frac{V^2 t}{4.2 \times \rho \times N \times 2\pi r} = Q = ms d\theta$$

$$\frac{t}{N} = \text{Constant}$$

$$\therefore \frac{t_1}{N_1} = \frac{t_2}{N_2}$$

$$\Rightarrow = \frac{N_2}{N_1} \times t_1 = \frac{9}{10} \times 16 = 14.4 \text{ min.}$$

115 (b)

7 Resistivity of the material of the rod

$$\rho = \frac{RA}{l}$$

$$= \frac{3 \times 10^{-3} \times \pi (0.3 \times 10^{-2})^2}{1}$$

$$= 27 \times 10^{-9} \pi \Omega \text{m}$$

Resistance of disc,


$$R = \frac{\text{Resistivity of rod} \times \text{Thickness}}{\text{Area of cross-section}}$$

$$= 27 \times 10^{-9} \pi \times \frac{10^{-3}}{\pi \times (1 \times 10^{-2})^2}$$

$$= 2.7 \times 10^{-7} \Omega$$

115 (b)

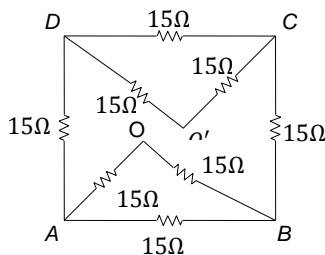8 The circuit can be shown as given below



The equivalent resistance between  $D$  and  $C$ .

$$\begin{aligned} R_{DC} &= \frac{15 \times (15 + 15)}{15 + (15 + 15)} \\ &= \frac{15 \times 30}{15 + 30} \\ &= \frac{15 \times 30}{45} = 10\Omega \end{aligned}$$

Now, between  $A$  and  $B$ , the resistance of upper part  $ADCB$ ,

$$R_1 = 15 + 10 + 15 = 40\Omega$$

Between  $A$  and  $B$ , the resistance of middle part  $AOB$

$$R_2 = 15 + 15 = 30\Omega$$

Therefore, equivalent resistance between  $A$  and  $B$

$$\frac{1}{R'} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{40} + \frac{1}{30} + \frac{1}{15}$$

$$= \frac{3 + 4 + 8}{120}$$

$$= \frac{15}{120}$$

$$\Rightarrow R' = \frac{120}{15} = 8\Omega$$


115 (a)

$$9 \quad i = \frac{m}{Zt} = \frac{2.0124}{1.118 \times 10^{-3} \times 3600} = 0.5 \text{ A}$$

$$\Rightarrow \text{Error} = 0.54 - 0.5 = 0.04 \text{ A}$$

116 (a)

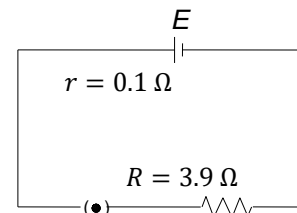0 When a cell of emf  $E$  is connected to a resistance of  $3.9\Omega$ , then the emf  $E$  of the cell remains constant, while voltage  $V$  goes on decreasing on taking more and more current from the cell.



$$\therefore V = E - ir$$

Where,  $r$  is internal resistance.

$$\text{Also, current } i = \frac{E}{R+r}$$

$$\therefore V = E - \left(\frac{E}{R+r}\right)r$$

Putting the numerical values, we have

$$E = 2V, r = 0.1\Omega, R = 3.9\Omega$$

$$V = 2 - \left(\frac{2}{3.9 + 0.1}\right) \times 0.1$$

$$V = 1.95 \text{ Volt}$$

116 (a)

$$1 \quad R_1 = \frac{(220)^2}{100} = 484 \Omega$$

$$\text{And } R_2 = \frac{(220)^2}{200} = 242 \Omega$$

$$\text{So, } i = \frac{220}{484+242} = 0.3 \text{ A}$$

Hence, total power consumed will be

$$P = i^2 R = (0.3)^2 \times (484 + 242) = 65.34 \approx 65 \text{ W}$$

116 (b)

$$2 \quad n = \frac{1 \times 10^{-3}}{1.6 \times 10^{-19}} = 6.25 \times 10^{15}$$

116 (b)

3

Resistance of the wire,  $R = \rho \frac{L}{A}$

When the wire is elongated to  $n$  –fold, its length becomes  $L' = nL$

As the volume of the wire remains constant

$$\therefore A'L' = AL \Rightarrow A' = \frac{AL}{L'} = \frac{A}{n}$$

$$\text{New resistance, } R' = \rho \frac{L'}{A'} = \rho \frac{(nL)}{(A/n)} = n^2 \rho \frac{L}{A} = n^2 R$$

116 (b)

4 Let the resistances be  $R_1, R_2$  and  $R_3$

$$\therefore \frac{R_1}{R_2} = \frac{1}{2} \Rightarrow R_1 = k, R_2 = 2k$$

$$\text{In parallel } \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{1} = \frac{1}{k} + \frac{1}{2k} + \frac{1}{R_3}$$

$$\frac{1}{R_3} = 1 - \frac{1}{k} = \frac{1}{2k}$$

$$= \frac{2k - 2 - 1}{2k} = \frac{2k - 3}{2k}$$

$$R_3 = \frac{2k}{2k - 3}$$

If  $k=1$ , then  $R_3$  is found to be negative, which is impossible.

If  $k=2$ , then  $R_1 = 2, R_2 = 4, R_3 = 4$

$R_2 = R_3$ , not satisfying the condition of the question that all resistance are unequal.

If  $k = 3$ , then  $R_1 = 3, R_2 = 6$

$$R_3 = 2\Omega$$

$\therefore$  Largest resistance =  $6\Omega$

116 (a)

5 In parallel  $\frac{1}{t_p} = \frac{1}{t_1} + \frac{1}{t_2} \Rightarrow t_p = \frac{t_1 t_2}{t_1 + t_2}$

$$= \frac{5 \times 10}{5 + 10} = \frac{50}{15} = 3.33 \text{ min} = 3 \text{ min. } 20 \text{ sec}$$

116 (b)

6 Electric power consumed by kettle  $P = 220 \times 4W$   
Heat required

$$H = 1000 \times 1(100 - 20) = 1000 \times 80 \text{ cal} \\ = 4200 \times 80 J$$

$$P = \frac{H}{t} \Rightarrow H = P \times t$$

$$\therefore 220 \times 4 \times t = 4200 \times 80 \Rightarrow t = 6.3 \text{ minutes}$$

116 (a)

7  $P = i^2 R$

Current is same, so  $P \propto R$

In the first case  $I$  is  $3r$ , in second case it is  $\frac{2}{3} r$ , in third case it is  $\frac{r}{3}$  and in fourth case the net resistance is  $\frac{3r}{2}$ .

$$R_{III} < R_{II} < R_{IV} < R_I$$

$$\therefore P_{III} < P_{II} < P_{IV} < P_I$$

116 (a)

8 As the resistance of metal increases on increasing the temperature, so resistance of metal conductor in left arm will increase on heating. For meter bridge

$$\frac{R_1}{R_2} = \frac{l}{100 - l}$$

As  $R_1$  increases  $l$  also increases.

Hence, balancing point shifts towards right.

116 (a)

9 Mass of substance liberated at cathode  $m = zit$

Where,  $z$  = electro chemical equivalent

$$= 3.3 \times 10^{-7} \text{ kg} \cdot \text{C}^{-1}$$

$i$  = current flowing =  $3 \text{ A}$ ,

$$t = 2 \text{ s}$$

$$m = 3.3 \times 10^{-7} \times 3 \times 2$$

$$= 19.8 \times 10^{-7} \text{ kg}$$

117 (a)

$$0 \quad \frac{R_1}{R_2} = \frac{(1 + \alpha t_1)}{(1 + \alpha t_2)} \Rightarrow \frac{10}{R_2} = \frac{(1 + 5 \times 10^{-3} \times 20)}{(1 + 5 \times 10^{-3} \times 120)} \\ \Rightarrow R_2 \approx 15\Omega$$

$$\text{Also } \frac{i_1}{i_2} = \frac{R_2}{R_1} \Rightarrow \frac{30}{i_2} = \frac{15}{10} \Rightarrow i_2 = 20 \text{ mA}$$

117 (a)

$$1 \quad 1 \text{ kWh} = 1000 \text{ W} \times 3600 \text{ sec} = 36 \times 10^5 \text{ W-sec (or J)}$$


117 (a)

2 Here same current is passing throughout the length of the wire, hence  $V \propto R \propto l$

$$\Rightarrow \frac{V_1}{V_2} = \frac{l_1}{l_2} \Rightarrow \frac{6}{V_2} = \frac{300}{50} \Rightarrow V_2 = 1 \text{ V}$$

117 (d)

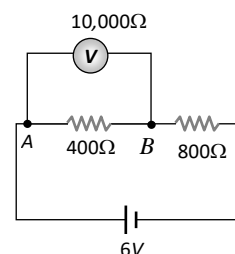3 Before connecting voltmeter potential difference across  $400\Omega$  resistance is



$$V_i = \frac{400}{(400 + 800)} \times 6 = 2 \text{ V}$$

After connecting voltmeter equivalent resistance between  $A$  and

$$B = \frac{400 \times 10,000}{(400 + 10,000)} = 384.6\Omega$$

Hence, potential difference measured by

voltmeter

$$V_f = \frac{384.6}{(384.6 + 800)} \times 6 = 1.95V$$

$$\text{Error in measurement} = V_i - V_f = 2 - 1.95 = 0.05V$$

117 (d)

$$R = \frac{V}{i} = \frac{100 \pm 0.5}{10 \pm 0.2} = 10 \pm 0.25\Omega$$

117 (b)

$$P = VI, I = \frac{P}{V}$$

$$\text{or } I = \frac{500W}{100V} = 5A$$

$$\text{Now, } 5R = 100$$

$$\text{or } R = 20\Omega.$$

117 (c)

6 If resistance of ammeter is  $r$  then

$$20 = (R + r)4 \Rightarrow R + r = 5 \Rightarrow R < 5\Omega$$

117 (b)

7 Current through each arm  $DAC$  and  $DBC = 1A$

$$V_D - V_A = 2 \text{ and } V_D - V_B = 3 \Rightarrow V_A - V_B = +1V$$

117 (b)

$$R = \frac{V^2}{P} = \frac{(250)^2}{10^3} = 62.5\Omega$$

118 (c)

$$0 \text{ Total resistances} = 1 + 2 + \frac{2 \times 2}{2+2} + 4 = 8\Omega$$

118 (b)

$$1 \text{ Current in the given circuit } i = \frac{50}{(5+7+10+3)} = 2A$$

$$\text{Potential difference between } A \text{ and } B, V_A - V_B = 2 \times 12$$

$$\Rightarrow V_A - 0 = 24V \Rightarrow V_A = 24V$$

118 (b)

$$2 \quad P = \frac{V^2}{R_{eq}} \Rightarrow 150 = \frac{(15)^2}{[2R/(R+2)]} = \frac{225 \times (R+2)}{2R}$$

$$\Rightarrow R = \frac{450}{75} = 6\Omega$$

118 (d)

3 Total external equivalent resistance  $R_{eq} = 4\Omega$

$$\text{Current supply by cell } i = \frac{E}{R_{eq} + r} = \frac{10}{(4+1)} = 2A$$

$$\therefore (V_A - V_B) = \frac{i}{2}(R_2 - R_1) = \frac{2}{2}(2 - 4) = -2V$$


118 (a)

$$4 \quad r = \left(\frac{l_1 - l_2}{l_2}\right)R = \left(\frac{25}{100}\right)2 = 0.5\Omega$$

118 (a)

5 Let  $Q$  is divided into two parts. If one part is  $q$  then other will  $(Q-q)$ .

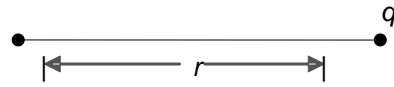Let these parts are kept a  $(Q-q)$  distance  $r$ .



The electrostatic force between them

$$F = K \cdot \frac{q(Q-q)}{r^2} \dots \dots (i)$$

(where  $K = \text{constant} - (1/4\pi\epsilon_0)$ )

On differentiating Eq. (i) w.r.t.  $q$ , we get

$$\frac{dF}{dq} = \frac{d}{dq} \left[ \frac{Kq}{r^2} (Q-q) \right]$$

$$\text{or } \frac{dF}{dq} = \frac{K}{r^2} \frac{d}{dq} [Qq - q^2]$$

$$\text{or } \frac{dF}{dq} = \frac{K}{r^2} [Q - 2q] \dots \dots (ii)$$

But we know that, when force is maximum then

$$\frac{dF}{dq} = 0$$

Then from Eq. (ii), we have

$$\frac{K}{r^2} [Q - 2q] = 0 \text{ or } Q - 2q = 0$$

$$\text{Or } Q = 2q \text{ or } q = \frac{Q}{2}$$

$$\text{So, the other part} = Q - \frac{Q}{2} = \frac{Q}{2}$$

Hence, the each part have the same charge.

$$\frac{Q}{2}$$

118 (c)

$$6 \quad q = \frac{m}{z} = \frac{1 \times 10^{-3}}{1.044 \times 10^{-8}} = \frac{10^5}{1.044} C;$$

Given,  $H = 43 \text{ k cal.}$

$$= 34 \times 10^3 \times 4.2 J$$

$$H = VIt = Vq$$

$$\therefore V = \frac{H}{q} = \frac{34 \times 4.2 \times 10^3}{10^5/1.044} = 1.49V$$

118 (c)

$$7 \quad E = \frac{iR}{L} = \frac{i \cdot \rho}{A} = \frac{neAv_d \rho}{A} \Rightarrow v_d \propto E \text{ [Straight line]}$$

$$P = i^2 R = \left(\frac{EA}{\rho}\right)^2 R \Rightarrow P \propto E^2 \text{ [Symmetric}$$

parabola]

Also  $P \propto i^2$  (parabola)

Hence all graphs  $a, b, d$  are correct and  $c$  is incorrect

118 (b)


8 When we move in the direction of the current in a uniform conductor, the potential difference decreases linearly. When we pass through the cell, from its negative to its positive terminal, the potential increases by an amount equal to its potential difference. This is less than its emf, as there is some potential drop across its internal resistance when the cell is driving current

118 (d)

- 9 At cold junction, current flows from copper to nickel and from iron to copper, and at hot junction from nickel to iron, thus the contributions add

119 (d)

- 0 The equivalent circuit is shown as

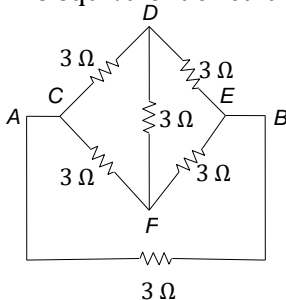

We can emit the resistance in the arm  $DF$  as balance condition is satisfied.

Therefore, the  $3\Omega$  resistances in arm  $CD$  and  $DE$  are in series.

$$\therefore R' = 3 + 3 = 6\Omega$$

Similarly, for arms  $CF$  and  $FE$ ,  $R'' = 6\Omega$

$R'$  and  $R''$  are in parallel

$$\therefore \frac{1}{R'''} = \frac{1}{6} + \frac{1}{6} = \frac{2}{6} = \frac{1}{3}$$

$$R''' = 3\Omega$$

Now,  $R'''$  and  $3\Omega$  resistances are in parallel

$$\therefore \frac{1}{R} = \frac{1}{3} + \frac{1}{3}$$

$$\Rightarrow R = 1.5\Omega$$

Moreover,  $V$  across  $AB = 3V$  and resistance in the arm  $= 3\Omega$

$\therefore$  Current through the arm will be

$$= \frac{3V}{3\Omega} = 1A.$$


119 (a)

- 2 Both  $R$  and  $2R$  are in parallel [ $V$  – constant]

$$\text{So using } P = \frac{V^2}{R} \Rightarrow \frac{P_1}{P_2} = \frac{R_2}{R_1} \Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = \frac{2}{1}$$

119 (a)

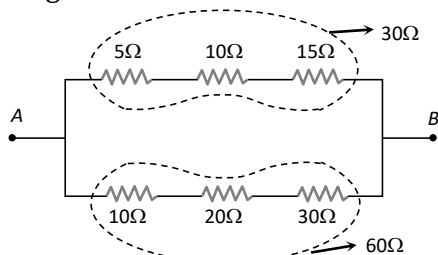- 4 By the concept of balanced Wheatstone bridge, the given circuit can be redrawn as follows



$$\Rightarrow R_{AB} = \frac{30 \times 60}{30 + 60} = 20\Omega$$

119 (a)

- 5 For applying Faraday's second law of electrolysis the same charge should be passed through copper and silver voltmeters.

Charge passed to liberate copper

$$= 9 \times 20 \times 60 = 10800 \text{ C}$$

Charge passed to liberate silver

$$= 10 \times 15 \times 50 = 9000 \text{ C}$$

As 9000 C charge liberates 10.8 g of Ag.

So 10800 C charge liberates

$$= \frac{10.8 \times 10800}{9000} = 10.8 \times 1.2 \text{ g of Ag.}$$

Using Faraday's second law of electrolysis

$$\frac{m_{\text{Cu}}}{m_{\text{Ag}}} = \frac{E_{\text{Cu}}}{E_{\text{Ag}}} = \frac{63.5/2}{108/1}$$

$$\text{or } m_{\text{Cu}} = \frac{63.5 \times 10.8 \times 1.2}{2 \times 108} = 3.81 \text{ g.}$$

119 (d)


- 7  $R_p = \frac{R_1 R_2}{R_1 + R_2} = \frac{3}{5}$  and  $R_1 = 3\Omega$  then

$$\frac{3 \times R_2}{3 + R_2} = \frac{3}{5} \text{ or } 15R_2 = 9 + 3R_2$$

$$\text{or } 12R_2 = 9 \text{ or } R_2 = \frac{3}{4}\Omega$$

119 (c)

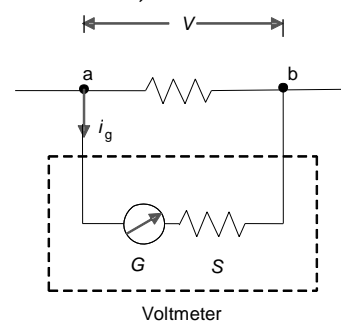- 8 Let  $G$  be resistance of galvanometer and  $i_g$  the current through it. Let  $V$  is maximum potential difference, then from Ohm's law



$$i_g = \frac{V}{G + R}$$

$$\Rightarrow R = \frac{V}{i_g} - G$$

Given  $G = 10\Omega$ ,  $i_g = 0.01A$

$$V = 10 \text{ volt}$$

$$\therefore R = \frac{10}{0.01} - 10 = 990\Omega$$

Thus, on connecting a resistance  $R$  of  $990\Omega$  in series with the galvanometer, the galvanometer will become a voltmeter of range zero to 10V.

120 (c)

$$0 \text{ Potential gradient } x = \frac{e}{(R + R_h + r)} \cdot \frac{R}{L}$$

$$= \frac{3}{(20 + 10 + 0)} \times \frac{20}{10} = 0.2$$

120 (b)

$$1 \frac{\text{Mass of } O_2 \text{ ions}}{\text{Mass of Ag ions}} = \frac{\text{Chemical equivalent of } O_2}{\text{Chemical equivalent of Ag}}$$

$$\Rightarrow \frac{0.8}{m} = \frac{8}{108} \Rightarrow m = 10.8 \text{ gm}$$

120 (b)

$$2 \quad E = V + ir \Rightarrow V = -ri + E$$

Comparing it with  $y = mx + c$ ; Slope ( $m$ ) =  $-r$  and intercept =  $E$

120 (c)

$$3 \quad I = \frac{R}{R_2 + r}$$

(since finally no current flows through capacitor)

$\therefore$  Potential difference across

$$R_2, V = IR_2 = \frac{ER_2}{R_2 + r}$$

$\therefore$  Charge on the capacitor

$$Q = CV = \frac{CER_2}{R_2 + r}$$

120 (c)

4 In a meter bridge the ratio of two resistances is

$$\frac{R}{R'} = \frac{l}{l'}$$

Where  $l$  and  $l'$  are balancing lengths.

$$\text{Resistance } R = \frac{\rho l}{A} = \frac{\rho l}{\pi r^2}$$

In material remains same  $\rho = \rho'$

Given,  $l' = 2l$

$$r' = \frac{r}{2}$$


$$\therefore R' = \frac{\rho l'}{A'} = \frac{\rho 2l}{\pi \left(\frac{r}{2}\right)^2} = \frac{8\rho l}{\pi r^2}$$

$$R' = 8R$$

Therefore, the new balancing point is expected to be  $8l$ .

120 (b)

5

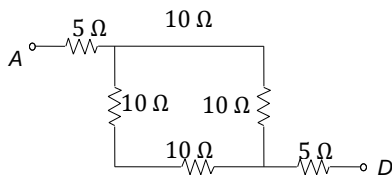


$10\Omega$  in series with  $10\Omega$  will gives

$$(10+10)=20\Omega$$

and  $10\Omega$  in series with  $10\Omega$  will gives


$$(10+10)=20\Omega$$

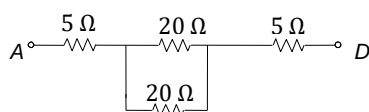

$20\Omega$  in parallel with  $20\Omega$  will gives

$$\left(\frac{20 \times 20}{20 + 20}\right) = \frac{400}{40} = 10\Omega$$

$$5\Omega \quad 10\Omega \quad 5\Omega$$

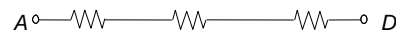

Resistance in series between points  $A$  and  $D$


$$= 5 + 10 + 5$$

$$= 20\Omega$$

120 (a)

$$6 \quad a = 1, b = 2, c = 3$$
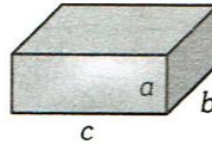
$$\Rightarrow R_{\max} = \frac{\rho \cdot L}{A} = \frac{\rho \cdot c}{a \cdot b}$$



$$R_{\min} = \frac{\rho \cdot L''}{A''} = \frac{\rho \cdot a}{b \cdot c}$$

$$\Rightarrow \frac{R_{\max}}{R_{\min}} = \frac{\frac{\rho \cdot c}{a \cdot b}}{\frac{\rho \cdot a}{b \cdot c}} = \frac{c}{a} \times \frac{c}{a} \Rightarrow \frac{c^2}{a^2} = \left(\frac{c}{a}\right)^2 = \left(\frac{3}{1}\right)^2 = 9$$

120 (a)

$$7 \quad R = \rho \frac{l}{A} \Rightarrow \frac{R_1}{R_2} = \frac{A_2}{A_1} [\rho, L \text{ constant}] \Rightarrow \frac{A_1}{A_2} = \frac{R_2}{R_1} = 2$$

Now, when a body dipped in water, loss of weight

$$= V\sigma_L g = AL\sigma_L g$$

So,  $\frac{(\text{Loss of weight})_1}{(\text{Loss of weight})_2} = \frac{A_1}{A_2} = 2$ ; so  $A$  has more loss of

weight

120 (c)

$$8 \quad \frac{1}{R} = \frac{1}{1} + \frac{1}{1} + \frac{1}{1} = \frac{3}{1} \Rightarrow R = \frac{1}{3} \text{ ohm}$$

Now such three resistance are joined in series, hence total

$$R = \frac{1}{3} + \frac{1}{3} + \frac{1}{3} = 1 \text{ ohm}$$

121 (b)

0 As temperature increases resistance of filament also increase

121 (b)

$$1 \quad \frac{i_g}{i} = \frac{S}{G + S} \Rightarrow i_g G = (i - i_g)S$$

$$\therefore i_g G = (0.03 - i_g)4r \quad \dots(i)$$

$$\text{and } i_g G = (0.06 - i_g)r \quad \dots(ii)$$

from (i) and (ii)

$$0.12 - 4i_g r = 0.06 - i_g r \Rightarrow i_g = 0.02A$$

121 (d)

$$3 \quad \text{Resistance of the bulb} = \left(1.5 \times \frac{1.5}{4.5}\right) = 0.5 = \frac{1}{2} \Omega$$

$$\text{Resistance of the circuit } R = \frac{1 \times \frac{1}{2}}{1 + \frac{1}{2}} = \frac{1}{3} \Omega$$

$$\text{Now, } r = \frac{E - V}{V} R$$


$$\frac{8}{3} = \frac{E - 15}{1.5} \times \frac{1}{3} \text{ or } E = 13.5 \text{ volt}$$

121 (b)

$$4 \quad P = Vi \Rightarrow i = \frac{P}{V} = \frac{60}{220} = \frac{3}{11} \text{ amp}$$

121 (d)

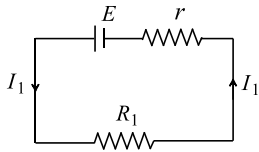
5 Let  $E$  and  $r$  be the emf and internal resistance of a battery respectively



In the first case current flowing in the circuit

$$I_1 = \frac{E}{R_1 + r}$$

$$\text{Or } E = I_1(R_1 + r)$$

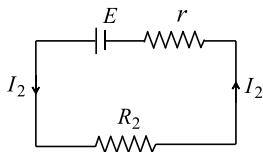

In the second case current flowing in the circuit

$$I_2 = \frac{E}{R_2 + r}$$

$$\text{Or } E = I_2(R_2 + r)$$


Equating equations (i) and (ii), we get

$$I_1(R_1 + r) = I_2(R_2 + r) \Rightarrow I_1R_1 + I_1r = I_2R_2 + I_2r$$

$$I_1R_1 - I_2R_2 = (I_2 - I_1)r \Rightarrow (I_2 - I_1)r = I_1R_1 - I_2R_2$$

$$r = \frac{I_1R_1 - I_2R_2}{I_2 - I_1}$$

121 (d)

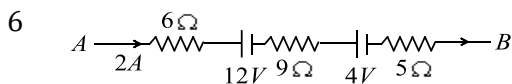

This is a series connection. Further, whatever current enters  $A$  has to pass.  $I = 2 \text{ A}$ .

The total resistance =  $6 + 9 + 5 = 20\Omega$ . The effective potential across the resistances is  $20\Omega \times 2\text{A} = 40\text{V}$ . But  $(+12 - 4)\text{V}$  is opposing the potential difference across  $AB$  therefore the potential difference applied across  $AB$  is  $40\text{V} + 8\text{V} = 48\text{V}$

121 (a)


7  $ABCD$  forms a balanced Wheatstone bridge. Hence the resistances of arm  $BD$  will be ineffective. Now we have resistance  $(2 + 2)\Omega$ ,  $(4 + 4)\Omega$  and  $(2 + 2)\Omega$  in parallel between  $A$  and  $B$ .

Potential difference across  $A$  and  $C$  = EMF of battery =  $8\text{V}$

$$\therefore \text{Current } i_1 = \frac{8}{(4+4)} = 1\text{A}$$

121 (b)

8 The given circuit can be redrawn

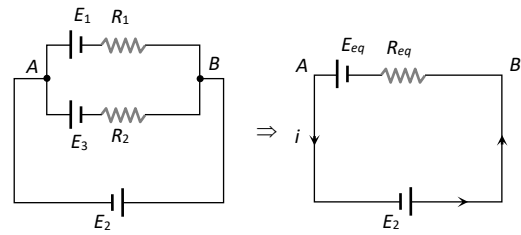

$$E_{eq} = \frac{E_1R_2 + E_3R_1}{R_1 + R_2} = \frac{2 \times 4 + 2 \times 4}{4 + 4} = 2\text{V and}$$

$R_{eq} = \frac{4}{2} = 2\Omega$ . Current  $i = \frac{2+2}{2} = 2\text{A}$  from  $A$  to  $B$  through  $E_2$

121 (b)

$$9 \quad i = \frac{E}{R + r} \Rightarrow 0.5 = \frac{10}{R + 3} \Rightarrow 10 = 0.5R + 1.5 \Rightarrow R = 17\Omega$$

122 (d)

0 The given circuit having parallel and series combination of resistance  $3\Omega$ , we can calculate as

$$R_1 = 3 + 3 = 6\Omega$$

$$R_2 = 3 + 3 = 6\Omega$$

$$\frac{1}{R_3} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{6} + \frac{1}{6} = 3\Omega$$

$$R_4 = 3\Omega$$

$$\frac{1}{R} = \frac{1}{R_3} + \frac{1}{R_4}$$

$$= \frac{1}{3} + \frac{1}{3} = \frac{2}{3}$$

$$R = 1.5\Omega$$


122 (b)

2 Remember mass of the metal deposited on cathode depends on the current through the voltmeter and not on the current supplied by the battery. Hence by using

$$m = Zit, \text{ we can say } \frac{m_{\text{Parallel}}}{m_{\text{Series}}} = \frac{i_{\text{Parallel}}}{i_{\text{Series}}}$$

$$\Rightarrow m_{\text{Parallel}} = \frac{5}{2} \times 1 = 2.5 \text{ gm.}$$

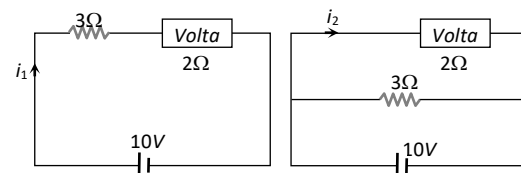Hence increase in mass =  $2.5 - 1 = 1.5 \text{ g}$



122 (d)

3  $V \propto l$

$$\Rightarrow \frac{V}{E} = \frac{l}{L}$$

Where,  $l$  = balance point

$L$  = length of potentiometer wire.

$$\text{Or } V = \frac{l}{L} E$$

$$\text{or } V = \frac{30 \times E}{100} = \frac{30}{100} E$$

122 (c)

4  $\frac{R_{150}}{R_{500}} = \frac{[1+\alpha(150)]}{[1+\alpha(500)]}$ . Putting  $R_{150} = 133\Omega$  and  $\alpha = 0.0045/^\circ\text{C}$ , we get  $R_{500} = 258\Omega$

122 (c)

5 As ammeter must be connected in series of  $20\Omega$  resistor, and the voltmeter in parallel to  $20\Omega$  resistor, the correct arrangement is as shown in figure(c).

122 (b)

6 For maximum energy equivalent resistance of combination should be minimum

122 (b)

7 In the given case cell is in open circuit ( $i = 0$ ) so voltage across the cell is equal to its e.m.f

122 (d)

$$8 \quad R_2 = n^2 R = (2)^2 \times 5.5 = 22\Omega$$

122 (d)

9 Current in silver voltmeter.

$$i_1 = \frac{m_1}{z_1 t_1} = \frac{1}{(11.2 \times 10^{-4}) \times (30 \times 60)} = 0.5 \text{ A}$$

$$\text{Current in copper voltmeter } i_2 = \frac{m_2}{z_2 t_2}$$

$$i_2 = \frac{1.8}{(6.6 \times 10^{-4}) \times (30 \times 60)} = 1.51 \text{ A}$$

So, total current given by battery  $i_1 + i_2 = 2.01 \text{ A}$

Energy supplied by battery =  $Eit$

$$W = (12) \times (2.01) \times (30 \times 60) \text{ J} = 4.34 \times 10^4 \text{ J}$$

123 (d)

0 Two bulbs of  $100 \text{ W}$  are connected in series, the total power

$$P' = \frac{100 \times 100}{100 + 100} = \frac{10000}{200}$$

$$P' = 50 \text{ W}$$

When two bulbs are connected in parallel the total power

$$P'' = 100 + 100 = 200 \text{ W}$$

123 (b)

1 From the formula shunt resistance

$$S = \frac{i_g \times g}{i - i_g}$$

$$\Rightarrow S = \frac{2 \times 12}{5 - 2} = 8\Omega \quad (\text{in parallel})$$

123 (d)

$$2 \quad R = \frac{\rho l}{A}. \text{ So } R_1 = \frac{\rho(4a)}{(2a)(a)} = \frac{2\rho}{a}$$

$$R_2 = \frac{\rho(a)}{(4a)(2a)} = \frac{\rho}{8a} \text{ and } R_3 = \frac{\rho(2a)}{(4a)(a)} = \frac{\rho}{2a}$$

$$\therefore R_1 > R_3 > R_2$$

123 (d)

$$3 \quad i_g = \frac{i}{10} \Rightarrow \text{Required shunt } S = \frac{G}{(n-1)} = \frac{90}{(10-1)} = 10 \Omega$$

123 (c)

4 At room temperature, the free electrons in a conductor move randomly with speed of the order of  $10^5 \text{ ms}^{-1}$ . Since, the motion of the electrons is random there is no net charge flow in any direction.

123 (a)

5 Let the resistance of  $P, Q$  and  $R$  be  $r$ .

The total resistance across the battery is

$$r_{\text{total}} = r + \frac{r}{2} = \frac{3}{2} r.$$

Current through  $P$ ,

$$I_P = \frac{\sqrt{\text{Power}}}{\sqrt{r_{\text{total}}}} = \frac{\sqrt{12}}{\sqrt{\frac{3}{2} r}} = \sqrt{\frac{8}{r}}.$$

Current through  $R$ ,

$$I = \frac{1}{2} I_P = \sqrt{\frac{2}{r}}.$$

Power dissipated in  $R$  is thus

$$P_R = I^2 r = \left(\frac{2}{r}\right) r = 2 \text{ W}$$

123 (c)

6 The resistance of a metallic wire at temperature  $t^\circ\text{C}$  is given by

$$R_t = R_0(1 + \alpha t) \quad \dots (i)$$

Given,  $\alpha = 0.00125 \text{ K}^{-1}$

$$R_{300} = 1 \Omega$$

From Eq. (i), we have

$$1 = R_0(1 + 0.00125 \times 300) \quad \dots (ii)$$

$$\text{and } 2 = R_0(1 + 0.00125 \times T) \quad \dots (iii)$$

$$\therefore \frac{2}{1} = \frac{1 + 0.00125 \times T}{1 + 0.00125 \times 300}$$


$$\text{or } 2.75 = 1 + 0.00125 \times T$$

$$\text{or } T = \frac{1.75}{0.00125} = 1400 \text{ K}$$

123 (a)

7 Power consumed by heater is  $110 \text{ W}$ , so by using

$$P = \frac{V^2}{R}$$

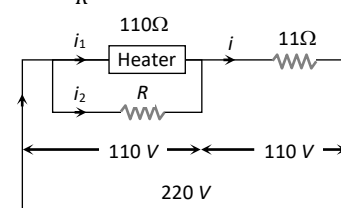

$$110 = \frac{V^2}{110} \Rightarrow V = 110 \text{ V}. \text{ Also from figure } i_1 =$$

$$\frac{110}{110} = 1 \text{ A}$$

$$\text{and } i = \frac{110}{11} = 10 \text{ A}. \text{ So } i_2 = 10 - 1 = 9 \text{ A}$$



Applying Ohms law for resistance  $R, V = iR$   
 $\Rightarrow 110 = 9 \times R \Rightarrow R = 12.22 \Omega$

123 (b)

8  $R_t = R_0(1 + \alpha t)$

Initially,  $R_0(1 + 30\alpha) = 10\Omega$

Finally,  $R_0(1 + \alpha t) = 11\Omega$

$$\therefore \frac{11}{10} = \frac{1 + \alpha t}{1 + 30\alpha}$$

$$\Rightarrow 10 + (10 \times 0.002 \times t) = 11 + 330 \times 0.002$$

$$\Rightarrow 0.02t = 1 + 0.66 = 1.66 \Rightarrow t = \frac{1.66}{0.02} = 83^\circ\text{C}$$

123 (b)

9  $H = i^2 R t \Rightarrow R = \frac{H}{i^2 t} = \frac{80}{4 \times 10} = 2 \Omega$

124 (b)

0 An electric fuse of length  $l$ , radius  $r$  when used in series of the circuit can withstand only if the rate of heat produced due to current in it is equal to the rate of heat lost due to radiation. If  $H$  is the rate of lost per unit area of the fuse wire, then  $H \times 2\pi r l = I^2 R = I^2 \rho l / \pi r^2$

or  $H = \frac{I^2 \rho}{2\pi^2 r^3}$  ie,  $H$  is independent of  $l$ .

124 (c)

1 Short circuit current  $i_{SC} = \frac{E}{r} \Rightarrow 3 = \frac{1.5}{r} \Rightarrow r = 0.5\Omega$

124 (d)

2  $\frac{H}{t} = \frac{V^2}{R} \Rightarrow \frac{H}{t} \propto \frac{1}{R}$

124 (a)

3 Thermo electric power  $P = \frac{dE}{d\theta} = \alpha + \beta\theta$

Comparing it with  $y = mx + c$ , option (a) is correct

124 (d)

4 In series, total resistance of 5 resistance =  $5R$

Power dissipated =  $\frac{V^2}{5R} = 5$

or =  $\frac{V^2}{R} = 25$

In parallel, total power =  $5 \left( \frac{V^2}{R} \right) = 5 \times 25 = 125$  W

124 (b)


5 1 faraday (96500C) is the electricity which liberates that amount of substance which is equal to equivalent wt

So liberated amount of Cu is  $\frac{63.5}{2}$

=  $31.25 \text{ gm} \approx 32 \text{ gm}$

124 (b)

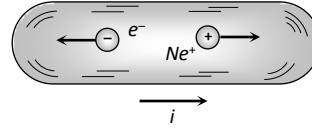6 Net current  $i = i_+ + i_- = \frac{(n_+)(q_+)}{t} + \frac{(n_-)(q_-)}{t}$



$$\Rightarrow i = \frac{(n_+)}{t} \times e + \frac{(n_-)}{t} \times e$$

$$= 2.9 \times 10^{18} \times 1.6 \times 10^{-19} + 1.2 \times 10^{18} \times 1.6 \times 10^{-19}$$

$$\Rightarrow i = 0.66 \text{ A}$$

124 (b)

7 The resistance of a metallic wire at temperature  $t^\circ\text{C}$  is given by

$$R_t = R_0(1 + \alpha t)$$

Where  $\alpha$  is coefficient of expansion.

Hence, resistance of wire increases on increasing the temperature. Also, from Ohm's law, ratio of  $\frac{V}{i}$  is equal to  $R$  ie,

$$\frac{V}{i} = R$$

Hence, on increasing the temperature the ratio  $\frac{V}{i}$  increases.

124 (a)

8 Let resistances are  $R_1$  and  $R_2$ ,

Then  $S = R_1 + R_2$

And  $P = \frac{R_1 R_2}{R_1 + R_2}$

$$\therefore (R_1 + R_2) = \frac{n \times R_1 R_2}{R_1 + R_2} \text{ (From } S = nP \text{)}$$

$$\Rightarrow (R_1 + R_2)^2 = n R_1 R_2$$

$$\Rightarrow n = \left[ \frac{R_1^2 + R_2^2 + 2R_1 R_2}{R_1 R_2} \right]$$

$$= \left[ \frac{R_1}{R_2} + \frac{R_2}{R_1} + 2 \right]$$

We know,

Arithmetic Mean  $\geq$  Geometric Mean

$$\frac{\frac{R_1}{R_2} + \frac{R_2}{R_1}}{2} \geq \sqrt{\frac{R_1}{R_2} \times \frac{R_2}{R_1}}$$

$$\Rightarrow \frac{R_1}{R_2} + \frac{R_2}{R_1} \geq 2$$

So,  $n$ (minimum value) =  $2+2=4$

124 (c)

9 From  $v_d = \frac{i}{neA} \Rightarrow i \propto v_d A \Rightarrow i \propto v_d r^2$

125 (c)

0  $P = \frac{V^2}{R} \Rightarrow R_1 = \frac{V_1^2}{P_1} = \frac{(200)^2}{40} = 1000\Omega$

and  $R_2 = \frac{V_2^2}{P_2} = \frac{(200)^2}{100} = 400\Omega$

125 (d)

2 Resistance  $R$  bisecting the circuit can be neglected due to the symmetry of the circuit.

Now, there are four triangles


Effective resistance of each triangle

$$\frac{1}{R'} = \frac{1}{R} + \frac{1}{2R}$$

$$= \frac{2+1}{2R} = \frac{3}{2R}$$

$$\therefore R' = \frac{2}{3}R$$

Now the given circuit reduced to

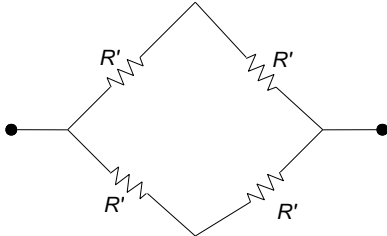

Therefore, effective resistance between  $A$  and  $B$ ,

$$\frac{1}{R_{AB}} = \frac{1}{2R'} + \frac{1}{2R'} = \frac{1}{R'}$$

$$\Rightarrow R_{AB} = R' = \frac{2R}{3} \Omega$$

125 (c)

3 Given,  $l_1 = l + \frac{25}{100}l = \frac{5l}{4}$ . Since volume of wire remains unchanged on increasing length, hence

$$Al = A_1 \times 5l/4 \text{ or } A_1 = 4A/5$$

Given,  $R = 10 = \rho l/A$ , and

$$R_1 = \frac{\rho l_1}{A_1} = \frac{\rho 5l/4}{4A/5} = \frac{25\rho l}{16A}$$

$$\text{or } R_1 = \frac{25}{16} \times 10 = \frac{250}{16} = 15.6\Omega$$

125 (c)

4 Given,  $l_1 = 1K, l_2 = 3K, l_3 = 5K$   
or  $m_1 = 5m, m_2 = 3m, m_3 = 1m$   
We know

$$R = \frac{\rho l}{A}$$

$$\text{So } R_1 : R_2 : R_3 = \frac{l_1}{A_1} : \frac{l_2}{A_2} : \frac{l_3}{A_3}$$

$$= \frac{l_1^2}{V_1} : \frac{l_2^2}{V_2} : \frac{l_3^2}{V_3}$$

$$= \frac{l_1^2}{m_1} : \frac{l_2^2}{m_2} : \frac{l_3^2}{m_3}$$

$$= \frac{1}{5} : \frac{9}{3} : \frac{25}{1} = 1 : 15 : 125$$

125 (b)

$$5 \quad R = \frac{V}{I_g} - G = \frac{3}{30 \times 10^{-3}} - 20 = 10^2 - 20 = 80\Omega$$

125 (c)

6 Let  $\rho$  is the resistivity of the material

Resistance for contact  $A - A$

$$R_{AA} = \rho \frac{x}{2x \times 4x} = \frac{\rho}{8x}$$

Similar for contacts  $B - B$  and  $C - C$  are respectively

$$R_{BB} = \rho \cdot \frac{2x}{x \times 4x} = \frac{\rho}{2x} = \frac{4\rho}{8x}$$

$$\text{and } R_{CC} = \rho \frac{4x}{x \times 2x} = \frac{2\rho}{x} = \frac{16\rho}{8x}$$

It is clear maximum resistance will be for contact  $C - C$


125 (a)

7 At point  $A$  the slope of the graph will be negative. Hence resistance is negative

125 (d)

8 Equivalent resistance of the circuit  $R = 9\Omega$
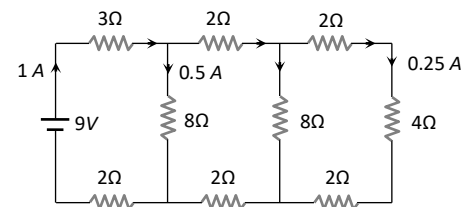
$$\therefore \text{Main current } i = \frac{V}{R} = \frac{9}{9} = 1A$$



After proper distribution, the current through  $4\Omega$  resistance is  $0.25A$

125 (a)

9 Potential gradient = Change in voltage per unit length

$$\therefore 10 = \frac{V_2 - V_1}{30/100} \Rightarrow V_2 - V_1 = 3 \text{ volt}$$

126 (d)

0 Drift velocity is given by

$$v_d = \frac{I}{nqA}$$

Where  $I$  is current,  $n$  the number of electrons,  $A$  the area,  $q$  the charge. Given

$$\frac{I}{A} = \frac{480A}{cm^2}, q = 1.6 \times 10^{-19}C$$

$$n = \frac{6 \times 10^{23} \times 9}{64}$$

$$\therefore v_d = 480 \times \frac{64}{6 \times 10^{23} \times 9 \times 1.6 \times 10^{-19}}$$

$$\Rightarrow v_d = \frac{480 \times 64}{6 \times 9 \times 1.6 \times 10000} \text{ cms}^{-1}$$

$$\Rightarrow v_d = \frac{32}{900} \text{ cms}^{-1}$$

$$= \frac{32 \times 10}{900} \text{ mms}^{-1}$$

$$= 0.36 \text{ mms}^{-1}$$

126 (d)

$$1 \quad v_d = \frac{i}{nAe} = \frac{i \times 4}{n\pi D^2 e} ie, v_d \propto \frac{1}{D^2}$$


$$\therefore \frac{vd_1}{vd_2} = \frac{D_2^2}{D_1^2} = \left(\frac{1}{2}\right)^2 = \frac{1}{4}$$

126 (b)

2  $W = qV = 6 \times 10^{-6} \times 9 = 54 \times 10^{-6} J$

126 (b)

3 Resistance of bulb 1

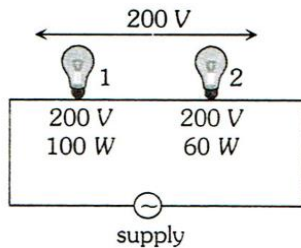

$$R_1 = \frac{V^2}{P} = \frac{(220)^2}{100}$$

$$R_1 = 484 \Omega$$

Resistance of bulb 2

$$R_2 = \frac{(220 V)^2}{60 W} = \frac{4840}{6} = 806.6 \Omega$$

$$R_{eq} = R_1 + R_2 = (220)^2 \left( \frac{1}{100} + \frac{1}{60} \right)$$

$$\Rightarrow \text{Current flowing } I = \frac{220 V}{R_{eq}} = \frac{220}{(220)^2} \left( \frac{100 \times 60}{160} \right)$$

$$I = \frac{1}{220} \left( \frac{75}{2} \right), I = \frac{15}{88} A$$

Power consumed by 100W bulb =  $I^2 R_1$

$$= \left( \frac{15}{88} \right)^2 \times \frac{(220)^2}{100} = \frac{225}{16} = 14W$$

126 (b)

4  $H = \sigma it \Delta \theta \Rightarrow$  If  $i = 1A, \Delta \theta = 1^\circ C, t = 1sec$   
then  $H = \sigma$

126 (b)

5 P.d. across the circuit =  $1.2 \times \frac{6 \times 4}{6+4} = 2.88 \text{ volt}$

Current through 6 ohm resistance =  $\frac{2.88}{6} = 0.48 A$

126 (d)

6 Thermocouples are widely used type of temperature sensor and are used as means to convert thermal potential difference into electric potential difference, using different combinations of metals. If metals were arranged according to their heating contrasts a series were formed antimony, iron, zinc, silver, gold, lead, mercury, copper, platinum and bismuth. The greater the heating contrasts between metals, the greater the electromotive force (EMF). Antimony and bismuth formed the best junction for emf.

126 (c)

7 The resistance of ideal voltmeter is always infinite.

126 (b)

8


$$R = \frac{V^2}{P} \Rightarrow R_1 = \frac{200 \times 200}{100} = 400 \Omega \text{ and}$$

$$R_2 = \frac{100 \times 100}{200} = 50 \Omega. \text{ Maximum current rating } i = \frac{P}{V}$$

$$\text{So } i_1 = \frac{100}{200} \text{ and } i_2 = \frac{200}{100} \Rightarrow \frac{i_1}{i_2} = \frac{1}{4}$$

126 (b)

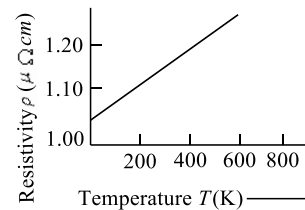9 For a limited range of temperatures, the graph between resistivity and temperature is a straight line for a material like nichrome as shown in the figure



127 (c)

0 Total resistant =  $2.5 + 0.5 = 3.0 \text{ k}\Omega = 3000 \Omega$

$$\therefore \text{Current, } i = \frac{6}{3000} A;$$

Reading of voltmeter =  $i \times (2.5 \times 1000)$

$$= \frac{6}{3000} \times 2500 = 5V$$

127 (c)

1 In the absence of electric field (or potential difference applied) across the conductor, the average thermal velocity of electron is zero

127 (d)

2  $m = zq = \frac{E}{F} It = \frac{M}{pF} It$  or  $I = \frac{mpF}{Mt}$

$$\therefore I' = \frac{2.60 \times 1 \times 96500}{108 \times (40 \times 60)} = 0.968 A$$

% error in reading of ammeter

$$= \left( \frac{I - I'}{I'} \right) \times 100 = \left( \frac{0.90 - 0.986}{0.968} \right) \times 100$$

$$= -7\%$$

127 (c)

4 When the key is in contact with 1, then energy stored in

$$\text{the condenser} = \frac{1}{2} CE^2$$

But when the key is thrown to contact 2, total heat

$$H = I^2(500 + 330) = \frac{1}{2} CE^2$$

$$H_1 = I^2(500)$$

$$\frac{H_1}{H} = \frac{R_1}{(R_1 + R_2)}$$

$$H_1 = \frac{500}{830} \times \frac{1}{2} \times 5 \times 10^{-6} \times (200)^2$$

$$H_1 = 60 \times 10^{-3} \text{ J}$$

127 (c)

5 Before adding, resistance is 5 ohms. After the addition, the central one is a Wheatstone's network.

$\therefore$  Total resistance is  $1 + (2 \text{ \& } 2 \text{ in parallel}) + 1 = 3\Omega$

$\therefore$  The ratio of resistances  $= \frac{5}{3}$

127 (a)

6 Resistance of bulb  $R = \frac{V^2}{P}$

$$R \propto \frac{1}{P}$$

Here  $P_X = 40 \text{ W}$ , and  $P_Y = 60 \text{ W}$

$\therefore R_X > R_Y$

So, potential drop across bulb  $X$  i.e., of  $40 \text{ W}$  bulb will be greater and it will glow brighter.

127 (b)

7 We know  $m = zq$

$$\Rightarrow z \propto \frac{1}{q}$$

$$\therefore \frac{z_2}{z_1} = \frac{q_1}{q_2}$$

Total charge  $q = q_1 + q_2$

$$\frac{q}{q_2} = \frac{q_1}{q_2} + 1$$

$$\Rightarrow q_2 = \frac{q}{\left(1 + \frac{q_1}{q_2}\right)}$$

$$\therefore q_2 = \frac{q}{\left(1 + \frac{z_2}{z_1}\right)}$$

127 (a)

8 Reading of galvanometer remains same whether switch  $S$  is open or closed, hence no current will flow through the switch i.e.  $R$  and  $G$  will be in series and same current will flow through them.

$$I_R = I_G$$

127 (d)

9 Density of copper,

$$\rho = 9 \times 10^3 \text{ kg/m}^3 = 9 \times 10^6 \text{ g/m}^3$$

$$\text{Avogadro number, } N_A = 6.023 \times 10^{23}$$

Mass of 1 mole of copper atom,  $M=63.5\text{g}$

Thus, number of free electrons per volume is

$$n = \frac{N_A}{M} \rho = \frac{6.023 \times 10^{23}}{63.5} \times 9 \times 10^6 \\ = 8.5 \times 10^{28} \text{ m}^{-3}$$

128 (c)

0 The temperature coefficient of the carbon is

negative so the resistance of carbon decreases with the increase of temperature.

128 (d)

1 To convert a moving coil galvanometer into a voltmeter, a high resistance is connected in series with it.

128 (d)

2 Due to high resistance of voltmeter, connected in series, the effective resistance of circuit will increase and hence the current in circuit will decrease. Due to which the ammeter and voltmeter will not be damaged.

128 (c)

$$4 \quad P_p = nP = 2 \times 40 = 80 \text{ W}$$

128 (a)

5  $A$  is false because at neutral temperature thermo emf is maximum.  $B$  is true


128 (d)

6 From the curve it is clear that slopes at points  $A, B, C, D$  have following order  $A > B > C > D$  And also resistance at any point equals to slope of the  $V - i$  curve.

So order of resistance at three points will be  $R_A > R_B > R_C > R_D$

128 (c)

7 The equivalent circuit is given by

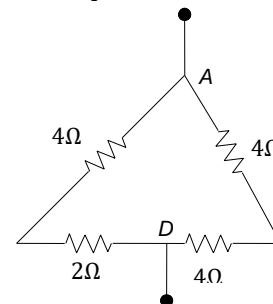

$4\Omega$  and  $2\Omega$  resistances are in series on both sides.

$$\therefore 4\Omega + 2\Omega = 6\Omega$$

Then  $6\Omega$  and  $6\Omega$  resistances are in parallel on both sides

$$\frac{1}{R} = \frac{1}{6} + \frac{1}{6} = \frac{2}{6} = \frac{1}{3}$$

$$R=3\Omega$$

128 (c)

$$8 \quad E = \frac{V}{l} = \frac{iR}{l} = \frac{i\rho l}{Al} = \frac{i\rho}{A} = \frac{1 \times 1.7 \times 10^{-8}}{2 \times 10^{-6}}$$

$$= 8.5 \times 10^{-3} \text{ Vm}^{-1}$$

128 (d)

9  $E = a\theta + b\theta^2$  (given)

For neutral temperature ( $\theta_n$ ),  $\frac{dE}{d\theta} = 0$

$$\Rightarrow a + 2b\theta_n = 0$$

$$\Rightarrow \theta_n = -\frac{a}{2b}$$

$$\therefore \theta_n = -\frac{700}{2} \quad \left( \because \frac{a}{b} = 700^\circ\text{C} \right)$$

$$= -350^\circ\text{C} < 0^\circ\text{C}$$

But neutral temperature can never be negative (less than zero), i.e.,  $\theta_n \not< 0^\circ\text{C}$ .

Hence, no neutral temperature is possible for this thermocouple.

129 (a)

$$0 \quad R_1 = 1/2\Omega, R_2 = 1/4\Omega; R_3 = 1/6\Omega$$

$$\text{In parallel; } \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = 2 + 4 + 6 = 12$$

$$\text{or Equivalent conductance, } G = \frac{1}{R_p} = 12S$$

129 (c)

1 Let  $S$  be the large and  $R$  be the smaller resistance.

From formula for meter bridge

$$S = \left( \frac{100-l}{l} \right) R = \frac{100-20}{20} R = 4R$$

$$\text{Again, } S = \left( \frac{100-l}{100} \right) (R+15)$$

$$= \frac{100-40}{40} (R+15) = \frac{3}{2} (R+15)$$

$$\therefore 4R = \frac{3}{2} (R+15)$$

$$\frac{8R}{3} - R = 15$$

$$\Rightarrow \frac{5R}{3} = 15$$

$$R = 9\Omega$$

129 (c)

2 Reading of voltmeter

$$= E_{eq} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2} = \frac{18 \times 1 + 12 \times 2}{1 + 2} = 14V$$

129 (a)

4  $\therefore$  Peltier coefficient  $\pi = T \frac{de}{dT}$  and  $t^\circ\text{C} = T - 273$

$$\therefore e = a(T - 273) + b(T - 273)^2$$

Differentiating w.r.t.  $T \frac{de}{dT} = a + 2b(T - 273)$

$$\pi = T \frac{de}{dT} = T[a + 2b(T - 273)] \Rightarrow \pi = (t + 273)(a + 2bt)$$

129 (b)

5 Positive ions get deposited on cathode

129 (a)

$$6 \quad \text{Current through the combination } i = \frac{120}{(6+9)}$$

$$= 8A$$

So, power consumed by  $6\Omega$  resistance

$$P = (8)^2 \times 6 = 384W$$

129 (c)

7 As we know, for conductors, resistance  $\propto$  temperature.

From figure  $R_1 \propto T_1 \Rightarrow \tan \theta \propto T_1 \Rightarrow \tan \theta = kT_1$  ... (i)

and  $R_2 \propto T_2 \Rightarrow \tan(90^\circ - \theta) \propto T_2 \Rightarrow \cot \theta = kT_2$  ... (ii)

From equation (i) and (ii),  $k(T_2 - T_1) = (\cot \theta - \tan \theta)$

$$(T_2 - T_1) = \left( \frac{\cos \theta}{\sin \theta} - \frac{\sin \theta}{\cos \theta} \right) = \frac{(\cos^2 \theta - \sin^2 \theta)}{\sin \theta \cos \theta} = 2 \cot 2\theta$$

$$\Rightarrow (T_2 - T_1) \propto \cot 2\theta$$

129 (a)

$$8 \quad \text{Neutral temperature } T_n = \frac{T_c + T_f}{2}$$

$$320^\circ = \frac{T_c + 600^\circ}{2}$$

$$640^\circ = T_c + 600^\circ$$

$$T_c = 40^\circ\text{C}$$

129 (d)

9 As resistance of a bulb  $R = \frac{V^2}{P}$ ,

$$\text{Hence } R_1 : R_2 : R_3 = \frac{1}{100} : \frac{1}{60} : \frac{1}{60}$$

Now the combined potential difference across  $B_1$  and  $B_2$  is same as the potential difference across  $B_3$ . Hence,  $W_3$  is more than  $W_1$  and  $W_2$ , being in series, carry same current and  $R_1 < R_2$ , therefore  $W_1 < W_2$ ,

$$\therefore W_1 < W_2 < W_3$$

130 (a)

0 Given,

$$l = 5\text{cm} = 5 \times 10^{-2}\text{m},$$

$$\rho = 3.5 \times 10^{-5}\Omega\text{m}$$

$$A = \pi(1 \times 10^{-4} - 0.25 \times 10^{-4})$$

$$= 0.75\pi \times 10^{-4}\text{m}$$

$$= 7.5\pi \times 10^{-5}\text{m}$$

$$\therefore R = \frac{\rho l}{A} = \frac{3.5 \times 10^{-5} \times 5 \times 10^{-2}}{7.5\pi \times 10^{-5}}$$

$$= 7.42 \times 10^{-3}\Omega$$

130 (d)

1 At an instant approach the student will choose  $\tan \theta$  will be the right answer. But it is to be seen here the curve makes the angle  $\theta$  with the  $V$ -axis. So it makes an angle  $(90 - \theta)$  with the  $i$ -axis. So resistance = slope =  $\tan(90 - \theta) = \cot \theta$

130 (a)

$$2 \quad R = \frac{Sl}{A} = \frac{Sl^2}{V}$$

$$\therefore \frac{\Delta R}{R} = 2 \frac{\Delta l}{l} = +2.0\%$$

130 (c)

$$3 \quad R_S = R + R = 2R \text{ and } R_P = \frac{R \times R}{R + R} = R/2$$

$$\frac{H_1}{H_2} = \frac{I^2 R_S}{I^2 R_P} = \frac{R_S}{R_P} = \frac{2R}{R/2} = \frac{4}{1}$$

130 (c)

$$4 \quad H = \frac{V^2}{R} t$$

Since supply voltage is same and equal amount of heat is produced, therefore

$$\frac{R_1}{t_1} = \frac{R_2}{t_2} \text{ or } \frac{R_1}{R_2} = \frac{t_1}{t_2} \dots (i)$$

$$\text{But } R \propto l \Rightarrow \frac{R_1}{R_2} = \frac{l_1}{l_2} \dots (ii)$$

$$\text{By (i) and (ii), } \frac{l_1}{l_2} = \frac{t_1}{t_2} \dots (iii)$$

$$\text{Now } l_2 = \frac{2}{3} l_1 \Rightarrow \frac{l_1}{l_2} = \frac{3}{2}$$

$$\therefore \text{By equation (iii), } \frac{3}{2} = \frac{15}{t_2} \Rightarrow t_2 = 10 \text{ minutes}$$

130 (c)

6 The best conductor of electricity is one whose resistance is least. As  $R = \rho l/A$ . Therefore for the given value of  $l$  and  $A$ ,  $R \propto \rho$ . Hence, silver is the best conductor of heat and electricity

130 (a)

7 Current flowing through both the bars is equal. Now, the heat produced is given by

$$H = I^2 R t$$

$$H \propto R \text{ or } \frac{H_{AB}}{H_{BC}} = \frac{R_{AB}}{R_{BC}}$$

$$= \frac{(1/2r)^2}{(1/r)^2} \quad \left( \text{as } R \propto \frac{1}{A} \propto \frac{1}{r^2} \right)$$

$$= \frac{1}{4} \text{ or } H_{BC} = 4H_{AB}$$

130 (c)

$$8 \quad P = 100 \text{ watt, } V = 125 \text{ V}$$

$$\text{Since } P = VI, \therefore I = \frac{P}{V} = \frac{100}{125} \text{ ampere}$$

$$\text{Mass of chlorine liberated} = zIt$$

$$= 0.367 \times 10^{-6} \times \frac{100}{125} \times 60 = 0.0176 \times 10^{-3} \text{ kg} \\ = 17.6 \text{ mg}$$

131 (a)

$$0 \quad J = nqv = n(ze)v$$

$$= \frac{2 \times 10^8 \times 2 \times 1.6 \times 10^{-19} \times 10^5}{(10^{-2})^3}$$

$$= 6.4 \text{ A/m}^2$$

131 (d)

$$1 \quad \text{In series } P_S = \frac{P}{n} \Rightarrow 10 = \frac{P}{3} \Rightarrow P = 30 \text{ W}$$

$$\text{In parallel } P_P = nP = 3 \times 30 = 90 \text{ W}$$

131 (b)


3 Cells are joined in parallel when internal resistance is higher than external resistance. [ $R < r$ ]

$$i = \frac{E}{R + \frac{r}{n}}$$

131 (b)

5 Since the value of  $R$  continuously increases, both  $\alpha$  and  $\beta$  must be positive.

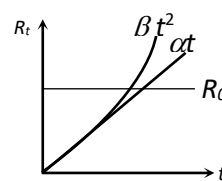Actually the components of the given equation are as follows



131 (b)

6 In series : Potential difference  $\propto R$

$$\text{When only } S_1 \text{ is closed } V_1 = \frac{3}{4} E = 0.75E$$


$$\text{When only } S_2 \text{ is closed } V_2 = \frac{6}{7} E = 0.86E$$

And when both  $S_1$  and  $S_2$  are closed combined resistance of  $6R$  and  $3R$  is  $2R$

$$\therefore V_3 = \left(\frac{2}{3}\right) E = 0.67E \Rightarrow V_2 > V_1 > V_3$$

131 (a)

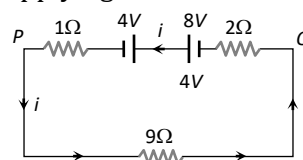7 Applying Kirchoff's voltage law in the given loop



$$-2i + 8 - 4 - 1 \times i - 9i = 0 \Rightarrow i = \frac{1}{3} \text{ A}$$

$$\text{Potential difference across } PQ = \frac{1}{3} \times 9 = 3 \text{ V}$$

131 (b)

8 Number of free electrons per unit volume,

$$n = \frac{N}{M} \rho = \frac{6.023 \times 10^{23}}{63.5 \times 10^{-3}} \times 9 \times 10^3$$

$$\therefore v_d = \frac{i}{nAe}$$

$$= \frac{1.5 \times 63.5 \times 10^{-3}}{6.023 \times 10^{23} \times 9 \times 10^3 \times 10^{-7} \times 1.6 \times 10^{-19}}$$

$$= 1.1 \times 10^{-3} \text{ ms}^{-1}$$

131 (c)

9 Chemical energy consumed per sec = heat energy produced per sec.

$$I^2(R + r) = (0.2)^2(21 + 4) = 1 \text{ J s}^{-1}$$

132 (d)

0 Potential gradient of a potentiometer

$$K = \frac{I\rho}{A} = \frac{0.2 \times 4 \times 10^{-7}}{8 \times 10^{-7}} = 0.1\text{V/m}$$

132 (b)

1 Let the current in the circuit =  $i = \frac{V}{R}$   
 Across the cell,  $E = V + ir \Rightarrow r = \frac{E-V}{i} = \frac{E-V}{V/R} = \left(\frac{E-V}{V}\right)R$

132 (b)


2 Charge  $Q = It = 1.6 \times 60 = 96\text{ C}$   
 Let  $n$  be the number of  $\text{Cu}^{+2}$  ions, then  
 $ne = Q \Rightarrow n = \frac{Q}{e} = \frac{96}{2 \times 1.6 \times 10^{-19}} = 3 \times 10^{20}$

132 (b)

3 Maximum number of resistances =  $2^{n-1} = 2^{3-1} = 4$

132 (b)

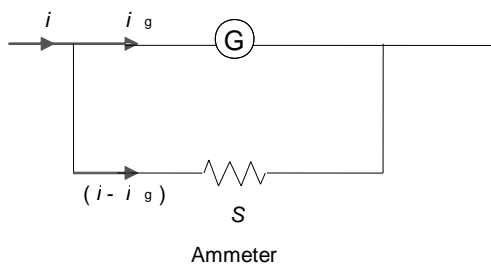4 Shunt is a low resistance used in parallel with the galvanometer to make it ammeter.  
 The circuit is shown in figure.




Voltage across galvanometer = voltage across

1 (b)

3 Given resistance of each part will be

2  
9

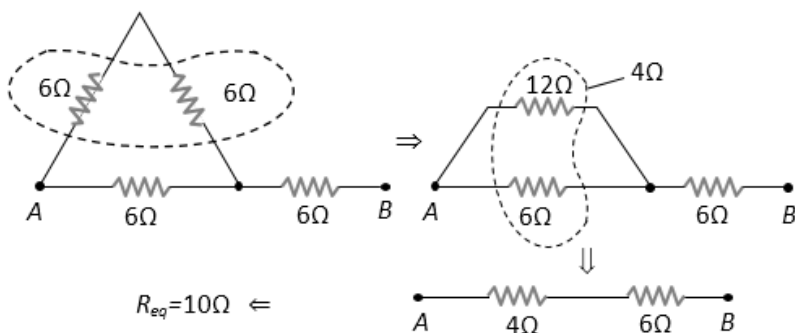

shunt

$$\text{ie., } i_g G = (i - i_g)S \text{ or } S = \frac{i_g G}{i - i_g}$$

Given,  $G = 22.8\Omega$ ,  $i = 20\text{A}$ ,  $i_g = 1\text{A}$

$$\therefore S = \frac{1 \times 22.8}{20 - 1} = \frac{22.8}{19} = 1.2\Omega$$

132 (d)

$$5 \quad P_{\text{Rated}} \propto \frac{1}{R} \Rightarrow \frac{R_1}{R_2} = \frac{P_2}{P_1} = \frac{60}{40} = \frac{3}{2}$$

132 (c)

6 According to Faraday's law of electrolysis

$$m = zq$$

$$\frac{m_{\text{Zn}}}{m_{\text{Cu}}} = \frac{z_{\text{Zn}}}{z_{\text{Cu}}}$$

$$\therefore \frac{0.13}{m_{\text{Cu}}} = \frac{32.5}{31.5}$$

$$m_{\text{Cu}} = 0.126\text{ g.}$$

132 (b)

8 It is the electric field that is set up which moves with the velocity of light in that medium