

concept

5)

$$y = \frac{\alpha^x \beta^y}{t^z} g$$

$$\frac{\Delta y}{y} = x \frac{\Delta \alpha}{\alpha} + y \frac{\Delta \beta}{\beta} + z \frac{\Delta t}{t} + \frac{\Delta g}{g}$$

$$\gamma = 0.35 \quad \Delta \gamma = 0.05$$

$$\lambda = 15, \quad \Delta \lambda = 0.2$$

$$R = 100, \quad \Delta R = 10$$

$$R = \frac{\rho l}{A}$$

$$e = \frac{R \cdot A}{l} \quad A = \pi r^2$$

$$e = \frac{R \cdot \pi r^2}{l}$$

$$\frac{\Delta e}{e} = \frac{\Delta R}{R} + 2 \frac{\Delta r}{r} + \frac{\Delta l}{l}$$


$$\frac{\Delta e}{e} = \frac{10}{100} + 2 \frac{0.05}{0.35} + \frac{0.2}{15} = 0.1 + \frac{2}{7} + \frac{2}{150} = 0.1 + 0.28 + 0.01 = 0.39 \text{ (b) Ans}$$

$$\frac{\Delta e}{e} \times 100 = \% \text{ error in } e$$


$$\frac{\Delta R}{R} \times 100 = \% \text{ error in } R$$

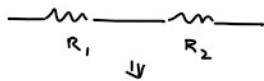12) $R_1 = R_2 = R_0$

$\downarrow \quad \downarrow$
 $\alpha_1 \quad \alpha_2$



$$R_{eq} = R_1 + R_2 = 2R_0$$

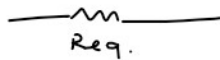

$$R_1 = R_0 (1 + \alpha_1 \Delta T)$$

$$R_2 = R_0 (1 + \alpha_2 \Delta T)$$

$$R_{eq} = R_1 + R_2 = R_0 (1 + \alpha_1 \Delta T) + R_0 (1 + \alpha_2 \Delta T) = \overset{2R_0}{R_{eq}} (1 + \alpha_{eq} \Delta T)$$

$$R_0 \{1 + (\alpha_1 + \alpha_2) \Delta T\} = R_0 \{1 + \alpha_{eq} (2) \Delta T\}$$

$$(\alpha_1 + \alpha_2) \Delta T = 2 \alpha_{eq} \Delta T$$

$$\alpha_{eq} = \frac{\alpha_1 + \alpha_2}{2}$$

R_1

Parallel

$$R_{eq} = \frac{R_0 \times R_0}{2R_0} = \frac{R_0}{2}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$\downarrow \Delta T$

$$\frac{1}{R_{eq} (1 + \alpha_{eq} \Delta T)} = \frac{1}{R_0 (1 + \alpha_1 \Delta T)} + \frac{1}{R_0 (1 + \alpha_2 \Delta T)}$$

$$\frac{2}{R_0 (1 + \alpha_{eq} \Delta T)} = \frac{1}{R_0 (1 + \alpha_1 \Delta T)} + \frac{1}{R_0 (1 + \alpha_2 \Delta T)}$$

$$(1 - \alpha_{eq} \Delta T)$$

$$2 (1 + \alpha_{eq} \Delta T)^{-1} = (1 + \alpha_1 \Delta T)^{-1} + (1 + \alpha_2 \Delta T)^{-1}$$

binomial approximation

$$(1+x)^n \approx 1+nx$$


$$x \ll 0$$

$$2 - 2\alpha_{eq}\Delta T = 1 - \alpha_1\Delta T + 1 - \alpha_2\Delta T$$


$$\alpha_{eq} = \frac{\alpha_1 + \alpha_2}{2}$$

Resistivity


Conductor

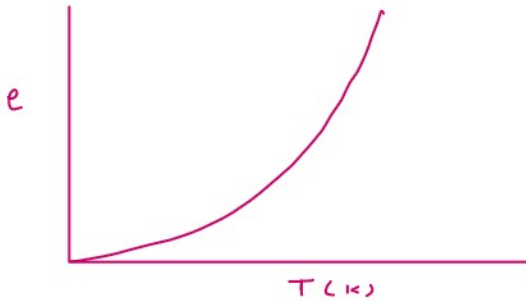

Semiconductor


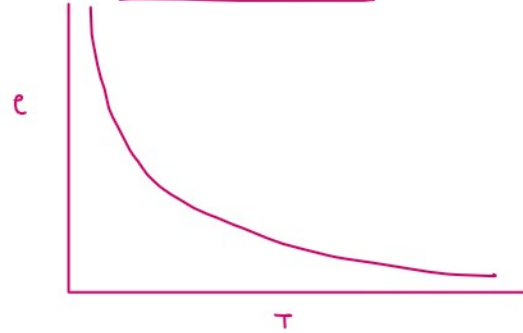


14)

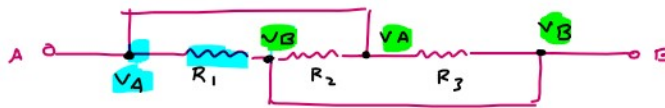

$$V_A - V_B = R_1, R_2, R_3$$

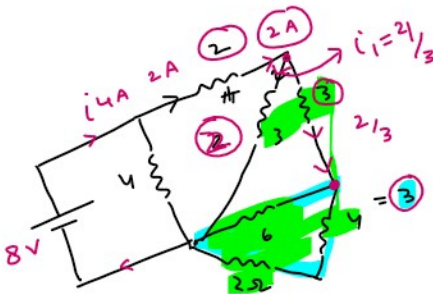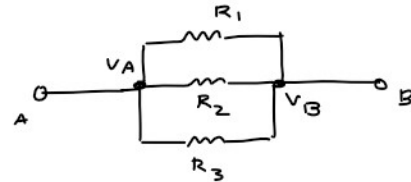Resistance in parallel have same voltage across them.




$$4 + 2 = 6 \Omega$$



$$\frac{6 \times 6}{6 + 6} = R_{eq} = \frac{6 \times 6}{12} = 3 \Omega$$


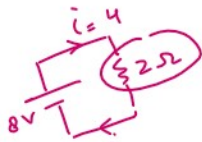
$$\frac{6 \times 3}{6 + 3} = \frac{6 \times 3}{9} = 2$$



$$i = \frac{8}{2} = 4A$$

$$\frac{4 \times 4}{4 + 4} = \frac{4 \times 4}{8} = 2$$

$$R_{eq} = 2$$

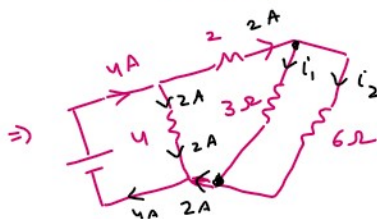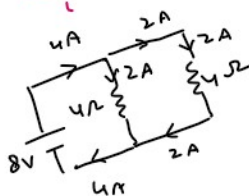


$$i_1 = 2i_2$$

$$i_1 = 2i_2$$


$$i_1 + i_2 = 2A$$

$$3i_2 = 2A$$


$$i_2 = 2/3 \quad i_1 = 4/3$$

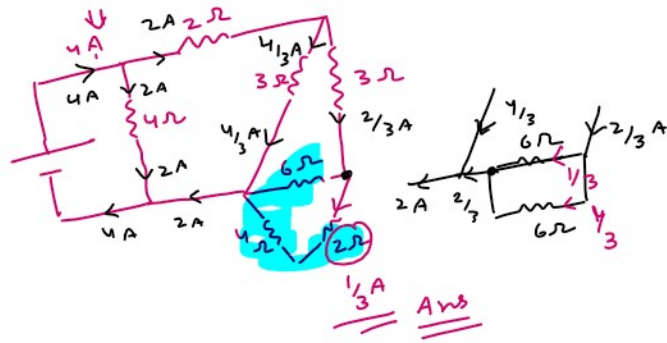

19)

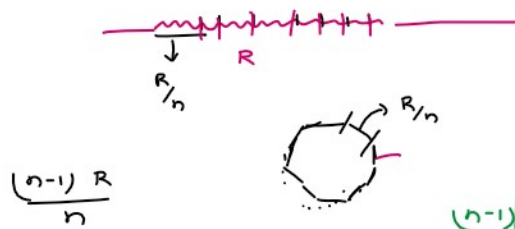

$$(n-1)\left(\frac{R}{n}\right)$$

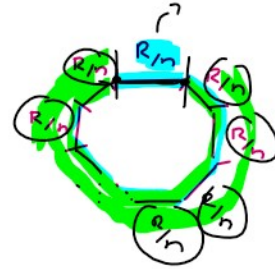

$$\Rightarrow R_{eq} = \frac{R/n \times \frac{(n-1)R}{n}}{\frac{R}{n} + \frac{(n-1)R}{n}}$$

$$= \frac{\frac{(n-1)R}{n}}{\frac{n}{n}} = \frac{(n-1)R}{n^2}$$